

BE Elec  
Sem VII  
HVDC

QP Code :15602

( 3 Hours)

[ Total Marks : 100

- N.B. : (1) Question No. 1 is **compulsory**.  
(2) **Attempt** any 4 Questions out of remaining **six**.  
(3) Assume suitable data if **necessary**.  
(4) **Figures** to right indicate **full** marks

- |    |                                   |  |    |
|----|-----------------------------------|--|----|
| 1. | (a)                               | What is current margin? Give its significance.   | 5  |
|    | (b)                               | Explain PLC-RI filter used in HVDC system.   | 5  |
|    | (c)                               | Draw and explain complete equivalent circuit of HVDC link.   | 5  |
|    | (d)                               | Find the effective commutation resistance of a 6-pulse rectifier which is fed from 400 kV, 3-phase ac voltage, when the dc current in HVDC link is 1 kA & rectifier dc voltage is 500 kV at firing angle of $20^\circ$ .                                       | 5  |
| 2. | (a)                               | Calculate the secondary line voltage of the transformer for 3-phase bridge rectifier to provide a DC voltage of 120 kV. Assume $\alpha=30^\circ$ , $\mu=15^\circ$ . What is the effective reactance $X_L$ , if the rectifier gives 800 A of DC output current. | 10 |
|    | (b)                               | Explain the equidistant pulse control scheme and individual phase control scheme used in HVDC system?  | 10 |
| 3. | (a)                               | Explain different types of HVDC links with neat diagrams.  | 10 |
|    | (b)                               | What do you understand by commutation resistance? Explain its effect on dc voltage produced by converters with appropriate derivation.   | 10 |
| 4. | (a)                               | Explain the different faults taking place in converters.   | 10 |
|    | (b)                               | What are the different types of harmonics getting produced in HVDC system?   | 10 |
| 5. | (a)                               | What is mode stabilization and how it is obtained?   | 10 |
|    | (b)                               | Explain starting and stopping of DC link.  | 10 |
| 6. | (a)                               | Compare AC and DC transmission on the basis of Economics of transmission and Technical performance.  | 10 |
|    | (b)                               | Explain different levels of control of HVDC.   | 20 |
| 7. | Write note on any <b>Three</b> :— |  |    |
|    | (a)                               | VDCOL Characteristics.   |    |
|    | (b)                               | Causes and effects of harmonics in HVDC.   |    |
|    | (c)                               | Ground Return advantages and problems.   |    |
|    | (d)                               | Commutation failure and its effect.  |    |