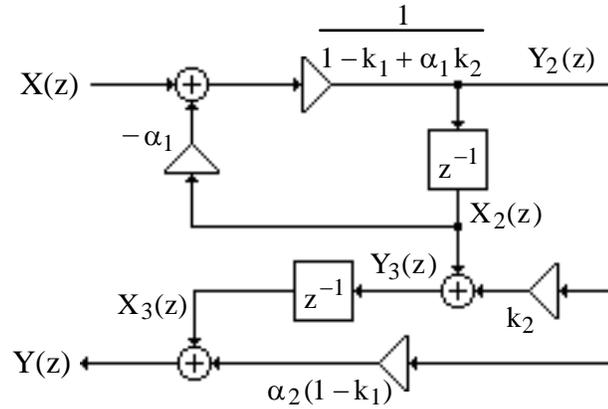


Additional Examples of Chapter 8: Digital Filter Structures



Example E8.2: Analyze the digital filter structure of Figure E8.2 and determine its transfer function $H(z) = Y(z)/X(z)$.


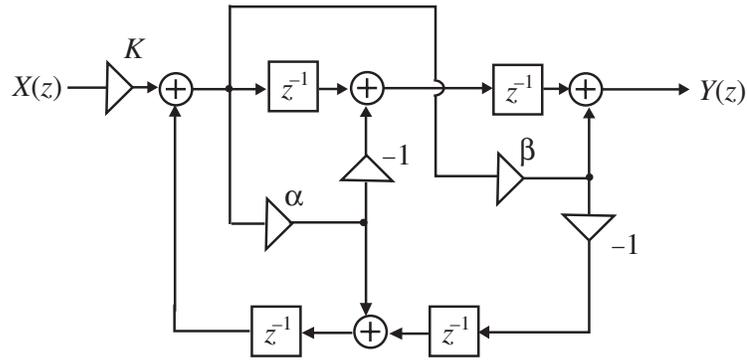


Figure E8.2

Answer:

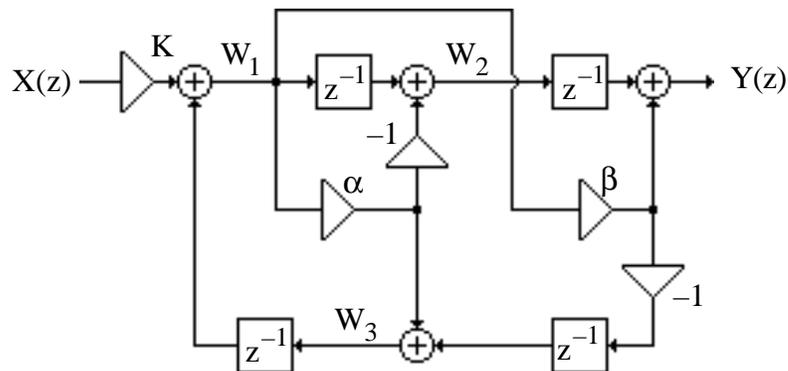

From the above figure, we get $W_1 = KX + z^{-1}W_3$, $W_2 = (z^{-1} - \alpha)W_1$, $W_3 = \alpha W_1 - \beta z^{-1}W_1 = (\alpha - \beta z^{-1})W_1$, and $Y = z^{-1}W_2 + \beta W_1$. Substituting the third equation in the first we get $W_1 = KX + z^{-1}(\alpha - \beta z^{-1})W_1$, or $[1 - \alpha z^{-1} + \beta z^{-2}]W_1 = KX$. Next,

Additional Examples of Chapter 8: Digital Filter Structures

substituting the second equation in the last one we get $Y = [z^{-1}(z^{-1} - \alpha) + \beta]W_1$. From the last two equations we finally arrive at $H(z) = \frac{Y}{X} = K \left(\frac{\beta - \alpha z^{-1} + z^{-2}}{1 - \alpha z^{-1} + \beta z^{-2}} \right)$.


Example E8.3: Realize the transfer function $H(z) = (1 - 0.7z^{-1})^5$ in the following forms:

(a) Two different direct forms, (b) cascade of 5 first-order sections, (c) cascade of one first-order and 2 second-order sections, and (d) cascade of one second-order and one third-order section.


Answer: (a) A direct form realization of

$$H(z) = 1 - 3.5z^{-1} + 4.9z^{-2} - 3.43z^{-3} + 1.2005z^{-4} - 0.16807z^{-5}$$

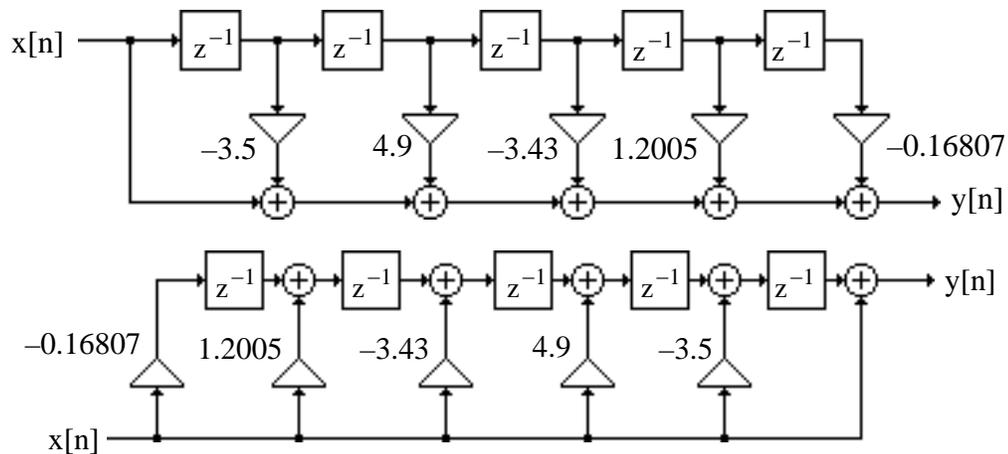
and its transposed structure are shown below:



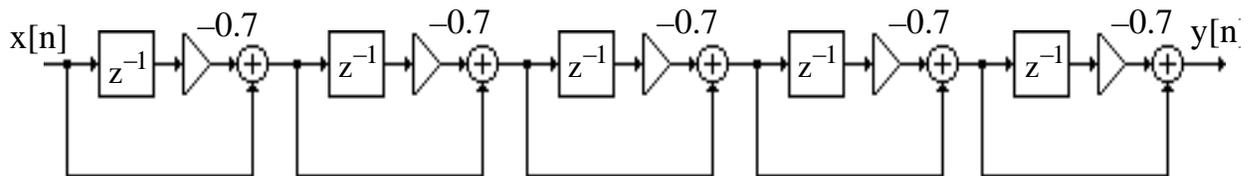(b) A cascade realization of $H(z) = (1 - 0.7z^{-1})(1 - 0.7z^{-1})(1 - 0.7z^{-1})(1 - 0.7z^{-1})(1 - 0.7z^{-1})$ is shown below:




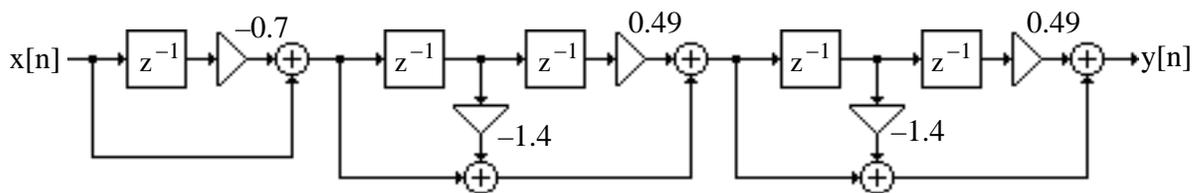(c) A cascade realization of $H(z) = (1 - 0.7z^{-1})(1 - 1.4z^{-1} + 0.49z^{-2})(1 - 1.4z^{-1} + 0.49z^{-2})$ is shown below:



Additional Examples of Chapter 8: Digital Filter Structures

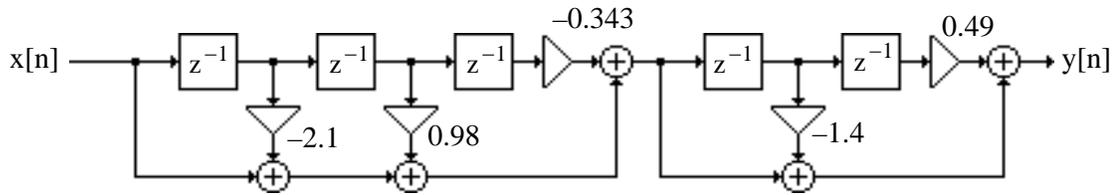(d) A cascade realization of $H(z) = (1 - 2.1z^{-1} + 1.47z^{-2} - 0.343z^{-3})(1 - 1.4z^{-1} + 0.49z^{-2})$ is shown below:



Example E8.4: Develop a three-branch polyphase realization of the FIR transfer function $H(z) = h[0] + h[1]z^{-1} + h[2]z^{-2} + h[3]z^{-3} + h[4]z^{-4} + h[5]z^{-5} + h[6]z^{-6} + h[7]z^{-7}$ and determine the expressions for the polyphase transfer functions $E_0(z)$, $E_1(z)$, and $E_2(z)$.


Answer:

$H(z) = (h[0] + h[3]z^{-3} + h[6]z^{-6}) + z^{-1}(h[1] + h[4]z^{-3} + h[7]z^{-6}) + z^{-2}(h[2] + h[5]z^{-3})$ Hence, $E_0(z) = h[0] + h[3]z^{-3} + h[6]z^{-6}$, $E_1(z) = h[1] + h[4]z^{-3} + h[7]z^{-6}$, $E_2(z) = h[2] + h[5]z^{-3}$.

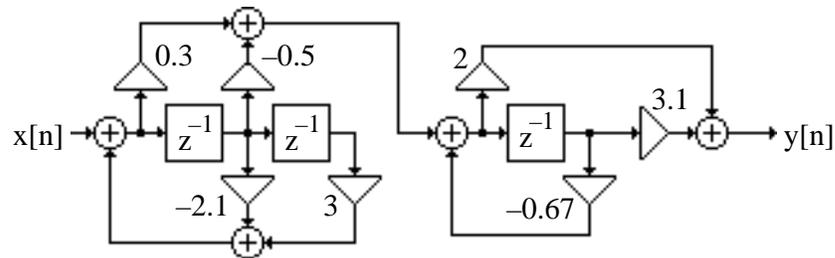Example E8.5: Develop two different canonic cascade realizations of the causal IIR transfer function


$$H(z) = \left(\frac{0.3 - 0.5z^{-1}}{1 + 2.1z^{-1} - 3z^{-2}} \right) \left(\frac{2 + 3.1z^{-1}}{1 + 0.67z^{-1}} \right)$$

Answer: A cascade realization of $H(z) = \left(\frac{0.3 - 0.5z^{-1}}{1 + 2.1z^{-1} - 3z^{-2}} \right) \left(\frac{2 + 3.1z^{-1}}{1 + 0.67z^{-1}} \right)$ is shown below:



A cascade realization of $H(z) = \left(\frac{2 + 3.1z^{-1}}{1 + 2.1z^{-1} - 3z^{-2}} \right) \left(\frac{0.3 - 0.5z^{-1}}{1 + 0.67z^{-1}} \right)$ is shown below:

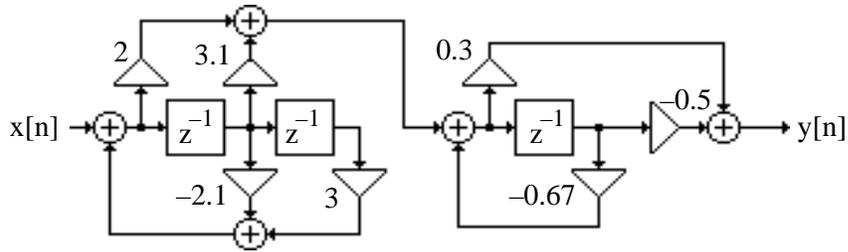Additional Examples of Chapter 8: Digital Filter Structures




Example E8.6: Realize the causal IIR transfer function

$$H(z) = \frac{0.5634(1+z^{-1})(1-1.10166z^{-1}+z^{-2})}{(1-0.683z^{-1})(1-1.4461z^{-1}+0.7957z^{-2})}$$


in the following forms: (a) direct canonic form, (b) cascade form, and (c) Gray-Markel form.

Answer: (a) Direct canonic form -

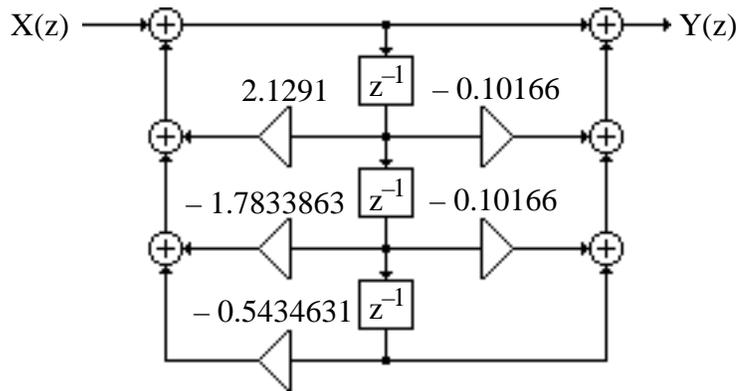

Hardware requirements: # of multipliers = 5, # of two-input adders = 6, # of delays = 3.


(b) Cascade Form

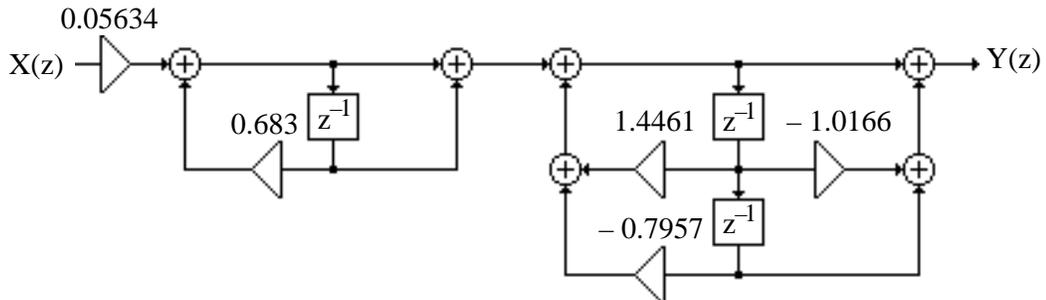

Hardware requirements: # of multipliers = 5, # of two-input adders = 6, # of delays = 3.

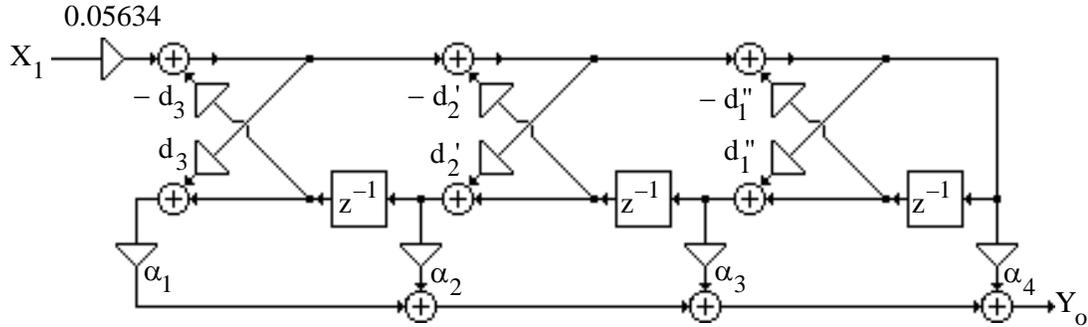(c) Gray-Markel Form -

Additional Examples of Chapter 8: Digital Filter Structures



$$d_3 = -0.5434631, \quad d_2' = 0.8881135, \quad d_1'' = -0.8714813.$$

$$\alpha_1 = p_3 = 1, \quad \alpha_2 = p_2 - \alpha_1 d_1 = 2.02744, \quad \alpha_3 = p_1 - \alpha_1 d_2 - \alpha_2 d_1' = 1.45224,$$

$$\alpha_4 = p_0 - \alpha_1 d_3 - \alpha_2 d_2' - \alpha_3 d_1'' = 1.00702.$$

Hardware requirements: # of multipliers = 9, # of two-input adders = 6, # of delays = 3.

Example E8.7: Realize the causal stable IIR transfer function

$$H(z) = \frac{3 + 9z^{-1} + 9z^{-2} + 3z^{-3}}{12 + 10z^{-1} + 2z^{-2}}$$

as a parallel connection of 2 allpass filters.

Answer:
$$H(z) = \frac{1}{2} \left(\frac{3 + 9z^{-1} + 9z^{-2} + 3z^{-3}}{(3+z^{-1})(2+z^{-1})} \right) = \frac{1}{2} \left[z^{-1} \left(\frac{1+3z^{-1}}{3+z^{-1}} \right) + \left(\frac{1+2z^{-1}}{2+z^{-1}} \right) \right]$$

$$= \frac{1}{2} (A_0(z) + A_1(z)), \quad \text{where } A_0(z) = z^{-1} \left(\frac{1+3z^{-1}}{3+z^{-1}} \right) \text{ and } A_1(z) = \left(\frac{1+2z^{-1}}{2+z^{-1}} \right).$$


Example E8.8: Develop a 3-multiplier realization of a digital sine-cosine generator obtained by setting $\alpha \sin \theta = \pm \beta$ in Eq. (8.123).

Answer: By setting $\alpha \sin \theta = \pm \beta$ in Eq. (8.123), the state-space description of the sine-cosine

generator reduces to
$$\begin{bmatrix} s_1[n+1] \\ s_2[n+1] \end{bmatrix} = \begin{bmatrix} \cos \theta & \pm 1 \\ \mp \frac{\beta^2}{\alpha^2} & \cos \theta \end{bmatrix} \begin{bmatrix} s_1[n] \\ s_2[n] \end{bmatrix},$$
 which leads to the three-multiplier

structure shown below:

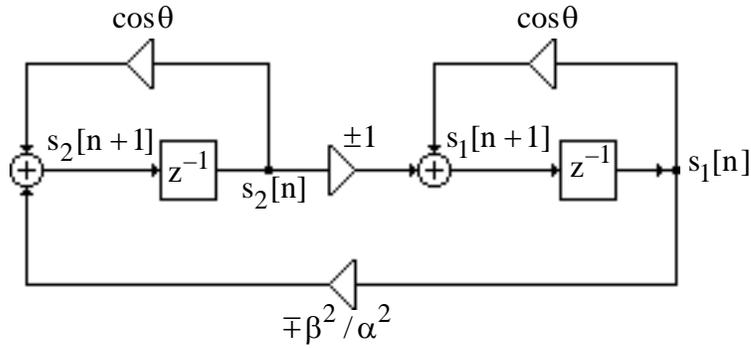Additional Examples of Chapter 8: Digital Filter Structures



Example E8.9: Develop a 1-multiplier realization of a digital sine-cosine generator obtained by setting $C = 0$ in Eq. (8.123) and then choosing and properly.


Answer:
$$\begin{bmatrix} s_1[n+1] \\ s_2[n+1] \end{bmatrix} = \begin{bmatrix} 0 & \frac{\alpha(C - \cos\theta)}{\beta \sin\theta} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} s_1[n+1] \\ s_2[n+1] \end{bmatrix} + \begin{bmatrix} C & \frac{\alpha(1 - C \cos\theta)}{\beta \sin\theta} \\ -\frac{\beta}{\alpha} \sin\theta & \cos\theta \end{bmatrix} \begin{bmatrix} s_1[n] \\ s_2[n] \end{bmatrix}.$$

If $C = 0$, choose $\alpha = \beta \sin\theta$. Then

$$\begin{bmatrix} s_1[n+1] \\ s_2[n+1] \end{bmatrix} = \begin{bmatrix} 0 & -\cos\theta \\ 0 & 0 \end{bmatrix} \begin{bmatrix} s_1[n+1] \\ s_2[n+1] \end{bmatrix} + \begin{bmatrix} 0 & 1 \\ -1 & \cos\theta \end{bmatrix} \begin{bmatrix} s_1[n] \\ s_2[n] \end{bmatrix},$$

which can be realized with two

multipliers as shown below:

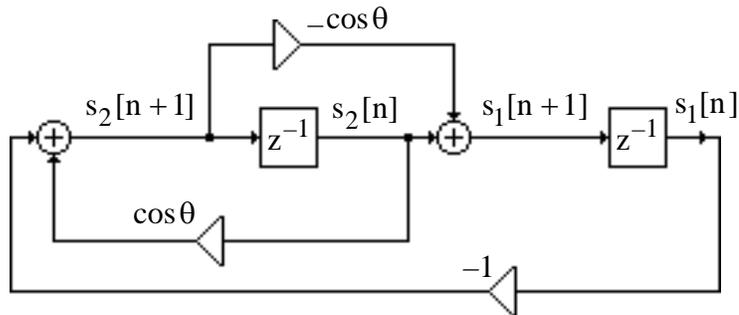

The above structure can be modified to yield a single multiplier realization as indicated below:

