

08/06/15

QP Code : 3498

(3 Hours)

[Total Marks : 80

N.B. (1) Question No. 1 is compulsory.

(2) Attempt any three questions from the remaining five questions.

(3) Assume suitable data if necessary.

1. Attempt any five :-

- (a) Draw pin diagram of IC 741. Mention any four practical values of op-amp parameters. 4
- (b) What are drawbacks of basic differentiator circuit? Suggest remedies. 4
- (c) Design high pass filter with a cut off frequency of 10 KHz and pass band of 2. Assume $C = 0.1 \mu\text{F}$ 4
- (d) Draw the combinational circuit using basic gates to obtain following output. 4
- $$Y = AB + \overline{BC} + \overline{A}\overline{B}$$
- (e) Convert the following - 4
- (i) 1011011 to gray code
- (ii) $(CD8.4)_{16}$ to octal
- (f) Explain in brief types of Registers. 4

2. (a) Design and draw astable multivibrator for output frequency of 5KHz and duty cycle of 60% using IC 555. Also draw waveforms across timing capacitor and the output. Assume $V_{cc} = 5\text{V}$. 10
- (b) Explain operation of op-amp as an adder. Draw a circuit for inverting summing amplifier with $V_1 = 2\text{V}$, $V_2 = 4\text{V}$ and $R_1 = R_2 = R_F = 10\text{k}\Omega$. Calculate output voltage. 10

3. (a) Design an adjustable voltage regulator for the range of 1.25 V to 15 V using IC 317. Also draw circuit for practical voltage regulator using IC 317. 10
- (b) Explain with waveforms positive and negative clipper circuit using opamp. 10

4. (a) Explain with diagram working and operation of successive approximation ADC. 10
- (b) Explain w.r.t. digital ICs 5
- (i) Propagation delay
- (ii) Noise margin
- (c) Write short note on interfacing between TTL and CMOS logic families. 5

5. (a) Simplify the following expression and implement using universal gate 10
$$Y = \sum m (1, 4, 8, 12, 13, 15) + \sum d (3, 14)$$
- (b) Implement following expression using – 10
- (i) one 8 : 1 mux
 - (ii) two 4:1 Mux
 - (iii) one 4 : 1 Mux
- $$F (A ,B, C) = \sum m (0, 2, 5, 6, 7)$$
6. (a) Convert S-R flip flop to T-flip flop. 5
- (b) Compare combinational and sequential circuits. 5
- (c) Explain with timing diagram the working of four bit asynchronous up counter using JK flip flop. 10
-