

QP Code : 1397

(3 Hours)

[Total Marks : 100]

N.B.

- Q 1 is compulsory
- Answer any four out of remaining six questions
- Assumptions made should be clearly stated
- Assume any suitable data wherever required but justify the same

- Q.1 (A) What are the different types of coupling used in BJT amplifiers? Draw the frequency response of a BJT amplifier and explain why the gain is dropping at low and high frequencies. (06)
- (B) State the 'Barkhausen Criteria' of oscillation and explain how the oscillations build up in an oscillator. (04)
- (C) Draw the frequency response for the open loop operation of an op-amp like IC 741 (typical gain bandwidth product- 1 MHz). If it is used for non-inverting amplifier application with gain of 50, what will be the modified frequency response? (05)
- (D) Compare Class A, B and AB power amplifiers. (05)
- Q.2 (A) Explain the impact of cascading on the performance of overall system (10)
- (i) A CC amplifier stage followed by a CE amplifier stage
- (ii) A CE amplifier stage followed by a CB amplifier stage
- (B) What is Darlington pair? What are its features? Derive expression for its ac parameters. State and explain any one application of it in detail. (10)
- Q.3 (A) Design a two stage RC coupled CE amplifier using BC147B transistors, with following specifications: (15)
- Voltage gain ( $A_v$ )  $\geq 2000$  Output Voltage ( $V_o$ ) = 2.5 volts
- Overall stability factor (S)  $\leq 10$  Lower cutoff freq. ( $f_{low}$ ) = 20Hz
- Assume the resistive load ( $R_L$ ) connected to the output of the second stage is 10k $\Omega$ . The specifications of BC147B are as given below:
- |                      |                      |                             |                     |
|----------------------|----------------------|-----------------------------|---------------------|
| $h_{FE\ typ} = 290$  | $h_{fe\ typ} = 330$  | $h_{fe\ min} = 240$         | $h_{fe(max)} = 500$ |
| $h_{ie} = 4.5\ kohm$ | $h_{oe} = 30\ \mu S$ | $h_{re} = 2 \times 10^{-4}$ |                     |
- (B) Draw the schematic of circuit which give output voltage  $V_o = -0.5*(V_1+V_2)$  where  $V_1$  and  $V_2$  are dc input voltages. Also calculate the values of components. (05)
- Q.4 (A) Draw the neat diagram of a RC phase shift oscillator. Explain its operation. Derive the expression for frequency of output signal. (10)
- (B) Derive the equation for frequency of oscillation of a Colpitts oscillator. Also derive the condition for sustained oscillation (10)
- Q.5 (A) Design a class A transformer coupled amplifier with output power of 6 watts, load resistance of 8 ohms. Assume transformer efficiency of 85% and supply voltage of 15 volts. Use the transistor with following specifications (15)
- $P_{Dmax}$  (at 25°C) = 30 W,  $V_{CEO} = 40$  V,  $I_{Cmax}$  (at 25°C) = 5A,  $V_{CEsat} = 1$  V
- (B) For the above design calculate the power dissipation in the transistor when delivering full power output and also its efficiency. (05)
- Q.6 (A) Draw the circuit diagram of subtractor using op-Amp and derive the expressions for output voltages (06)
- (B) With the help of a neat circuit diagram, explain the working of a Schmitt trigger circuit. Draw the relevant waveforms (08)
- (C) What are active filters? Explain the classifications of active filters with their frequency response curve. (06)
- Q.7 Write short notes on any three (20)
- (i) Precision Rectifier (ii) Sample and Hold circuit (iii) Gyrator
- (iv) UJT Relaxation Oscillator (v) Op-amp: Clipping and clamping circuits