

Q.P. Code : 1121


(Old Course)

(3 Hours)


[Total Marks : 100

- N.B. : (1) Question No.1 is compulsory.
 (2) Attempt any four questions from the remaining six questions.
 (3) Figure to the right indicates full marks.
 (4) Assume suitable data whenever necessary and mention the same.

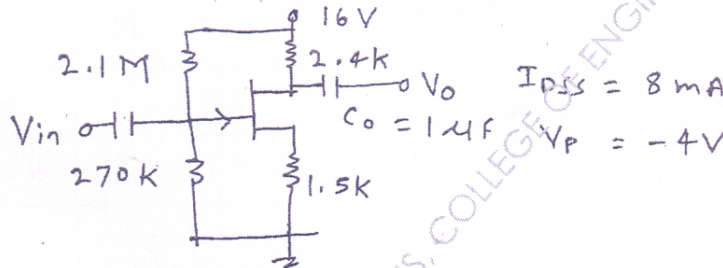1. Using BC 147 A transistor design single stage RC coupled BJT amplifier for following specifications $A_v = 100, V_o = 3$ Volts, $f_L = 10$ Hz, $S < 10$. For the designed amplifier determine input and output impedances, voltage gain. State any two applications of this amplifier. 20
2. (a) Derive the expressions of voltage gain, input impedance, output impedance for CS amplifier using JFET. 10
 (b) Determine V_{GS}, V_{DS}, I_D for the amplifier shown below : 10



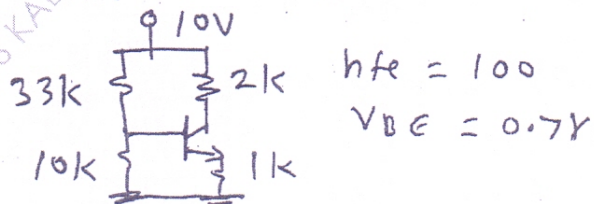3. (a) Derive the expressions of Voltage gain, current gain, input impedance and output impedance for CB AMPLIFIER. 10
 (b) Explain different biasing methods used for D MOSFET and E MOSFET. 10
4. (a) Draw the circuit diagram and explain the operation of Bridge rectifier with capacitor filter. Draw neat waveforms for current and voltage across load and diode. State application of this rectifier. 10
 (b) Find I_{BQ}, I_{CQ} and V_{CEQ} for the following circuit. Draw DC load line. 10



TURN OVER

Q.P. Code : 1121

2

5. Design CS amplifier for the following specifications :
 $A_v = 10$, $Z_{in} = 1M$ ohms, $V_o = 2$ Volts, $F_L = 10$ Hz 18
State applications of this amplifier. 2
6. Write short notes on the following : 20
(a) BJT as a switch,
(b) Thermal runaway,
(c) S.C.R.,
(d) Zener diode.
7. (1) Draw and explain hybrid π model of BJT. 5
(2) Explain biasing of FET for zero temperature drift. 5
(3) Explain the operation of BJT shunt voltage regulator. 5
(4) Compare different types of filters. 5

TURN OVER

Transistor type	F_{max} Watts @ 25°C	I_{cm} Amps	$V_{ce(sat)}$ volts d.c.	$V_{ce(sus)}$ volts d.c.	$V_{ce(sus)}$ volts d.c.	$V_{ce(sus)}$ volts d.c.	$V_{ce(sus)}$ volts d.c.	$V_{ce(sus)}$ volts d.c.	T_j max. °C	D.C. min	current typ.	gain max.	Small min.	Signal typ.	h_{fe} max.	V_{ce} max.	θ_{jc} °C/W	Derate above 25°C W/°C
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5	0.7
ECN 065	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5	0.4
ECN 140	30.0	4.0	1.0	50	40	-	-	6	150	30	50	110	33	60	115	1.2	4.0	0.3
ECN 100	5.0	0.7	0.6	70	60	65	-	6	200	50	90	280	50	90	280	0.9	35	0.05
BC 147A	0.25	0.1	0.25	50	45	50	-	6	125	115	180	220	125	220	260	0.9	-	-
2N 525 (PNP)	0.225	0.5	0.25	85	30	-	-	-	100	35	-	65	-	45	-	-	-	-
BC 147 B	0.25	0.1	0.25	50	45	50	-	6	125	200	290	450	240	330	500	0.9	-	-

Transistor type	h_{ie}	h_{oe}	h_{re}	h_{fe}	θ_{jc}
BC 147 A	2.7k Ω	18 μ mho	1.5×10^{-4}	1.5×10^{-4}	0.4°C/mW
2N 525 (PNP)	1.4k Ω	25 μ mho	3.2×10^{-4}	3.2×10^{-4}	-
BC 147B	4.5k Ω	30 μ mho	2×10^{-4}	2×10^{-4}	0.4°C/mW
ECN 100	50 Ω	-	-	-	-
ECN 140	150	-	-	-	-
ECN 055	120	-	-	-	-
2N 3055	6 Ω	-	-	-	-

BFW 11-JFET MUTUAL CHARACTERISTICS

$-V_{GS}$ volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
I_{DS} max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
I_{DS} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
I_{DS} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

Type	V_{DS} max. Volts	V_{GS} max. Volts	V_{DS} max. Volts	V_{GS} max. Volts	$P_{d(max)}$ @ 25°C	T_j max.	I_{DS}	I_{DS} (typical)	$-V_p$ Volts	r_c	Degate above 25°C	θ_{jc}
2N3622	50	50	50	50	300 mW	175°C	2 mA	3000 μ info	6	50 k Ω	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	30	30	300 mW	200°C	7 mA	5000 μ info	2.5	50 k Ω	-	0.59°C/mW

MUPDI5025 ANJUMAN... TECHNICAL CAMPUS... ENGINEERING... PANVEL 27-11-2015 14:12:20