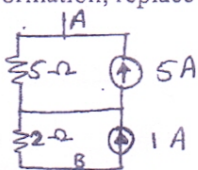


(OLD COURSE)
(3 Hours)

QP Code: 1264
[Total Marks: 100]


- N.B. : (1) Question No. 1 is compulsory.
(2) Attempt any four from the remaining questions.
(3) Assume suitable data, if required.

Q.1 Attempt any four (20)
(1) Using source transformation, replace the network with a single current source and a resistor.




- (2) Define Unilateral and Bilateral element.
(3) Define final steady state condition for resistor and capacitor.
(4) Obtain condition for reciprocity for Z parameters.
(5) Draw pole zero plot for $S(S+1)/(S+3)(S+2)^2$

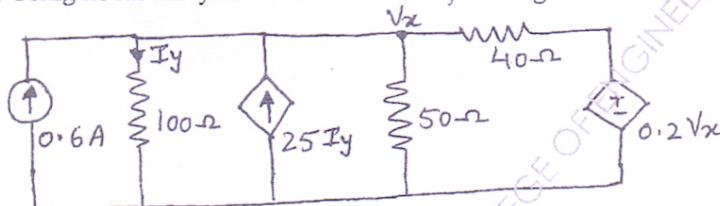
Q. 2 (a) Using nodal analysis calculate current I_y in the given network. (10)



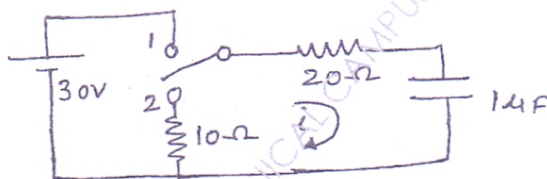
(b) In the given network switch initially is at position 1, and attains steady state condition. At $t=0$, it is moved from position 1 to position 2, find the value of $(i, di/dt \text{ and } d^2i/dt^2)$ at $t > 0^+$. (10)



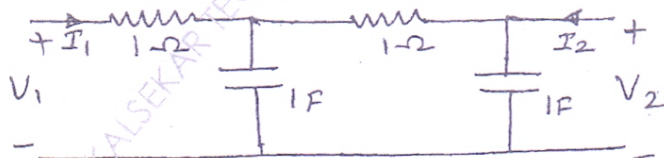Q. 3 (a) Find the network functions V_1/I_1 , V_2/I_1 , and V_2/V_1 . (10)



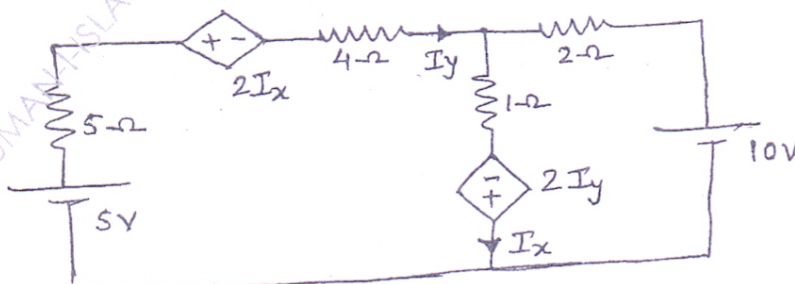(b) Calculate I_x and I_y for the given network (10)




(2)

QP Code : 1264

Q.4 (a) Find the current through 3ohm resistor.

(10)

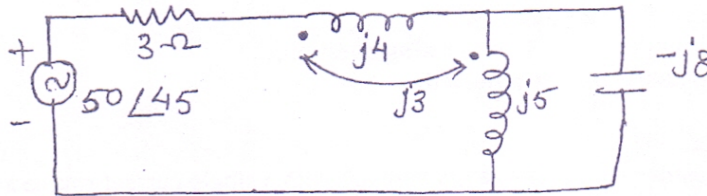

(b) Realise the function using Cauer I and Cauer II

(10)

$$Z(s) = (10S^4 + 12S^2 + 1) / (2S^3 + 2S)$$

Q. 5(a) Test the function is PRF or not

(05)

$$F(s) = (S^3 + 6S^2 + 7S + 3) / (S^2 + 2S + 1)$$

(b) Test whether the polynomials are Hurwitz or


(05)

(1) $P(s) = 2S^4 + 5S^3 + 5S^2 + 4S + 10$

(2) $P(s) = S^5 + S^3 + S$


(c) Find h parameters for the given network

(10)

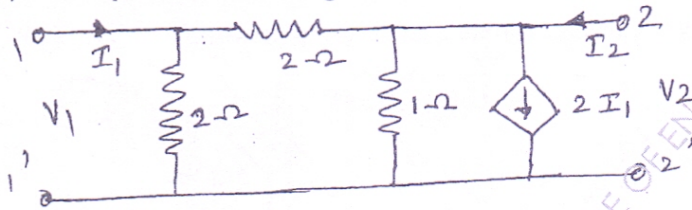

Q.6 (a) Find the driving point admittance $Y(s)$ for the network shown and plot the pole-zero plot.


(10)

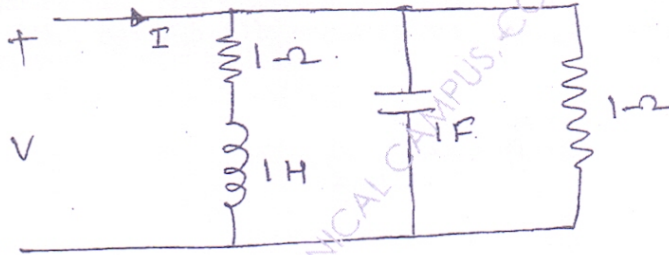

(b) For the given tree obtain

(10)

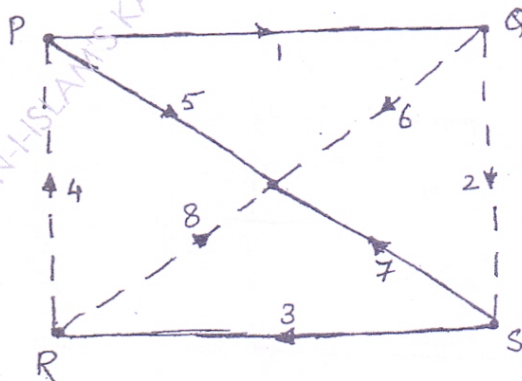- (1) Incidence matrix
- (2) Fundamental cutset matrix
- (3) Fundamental tieset matrix




QP-Con. 12207-15.

Turn over


(3)

QP Code : 1264

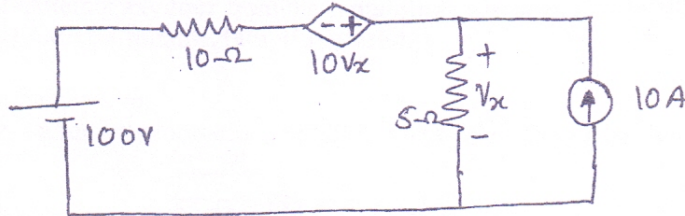Q.7(a) Find the current in 10 ohm resistor of the network, using thevenin's theorem. (10)



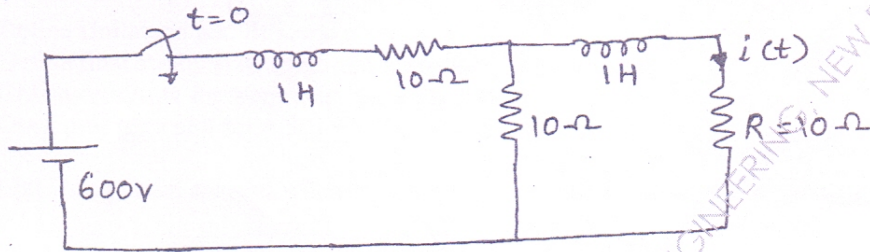(b) Find the current $i(t)$ through R in the circuit shown below using Laplace transform. (10)



QP-Con. 12207-15.

MUPDI5025 ANJUMAN-ISLAMIS KALSEKAR TECHNICAL CAMPUS, COLLEGE OF ENGINEERING, NEW PANVEL 21-12-2015 13:46:06