

QP Code : 30754

(3 Hours)

[Total Marks : 80

- N.B. : (1) Attempt questions No. 1 and any 3 from remaining questions. In all 4 questions are to be attempted.
 (2) All sub-questions of the same question should be answered at one place only in their serial orders, and not scattered.
 (3) Assume suitable data with justification if missing.

1. (a) Determine Y - parameters for the network shown in fig 1 (a)

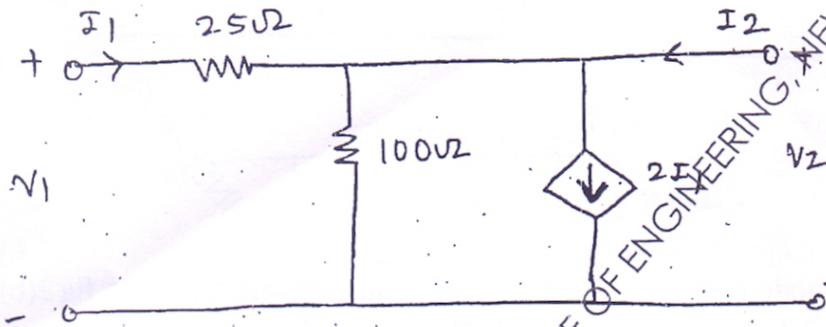


Fig 1 (a)

- (b) Test if $F(s) = s^4 + s^3 + 5s^2 + 3s + 4$ is a Hurwitz polynomial. 5
 (c) Two coils connected in series have self inductance 80 mH & 20 mH respectively. The total inductance of the circuit is found to be 140 mH. Determine the
 (i) mutual inductance between two coils and
 (ii) The coefficient of coupling 5
 (d) Synthesize the following function into a network. 5

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1} \text{ using cauer -1 form.}$$

[TURN OVER]

2. (a) Find the Thevenin's equivalent across the terminals XY for the circuit shown in fig 2 (a) 10

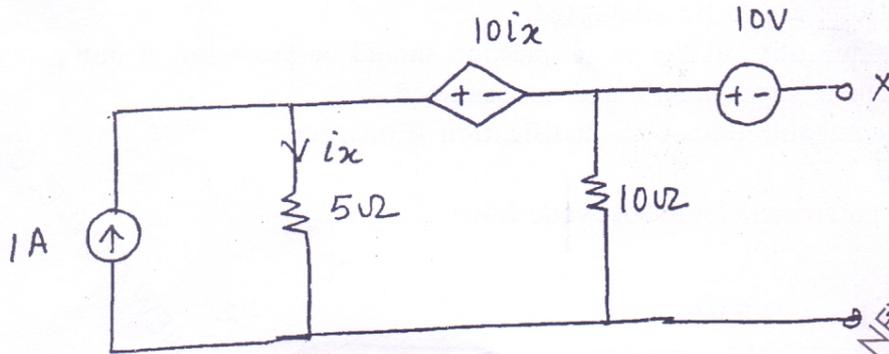


Fig 2(a)

- (b) Determine the node voltage at node (1) & (2) of the Network Shown in fig 2(b) by using nodal analysis. 5

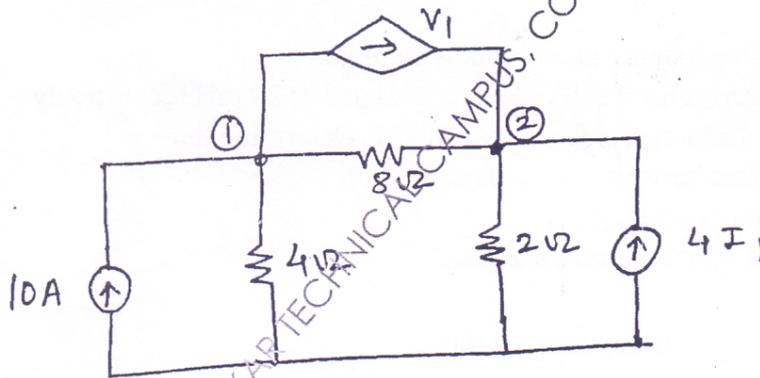


Fig 2(b)

- (c) Test Whether

$$F(s) = \frac{s(s+3)(s+5)}{(s+1)(s+4)}$$

is a positive real function. 5

3. (a) Synthesize the driving point function using Foster -I and Foster -II form. 10

$$z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- (b) State and prove Initial value theorem.
 (c) A Transmission line has distributed parameters $R=6$ Ohms / km, $L=2.2$ mH/km
 $C=0.005$ μ F /km & $G=0.005$ μ mho/km
 Determine characteristics impedance and propagation constant at 1KHz frequency.

4. (a) Find ABCD parameters for the two port Network shown in fig 4 (a). 10

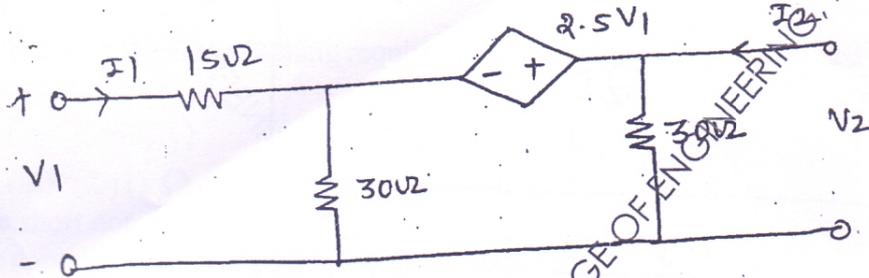


Fig 4(a)

- (b) Find the Network functions $\frac{V_1}{I_1}, \frac{V_2}{I_1}, \frac{V_2}{V_1}$ for the network shown in fig 4 (b) 5

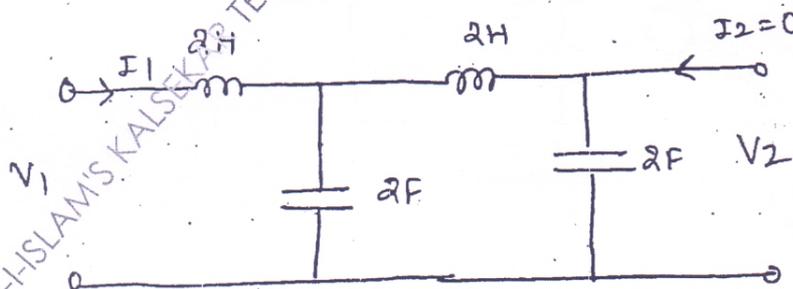


Fig 4(b)

- (c) A Transmission line has a characteristics impedance of $50 + j 100 \Omega$ and is terminated in a load impedance of $73 - j 42.5 \Omega$ Calculate 5
 (a) The reflection coefficient.
 (b) The standing wave ratio

5. (a) The Network shown in fig 5 (a), switch K is closed at $t = 0$, Assume all initial conditions as zero. Find i , $\frac{di}{dt}$ & $\frac{d^2i}{dt^2}$ at $t = 0^+$

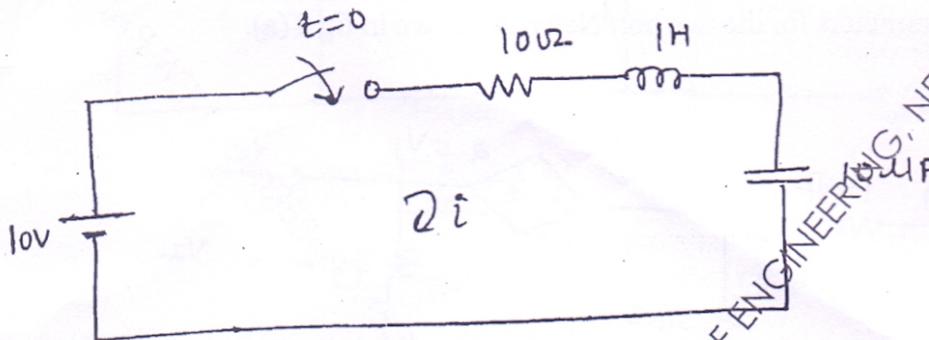


Fig 5(a)

- (b) Write the KVL equations in standard form for the N/W shown in fig 5(b)


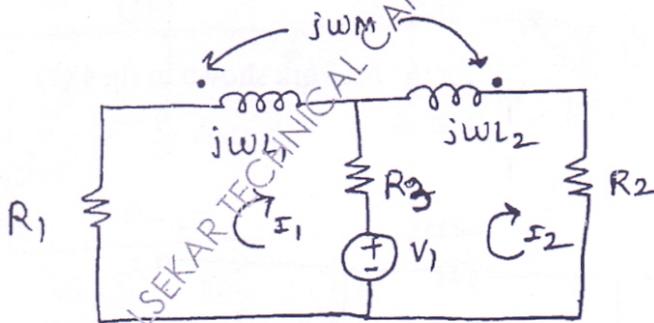


Fig 5(b)

MUPD16025 ANJUMAN-ISLAM'S KAISEKAR TECHNICAL CAMPUS COLLEGE OF ENGINEERING, NEW PANVEL 03-06-2016 13:47:40

(c) Find poles and zero of the Impedance $Z(s)$ for the Network Shown in fig 5 (c)

5

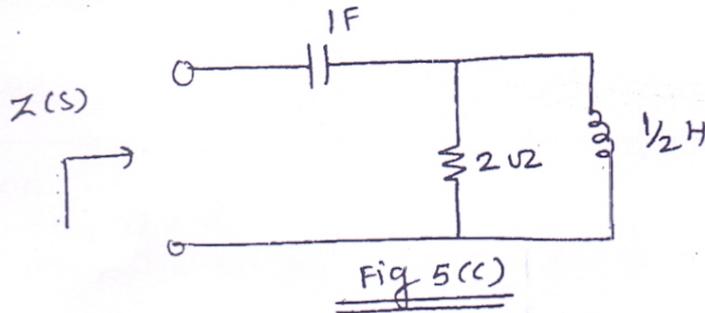

6. (a) Why is the Impedance matching required? Draw the following normalized quantities on the smith chart. 10

- (i) $(3+j3) \Omega$
- (ii) $(1.0) \Omega$
- (iii) $(2-j1) \Omega$
- (i) $j 1.0 \Omega$

(b) Write short note on :
Time domain analysis using Laplace Transform. 5

(c) Define the following terms 5

- (i) Phase Velocity
- (ii) Characteristic impedance
- (iii) Reflection coefficients

MUPD16025 ANJUMAN-ISLAM'S KALSEKAR TECHNICAL CAMPUS, COLLEGE OF ENGINEERING, NEW PANVEL 03-06-2016 13:47:53

Course: SE (all Branches)

QP Code 30754

Correction

Q.No.2 (b)

In Q.2 (b),
Replace by $\textcircled{\uparrow} 4I_1$ by $\textcircled{\uparrow} 4I_1$

Q. No. 6 (a) (i)

Replace (3+i3) by (3+j3)

Date and Time 03/06/2016 04:18 PM