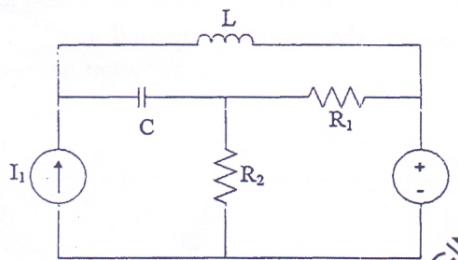


N.B:- (1) Question 1 is compulsory

- (2) Solve any three questions from remaining five questions.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.

Q1 Attempt the following

a) Draw the dual of following circuit.




b) Find the condition of symmetry for Z- parameters.

c) Write the properties of positive real function.

d) State and explain Reciprocity theorem.

Q2 a) Write f-cutset, f-tieset and incidence matrix for the given network.


10

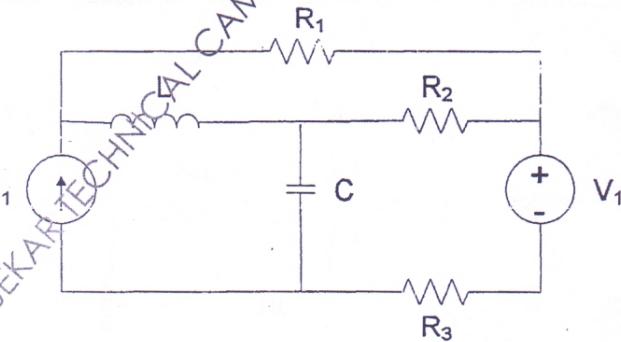


[TURN OVER]

FW-Con.12079-16.

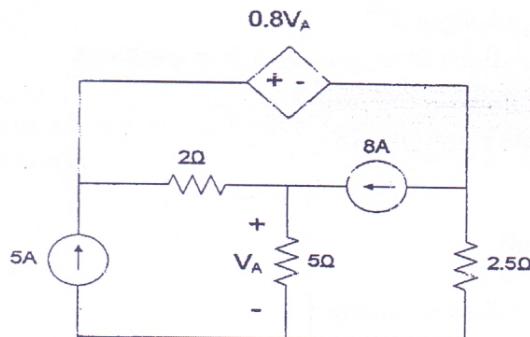- Q2 b) Use nodal analysis to find V_A and the power dissipated in 2.5Ω resistor in given 10 circuit.




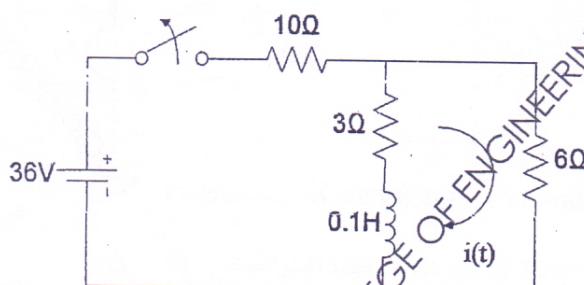- Q3a) In the network shown below, the switch is opened at $t=0$. Find $i(t)$ using laplace 06 transform.



- Q3b) Explain Millman's Theorem. 04

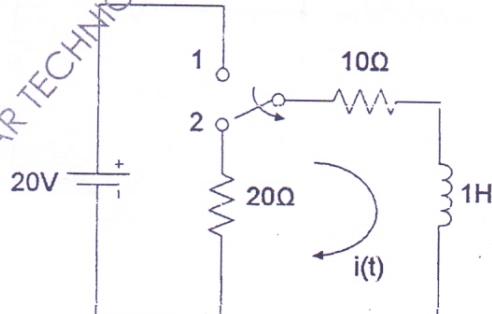
- Q3c) In the network shown in figure, the switch is changed from position 1 to 2 at $t=0$, 10 steady state condition having reached before switching. Find the values of $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t=0^+$.



[TURN OVER]


Q4 a) Find h_{12} , Z_{12} , Y_{12} and h_{22} for the given two port network.

10

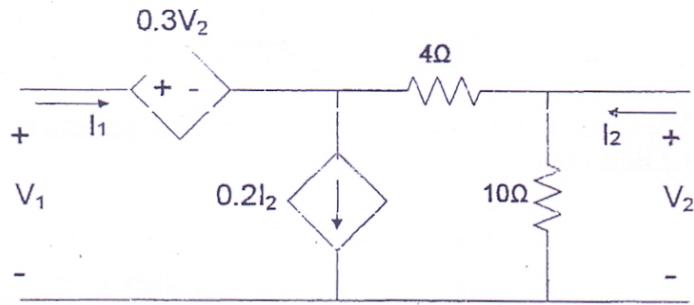



Q4 b) Determine the driving point impedance $\frac{V_1}{I_1}$, transfer impedance $\frac{V_2}{I_1}$ and voltage transfer ratio $\frac{V_2}{V_1}$ in the given network.

10

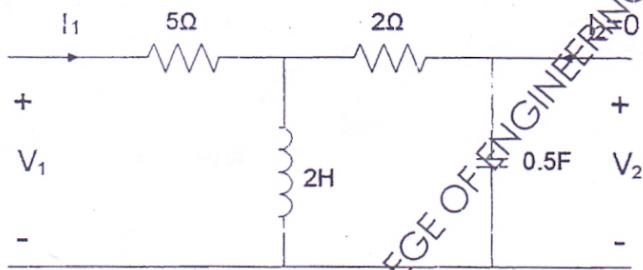

Q5 a) A network and pole zero diagram for a driving point impedance $Z(s)$ are shown in figures. Calculate the values of the parameters R, L, G and C if $Z(j0)=1$.

10

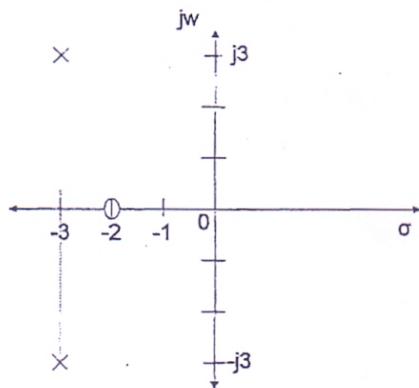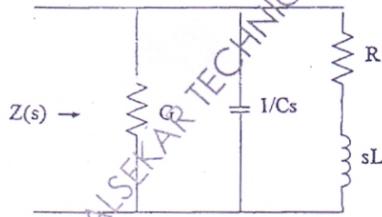


[TURN OVER]

FW-Con.12079-16.

Q5 b) Realize Cauer I and Cauer II forms of following impedance function. 10

$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$$

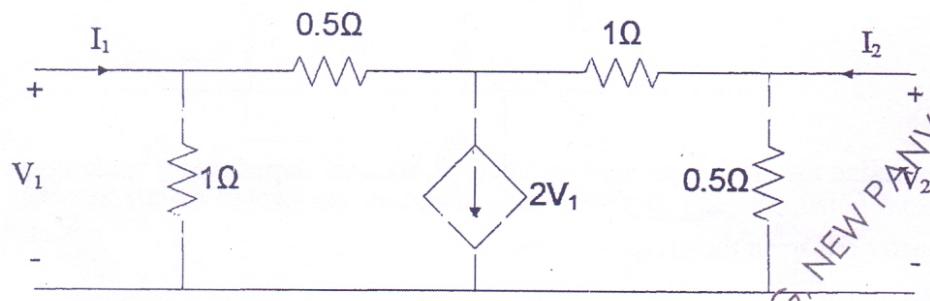Q6 a) Determine Y parameters for given circuit. Express Z parameter in terms of Y parameter and find values. 10



Q6 b) Calculate mesh currents in given circuit 10

