

QP Code :544002

(3 Hours)

[Total Marks: 80]

- N.B.:-** (1) Question No. **One** is compulsory.
 (2) **Attempt** any **Three** questions out of remaining **five** questions.
 (3) Assume suitable data wherever necessary.

Q 1. Answer any **Five** of the following :

- a. State important characteristic of IC 741 and compare their value with those of an ideal op-amp. 4
- b. Show how op-amp can be used to give output
 $V_o = (V_1 + V_2 + V_3)/3$
- c. Draw and explain the output waveforms of a differentiator for step and square input. 4
- d. Convert SR flip-flop to T flip-flop. 4
- e. Define: i> Propagation delay ii> Noise Margin 4
- f. Convert 4
 i> Convert gray to binary (101011)
 ii> $(11101101110.1001101)_2$ to hexadecimal equivalent.
- Q 2 a) What is instrumentation amplifier? State its advantages. State its applications and explain any one application in details. 10
- Q 2 b) Draw and explain the operation of first order high pass filter. Derive expression for voltage gain and explain its frequency response. 10
- Q 3 a) Draw schematic diagram of IC 555 as astable multivibrator. An IC 555 is configured to run in astable mode with $R_A = 4 \text{ k}\Omega$ $R_B = 4 \text{ k}\Omega$ and $C = 0.01 \text{ }\mu\text{F}$. Determine the frequency of the output and duty cycle. Also draw the waveform for output voltage and voltage across capacitor. 10
- Q 3 b) i> Explain op-amp as zero crossing detector. 10
 ii> Compare Schmitt trigger with comparator.
- Q 4 a) List the various methods of A/D conversion. Explain successive approximation type ADC with neat diagram. 10
- Q 4 b) Design a 3 bit synchronous up-counter using T flip-flop. 10
- Q5 Solve
- Q 5 a) Prove : $(X + XY)(X + \bar{X}Y)(X + Z) = X$ 5
- Q 5 b) Write short note on full adder. 5
- Q5 c) Implement Ex-OR gate using NAND gates. 5
- Q5 d) Implement the following Boolean expression using 8 : 1 multiplexer 5
 $f(A, B, C, D) = \sum m (2,4,5,7,10,14)$
- Q 6 a) Minimize the function using K map and realize using logic gates. 10
 $f(A, B, C, D) = \sum m(1,4,8,12,13,15) + d(3,14)$
- Q 6 b) i> Write a note on parity generators. 10
 ii> Compare between CMOS and TTL logic families.