

QP Code : 554602

(3 Hours)

[Total Marks : 100

- N.B.**
- (1) Question No. 1 is **compulsory**
 - (2) Answer any 4 of the remaining six questions
 - (3) Figure to be right indicate ull marks.
 - (4) Assume suitable data if necessary.

1. Solve any four of the following :-

- (a) Define following terms.
 - i) Fan in ii) Fan out
 - iii) Noise immunity iv) Propagation delay
 - (b) Draw all basic gates using NOR gate only.
 - (c) Enlist specification of practical Op-amp.
 - (d) Compare sequential and combinational logic.
 - (e) Compare series and parallel inverter.
2. (a) Draw and explain light dimmer circuit using diac and triac. 10
 - (b) Draw and explain Astable M.V. (multivibrator) using IC-555. 10
 3. (a) What is Chopper? Explain any one chopper circuit in detail. 10
 - (b) Explain with diagram 2-input totem pole logic family. 10
 4. (a) Draw neat block diagram of msp 430 controller and explain it. 10
 - (b) i) Explain subtractor using op-amp. 5
 - ii) Difference Ampr 5
 5. (a) Discuss in detail the over voltage protection of D.C. motor. 10
 - (b) Explain in detail rotate and shift instructions set of M.C.-8085 10
 6. (a) Explain with neat diagram active high pass filter. 10
 - (b) How speed of A.C. motor are controlled by frequency controlled method? Explain 10
 7. Write short notes on the following (Any Four): 20
 - (a) Summing amplifier
 - (b) De'morgans theorem
 - (c) Encoder and decoder
 - (d) V-I Characteristic of SCR
 - (e) J.K. Flip - Flop
 - (f) Parallel Adder

MUPD16025 ANJUMAN ISLAMIA KANSEKAR TECHNICAL CAMPUS, COLLEGE OF ENGINEERING, NEW PANVEL 06-06-2016 15:38:19