

QP Code : 28715

2

- (b) Draw circuit diagram of JFET small signal CS amplifier with self-bias and derive the expression for, small signal mid-band voltage gain, input impedance and output impedance. 10
5. (a) Explain the biasing techniques for D- MOSFET and E-MOSFET. 10
 (b) A JFET amplifier with voltage divider biasing circuit shown in figure 2 below has the following parameters: $I_{DSS} = 4\text{mA}$, $V_p = -2\text{V}$. The circuit parameters: $R_D = 1\text{k}\Omega$, $R_1 = 12\text{M}\Omega$, $I_{DQ} = 3.4\text{mA}$ and $V_{DS} = 10.5\text{V}$, $V_{DD} = 24\text{V}$. Determine the values of R_2 and R_s 10
6. (a) Design L section LC filter with full wave rectifier to meet following specifications: The DC output voltage $V_{DC} = 220\text{V}$, deliver $I_L = 70\text{mA} \pm 20\text{mA}$ to the resistive load, and required ripple factor is 0.04. Also find bleeder resistance if required. 12
 (b) Design a simple Zener voltage regulator to meet the following specifications: Output voltage $V_o = 6.8\text{V}$, Load current $I_{L_{max}} = 60\text{mA}$, $I_{L_{min}} = 0\text{mA}$, $I_{Z_{max}} = 100\text{mA}$, $I_{Z_{min}} = 5\text{mA}$, $P_Z = 440\text{mW}$ and Input voltage $V_i = 20\text{V to } 30\text{V}$. 8
7. Write a short note on following (any two) 20
 (a) SCR (Construction and Characteristics).
 (b) Bias compensation techniques.
 (c) E-MOSFET (Construction and Characteristics).

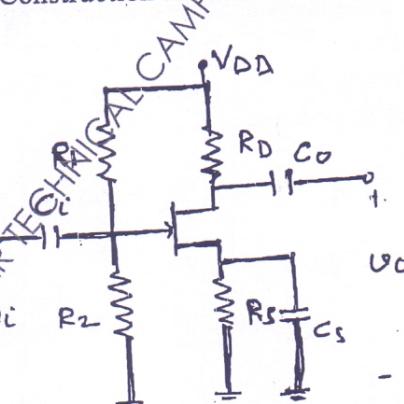


Fig.2

[TURN OVER

(3 Hours)

[Total Marks : 100]

- N.B. : (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions out of the remaining **six** questions.
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data whenever **necessary** but **justify** the same.

1. (a) Design single stage RC coupled C E amplifier for the following specifications: $A_v \geq 110$, $V_o = 3.5V$, $F_L = 20\text{Hz}$. Use $V_{cc} = 15V$. 15
 (b) For the above designed amplifier determine; voltage gain, input impedance, output impedance. 5

2. (a) Design single stage CS amplifier employing JFET type BFW11 for the following specifications; $A_v \geq 12$, $V_o = 4.2V$, $I_{DSQ} = 1.2\text{mA}$, $V_{cc} = 21V$ and $F_L = 20\text{Hz}$. 15
 (b) For the designed amplifier, determine what will be the maximum output voltage that can be obtained without distortion and corresponding input voltage that can be applied in the worst condition. 5

3. (a) Draw small signal hybrid parameter equivalent circuit for CE amplifier and define the same. What are the advantages of h-parameters? 10
 (b) Design voltage divider bias circuit for $I_E = 1.2\text{mA}$, $V_{ce} = 2.2V$, $R_E = 1k\Omega$ and $\beta = 60$. $S_{ICO} = 8$. Assume $V_{cc} = 9V$. 10

4. (a) For the amplifier shown in figure 1 analyze and determine 10
 (i) D C bias condition
 (ii) Small-signal voltage gain
 (iii) Input and output impedance.

The circuit parameters are:

$R_1 = 56k\Omega$, $R_2 = 12.2k\Omega$, $R_E = 0.4k\Omega$, $R_C = 2k\Omega$, $R_L = 10k\Omega$, $R_s = 0.5k$, $V_{cc} = 10V$
 and BJT parameters are $\beta = 100$, $V_{BE} = 0.7V$

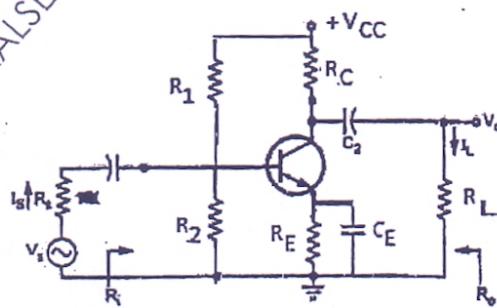


Fig.1

QP Code : 28715

3

ANVEL 18-05-2016 13:53:22

Transistor type	Pdmax @ 25°C	Icmax Watts, Amps	V _{ceo} Volts	V _{ces} (Sur)	V _{ces} Volts	V _{ceo} Volts	D.C. current min.	Gain	Small Signal gain	k _m	V _{beq} max.	θ _{av} °C/W	Derate above 25°C
	@ 25°C	d.c.	d.c.	d.c.	d.c.	d.c.	typ.	max.	min.	typ.	max.		
2N3055	115.5	15.0	1.1	100	50	70	1.7	200	20	50	15	120	1.8
ECN055	50.0	5.0	1.0	60	50	55	5	200	25	100	25	125	1.5
ECN149	30.0	4.0	1.0	50	40	—	8	150	30	50	110	33	1.2
ECN100	5.0	0.7	0.6	70	60	—	5	200	50	90	60	115	4.0
BC147A	0.25	0.1	0.25	50	45	—	6	125	115	180	230	280	0.9
2N525(PNP)	0.225	0.5	0.25	85	30	—	6	100	220	125	220	260	0.9
BC147B	0.25	0.1	0.25	50	45	—	6	125	35	65	45	—	—

3

BJT & PNP VIRTUAL CHARACTERISTICS

Transistor type	HFE	Hoe	Hie	oia	BRW, 11-12	BJT & PNP VIRTUAL CHARACTERISTICS
BC 147A	2.7 KΩ	184 U	15 x 10 ⁻⁴	0.4°C/mw	Npn Volts	0.0
2N 525 (PNP)	14 KΩ	254 U	3.2 x 10 ⁻⁴	—	Ios max., mA	-10
BC 147B	45 KΩ	304 U	2 x 10 ⁻⁴	0.4°C/mw	Ios typ., mA	7.0
					Ios min., mA	4.0

N-Channel JFET

Type	V _{ds max.} Volts	V _{gs max.} Volts	V _{ar max.} Volts	P _{d max.} @25°C	T _{j max.}	I _{ass}	R _s	—V _f Volts	I _f	Density above 25°C	θ _{fb}
2N3802	50	50	50	300 mW	175°C	2 mA	3000 μΩ	—	50 kΩ	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μΩ	—	50 kΩ	—	0.59°C/mW

JJT type	P _d max. @25°C	I _e max. @25°C	I _p max. peak pulse current max.	V _{ds} Volts max.	T _j max.	η	R _{ds} KΩ	—I _f max.	I _f typ.	I _{fb} min.	I _{fb} max.	I _{fb} θ _{fb}
2N2646	300mW	150mA	2Amp.	.30	35	0.56	0.75	4.7	7.0	9.4	5.0	4.0