


Q.P. Code : 544902

(3 Hours)

[Total Marks : 100

- N.B. :** (1) Question No.1 and 2 is compulsory.
 (2) Answer any **three** from remaining questions.
 (3) **Figures** to the **right** indicate **full marks**.
 (4) Assume suitable **data** if **required**.

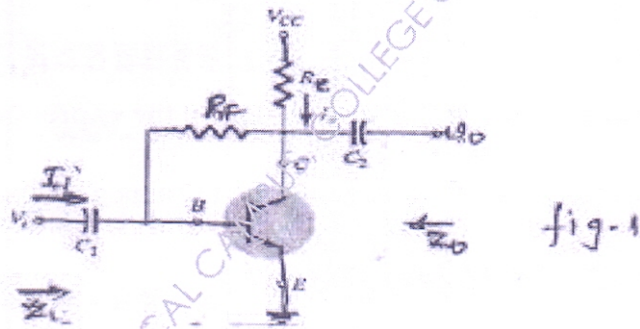
1. (a) Design a two stage R-C coupled BC547 amplifier for the following parameters: **15**
 $A_v \geq 900$, $V_O = 3V$, $F_L \leq 15Hz$.
 (b) For the above designed amplifier determine V_o (max), V_i (min) and R_{in} **5**
2. (a) Design large signal class A transformer coupled power amplifier to provide **15**
 $8W$ to 5Ω load
 (b) For designed circuit find efficiency at full load. **5**
3. (a) For the feedback amplifier shown in figure identify type of feedback and **12**
 calculate A_{vf} , R_{if} and R_{of} . $h_{fe} = 60$, $h_{ie} = 1.2K\Omega$, $h_{re} = h_{oe} = 0$. ($V_{CC} = 12V$,
 $R_c = 3 K\Omega$, $R_f = 50 K\Omega$)



- (b) Explain working of transistorised Schmitt trigger circuit with appropriate **8**
 waveforms.
4. (a) Derive the expression for frequency of oscillation and gain of Wein Bridge **10**
 oscillator.
 (b) Design RC phase shift oscillator using JFET BFW 11 for frequency of **10**
 oscillation 2 KHz.
5. (a) Explain with block diagram different topologies of negative Feedback **10**
 amplifier.

[TURN OVER

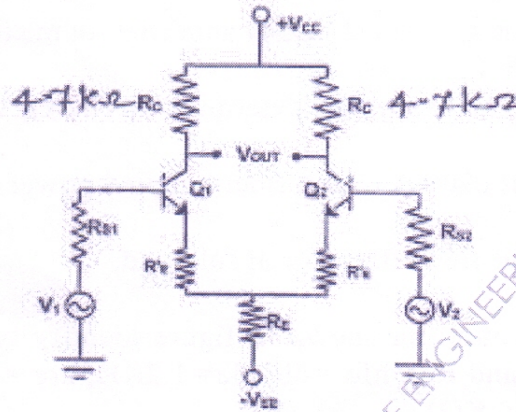- (b) For the circuit shown in figure 2 ($V_{BE} = 0.7 \text{ V}$, $\beta_{ac} = \beta_{dc} = 100$, $V_{CC} = 12 \text{ V}$, $V_{EE} = -12 \text{ V}$, $R_E = 10 \text{ K}\Omega$, $R_S = 100 \Omega$ and $R'_E = 100 \Omega$) Calculate i) Q point ii) A_d iii) A_c iv) CMRR 10



6. (a) Explain practical cascode amplifier and derive the expression for A_v , R_i and R_o 12
 (b) Explain why a voltage amplifier can not be used as good power Amplifier. 8
7. Write a short note on following. (any four) 20
- Voltage series feedback
 - Distortion in power amplifier
 - Darlington connection
 - Design of Heat Sink
 - Barkhausen's Criteria for oscillation

[TURN OVER

