
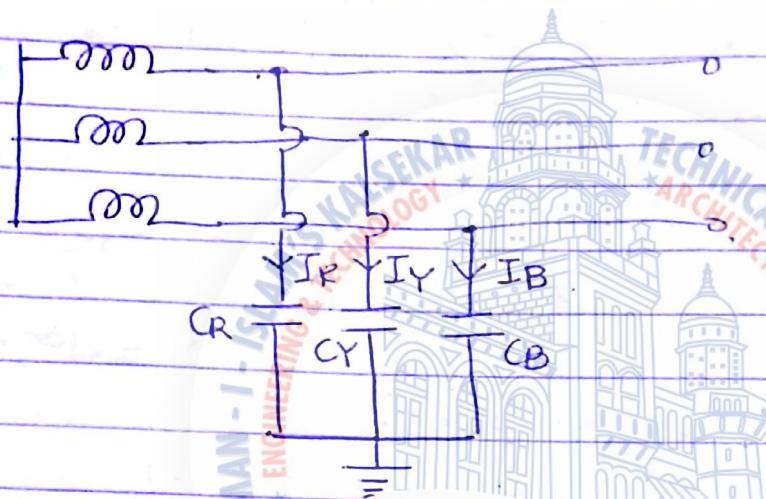


*Module 6:

- Ungrounded neutral system:

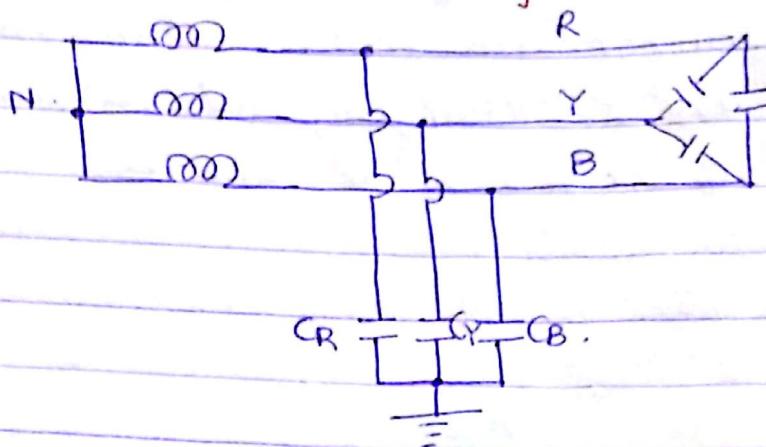


(a) Normal condition

→ line is perfectly transposed, so $C_R = C_Y = C_B$.



→ Phase voltages V_{RN} , V_{BN} , V_{YN} have same value,
 $\therefore I_R = I_Y = I_B = \frac{V_{ph}}{X_C}$ → line to neutral voltage.

→ I_R, I_Y, I_B lead V_{RN}, V_{BN}, V_{YN} by 90°

→ $I_R + I_Y + I_B = 0$.

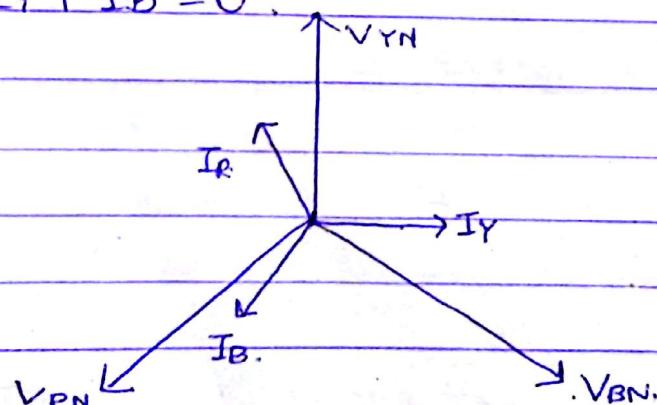

b) Abnormal Condition : (1-G fault)

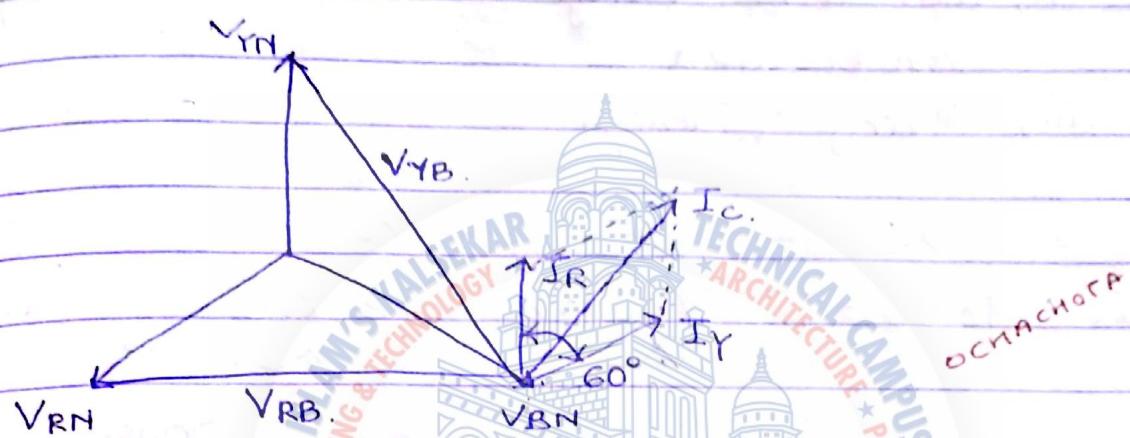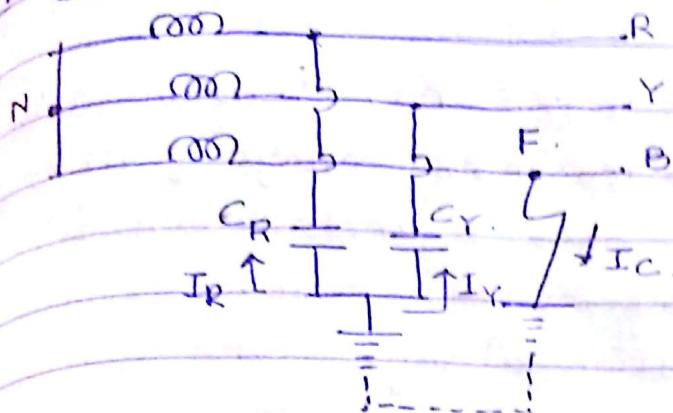

→ Consider single line to ground fault at pt Fin^c B driving

→ Voltages V_{BR} & V_{BY} are V_{BR} & V_{BY} .

→ Since I_R & I_Y are capacitive, I_R leads V_{BR} &

I_Y leads V_{BY} by 90°

$$\rightarrow I_C = I_R + I_Y$$

$$\rightarrow I_R = \frac{V_{BR}}{X_C} = \frac{\sqrt{3} V_{ph}}{X_C}$$

$$\rightarrow I_Y = \frac{V_{BY}}{X_C} = \frac{\sqrt{3} V_{ph}}{X_C}$$

$$\therefore I_R = I_Y = \frac{\sqrt{3} V_{ph}}{X_C}$$

$= \sqrt{3} \times$ per phase capacitive current under normal condition


$$\rightarrow I_C = I_R + I_Y$$

$$= 2 I_R \cos(60/2) = 2 I_R \cos 30 = 2 I_R \times \frac{\sqrt{3}}{2} = \sqrt{3} I_R$$

(magnitude of I_R & I_Y are equal & angle between them is 60°)

Prof. Tahoora Qureshi

* Measurement of Soil Resistivity

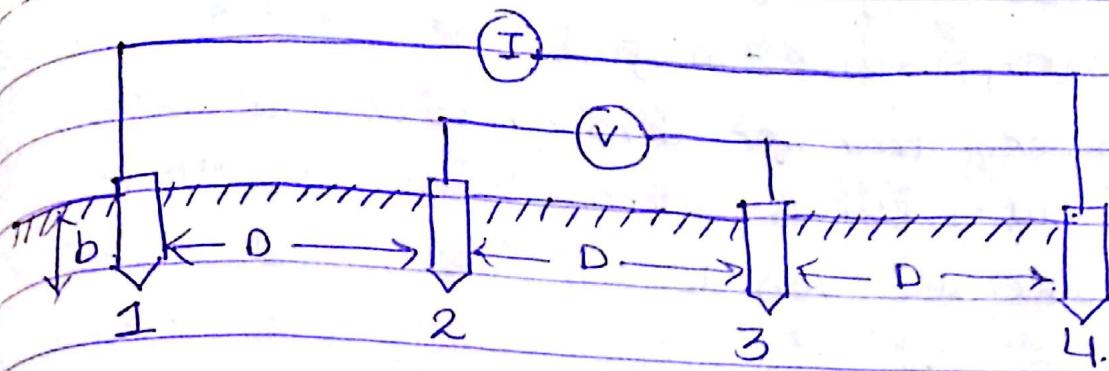

It is measured by 4 electrodes suggested by F. Wenner.

- 4 rods are driven inside earth at ^{equal} _{different} distances.

- 'I' known current is passed between electrode 1 & 2.
- 8 voltage is measured across rod 2 & 3.

- We know that $R = \frac{V}{I}$, ρ is deduced from following,

$$\rho = \frac{4\pi D V}{I} \cdot \frac{1 + 2D}{ND^2 + 4b^2} - \frac{2D}{\sqrt{4D^2 + 4b^2}}$$

$\rho \rightarrow$ Soil Resistivity

$D \rightarrow$ horizontal distance between 2 successive electrodes

$b \rightarrow$ depth of burial.

if,






$b \ll D$ then

$$\rho = 2\pi D V / I$$

- A number of readings with different values of spacing, & in different directions should be taken. Average value of ' ρ ' should then be used in design.

* Tower footing Resistance & Counterpoise.

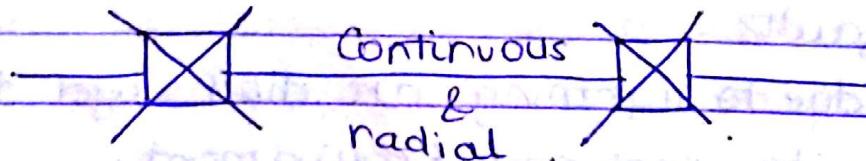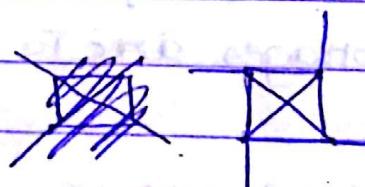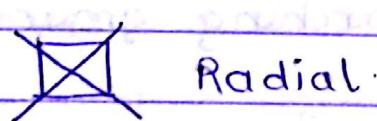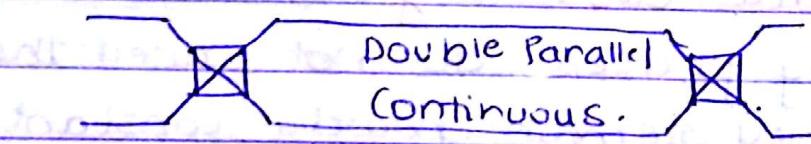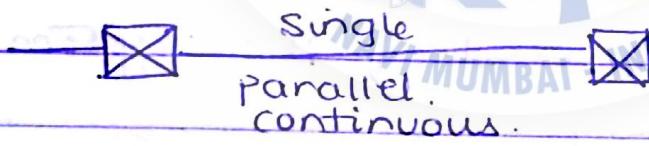
- (1) Effectiveness of ground wire depends on 'TFR'
- (2) TFR is the resistance offered by the tower footing to the dissipation of 'I'
- (3) 'V' depends on the 'R' $V = IR$
- (4) \therefore value of 'TFR' causes the voltage between earth & ground to be \downarrow . $\therefore \downarrow$ line insulation stress
- (5) $TFR = 20\text{-}\Omega$ (EHY line)
 $= 10\text{-}\Omega$ (HV lines)
- (6) It is normal practice to provide one or two driving rods at tower footing to achieve low 'R'
- (7) In soils of high resistivity (sandy soil, rocks) use of driving rods do not adequate \downarrow Resistance
- (8) In such cases counterpoise is used, tied to tower base run 'll' or at some angle to line.
- (9) Aim is to $\downarrow R$ by increasing area of contact of earth with grounding system.



* Neutral Grounding.

The process of connecting neutral point of a 3ϕ system to earth either directly or through some circuit element (Resistance, Reactance)

Neutral grounding.

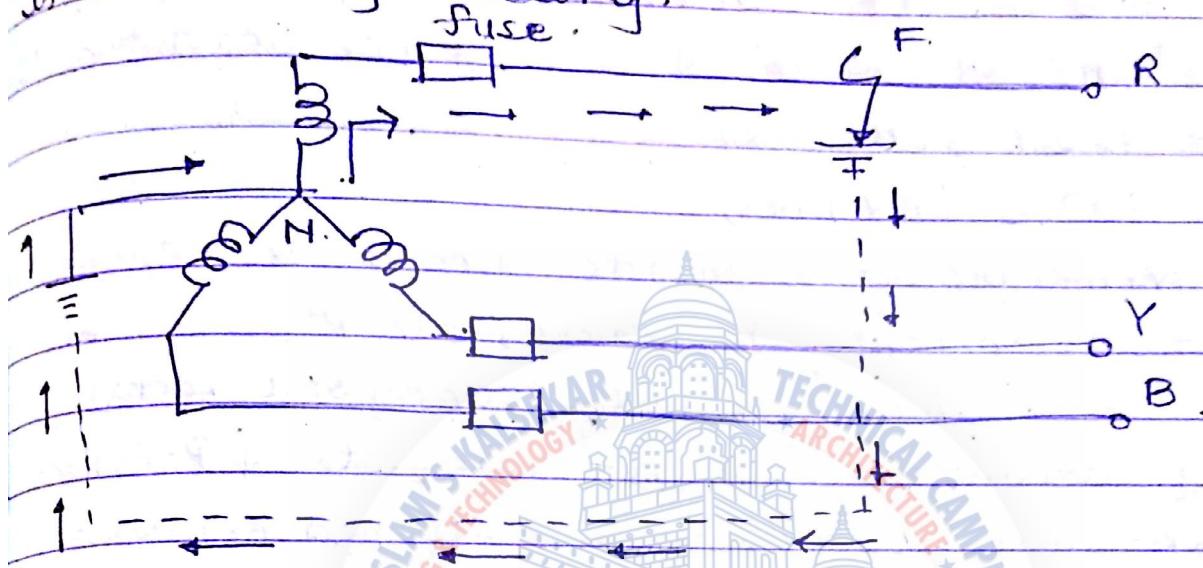

- During earth fault, the 'I' path is completed through the earthed neutral & the protective device (fuse, etc). operate to isolate the faulty conductor from the rest of the system


*Advantages of Neutral Grounding:

- (1) Voltages of healthy phases do not exceed their V_{ph} values ie they remain nearly constant.
- (2) The high voltages due to arching ground is eliminated.
- (3) Protective relays can be provided for protection against earth faults.
- (4) Overvoltages due to lightning are discharged to earth.
- (5) Greater safety to personnel & equipment.
- (6) Improved service reliability.
- (7) Operating & maintenance expenditures are reduced.


Methods of neutral Grounding

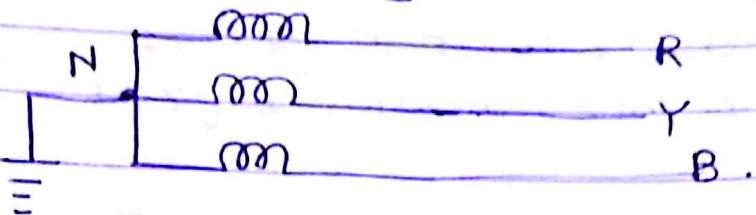(i) Solid or effective grounding:

When the neutral pt of a 3ϕ system (3ϕ generator, 3ϕ transformer) is directly connected to earth through a wire of negligible 'R' is called as solid grounding or effective grounding.



Advantages:

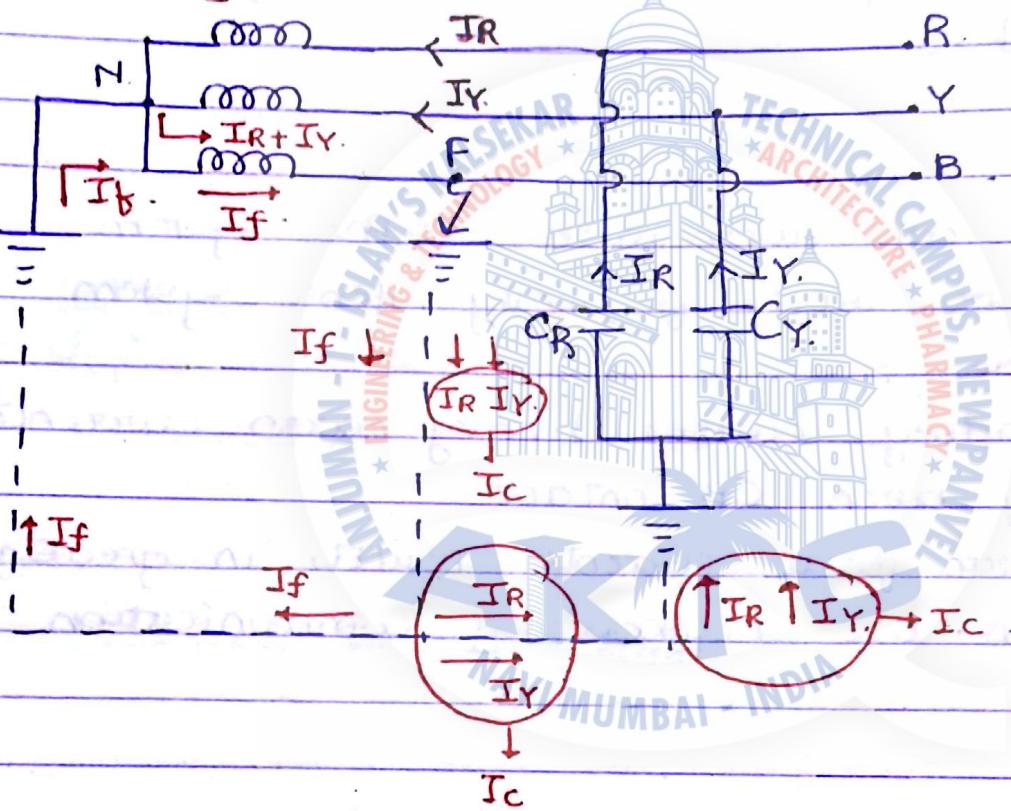

- (1) Neutral is effectively earthed at ground potential.
- (2) Consider (L-G) fault in 'B'. The capacitive currents flowing in healthy phases are I_R & I_Y . Total capacitive current is I_C . Plus there is I_F supplied by the power source.

Path of I_F : Point F - Ground - Neutral pt — winding — fault

Path of I_C = fault pt F - Ground - Capacitance - line
R & Y - neutral - ~~Ground~~ - ~~Neutral~~ phase B

Respective

Prof. Tahoor Qureshi

Path of I_C is capacitive & I_B is inductive. Two currents are in phase opposition & cancel each other. \therefore No arcing ground & no overvoltages.

- (3) Earth fault causes the faulted phase voltage to go zero &. But with this arrangement, the other two healthy phases will have the same voltage level because neutral is fixed at zero potential.
- (4) Earth faults frequently occur. Earth fault relay can be provided with this type of arrangement.

Disadvantages:

- (1) Most faults are earth faults so the system has to bear shocks frequently. Hence system goes unstable.
- (2) Solid grounding causes heavy earth currents which may burn CB contact.
- (3) Increased earth fault currents results in greater interference in the neighbouring communication lines.

Applications:


- (1) used where ' Z ' of ct is high to keep ' I ' \downarrow .
- (2) voltages upto 33KV. - Power Capacity 5000 kVA.

(2) Resistance Grounding

- When neutral point of 3ϕ system (eg. 3ϕ generator, 3ϕ Xmer) is connected to earth through resistor, it is called resistance grounding.
- Value of ' R ' should not be too low or too high.
 - too low → acts like solid grounding which ↑ ground currents.
 - too high → acts like ungrounded system,
- R is so selected that it limits the earth fault currents to 2 times the normal full load current.

Advantages:

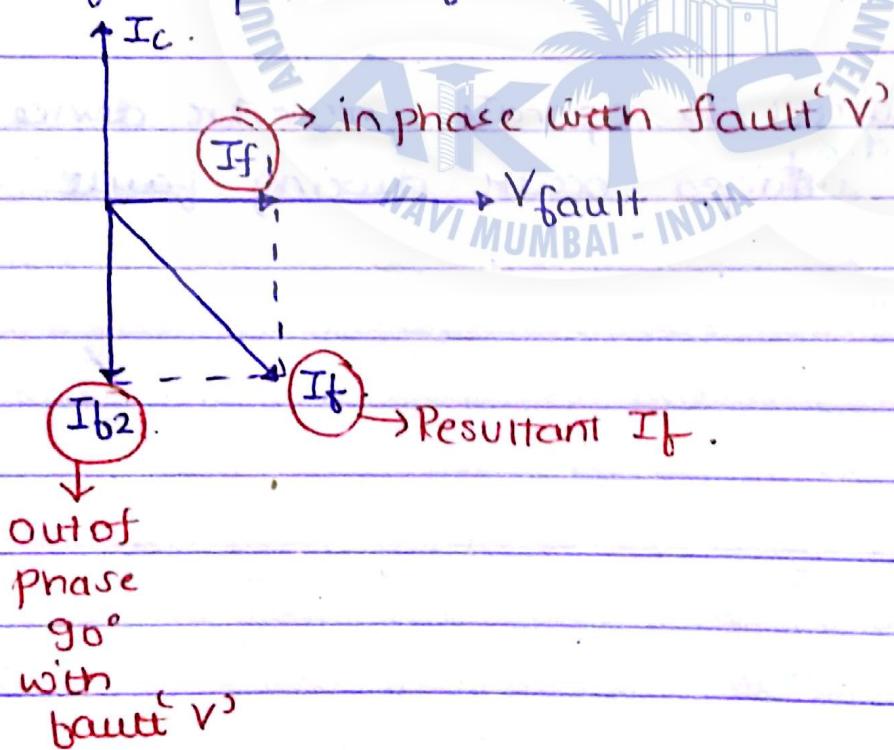- (1) Suppose ($E - \theta$) fault occurs on B. We know If is inductive & it lags faulted voltage by 90° angle. depending upon value of ' R ' & ' X ' of system upto fault point. If can be resolved as.



So if $I_{b2} = I_c$ by adjusting ' R ' system can be made to behave like solidly grounded system

(2) Earth fault current is \downarrow due to 'R' $\therefore \downarrow$ interference with communication ckt.


(3) Improves stability of the system.

Disadvantages:

(1) Costlier.

(2) Large energy is generated in 'R' which has to be dissipated.

* Reactance Grounding:

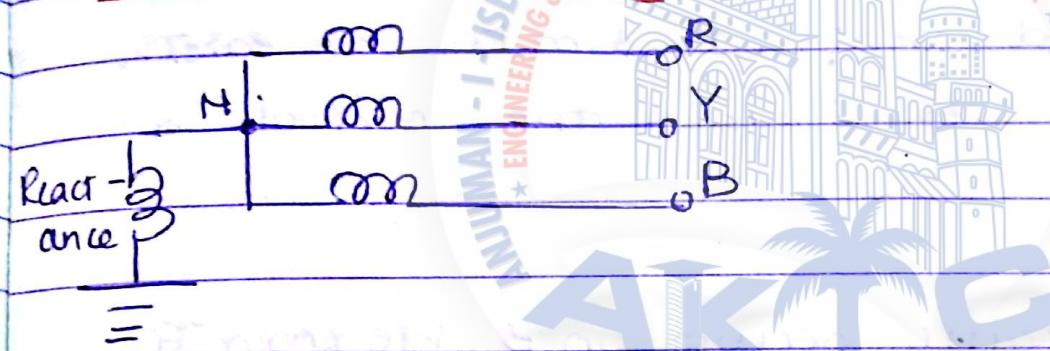

→ Same as that of Resistance Grounding. \downarrow Earth fault current & by adjusting R the current can be limited.

Disadvantages:

- (1) Fault 'I' required to operate protective device is \uparrow than 'R' grounding.
- (2) High transient voltages occur during fault condition.