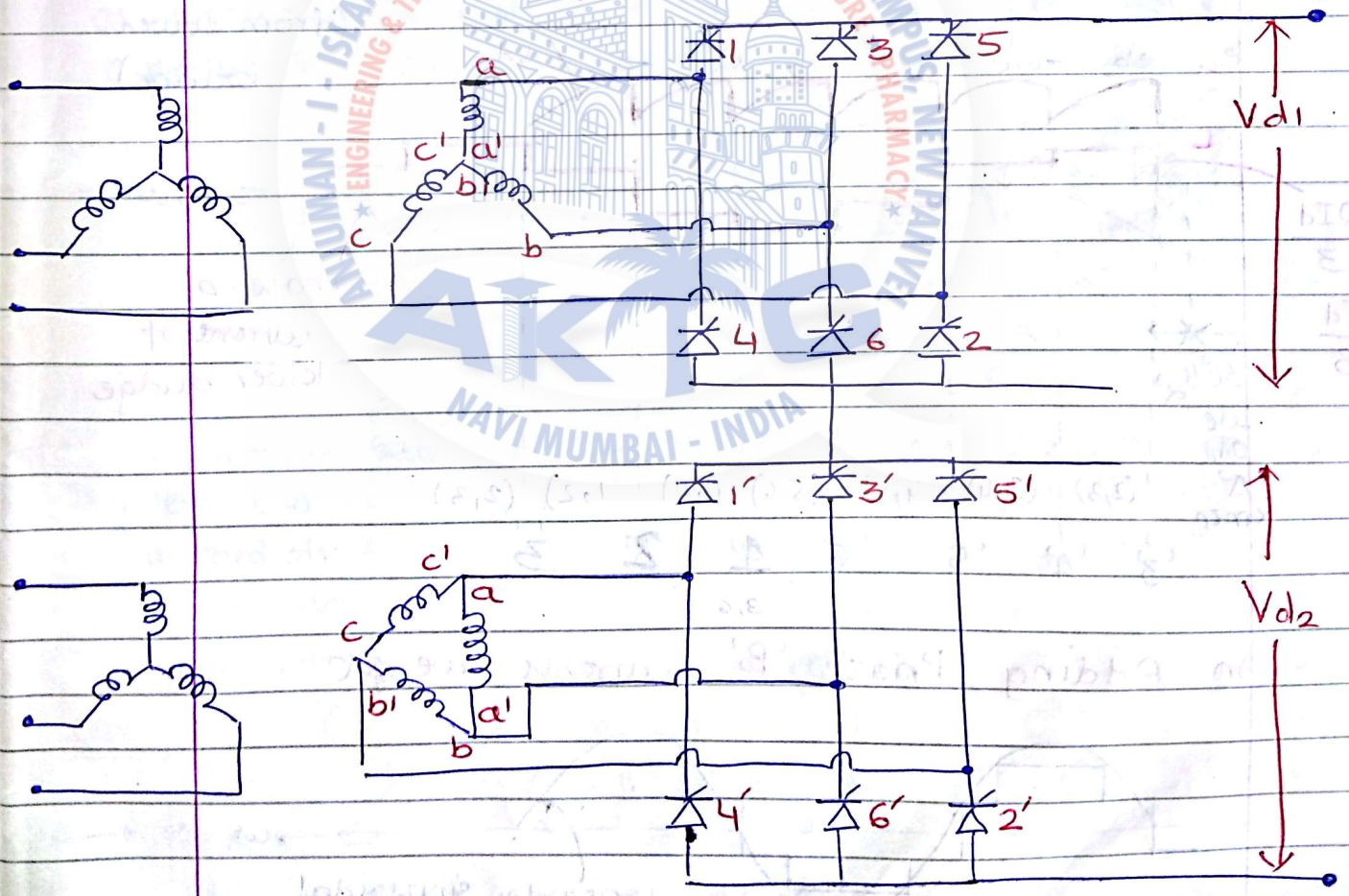




* 12 pulse Bridge Converter.

- Two 6 pulse converter is the best option
- One 6 pulse converter is connected with $\lambda-\lambda$ Xmer and the second one with $\lambda-\Delta$ transformer
- This provides 30° phase shift & thus 12 pulses in one cycle.
- It reduces harmonic current injection in the ac system & less harmonic in the dc voltage.
- for $u=0$ there will always be 4 valves conducting
- for $u>0$ following modes are possible.




Page No.
 Date: / /

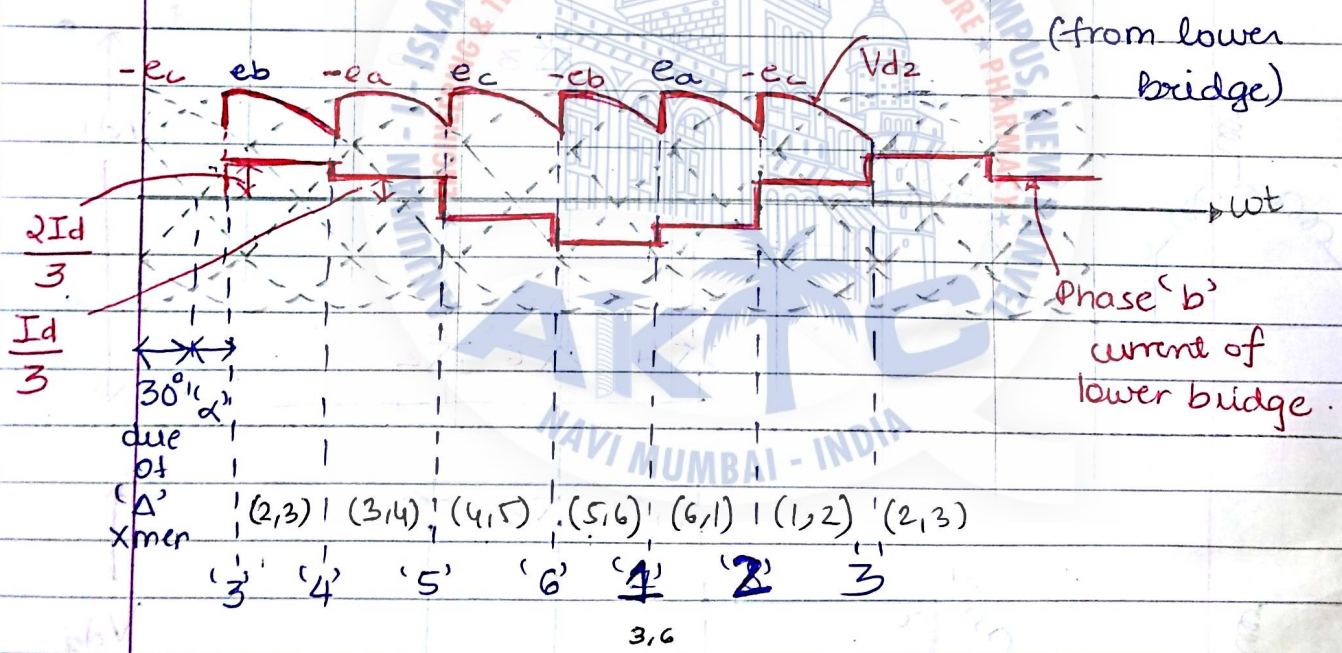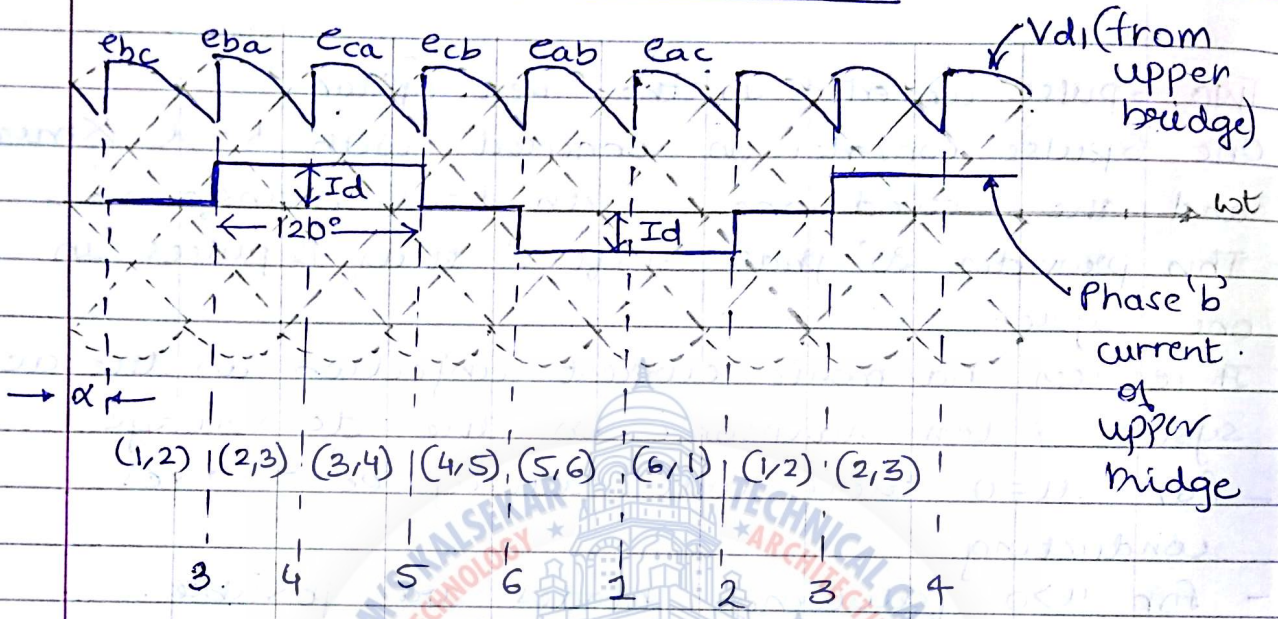Consider;
 $\alpha = 15^\circ$; $\mu = 0^\circ$




→ On Adding Phase 'B' currents we get

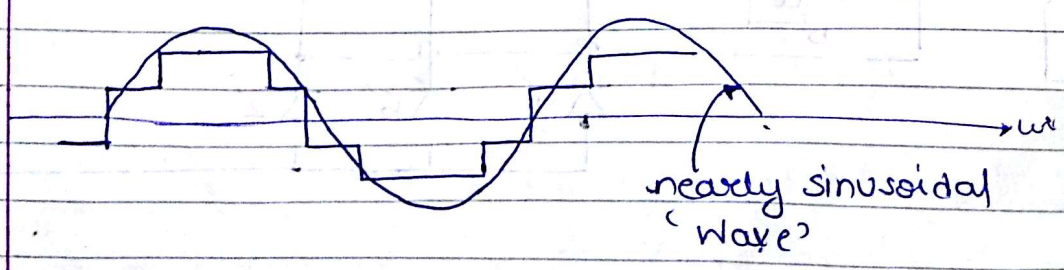

(lec 12)
 Page No. 39
 Date: / /

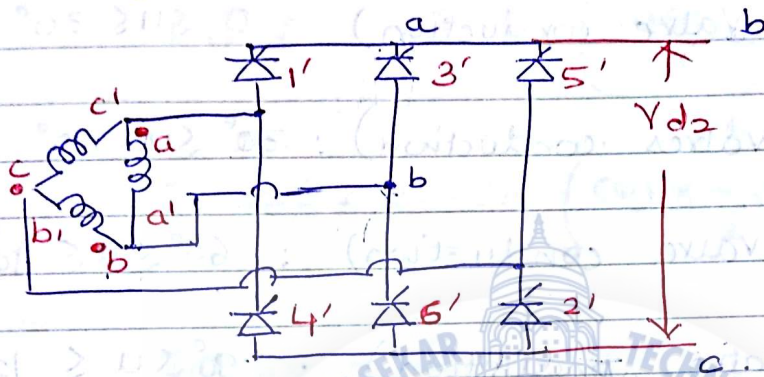- To calculate 'Vd2', to draw waveform just consider 2nd half of the converter



CASE I (2 & 3 conduct)

- When 3' conducts; voltage at cathode of 3' is e_a & at anode is e_a but we take voltage from anode to cathode so $-e_a$ appears across valve 3'

$\therefore e_{ba} = -e_a$ (from a' to a it is -ve polarity)
 ↓
 consider dotted polarity

\therefore o/p voltage $e_{bc} = e_b$ (from b to b' it is +ve polarity)
 (Here 1 is turned off & 2 & 3 are conducting)

CASE II : (3 & 4 conduct)

→ $e_{ca} = e_c$

→ o/p voltage $e_{ba} = -e_a$

Page No.

Date: / /

* Modes of operation

- Mode 1 (4/5 Valve conduction) : $0 \leq u \leq 30^\circ$
- Mode 2 (5/6 valves conduction) : $30^\circ \leq u \leq 60^\circ$
- Mode 3 (6/7 valve conduction) : $60^\circ \leq u \leq 90^\circ$
- Mode 4 (7/8 Valve conduction) : $90^\circ \leq u \leq 120^\circ$

* Relationship between ac & dc quantities

We know that ;

$$V_d = V_{do} \left(\frac{\cos \alpha + \cos \delta}{2} \right) \quad \text{--- (1)}$$

$$= \frac{3\sqrt{3}}{\pi} E_m \left(\frac{\cos \alpha + \cos \delta}{2} \right)$$

→ for lossless converter;

$$P_{ac} = P_{dc}$$

$$\bullet P_{ac} = \sqrt{3} E_L I_1 \cos \phi$$

$$\bullet P_{dc} = V_d I_d = \frac{3\sqrt{3} E_m}{\pi} \left(\frac{\cos \alpha + \cos \delta}{2} \right) (I_d)$$

$$= \frac{3\sqrt{3}}{\pi} \left(\frac{\sqrt{2}}{\sqrt{3}} \frac{E_L}{\sqrt{3}} \right) \left(\frac{\cos \alpha + \cos \delta}{2} \right) (I_d)$$

Page No.

Date: / /

$$\sqrt{3} E_L I_1 \cos \phi = \frac{3\sqrt{2}}{\pi} E_L \left(\frac{\cos \alpha + \cos \delta}{2} \right) I_d$$

$$\therefore I_1 \cos \phi = \frac{3\sqrt{2}}{\sqrt{3} \pi} \left(\frac{\cos \alpha + \cos \delta}{2} \right) I_d$$

$$\therefore I_1 \cos \phi = \frac{\sqrt{6}}{\pi} I_d \left(\frac{\cos \alpha + \cos \delta}{2} \right)$$

With ; $\mu = 0$

$$I_1 \cos \phi = \frac{\sqrt{6}}{\pi} I_d \left(\frac{\cos \alpha + \cos (\alpha + 0)}{2} \right)$$

$$I_1 \cos \phi = \frac{\sqrt{6}}{\pi} I_d \left(\frac{2 \cos \alpha}{2} \right)$$

$$I_1 \cos \phi = \frac{\sqrt{6}}{\pi} I_d \cos \alpha$$

$$\therefore \boxed{I_1 = \frac{\sqrt{6}}{\pi} I_d} \dots \dots (\cos \phi = \cos \alpha)$$

→ Now we can say that;

$$\cos \phi \cong \frac{\cos \alpha + \cos \delta}{2}$$

$$\therefore V_d \cong V_{d0} \cos \phi \quad (\text{from (1)})$$

$$\therefore \cos \phi \cong \frac{V_d}{V_{d0}} \cong \frac{V_{d0} \cos \alpha - R_c I_d}{V_{d0}}$$

$$\boxed{\cos \phi \cong \frac{V_{d0} \cos \alpha - R_c I_d}{V_{d0}}}$$

Page No.


Date: / /

* Relationship between AC & DC Quantities, with multiple bridges:

let;

B = no of Bridges in series

T = Transformer ratio.

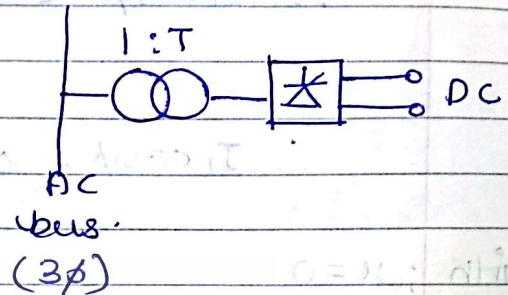

→ The ideal no load voltage for multiple bridge;

$$V_{d0} = \frac{3\sqrt{3} E_m}{\pi} (B)(T)$$

$$= \frac{3\sqrt{3}}{\pi} \times \frac{\sqrt{2}}{\sqrt{3}} E_{LL} (B)(T)$$

$$= \frac{3\sqrt{2}}{\pi} E_{LL} (B)(T)$$

→ Voltage drop/bridge = $\left(\frac{3\omega L}{\pi}\right) I_d$

∴ for B bridges = $B \left(\frac{3\omega L}{\pi}\right) I_d$

⇒ Therefore the dc voltage is

$$V_d = V_{d0} \cos \alpha - I_d (B) \left(\frac{3\omega L}{\pi}\right)$$

or

$$V_d = V_{d0} \cos \gamma - I_d (B) \left(\frac{3\omega L}{\pi}\right)$$

→ Also; in terms of P.f;
 $V_d \cong V_{do} \cos \phi$.

Page No.

Date: / /

→ The average dc/P voltage of R bridge is twice of the 6 pulse bridge converter.

→ Also;

$$I_1 = \frac{\sqrt{6}}{\pi} (B) I_d.$$

$$V_d = \frac{3\sqrt{3}}{\pi} E \cos \alpha$$

