

Knowledge Resource & Relay Centre (KRRC)

AIKTC/KRRC/SoET/ACKN/QUES/2017-18/

Date: _____

School: SoET-CBSGS Branch: ELECT. ENGG. SEM: III

To,
Exam Controller,
AIKTC, New Panvel.

Dear Sir/Madam,

Received with thanks the following [✓]Semester/[✓]Unit Test-I/Unit Test-II (Reg./ATKT) question papers from your exam cell:

Sr. No.	Subject Name	Subject Code	Format		No. of Copies
			SC	HC	
1	Applied Mathematics- III	EEC301		✓	02
2	Electronic Devices & Circuits	EEC302		✓	02
3	Conventional And Non-Conventional Power Generation	EEC303			
4	Electrical Networks	EEC304		✓	02
5	Electrical And Electronic Measurement	EEC305			

Note: SC – Softcopy, HC - Hardcopy

(Shaheen Ansari)
Librarian, AIKTC

37

28/11/18

Q. P. Code : 37078

(3 Hours)

[Total marks : 80

- Note :-
- 1) Question number 1 is compulsory.
 - 2) Attempt any three questions from the remaining five questions.
 - 3) Figures to the right indicate full marks.

- Q.1
- a) Evaluate $\int_0^{\infty} e^{-2t} \sin^2 2t dt.$ 05
 - b) Find an analytic function $f(z) = u + iv$ where $u + v = e^x (\cos y + \sin y).$ 05
 - c) Obtain Fourier series of $x \cos x$ in $(-\pi, \pi).$ 05
 - d) Evaluate $\int_C \vec{F} \cdot d\vec{r}$ where $\vec{F} = x^2 i + xy j$ from $(0, 0)$ to $(1, 1)$ along the parabola $y^2 = x.$ 05
- Q.2
- a) Find half-range cosine series for $f(x) = e^x, 0 < x < 1.$ 06
 - b) Prove that $\vec{F} = (x + 2y + az) i + (bx - 3y - z) j + (4x + cy + 2z) k$ is solenoidal and determine the constants a, b, c if \vec{F} is irrotational. 06
 - c) Prove that $w = i \left(\frac{z-i}{z+i} \right)$ maps upper half of the z -plane into the interior of the unit circle in the w -plane. 08
- Q. 3
- a) Prove that $J_n(x)$ is an even function if n is even integer and is an odd function if n is odd integer. 06
 - b) Find the inverse Laplace transform of $\frac{s^2+2s+3}{(s^2+2s+5)(s^2+2s+2)}$ 06
 - c) Obtain the complex form of Fourier series for $f(x) = e^{ax}$ in $(0, a).$ 08
- Q. 4
- a) Prove that $\nabla f(r) = f'(r) \frac{\vec{r}}{r}$ and hence, find f if $\nabla f = 2r^4 \vec{r}.$ 06
 - b) Prove that $4J''_n(x) = J_{n-2}(x) - 2J_n(x) + J_{n+2}(x).$ 06

- c)
- (i) Find the Laplace transform of $e^{4t} \sin^3 t$. 04
- (ii) Find the Laplace transform of $t \sqrt{1 + \sin t}$. 04
- Q. 5 a) Prove that $\int x \cdot J_{\frac{2}{3}}(x^{\frac{3}{2}}) dx = -\frac{2}{3} x^{-\frac{1}{2}} J_{-\frac{1}{3}}(x^{\frac{3}{2}})$. 06
- b) Find p if $f(z) = r^2 \cos 2\theta + i r^2 \sin p\theta$ is analytic. 06
- c) If $f(x) = \begin{cases} \pi x, & 0 \leq x \leq 1 \\ \pi(2-x), & 1 \leq x \leq 2 \end{cases}$ with period 2, show that 08
- $$f(x) = \frac{\pi}{2} - \frac{4}{\pi} \sum_{n=0}^{\infty} \frac{1}{(2n+1)^2} \cos(2n+1)\pi x.$$
- Q. 6 a) Show that the set of functions $\cos nx$, $n = 1, 2, 3, \dots$ is orthogonal on $(0, 2\pi)$. 06
- b) Use Stoke's theorem to evaluate $\int_C \vec{F} \cdot d\vec{r}$ where 06
- $$\vec{F} = (2x - y) i - yz^2 j - y^2 z k$$
- and S is the surface of hemisphere $x^2 + y^2 + z^2 = a^2$ lying above the xy -plane.
- c) Use Laplace transform to solve 08
- $$\frac{d^2 y}{dt^2} + y = t \text{ with } y(0) = 1, y'(0) = 0.$$

20/11/18

SE-SEM III - Electrical - CBQS

(3 Hours)

[Total Marks:80]

- N.B.** (1) Question no.1 is compulsory.
 (2) Attempt any three questions from Question No. 2 to 6
 (3) Make any suitable assumption wherever required.
- Q.1** Answer any four.
- (a) Give the working principle of Photodiode with its application 5M
 (b) Explain the various bias compensation techniques in a BJT. 5M
 (c) Determine the operating point parameters I_{CQ} and V_{CEQ} for the Fixed Bias circuit. 5M
 Assume $\beta = 100$ and $V_{BE} = 0.7V$, $R_C = 3k\Omega$, $R_B = 470K\Omega$, $V_{CC} = 12V$.
 (d) Explain the Effect of negative feedback on voltage gain, input impedance, output impedance, and bandwidth. 5M
 (e) State and Explain Barkhausen's criteria for sustained oscillations. 5M
- Q.2** (a) Analyze Voltage Shunt Negative feedback Amplifier with respect to Input Resistance, Output Resistance and Voltage gain. 10M
 (b) Derive expression for voltage gain, input impedance and output impedance of a CS amplifier. 10M
- Q.3** (a) Draw FWR with C filter and describe the circuit operation with waveform. 10M
 Compare the performance of C, L, LC filters
 (b) Explain the Colpitts Oscillator in detail with circuit diagram and equations. 10M
- Q.4** (a) Explain Crystal oscillator with the help of suitable diagram and waveforms. 10M
 (b) Give the DC and AC analysis of Dual Input Unbalanced output differential Amplifier 10M
- Q.5** (a) Explain the Construction and Working of E-MOSFET with the help of its characteristics. 10M
 (b) Explain various types of coupling and their effect on the performance of BJT. 10M
- Q.6** Write short note on following. (Any TWO) 20M
 (a) Zener Diode as voltage Regulator.
 (b) Hartley Oscillator.
 (c) re-model used in Transistor

2

17/12/18

(Time: 3 Hours)


[Total marks: 80]

- N.B:- (1) Question 1 is compulsory
 (2) Solve any **three** questions from remaining **five** questions.
 (3) Figures to the right indicate **full** marks.
 (4) Assume suitable data if necessary.


Q1 Attempt the following 20

- a) Derive the response on unit step signal in case of series RL circuit.
- b) Explain Millman's theorem.
- c) What do you understand by tree, link and twig. Explain with example
- d) Test whether $P(s) = s^5 + 2s^4 + 4s^3 + 6s^2 + 2s + 5$ is hurwitz

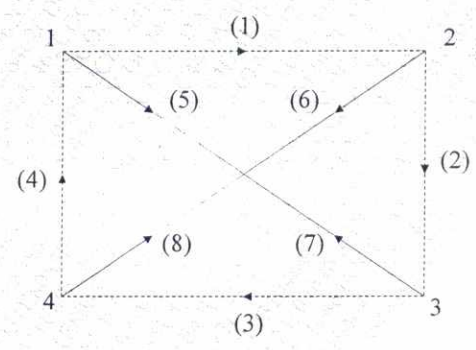
Q2 a) For a given graph, write incidence matrix, f-cutset and f-tieset matrix. 10



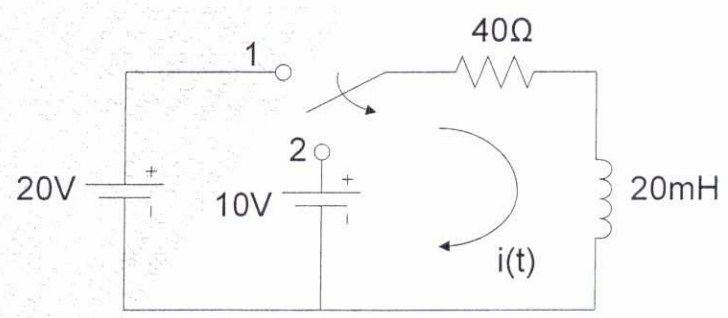
Q2 b) The network shown is under steady state with switch at position 1. At t=0, switch is moved to position 2. Find i(t). 10



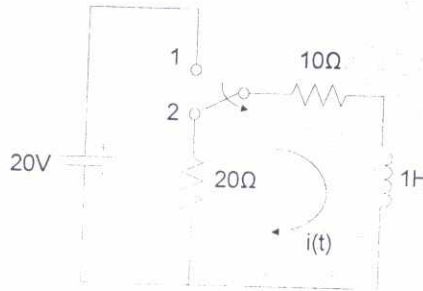
- Q3 In the network shown in figure, the switch is changed from position 1 to 2 at $t=0$, steady state condition having reached before switching. Find the values of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$. 10



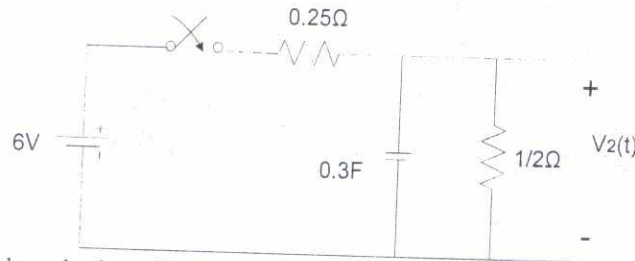
- Q3 In the network shown, the switch is open for a long time and at $t=0$, it is closed. Determine $V_2(t)$. 10



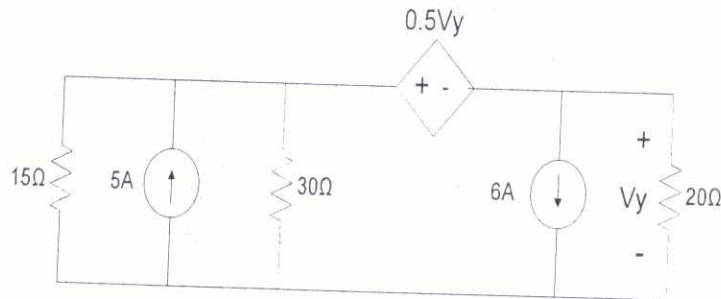- Q4 Use nodal analysis to find V_y in the given circuit. 10



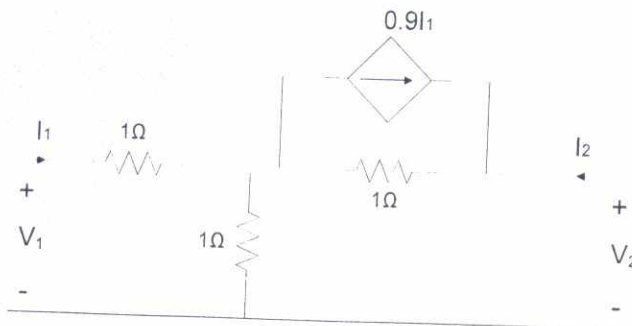- Q4 Find the Z parameters for the network shown. Hence find h parameters. 10




- Q5 a) For a series RLC circuit $H=1$, for its driving point admittance. Pole diagram is given in figure. Find values of R, L and C. 10



- Q5 b) Realize Foster I and Foster II for following impedance function 10

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$

- Q6 a) Find V_0 in the network shown 10

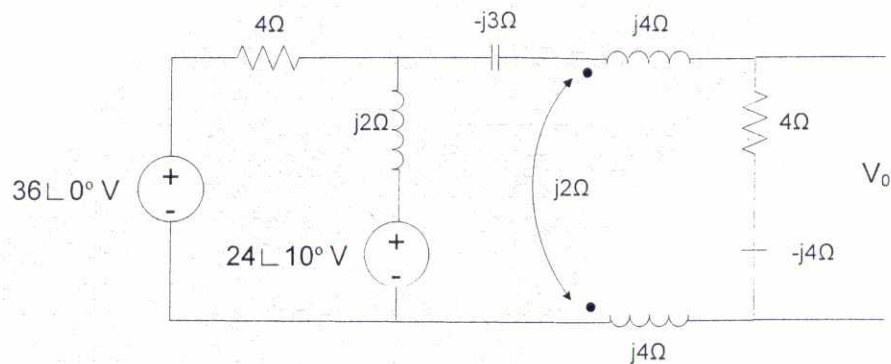

- Q6 b) Find h_{12} , Z_{12} , Y_{12} and h_{22} for the given two port network . 10

