



AIKTC/KRRC/SoET/ACKN/QUES/2019-20/

Date: 15/01/2020School: SoET-CBSGSBranch: EXTC ENGG.SEM: III

To,
Exam Controller,
AIKTC, New Panvel.

Dear Sir/Madam,

Received with thanks the following Semester/Unit Test-I/Unit Test-II (Reg./ATKT) question papers from your exam cell:

Sr. No.	Subject Name	Subject Code	Format		No. of Copies
			SC	HC	
1	Applied Mathematics- III	ETS301		✓	02
2	Analog Electronics - I	ETC302		-	-
3	Digital Electronics	ETC303		-	-
4	Circuits & Transmission Lines	ETC304		✓	02
5	Electronics Instruments & Measurement	ETC305		-	-

Note: SC - Softcopy, HC - Hardcopy

(Shaheen Ansari)
Librarian, AIKTC

9+2

18/11/19

(3 Hours)

[Total Marks : 80]

- Note:-
- 1) Question number 1 is compulsory.
 - 2) Attempt any **three** questions from the remaining **five** questions
 - 3) **Figures** to the **right** indicate **full** marks.

- Q.1 a) Find the Laplace transform of $\cos t \cos 2t \cos 3t$ 05
- b) Show that the set of functions $\cos nx, n=1,2,3,\dots$ is orthogonal over $(0, 2\pi)$ 05
- c) Prove that $f(z) = (x^3 - 3xy^2 + 2xy) + i(3x^2y - x^2 + y^2 - y^3)$ is analytic and find $f'(z)$ in terms of z . 05
- d) Find the directional derivative of $\phi = x^2 + y^2 + z^2$ in the direction of the line $\frac{x}{3} = \frac{y}{4} = \frac{z}{5}$ at $(1, 2, 3)$ 05
- Q.2 a) Find the fourier series for $f(x) = x^2$ in $(0, 2\pi)$ 06
- b) Show that the vector $\vec{F} = (x^2 + xy^2)\mathbf{i} + (y^2 + x^2y)\mathbf{j}$ is irrotational and find its scalar potential 06
- c) Prove that the transformation $w = \frac{1}{z+i}$ transforms real axis of z - plane into a circle of w - plane 08
- Q.3 a) Using convolution theorem, find inverse Laplace transform of $\frac{s^2}{(s^2+2)^2}$. 06
- b) Prove that $J_{5/2}(x) = \sqrt{\frac{2}{\pi x}} \left(\frac{3-x^2}{x^2} \sin x - \frac{3}{x} \cos x \right)$ 06
- c) Find half range cosine series for $f(x) = x(\pi - x), 0 < x < \pi$. Hence show that $\sum_{n=1}^{\infty} \frac{1}{n^4} = \frac{\pi^4}{90}$ 08

- Q.4 a) Evaluate by Green's theorem $\int_C (e^{x^2} - xy) dx - (y^2 - ax) dy$ where C is the circle $x^2 + y^2 = a^2$. 06
- b) Prove that $2 J_0''(x) = J_2(x) - J_0(x)$. 06
- c) i) Evaluate $\int_0^{\infty} \frac{e^{-t} - e^{-3t}}{t} dt$ 08
- ii) Find Laplace transform of $t \sqrt{1 + \sin t}$
- Q.5 a) Find the orthogonal trajectory of the family of curves $x^5 y - xy^3 = c$. 06
- b) Prove that $\int x \cdot J_{2/3}(x^{3/2}) dx = -\frac{2}{3} x^{-1/2} J_{-1/3}(x^{3/2})$. 06
- c) Obtain complex form of Fourier Series for $f(x) = e^{2x}$ in $(0, 2)$. 08
- Q.6 a) Use Stoke's Theorem to evaluate $\int_C \vec{F} \cdot d\vec{r}$ where $\vec{F} = yz \mathbf{i} + zx \mathbf{j} + xy \mathbf{k}$ and C is the boundary of the circle $x^2 + y^2 + z^2 = 1$ and $z = 0$. 06
- b) Find the Fourier integral representation for 06
- $$f(x) = \begin{cases} e^{ax} & , x \leq 0, a > 0 \\ e^{-ax} & , x \geq 0, a > 0 \end{cases}$$
- Hence show that $\int_0^{\infty} \frac{\cos wx}{w^2 + a^2} dx = \frac{\pi}{2a} e^{-ax}, x > 0, a > 0$
- c) Solve using Laplace transform $(D^2 + 2D + 5)y = e^t \sin t$ where $y(0) = 0, y'(0) = 1$. 08

Paper / Subject Code: 49605 / CIRCUITS AND TRANSMISSION LINES

26/11/19

2

DE-sem-III-BSGS-EATC

Q.P. Code : 50501

[Time: Three Hours]


[Marks:80]

N.B.

- 1) Question No. 1 is Compulsory
- 2) Out of remaining questions, attempt any three
- 3) Assume suitable data if required
- 4) Figures to the right indicate full marks

1 (A) Draw equivalent circuit for given magnetically coupled circuit.

05

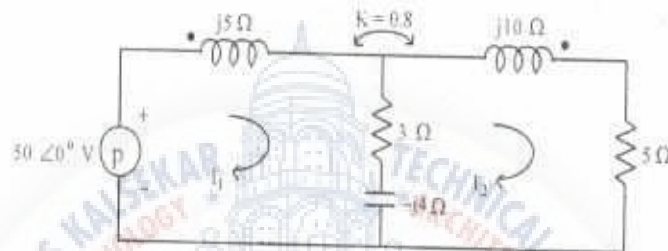

(B) In the network shown in Fig., switch is closed. Assuming all initial conditions as zero, find i and $\frac{di}{dt}$ at $t = 0^+$.


05



(C) In the two port network shown in Fig., compute h-parameters from the following data

05

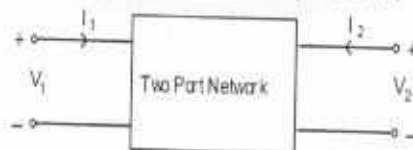- (a) With the output port short circuited : $V_1 = 25$ V, $I_1 = 1$ A, $I_2 = 2$ A
- (b) With the input port open circuited : $V_1 = 10$ V, $V_2 = 50$ V, $I_2 = 2$ A




(D) Design an m-derived T section high pass filter with a cut-off frequency of 2 kHz. Design impedance of 700Ω and $m = 0.6$.


05

Q.P. Code : 50501

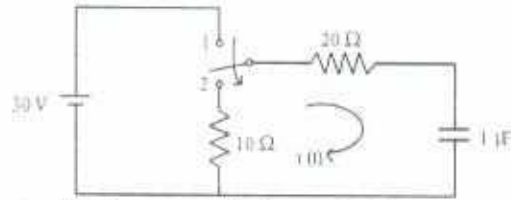
- 2 (A) In the network shown in Fig., switch is changed from position 1 to position 2 at $t = 0$, steady condition having reached before switching. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. 10



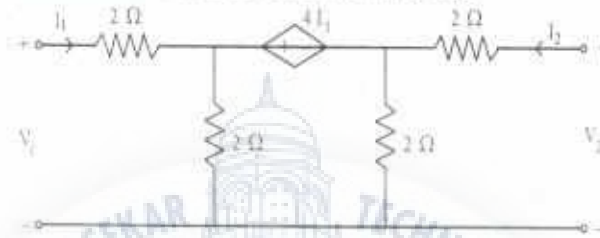- (B) Find Z and h-parameters for the network shown in Fig. 10



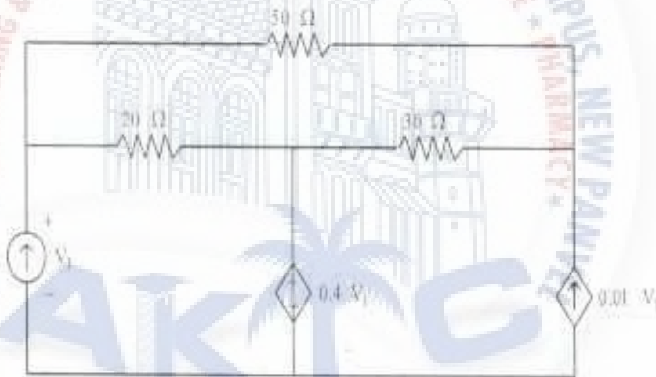- 3 (A) Find the power supplied by the dependent voltage source. 10



- (B) The parameters of a transmission lines are $R = 65\Omega/\text{km}$, $L = 1.6\text{mH}/\text{km}$, $G = 2.25\text{mmho}/\text{km}$, $C = 0.1\mu\text{F}/\text{km}$. Find 10
- i) Characteristic Impedance
 - ii) Propagation Constant
 - iii) Attenuation Constant
 - iv) Phase Constant at 1 kHz

- 4 (A) Determine whether following functions are positive real 10

i)
$$\frac{s^4 + 3s^3 + s^2 + s + 2}{s^3 + s^2 + s + 1}$$


ii)
$$\frac{s(s+3)(s+5)}{(s+1)(s+4)}$$

Paper / Subject Code: 49605 / CIRCUITS AND TRANSMISSION LINES

Q.P. Code : 50501


- (B) Obtain Thevenin equivalent network of Fig.

10

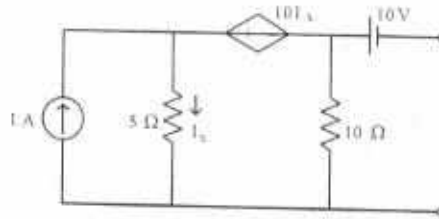

- 5 (A) Find Y-parameters for the network shown in Fig.

10

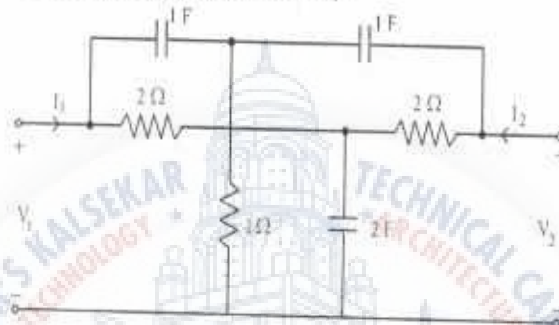

- (B) Realize the following functions in Foster II and Cauer I form

10

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- 6 (A) A transmission line has a characteristics impedance of 50 ohm and terminate in a load $Z_L = 25 + j50$ ohm. Use smith chart and Find VSWR and Reflection coefficient at the load.

10

- (B) The network of Fig. is under steady state with switch at position 1. At $t = 0$, switch is moved to position 2. Find $i(t)$.

10

