

Attenuators

Attenuator is a two port resistive network. It is used to reduce the signal level when used between a generator and load. Attenuators may be symmetrical or asymmetrical. They may provide fixed or variable attenuation. A fixed attenuator is also called a pad. The attenuation is measured in decibels (dB) or nepers.

$$\begin{aligned} \text{Attenuation in dB} &= 10 \log_{10} \frac{P_1}{P_2} \\ &= 20 \log_{10} \frac{V_1}{V_2} \\ &= 20 \log_{10} \frac{I_1}{I_2} \end{aligned}$$

There are 4 types of attenuators.

- (i) T = type attenuator
- (ii) π = type attenuator
- (iii) Lattice type attenuator
- (iv) Bridged T = type attenuator

T-type attenuator

Figure 1 show a symmetrical T = attenuator. Each series arm is assumed to have a resistance of $R_1 \Omega$ while the resistance of shunt arms equals $R_B \Omega$.

Applying KVL to the network,

$$\begin{aligned} R_2(I_1 - I_2) &= I_2(R_1 + R_0) \\ I_2(R_2 + R_1 + R_0) &= I_1R_2 \end{aligned}$$

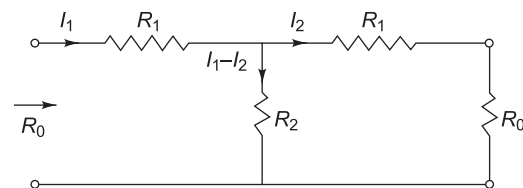


Fig. 1

$$\frac{I_1}{I_2} = \frac{R_2 + R_1 + R_0}{R_2} = N \quad (i)$$

Characteristic impedance is R_0 when it is attenuated in a load of R_0

$$R_0 = \frac{R_1 + R_2 + (R_1 + R_0)}{R_2 + R_1 + R_0}$$

Substituting Eq. (i),

$$\begin{aligned} R_0 &= R_1 + \frac{(R_1 + R_0)}{N} \\ NR_0 &= NR_1 + R_0 + R_0 \\ R_0(N - 1) &= R_1(N + 1) \\ R_1 &= \frac{R_0(N - 1)}{N + 1} \end{aligned} \quad (ii)$$

From Eq. (ii)

$$\begin{aligned} NR_2 &= R_2 + R_1 + R_0 \\ (N - 1) R_2 &= R_1 + R_0 \end{aligned}$$

Substituting Eq. (ii),

$$\begin{aligned} (N - 1) R_2 &= \frac{R_0(N - 1)}{N + 1} + R_0 \\ (N - 1) R_2 &= \frac{2NR_0}{N + 1} \\ R_2 &= \frac{2NR_0}{N^2 - 1} \end{aligned}$$

π -Type Attenuator

Figure 2 show a symmetrical π attenuator. The series and shunt elements of this attenuator can be specified in terms of characteristic impedance and propagation constant.

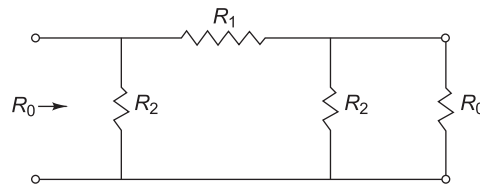


Fig. 2

For resistive network $z_0 = R_0$ and $\gamma = \alpha$

$$R_1 = R_0 \sinh \alpha$$

$$R_2 = \frac{R_0}{\tanh \alpha / 2}$$

$$R_1 = R_0 \frac{e^{\alpha} - e^{-\alpha}}{2}$$

$$e^\gamma = \frac{I_1}{I_2} = N$$

$$R_1 = R_0 \frac{N - \frac{1}{N}}{2} = R_0 \frac{N^2 - 1}{2N}$$

Similarly

$$\tanh \frac{\theta}{2} = \frac{e^{\theta/2} - e^{-\theta/2}}{e^{\theta/2} + e^{-\theta/2}}$$

$$= \frac{e^\theta - 1}{e^\theta + 1}$$

$$= \frac{N - 1}{N + 1}$$

$$R_2 = \frac{R_0(N + 1)}{(N - 1)}$$

Lattice Attenuator

Figure 3 shows a lattice attenuator. The elements of lattice attenuator can be specified in terms of characteristic impedance and propagation constant.

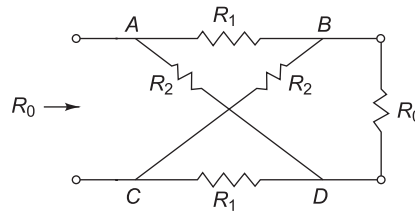


Fig. 3

We know that

$$z_0 = \sqrt{z_{SC} z_{OC}}$$

Redrawing the lattice network,

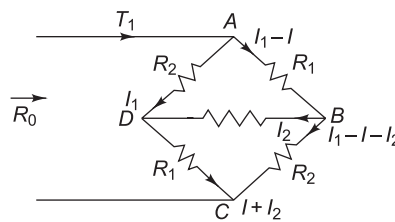


Fig. 4

$$\begin{aligned}z_{SC} &= \frac{2R_1R_2}{R_1 + R_2} \\z_{OC} &= \frac{R_1 + R_2}{2} \\z_0 = R_0 &= \sqrt{z_{SC}z_{OC}} \\&= \sqrt{\left(\frac{2R_1R_2}{R_1 + R_2}\right)\left(\frac{R_1 + R_2}{2}\right)} \\&= \sqrt{R_1R_2}\end{aligned}$$

Applying KVL to the network,

$$\begin{aligned}I_1R_0 &= (I_1 - I)R_1 + I_2R_0 + (I + I_2)R_1 \\I_1R_0 &= R_1(I_1 + I_2) + I_2R_0 \\I_1(R_0 - R_1) &= I_2(R_1 + R_0)\end{aligned}$$

$$\frac{I_1}{I_2} = \frac{R_1 + R_0}{R_0 - R_1} = \frac{1 + \frac{R_1}{R_0}}{1 - \frac{R_1}{R_0}}$$

$$N = e^\alpha = \frac{I_1}{I_2} = \frac{1 + \frac{R_1}{R_0}}{1 - \frac{R_1}{R_0}}$$

$$e^\alpha = \frac{1 + \sqrt{R_1/R_0}}{1 - \sqrt{R_1/R_2}}$$

$$\alpha = \log \left[\frac{1 + \sqrt{R_1/R_2}}{1 - \sqrt{R_1/R_2}} \right]$$

$$N \left(1 - \frac{R_1}{R_0} \right) = \left(1 + \frac{R_1}{R_0} \right)$$

$$R_1 = R_0 \left(\frac{N - 1}{N + 1} \right)$$

Similarly

$$R_2 = R_0 \left(\frac{N + 1}{N - 1} \right)$$