

Con. 8868-13.

GS-7083

(3 Hours)

[Total Marks : 100

N.B.

1. Q 1 is compulsory
2. Answer **any four** out of remaining **six** questions
3. Assumptions made should be clearly stated
4. Assume any suitable data wherever required but justify the same
5. Figures to the right indicate marks.

- Q.1 Answer **any four** of the following (20)
- (i) Show that the optimum conversion efficiency of the Class 'B' push pull amplifier is 78.5%
 - (ii) State the 'Barkhausen Criteria' of oscillation and explain how the oscillations build up in an oscillator.
 - (iii) State the significance of CMRR and slew rate parameters with reference to op-amp
 - (iv) What is crossover distortion in power amplifiers?
 - (v) What is the impact of cascading a CC stage at the input of a CE amplifier?
- Q.2 (a) What are the different types of coupling used in BJT amplifiers? Draw the frequency response of BJT amplifiers and explain why the gain is dropping at low and high frequencies. (07)
- (b) What is Darlington pair? What are its features? Derive the expression for voltage and current gain of an Darlington pair emitter follower circuit? (08)
- (c) Write a short note on crystal oscillator. (05)
- Q.3 Design a two stage RC coupled amplifier using BC147B transistors, with following specifications: (20)
- Stage I voltage gain (A_{v1}) ≈ 100
 Stage II voltage gain (A_{v1}) $= 50$
 Overall stability factor (S) $<= 10$
 Lower Cutoff frequency (f_{low}) ≈ 100 Hz
- While designing, optimize the design for having high input impedance. Consider the loading effect of second stage on first stage. The specifications of BC147B are as given below:
- | | |
|------------------------|-----------------------------------|
| $h_{ie} = 4.5$ Kohm | $h_{FE typ} \approx 290$ |
| $h_{oe} = 30$ micromho | $h_{re} \approx 2 \times 10^{-4}$ |
| $h_{FE typ} = 330$ | $h_{FE min} = 240$ |
- Q.4 (a) Draw the circuit diagram of a Dual Input Balanced Output differential amplifier and derive the relevant AC parameters for it. (10)
- (b) Describe the following application of op-amp in short. (10)
- (i) Non inverting DC amplifier with gain of 23
 - (ii) Summing amplifier
- Q.5 (a) Draw the circuit diagram of integrator and differentiator using op-amp and derive the expressions for output voltages in both cases. (10)
- (b) What are active filters? Explain the classifications of active filters with their frequency response curve. Design a first order low pass filter for a cutoff frequency of 1 kHz and passband gain of 4. (10)

[TURN OVER

Con. 8868-GS-7083-13.

2

- Q.6 (a) Design a class A transformer coupled amplifier with output power of 5 watts, load resistance of 4 ohms. Assume transformer efficiency of 80% and supply voltage of 12 volts. Use the transistor with following specifications **(15)**
 P_{Dmax} (at 25°C) = 30 W; $V_{CEO} = 40$ Volts; I_{Cmax} (at 25°C) = 5Amps; $V_{CEsat} = 1.0$ volt
- (b) For the above design calculate the power dissipation in the transistor when delivering half the power output and also its efficiency. **(05)**
- Q.7 (a) Compare the RC oscillators with LC oscillators. Describe in short Wien Bridge oscillator with the help of suitable schematic. **(10)**
- (b) Draw the neat diagram of an UJT relaxation oscillator. Explain its operation. Derive the expression for frequency of output signal. Draw various waveforms. **(10)**
-