

**Duration: - Three Hours****Total Marks assigned to the paper: - 80**

Instructions to the candidates, if any: -

**Note:**

- Question No. 1 is compulsory.
- Answer any **three** from the remaining five questions.
- Assume suitable data if necessary and justify the same.
- Figures to the right indicate the marks.

Q1 Each question carry five marks.

- List the advantages and disadvantages of Current source inverter over Voltage source inverter.
- Once SCR is triggered, gate loses its control. Why?
- What is a DC-DC converter? List few applications of it.
- What problem is caused by sharp single pulse triggering in a single phase AC voltage controllers when the load is inductive? How can this be solved?

Q2 a Explain the concept of space vector modulation.

b Compare the properties of power BJT, power MOSFET and IGBT

c Explain with relevant circuit diagrams and waveforms the working of a single phase bidirectional phase control type AC voltage controllers connected to R load and obtain a relationship between the r.m.s. output voltage and ther.m.s. input voltage.

Q3 a Draw a neat circuit and explain the working of full wave fully controlled 6-pulse  $3\phi$  bridge circuit with resistive load. Draw the corresponding input and output voltage waveforms when the firing angle  $\alpha=90^\circ$ .

b A single phase full wave fully controlled bridge rectifier is operated with an R-L load. Calculate average D.C. output voltage, input power factor, displacement factor and Total Harmonic distortion, if a 50 Hz. Sinusoidal voltage of 220 V. peak is applied.

Q4 a Explain with a neat circuit diagram and relevant waveforms, the working of a boost regulator and derive the expression for output voltage, filter capacitance and filter inductance.