

(OLD COURSE)

QP Code :14400

(3 Hours)

[Total Marks : 100]


N.B.: (1) Question No. 1 and 2 are compulsory.

(2) Attempt any **three** questions from remaining **five** questions.

(3) **Figures** to the **right** indicate **full marks**.

(4) Assume **suitable** data wherever **necessary**.

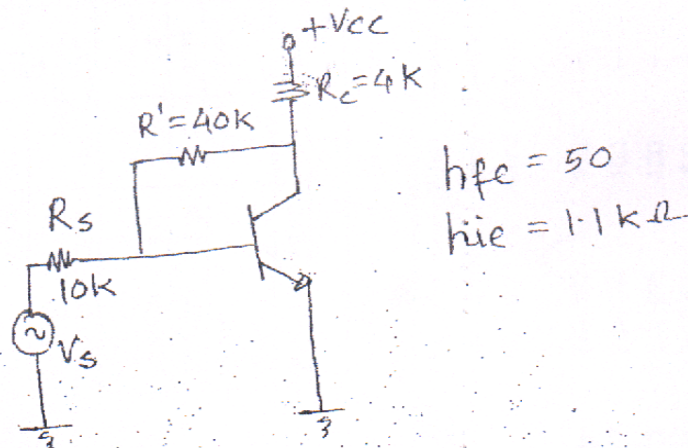1. Design a two stage RC coupled CE-CE amplifier for the following parameters. 20
 $A_v \geq 2500$, Frequency $\leq 30\text{Hz}$, stability factor ≤ 8 , $V_o = 2.5$ volts.
 Use BC 147 A transistor.
2. Design two stage RC coupled amplifier for the following parameters $A_v \geq 75$, 20
 frequency = 20Hz , $V_o = 3$ volts, $I_{OQ} = 1.38$ mA, $R_i = 1$ M Ω use BFW11 JFET.
3. (a) Design large signal transformer coupled class A power amplifier to provide 6W 10
 output power to the 4Ω load.
 (b) Draw two stage CE amplifier and derive the expression for 10
 (i) Small signal mid band voltage gain (ii) Input impedance
 (iii) Output impedance.
4. (a) Explain the working principle of a wein bridge oscillator. Derive the expression for 10
 the frequency of oscillation and the value of gain required for sustained oscillation.
 (b) Draw the circuit diagram for class B push-pull power amplifier and derive the 10
 expression for conversion efficiency.
5. (a) Explain the operation of transistorized ASTABLE multivibrator with appropriate 10
 waveforms.
 (b) For the feedback amplifier shown in figures, identify the type of feedback and find 10
 out A_{vf} , R_{if} , R_{of} using -ve f/b approach.



[TURN OVER