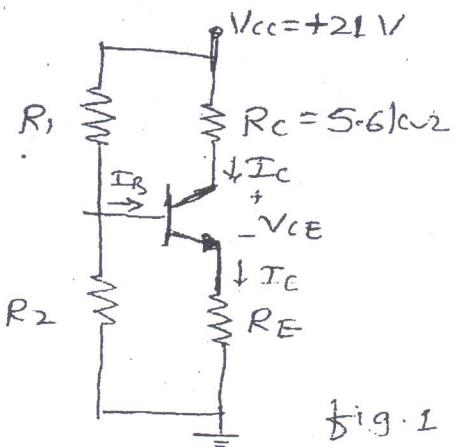


- N.B. :**
- (1) Question No. 1 and 2 **compulsory.**
  - (2) Attempt any **three** question from The remaining question.
  - (3) In all **five** questions to be attempted.
  - (4) **Figures to the right indicate full marks.**

- |    |  |
|----|--|
| 1. | (a) Design single stage CE Amplifier to provide following specifications<br>$A_v \geq 150$ , $V_o = 3.5v$ , $F_L \leq 40$ Hz, $S_{ICO} \leq 10$ use transistor BCI47A. <b>15</b>   |
|    | (b) For the above designed amplifier find expected voltage gain, input impedance output impedance and maximum undistorted output voltage and its corresponding input voltage. <b>5</b>   |
| 2. | (a) The circuit shown uses a silicon transistor with $\beta=50$ , $V_{BE} = 0.6$ v, $V_{CC} = 21$ v, and $R_C = 5.6$ k $\Omega$ . Find the values of the resistors $R_E$ , $R_1$ and $R_2$ so that Q point is set at $V_{CE} = 12$ v and $I_C = 1.5$ mA. The stability factor $S \leq 3$ . (fig.1) <b>10</b> |



- |    |   |
|----|---|
| 3. | (b) What are the important JFET parameters and define it from characteristics. <b>10</b>  |
| 3. | (a) Explain working of capacitor filter with full wave rectifier and derive the expression for the ripple factor. Also explain the effect of load resistor on ripple factor. <b>10</b>  |
|    | (b) Design a zener shunt voltage regulator to meet the following specification<br>$V_o = 7$ v, $I_L = 10$ mA, $P_{zmax} = 500$ mw, $I_{zmin} = 2$ mA, and $V_i = 15 \pm 5$ v. <b>10</b> |
|    | 10  |

4. (a) Draw small signal hybrid parameter circuit for CE amplifier and define h-parameters from characteristics of transistor. 10
- (b) For the amplifier shown in figure. 2 below. Analyse and determine,  $A_v$ ,  $A_I$ ,  $R_i$  and  $R_o$ . 10

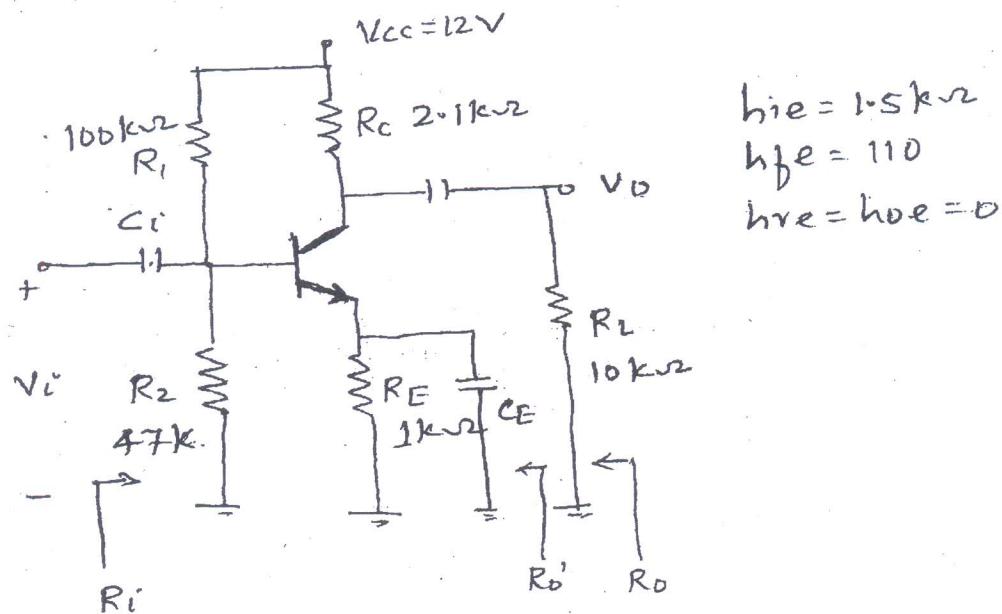



Fig. 2

5. (a) Draw common source amplifier with self bias circuit and derive the expression for voltage gain, input impedance and output impedance. 10  
What is the effect of removing bypass capacitor on voltage gain,  $R_i$  and  $R_o$ .
- (b) Explain with the help of neat circuit diagram, working of UJT relaxation oscillator and derive expression for frequency of oscillation. 10

LM-Con.:8045-14.

[ TURN OVER ]

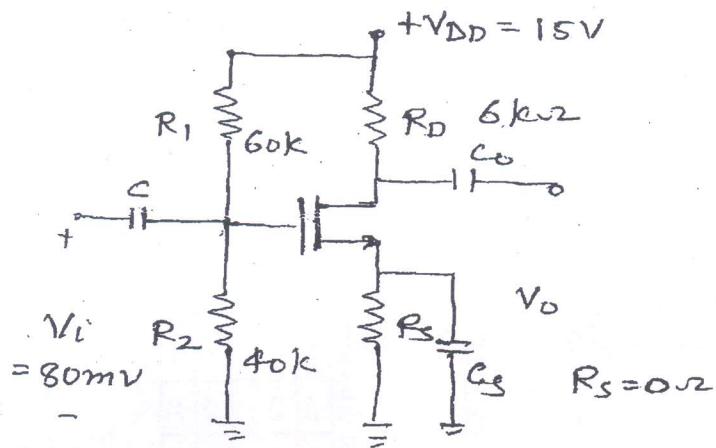- 10 6. (a) Compare JFETs and MOSFETs.  
 10 (b) An n-channel E-MOSFET with common source amplifier, shown in figure, has  
 the following parameters:  $I_{D(ON)} = 4\text{mA}$ , at  $V_{GS(ON)} = 8\text{v}$ ,  $V_{TN} = 4\text{V}$ .  $gm = 2000 \mu\text{s}$ . Determine  $V_{GS}$ ,  $I_D$ ,  $V_{DS}$ , output voltage,  $R_i$  and  $R_o$ .



- 10 7. Explain the following (any four) 20
- Latching and holding current in SCR.
  - Bleeder resistance and critical inductance
  - Power MOSFET
  - Opto couples
  - BJT as a switch.

**LM-Con.:8045-14.**

[ TURN OVER

Transistor type	P <sub>drain</sub> @ 25°C Watts	I <sub>ceon</sub> @ 25°C Amps.	V <sub>CE(on)</sub> volts d.c.	V <sub>cao</sub> volts d.c.	V <sub>cex</sub> (Sus) volts d.c.	V <sub>ceo</sub> (Sus) volts d.c.	T <sub>j</sub> max. °C	D.C. current, typ. mA	gain, typ. max.	Small signal typ. max.	h <sub>ie</sub>	V <sub>be</sub> max.	Q <sub>le</sub> @ CW °C/W	O <sub>drate</sub> above 25°C W/C			
2N 3055	115.5	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.5	0.7	
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	1.5	3.6	0.4
ECN 149	30.0	4.0	1.0	50	40	-	-	8	150	30	50	110	33	80	1.5	1.2	0.3
ECN 100	5.0	0.7	0.6	70	60	65	-	6	200	50	90	280	50	90	0.9	35	0.05
BC 147A	0.25	0.1	0.25	50	45	50	-	6	125	115	180	220	125	220	0.9	-	-
2N 525 (PNP)	0.5	0.25	0.25	85	30	-	-	-	100	35	-	65	-	45	-	-	-
BC 147 B	0.25	0.1	0.25	50	45	50	-	6	125	200	290	450	240	330	500	0.9	-

Transistor type	h <sub>ie</sub>	h <sub>oe</sub>	h <sub>re</sub>	θ <sub>ia</sub>
BC 147 A	2.7kΩ	18μmho	1.6 × 10 <sup>-4</sup>	0.4°C/mW
2N 525 (PNP)	1.4kΩ	25μmho	3.2 × 10 <sup>-4</sup>	-
BC 147B	4.5kΩ	30μmho	2 × 10 <sup>-4</sup>	0.4°C/mW
ECN 100	50Ω	-	-	-
ECN 149	15Ω	-	-	-
ECN 055	12Ω	-	-	-
2N 3055	6Ω	-	-	-

## BFW 11-JFET

BFW 11-JFET MUTUAL CHARACTERISTICS							
-V <sub>gs</sub> volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2
I <sub>ds</sub> max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4
I <sub>ds</sub> typ. mA	7.0	6.0	5.4	4.6	4.0	3.4	2.8
I <sub>ds</sub> min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0

## N-Channel JFET

Type	V <sub>DS</sub> max. Volts	V <sub>GDS</sub> max. Volts	I <sub>DS</sub> max. mA	P <sub>dmax</sub> @ 25°C mW	T <sub>jmax</sub> °C	I <sub>DS</sub>	R <sub>DS(on)</sub> (Typical) mho	-V <sub>P</sub> Volts	I <sub>G</sub>	Delta I <sub>G</sub> above 25°C mA	θ <sub>A</sub>
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ	6	50 kΩ	2 mA	0.69°C/mW
BFW 11 (Typical)	30	30	30	300 mW	200°C	7 mA	5800 μ	2.5	50 kΩ	-	0.61°C/mW