

SE-comp.
III - CBSGS)
DLDA

08/12/2014

QP Code : 14644

(3 Hours)

[Total Marks : 80

- N.B. (1) Question No. 1 is compulsory.
(2) Assume suitable data if necessary.
(3) Attempts any three questions from remaining questions.

1. (a) Represent $(29)_{10}$ into Excess-3 code and Gray code. 2
 (b) Convert the following hex no. $(67.4A)_{16}$ into equivalent Octal no. 2
 (c) Convert decimal (215.32) into base '7'. 4
 (d) Convert $(670.17)_8$ into binary and hex. 4
 (e) Add $(57)_{10}$ and $(26)_{10}$ in BCD. 2
 (f) Explain uses of Gray code. 4
 (g) Add $(DDCC)_{16}$ and $(BBAA)_{16}$. 2

2. (a) (i) State the boolean algebra laws used in k-map simplification. 5
 (ii) Simplify $Y = ABC(\overline{CD}) + \overline{BCD} + (\overline{A}\overline{C})(B + D)$. 5
 (b) A misguided mathematician would like to subtract term $A\overline{C}$ from both sides of equality. 10

$$BC + ABD + A\overline{C} = BC + A\overline{C}$$
 Would they still be equal if he did so. Justify and simplify the expression.

$$F = (x + \overline{z})(\overline{z + wy}) + (vz + wx)(\overline{y + z})$$

3. (a) Simplify using boolean theorems and implement using AOI gate only. 5
 (i) $\overline{AB + \overline{A}\overline{B} + (A + B) \cdot (\overline{A} + \overline{B})}$ 5
 (ii) Implement the following expression using NAND-NAND logic $y = \Sigma m(0, 1, 5)$ 5
 (b) Simplify using k-map obtain SOP equation and realize using NAND gate. 10
 $f(A, B, C, D) = \Pi M(1, 2, 3, 8, 9, 10, 11, 14) + d(7, 15)$

4. (a) Implement the following expression using 8 : 1 mux 4
 $f(A, B, C, D) = \Sigma m(0, 1, 3, 5, 7, 10, 11, 13, 14, 15)$
 (b) Explain with example 4 bit BCD adder using IC-7483. 8
 (c) Compare the performance of TTL, CMOS and ECL logic. 8

5. (a) What is shift register ? Explain 4 bit bi-directional shift register. 10
 (b) Convert JK FF to SR and DFF. 10

6. Write short note on (any three) :— 20
 (a) State table
 (b) VHDL
 (c) Difference between CPLD and FPGA
 (d) Decade counters.