

10

TE - sem - V - EATC - CBGS

4/6/15

IC

Q.P. Code : 3387

(3 Hours)

[Total Marks :100

- N.B. :** (1) Question No. 1 is compulsory.
(2) Solve any Three out of remaining questions.
(3) Assume suitable data if required.

1. Solve the following: 20
 - (a) Design a circuit to keep LED 'ON' for 30 seconds once circuit is triggered.
 - (b) What is CMRR for op-amp and how to measure it practically?
 - (c) Explain first order active filter circuit.
 - (d) Design a 0.5A current source using IC7805. Assume $R_L = 100$.
 - (e) Explain 7490 Decade counter.
2. (a) Design triangular waveform generator for frequency for 5 kHz and $V_{opp} = 6V$ using op-amp. 10
(b) Explain IC 741 based RC phase shift oscillator with proper waveforms. 10
Design RC phase shift oscillator to produce sinusoidal frequency output of 5 kHz.
3. (a) Design a high pass second order filter for the cut off frequency of 1 kHz and passband gain $AF = 2$. 10
(b) Write the advantages of precision rectifier. Explain half wave precision rectifier along with neat waveforms. 10
4. (a) Design a voltage regulator using IC 723 to give $V_0 = 5V$ and output current of 2A. 10
(b) Draw instrumentation amplifier using opamp and hence derive equation for output voltage. 6
(c) Explain zero crossing detector with neat diagram. 4
5. (a) Draw and explain the functional diagram of IC 555 and explain its operation in astable mode. 10
(b) With the help of a neat circuit diagram explain the working of 74163 synchronous 4-bit binary counter. 10
Also illustrate the cascading connections for 74163 based counters.
6. Write short note on the following: 20
 - (a) 74181 Arithmetic Logic Unit.
 - (b) Current foldback protection.
 - (c) Any two applications of PLL 565.
 - (d) Voltage to frequency converter.