

QP Code : 4887

(3 Hours)

[Total Marks : 80]

N.B (1) Question Nos. 1 is compulsory.

(2) Attempt any three questions from the remaining five questions.

(3) Figure to the right indicates full marks.

(4) Assume suitable data whenever necessary but justify the same.


- 1 (a) Compare clipper and clamper circuit. [5]
 (b) Explain Barkhausen criteria for sustained oscillations. [5]
 (c) Compare Depletion and Enhancement type MOSFET. [5]
 (d) Transistor is a current controlled device while FET is a voltage controlled device. Justify. [5]

Q2 (a) Define Stability factor. Derive the equation for Stability factor. State which biasing technique is more stable. Justify your answer. [10]

- (b) For a NPN transistor in CE mode voltage divider bias configuration determine V_C and V_B . Given $V_{CC} = +20V$, $V_{EE} = -20V$, $R_1 = 8.2K\Omega$, $R_2 = 2.2K\Omega$, $R_C = 2.7K\Omega$, $R_E = 1.8 K\Omega$, $C_1 = C_2 = 10\mu F$ and $\beta = 120$. [10]

Q3 (a) Derive the equations for A_v , A_i , R_i and R_o for a NPN transistor in CE mode voltage divider bias configuration with R_E unbypassed. [10]

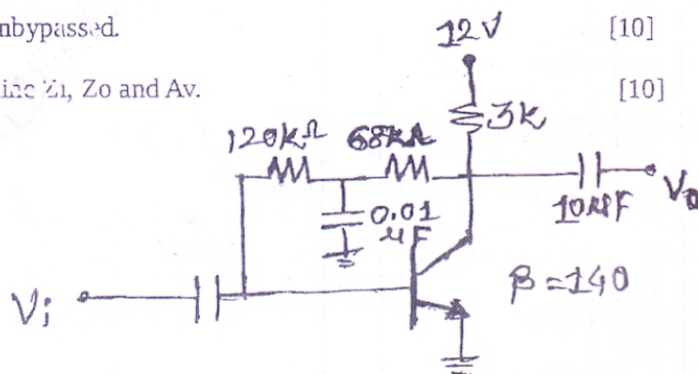
- (b) For the network given below determine Z_i , Z_o and A_v . [10]




Q4 (a) Explain the basic operation and characteristics of n-channel enhancement type MOSFET. [10]

- (b) Draw a neat circuit diagram of Wien bridge oscillator and derive an expression for its output frequency. [10]

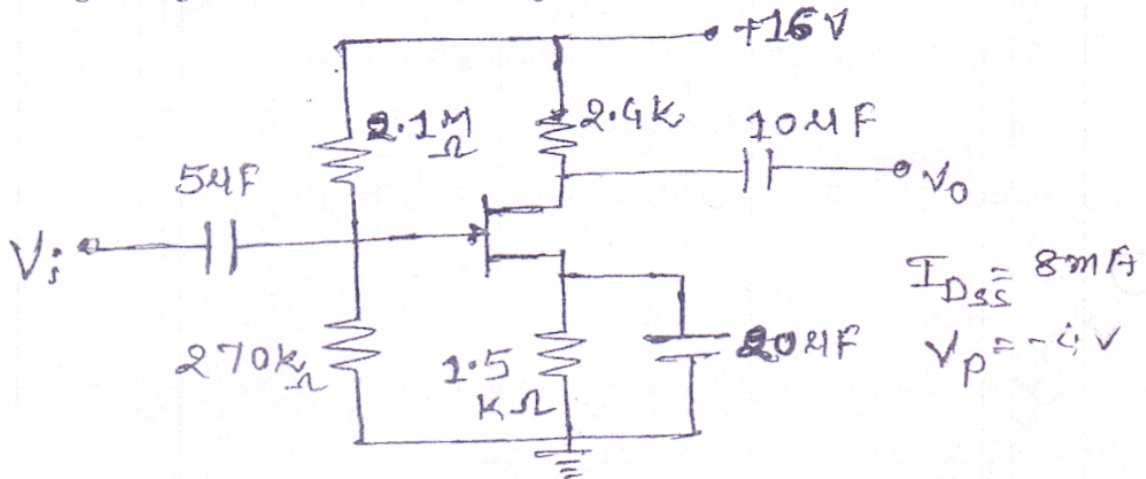Q5.) a) Determine I_{DQ} , V_{GSQ} , V_D & V_S for the network given below: [10]



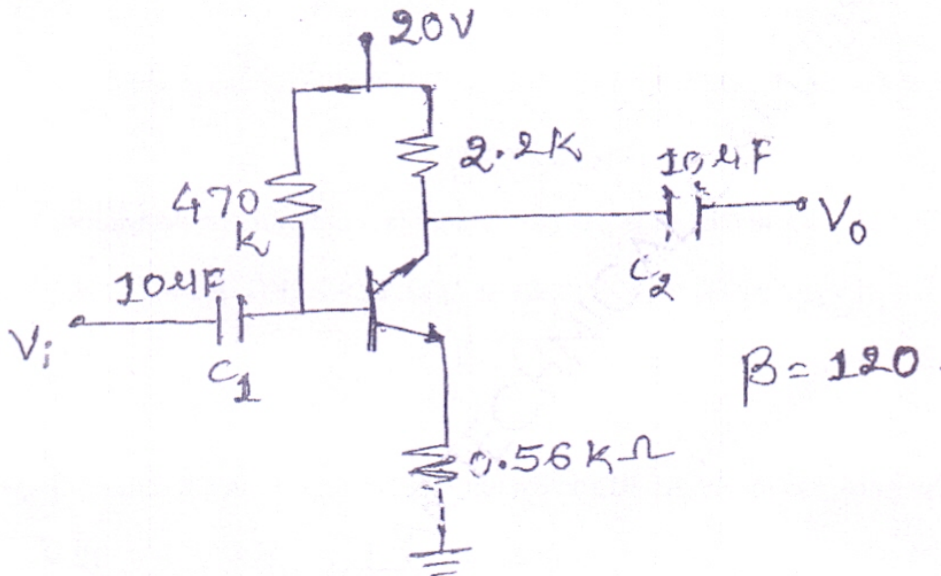b) Determine Z_i , Z_o & A_v for the circuit given below. [10]



Q6. Write short note on any Four:- [20]

- i) Biasing of JFET for Zero temperature drift.
- ii) Energy band diagram of MOS capacitor.
- iii) Small signal equivalent circuit of CC amplifier.
- iv) Crystal oscillator
- v) DC load line & significance of Q point.