

05/06/2015

QP Code : 4898


(3 Hours)

[Total Marks : 80

- N.B. : (1) Question no. 1 is compulsory.
 (2) Attempt any three questions from remaining questions.
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data if required.

1. (a) Determine y-parameters for the network.


5

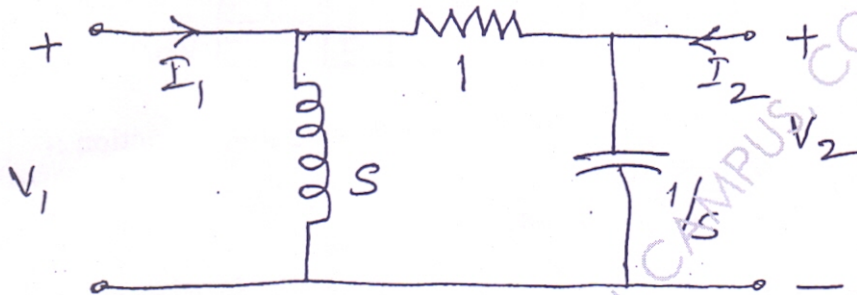

- (b) The constants of a transmission line are $R = 6 \Omega/\text{km}$, $L = 2.2 \text{ mH/Km}$, $G = 0.25 \times 10^{-6} \text{ S/km}$, $C = 0.005 \times 10^{-6} \text{ F/km}$. Determine the characteristic impedance, propagation constant and attenuation constant at 1 KHZ. 5
- (c) Test if $F(S) = 2S^6 + 4S^5 + 6S^4 + 8S^3 + 6S^2 + 4S + 2$ is a Hurwitz polynomial. 5
- (d) The current $I(S)$ in a network is given by $I(S) = \frac{2(S)}{(S+1)(S+2)}$. Plot the pole-zero pattern in the S-plane and hence obtain $i(t)$. 5

2. (a) Find the current through 10Ω resistor using Norton's theorem.


10

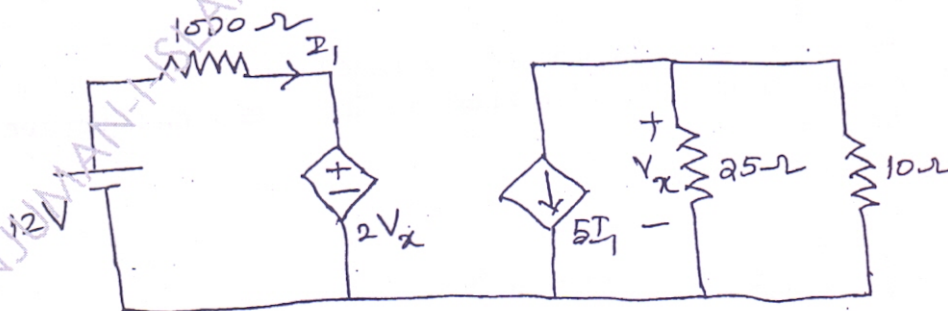

[TURN OVER

(b) Find the current $i(t)$ for $t > 0$.

10

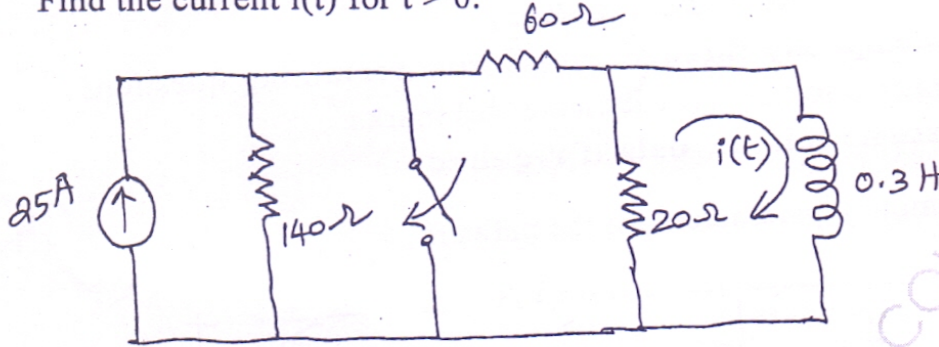


3. (a) Find Foster I and Foster II forms of the driving point function :-

10

$$F(S) = \frac{S^3 + 9S^2 + 23S + 15}{S(S^3 + 12S^2 + 44S + 48)}$$

(b) Determine ABCD parameters of the network shown :-

10

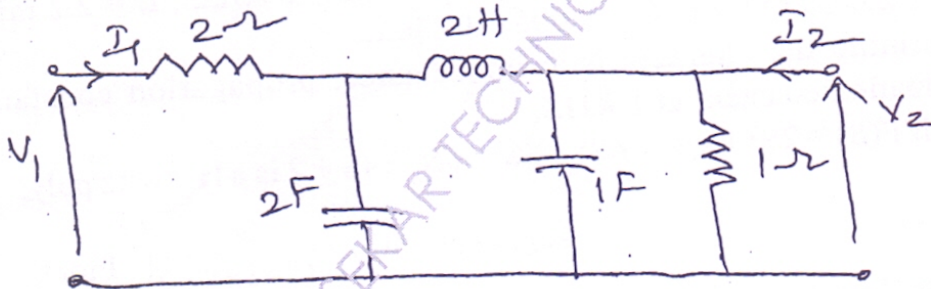


4. (a) A transmission line has a characteristic impedance of 50Ω and terminated in a load $Z_L = 75 - j100 \Omega$. Using switch chart, find

10

- (i) VSWR
- (ii) Reflection coefficient
- (iii) input impedance at a distance 0.1λ from the load
- (iv) location of first voltage maximum and first voltage minimum from the load.


(b) Find I_2 using mesh analysis.

10

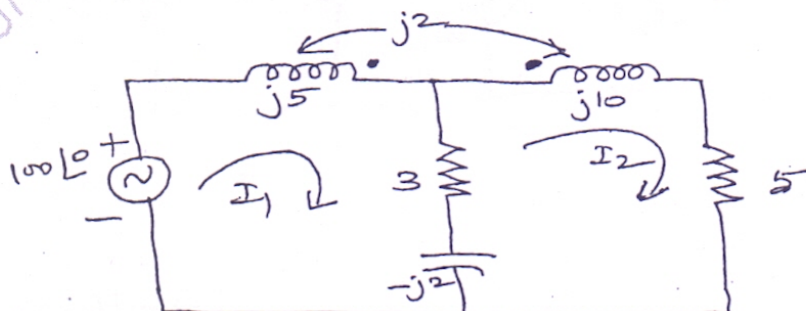


[TURN OVER

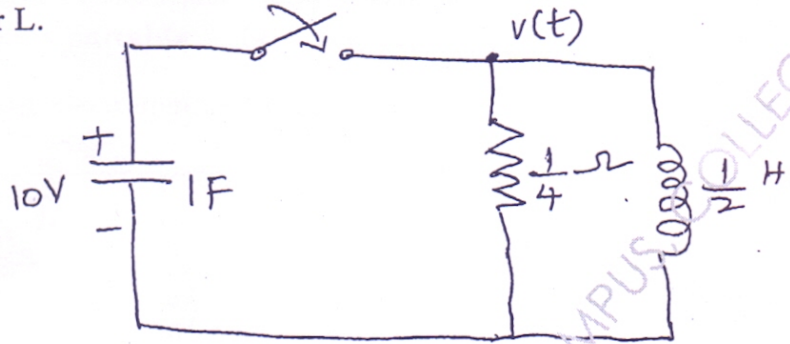
5. (a) For the network shown, capacitor C has an initial voltage $V_c(-0)$ of 10V and at the same instant, current in the inductor L is zero. The switch is closed at time $t = 0$. Obtain the expression for voltage $V(t)$ across the inductor L. 10



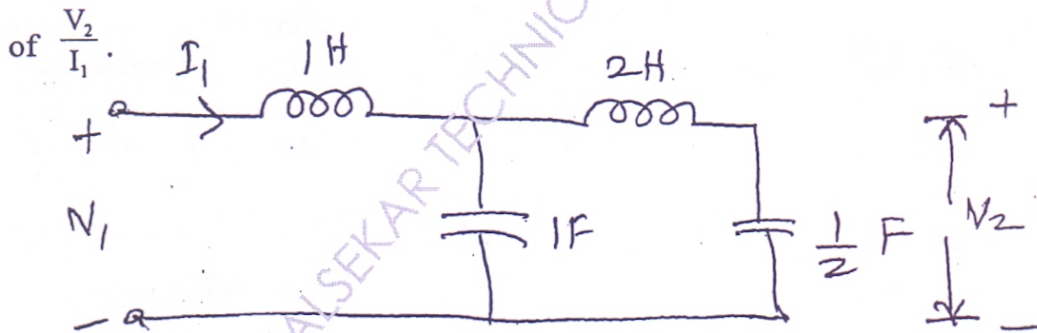- (b) For the network shown, determine $\frac{V_1}{I_1}$ and $\frac{V_2}{I_1}$. Plot the poles and zeros 10



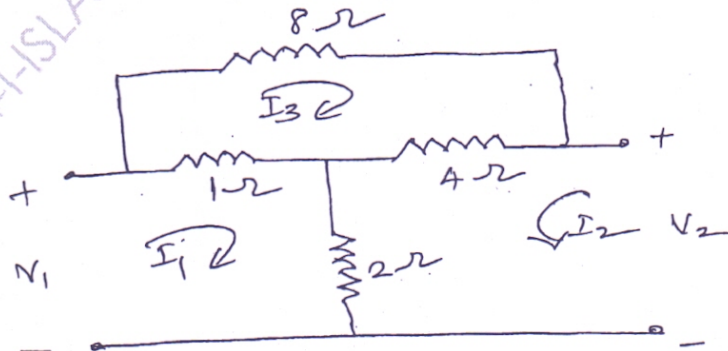6. (a) For the network shown, find the equivalent T - network. 10



- (b) Derive condition for reciprocity in terms of Z parameters and symmetry in terms of h parameters. 10
-