

55

BE-ExTC Sem VIII (Rev)
Adv. Microwave Engg.

14/5/15

QP Code : 8038

(3 Hours)

[Total Marks :100

- N.B. :** (1) Question No.1 is compulsory.
(2) Make use of complete Smith chart wherever necessary.
(3) Solve any four questions from remaining six questions.
(4) Assume suitable data wherever required.

- 1.(a) Find S-parameters of two port series network with $Z = 100 \Omega$ and $Z_0 = 50 \Omega$. 5
(b) Derive the expression of overall noise figure in three cascaded stages of amplifiers. 5
(c) Define stability. List the various criteria for stability. 5
(d) What are the characteristics of power amplifiers ? 5

2. (a) A BJT with $I_c = 30\text{mA}$ and $V_{CE} = 10\text{V}$ is operated at a frequency of 1.0 GHz in a 50Ω system. 10

Its S-parameters are :

$$S_{11} = 0.73 \angle 175^\circ; \quad S_{22} = 0.21 \angle -80^\circ$$

$$S_{12} = 0.0; \quad S_{21} = 4.45 \angle 65^\circ$$

Determine whether the transistor is unconditionally stable. If yes, calculate the optimum terminations.

G_s , max, G_L , max and G_{TU} , max.

- (b) Explain using suitable diagrams two methods of designing broad band amplifier. 10

3. (a) Determine stability of GaAs FET that has the following S-parameters at 2GHz in a $50\text{-}\Omega$ system both graphically and mathematically. 10

$$S = \begin{bmatrix} 0.89 \angle -60^\circ & 0.02 \angle 62^\circ \\ 3.1 \angle 123^\circ & 0.78 \angle -27^\circ \end{bmatrix}$$

- (b) Derive the transducer power gain as : 10

$$G_T \frac{P_L}{P_{\text{avg}}} = \frac{|s_{21}|^2 (1 - |s|^2) (1 - |L|^2)}{|1 - |s_{in}|^2| 1 - S_{22} |L|^2}$$

2/2

QP Code : 8038

2

4. Design a transistor oscillator at 6GHz using an FET in CS configuration driving a 50 Ω load on drain side. The S parameters at 50 Ω are 10

$$S = \begin{bmatrix} 0.9 \angle 150^\circ & 0.2 \angle -15^\circ \\ 2.6 \angle 50^\circ & 0.5 \angle 105^\circ \end{bmatrix}$$

Calculate and plot output stability circle for

$|\Gamma_{IN}| \gg 1$, choose Γ_T so that $|\Gamma_{IN}| \gg 1$

Design load and terminating networks.

5. (a) Discuss various mixer topologies. Compare performance of various topologies. 10
(b) Compare microwave amplifiers with microwave oscillators. 10
6. (a) A GaAs FET is biased for minimum noise figure and has following S parameters and noise parameters at 4GHz ($Z_0 = 50\Omega$) 15

$$S = \begin{bmatrix} 0.6 \angle -60^\circ & 0.05 \angle 26^\circ \\ 1.9 \angle 81^\circ & 0.5 \angle -60^\circ \end{bmatrix}$$

$$F_{min} = 1.6\text{dB}, \Gamma_{opt} = 0.62 \angle 100^\circ, R_N = 20\Omega$$

Design an amplifier with 2dB noise figure and maximum gain compatible with this noise figure. Assume device is unilateral.

- (b) prove that scattering matrix is symmetrical and reciprocal. 5
7. Write short notes on :
(a) Noise figure test equipment 5
(b) 1dB compression point 5
(c) Amplifier linearization methods 5
(d) Single ended diode mixer. 5

Course: B.E. (SEM.VIII) (ELECTRONICS & TELECOMMUNICATION ENGG.)(prog 758 To 772)

Q.P Code: 8038

Correction:

Q.no.(4)

Read AS: FET in Cg Configuration

Instead of: FET in Cs Configuration

Q.No.(4) is of 20 marks .

Q.No.(3)(b) (chk following img)

Q. 3(b)

Read

$$G_T = \frac{P_L}{P_{avg}}$$

as $G_T = \frac{P_L}{P_{avg}}$

Query Update time: 14/05/2015 11:40 AM

NOTE: Take printouts & distribute them to concerned students.