

(OLD COURSE) Q.P. Code : 4605

(3 Hours)

[Total Marks : 100]

- N.B.** (1) Question No. 1 is compulsory.
 (2) Attempt any four out of remaining Q.2 to Q.7.
 (3) Assume suitable data if required.
1. (a) Subtract $(10)_{10} - (33)_{10}$ using 2's complement number system. 5
 (b) Convert JK FlipFlop to T FlipFlop. 5
 (c) What are error detecting and error correcting codes. 5
 (d) Compare Asynchronous and synchronous counters. 5
 2. (a) Simplify the logic function using k-map and implement it using AND-OR gates. 10
 $F(A, B, C, D) = \sum m(0, 1, 2, 4, 8, 9, 12) + d(11, 15)$
 (b) Design 2 bit asynchronous up/down counter using T-Flip Flop. 10
 3. (a) Explain any one shift register using Jk Flip Flops 10
 (b) Design full adder using AND-OR gates. 10
 4. (a) Implement the following function using single 8:1 multiplexers. 10
 $f(A, B, C, D) = \sum m(0, 1, 4, 5, 9) + d(11)$
 (b) Perform without conversion. 10
 (i) $(44B)_H - (1AD)_H$ (ii) $(77)_8 * (32)_8$
 5. (a) Reduce using Boolean Algebra 10
 (i) $AB + \overline{AC} + ABC(AB + C)$ (ii) $(A + \overline{B} + AB)(A + \overline{B})(\overline{A}B)$
 (b) Design full subtractor using universal gates NAND. 10
 6. (a) Using Quine Mc-cluskey method, simplify the following function and design using NOR gates. 10
 $F(A, B, C, D) = \pi M(0, 1, 4, 5, 10, 11, 12, 14)$
 (b) Explain the transfer characteristics of TTL NAND gate. 10
 7. Write short notes on : 20
 (a) Arithmetic Logic Unit
 (b) Universal gates
 (c) Applications of Flip Flops
 (d) Weighted codes.