

(OLD COURSE)

(3 Hours)

QP Code:


[Total Marks:100]

N.B. : (1) Question No. 1 is compulsory.

(2) Attempt any four from the remaining questions.

(3) Assume suitable data, if required.

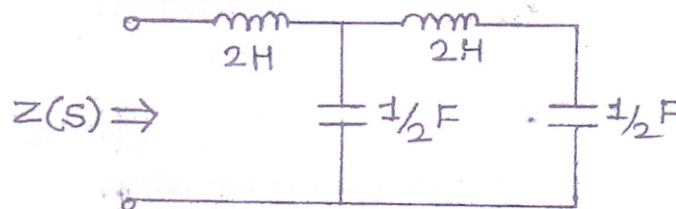
1.(a) Find the driving point impedance of network.



5


(b) For the given network find out z parameters and verify the condition of reciprocity.

5

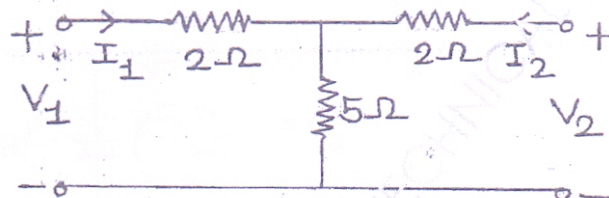

(c) Find current i_1 and i_2 in the given circuit.

5

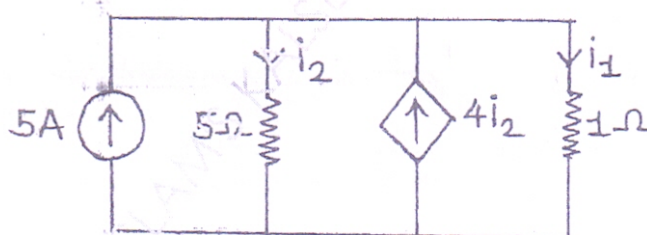


(d) Check for Hurwitz $P(s) = s^4 + 3s^2 + 2$.


5

2.(a) For the given tree (shown with firm lines) obtain.

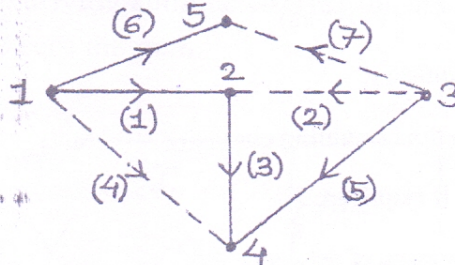
- (i) Incidence matrix
- (ii) Fundamental cutset matrix
- (iii) Fundamental tieset matrix.



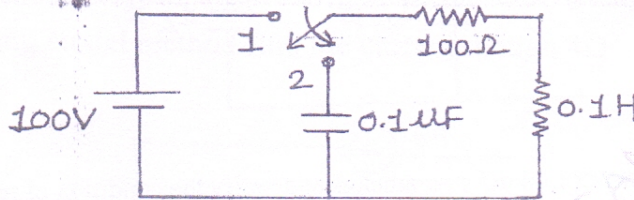(b) For the given the given network, the switch is changed from position 1 to 2 at time $t=0$. Find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$. Assume that steady state is reached at switch position 1.



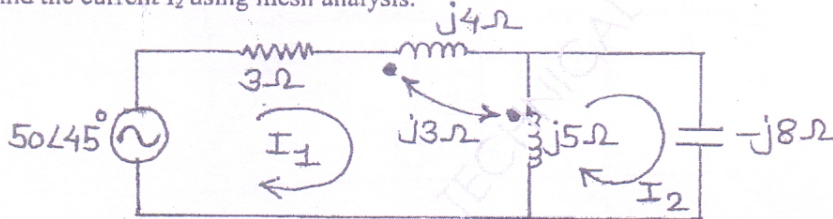
3.(a) Find the current I_2 using mesh analysis.



(b) Realize using Foster-I and Foster-II form.


$$Y(s) = \frac{s(s^2+2)(s^2+4)}{(s^2+1)(s^2+3)}$$

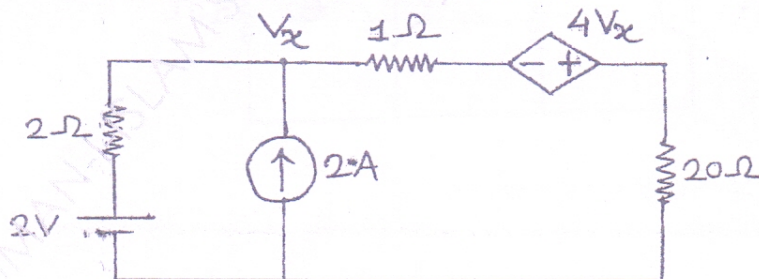4.(a) Find the current in 20Ω resistor using Thevenin's theorem.




(b) For the given network, find out $\frac{V_2}{V_1}$ and $\frac{I_2}{I_1}$.

10

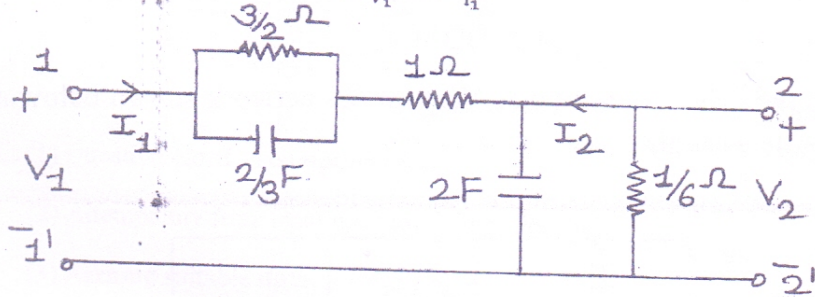

5.(a) For the given network at $t = 0$, switch is opened. Calculate v , $\frac{dv}{dt}$, $\frac{d^2v}{dt^2}$ at $t=0^+$.

10

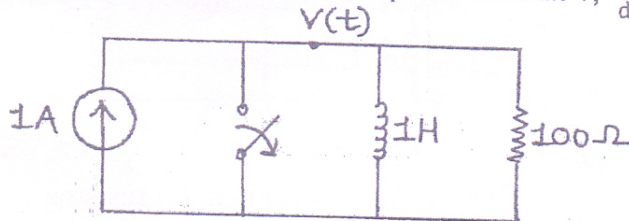


(b) Check the positive realness of the following functions:

10

(i) $\frac{(s^2 + s + 6)}{(s^2 + s + 1)}$ (ii) $\frac{(s^2 + 1)}{(s^3 + 4s)}$


6.(a) Find y parameters for the given network.

10

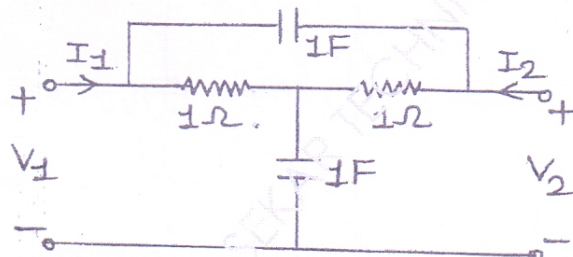

(b) For the network, calculate i_1 , i_2 , $\frac{di_1}{dt}$, $\frac{di_2}{dt}$, $\frac{d^2i_1}{dt^2}$, $\frac{d^2i_2}{dt^2}$ at $t=0^+$. Switch is closed at $t = 0$. Initially switch is open.


10

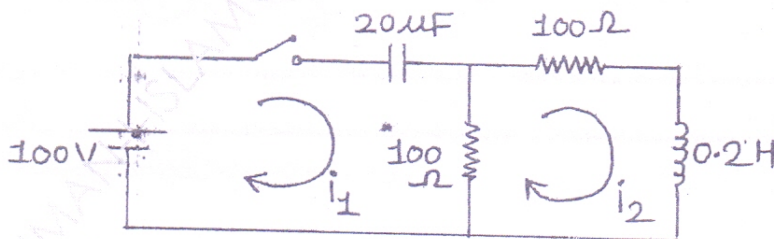

QP Code : 4689

4

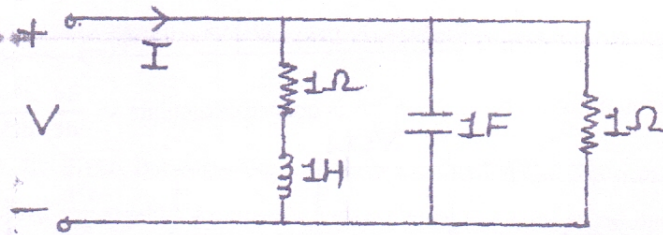7. (a) Find the driving admittance $Y(s)$ for the network shown below and plot the pole zero diagram. 10



- (b) Using Nodal method find the current through 4Ω resistor. 10

