

(OLD COURSE)**QP Code : 4136**

N. B.: (1) Question No. 1 is compulsory.

(2) Attempt any four questions out of remaining Six questions.

(3) Figures to the right indicate full marks.

(4) Assume suitable data whenever required.

(3 Hours)

Total Marks:100

- Q.1 a) Explain the principal of Antilog filter. 5
- b) Compare Moore Machine and Mealy Machine. 5
- c) Draw and Explain Schmitt Trigger. 5
- d) Write the difference between Synchronous and Asynchronous sequential circuit. 5
- Q.2 a) Explain the basic requirement of Instrumentation Amplifier and find output voltage expression for Instrumentation Amplifier using three Op-Amp. 10
- Q.2 b) Design second order KRC high pass filter with cut off frequency $F_0=1\text{KHz}$ and $Q=5$. Draw circuit diagram. 10
- Q.3 a) Design the circuit for an astable multivibrator to generate the output signal with frequency of 1KHz and duty cycle of 75% using IC 555. 10
- Assume value of $c=0.1\mu\text{F}$.
- Q.3 b) With the neat diagram explain positive Ramp generator using IC 566. 10
- Q.4 a) Draw and explain the block diagram of IC 810 audio power amplifier. 10
- Q.4 b) Explain the operation of sample and hold circuit and also draw input output waveforms. 10
- Q. 5a) Write the VHDL code for 8 bit Shift Register. 10
- Q. 5b) Design mealy state machine for sequence detector for the string 1110 10
- Q. 6a) Design modulo 10 counter with the counting sequence 5,6,7,8,9,10,11,12,13,14,5,6,7,8,9....14... Using MSI 74X163 10
- Q.6b) Explain Op-amp as a comparator and its applications 10
- Q. 7 Write short note on any three. 20
- Xilinx 4000 FPGA
 - Sequential circuit documentation standards
 - Function Generator IC 8038
 - Types of memory devices