

Q.P. Code : 5079

(3 Hours)


[Total Marks : 80

- N.B. : (1) Question No. 1 is compulsory.
 (2) Attempt any **three** questions out of the remaining **five** questions.
 (3) Assume suitable **data** wherever required.


1. Attempt any four.

20

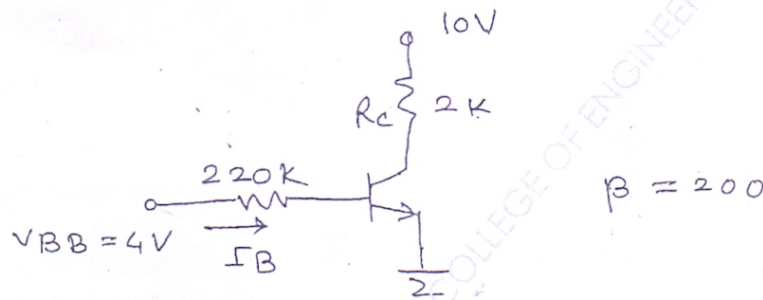- (a) Draw Input and Output characteristics of BJT in common emitter configuration.
 (b) Draw small signal hybrid π equivalent circuit for npn transistor.
 (c) Explain effect of temperature on JFET and derive equation for zero current drift.
 (d) Calculate I_B , I_C & V_{CE} for common emitter circuit.



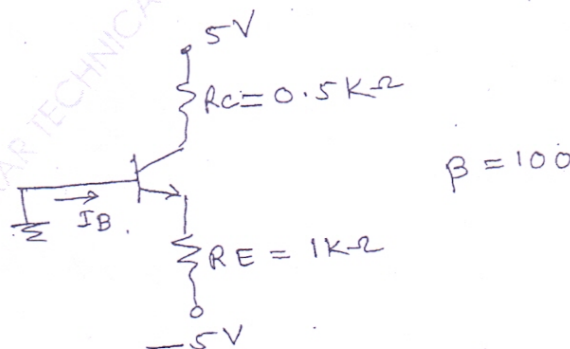
- (e) Find I_B , I_C & V_{CE} for following circuit.




[TURN OVER

2. (a) Draw output waveform for clamper and clipper circuits. 10

(i)

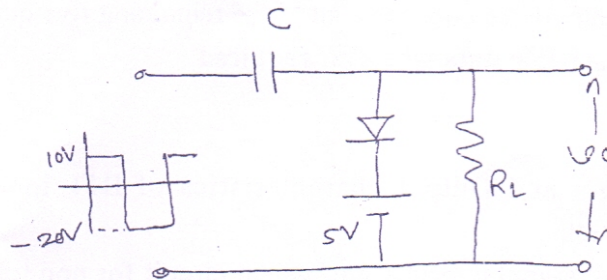


(ii)

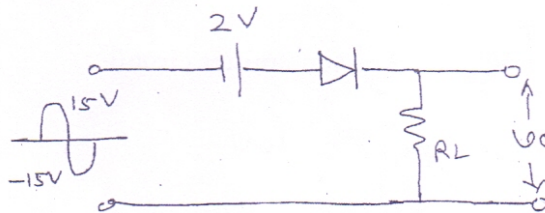


(b) Explain construction & characteristics of n channel Enhancement MOSFET. Draw transfer characteristics & drain characteristics. 10

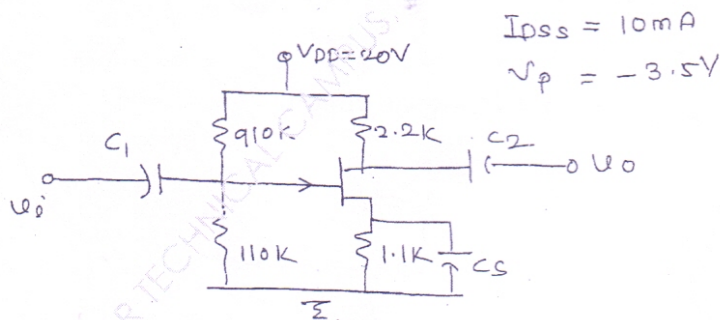3. (a) For JFET amplifier shown below, Calculate A_v , Z_i , Z_o 10



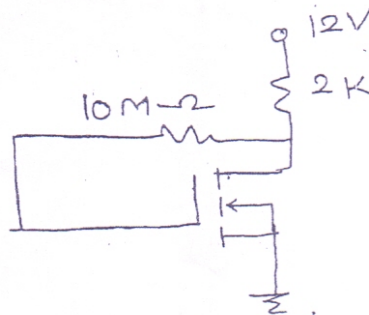(b) For the circuit shown below, calculate I_{DQ} & V_{DSQ} . It is given that $I_{D(ON)} = 6 \text{ mA}$, $V_{GS(ON)} = 8 \text{ V}$, $V_{th} = 3 \text{ V}$ 10




[TURN OVER

Q.P. Code : 5079

3

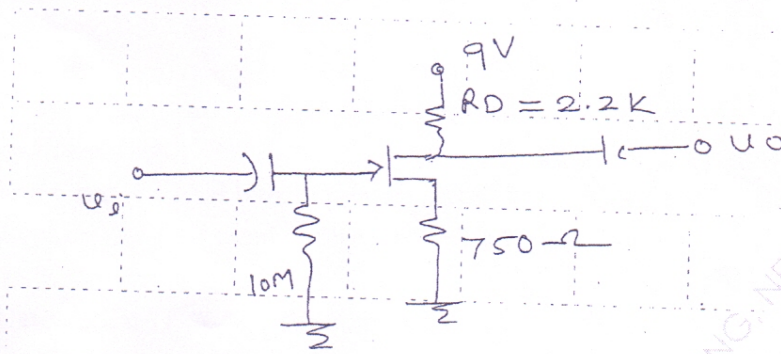4. (a) Explain the working of Wein Bridge Oscillator. Derive the expression for frequency of oscillation for sustained oscillations. 10
(b) Calculate voltage gain of FET amplifier. 10



$$Y_{OS} = 40\mu\text{s}$$
$$I_{DSS} = 8\text{ mA}$$
$$V_{GS\text{ off}} = -4\text{V}$$

5. (a) Draw & explain energy band diagram of MOS capacitor operating in
(i) Accumulation
(ii) Depletion
(iii) Inversion mode 10
(b) Draw emitter follower circuit and derive an expression for voltage gain A_v . 10
6. (a) Draw circuit diagram for phase shift oscillator & derive an expression for frequency of oscillation. 10
(b) Write short notes on any two. 10
(i) Photodiodes
(ii) LC oscillators
(iii) Transistor as a switch
(iv) Schottky diode.