

Q.P. Code : 1488

(3 Hours)

[ Total Marks : 100

- N.B. :** (1) Question No.1 is compulsory.  
 (2) Answer **any three** from remaining six.  
 (3) Assume data where ever needed.

1. (a) Convert JK flip flop to T flip flop. 5  
 (b) Explain subtraction using 2's compliment. 5  
 (c) Convert following 5  
     (i) 1101101 to gray code  
     (ii)  $(95)_{10}$  to excess3  
 (d) Implement OR gate using NAND gate only. 5
2. (a) Explain 555 timer working as Astable multivibrator 10  
 (b) Prove (i)  $(A + \bar{A}B)(A + AB)(A + C) = A$  10  
         (ii)  $AB + \bar{A}C = AB + \bar{A}C + BC$
3. (a) Design a twisted ring counter using J-K flip flop. 10  
 (b) Minimize the expression using K map and implement using basic gates only. 10  
 $F = \Sigma (0,5,9,12,13,14,15)$
4. (a) Explain 10  
     (i) TTL logic family  
     (ii) Integrated injection logic.  
 (b) Draw a logic diagram for 2 bit parallel in serial out register and explain the operation. 10
5. (a) Implement following expression using (i) 8:1 Mux(one) (ii) 4:1 Mux (two) 10  
 $F(A,B,C) = \Sigma (0,2,5,6, 7)$   
 (b) Minimize the following using Quine Mc clusky tabular method 10  
 $F(A,B,C,D) = \Sigma m(1,2,3,5,7,8,9,11)$
6. (a) Implement BCD to Exess 3 Converter. 10  
 (b) Design and implement 3 bit binary to gray code converter. 10
7. Write short notes on following : 20  
     (a) Error detecting and correcting codes  
     (b) Hazards in combinational logic circuits  
     (c) IC 723  
     (d) Master slave JK Flip-Flop