


QP Code : 1249

(3 Hours)


[Total Marks : 100

- N.B. : (1) Question No. 1 is compulsory.
 (2) Solve any four out of remaining six questions.
 (3) Each question carries 20 marks.
 (4) Assume suitable additional data if required.

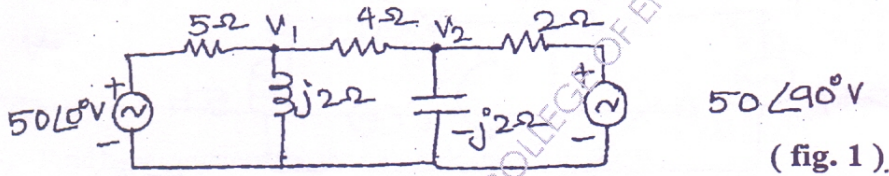
1. (a) State and explain Reciprocity theorem. 5
 (b) Define tree and its properties. 5
 (c) Test whether $F(s) = \frac{s+3}{s+1}$ is positive real function. 5
 (d) Obtain pole-zero plot $F(s) = \frac{s^2+4}{(s+2)(s^2+9)}$ 5
2. (a) Using nodal analysis, find voltages V_1 & V_2 . 10



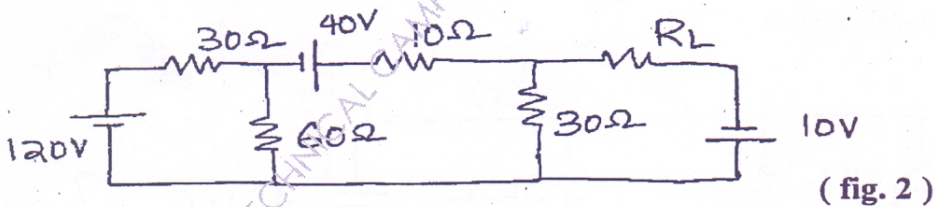- (b) Obtain Norton's equivalent network as seen by R_L . (fig 2) 10




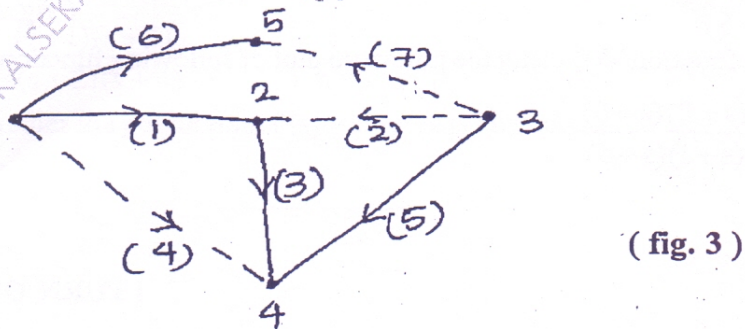3. (a) For the graph shown, write incidence matrix and tie-set matrix. 10




[TURN OVER

- (b) The network of fig 4 is under steady state with switch at position 1. At $t=0$, switch is moved to position 2. Find $i(t)$. 10

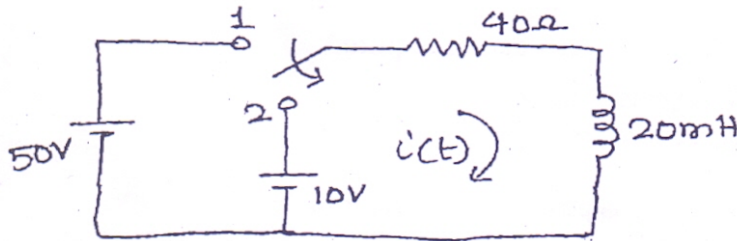


(fig. 4)

4. (a) Determine current $i(t)$ in the network show in fig.5, when switch S is closed at $t > 0$. (Using Laplace transform method.) 10

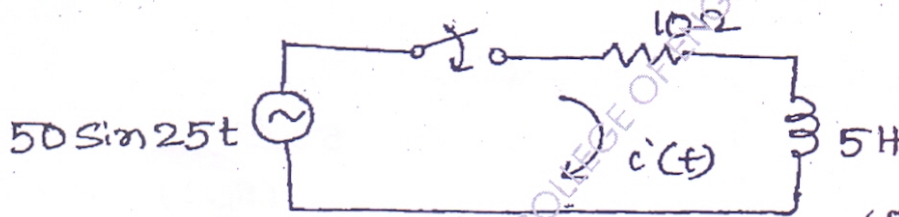

(fig. 5)

- (b) In the given network of fig 6. Switch is opened at $t=0$. Solve for V , dv/dt & d^2v/dt^2 at $t=0^+$. 10

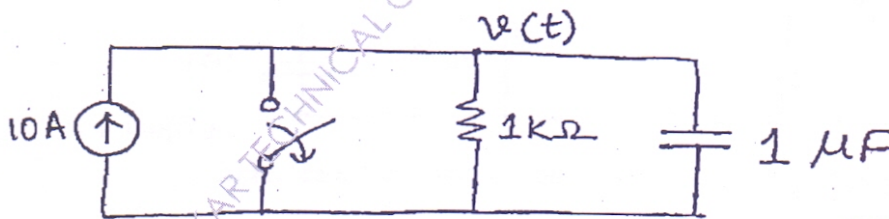


(fig. 6)

5. (a) Find the function $V(t)$ using the pole-zero plot of following function: 10

$$V(s) = \frac{(s+2)(s+6)}{(s+1)(s+5)}$$


[TURN OVER

- (b) Find the driving point admittance function of the network shown in fig. 7. 10

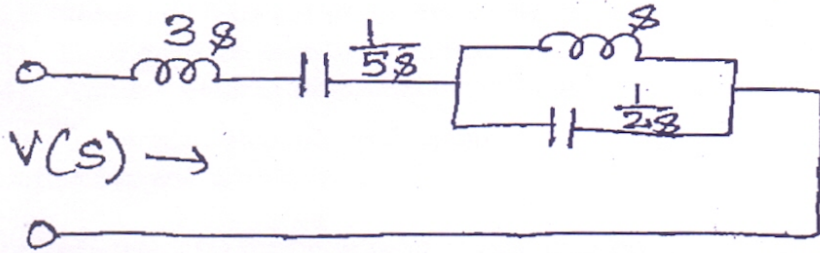


(fig. 7)

6. (a) Determine Y-parameters for the network shown in fig. 8. 10

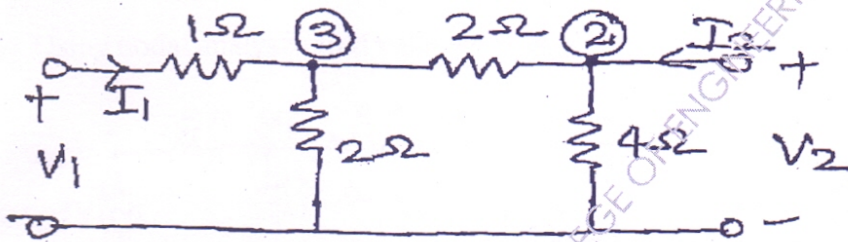

(fig. 8)

- (b) Find h-parameters for the network shown in fig. 9. 10

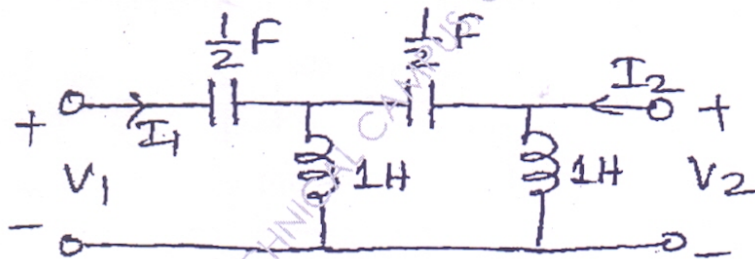

(fig. 9)

7. (a) Determine Foster form of realization of 15

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

- (b) Test whether the polynomial $P(s) = s^5 + s^3 + s$ is Hurwitz. 5