

(3 Hrs.)

[Total Marks 80]

N. B.

- (1) Question No. 1 is compulsory.
- (2) Attempt any three questions out of remaining questions.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.

1. Solve any four :- 20
 - a) Enlist limitations of AC transmission and advantages of HVDC
 - b) Derive the output dc voltage equation of a 6 pulse converter operating with delay angle (α) and overlap angle (μ). When ($\mu < 60$)
 - c) Compare IPC and EPC schemes of converter firing control
 - d) Explain By-pass valve
 - e) Explain causes and consequences of harmonics in HVDC system
2.
 - a) Explain protection against over voltage and over current in HVDC 10
 - b) Explain means of reducing characteristic and non-characteristic harmonics on ac as well as dc side of HVDC line 10
3.
 - a) Show the relation between delay angle and power factor angle with waveforms and phasors. Also show the effect of overlap angle (μ) on conduction of valves for $\mu = 0$, $\mu < 60^\circ$ and $\mu > 60^\circ$ 10
 - b) Explain basic control characteristics of HVDC, also explain the actual control characteristics with modifications 10
4.
 - a) In a monopolar HVDC link which is energized with 3 phase 50 Hz 440 KV source, the dc current is 1.2 KA and the rectifier (6 pulse converter) dc voltage is 500 KV. For delay angle of 15° - 10
 - a) Find commutation resistance
 - b) Find angle of overlap
 - c) If ac voltage is reduced to 200 KV. Find the overlap angle. Assume the dc current is constant
 - b) Explain two methods of IPC (individual phase control) 10
5.
 - a) Explain converter transformer in detail also explain how different it is from a normal power transformer 10
 - b) Explain power reversal in HVDC and significance of current margin 10
6.
 - a) Draw equivalent circuit of a 6 pulse bridge rectifier 10
 - b) Explain causes, analysis (with waveforms), symptoms, cure of a single commutation failure 10