

QP Code : 28859

(OLD COURSE)


(3 Hours)

[Total Marks: 100]


- NB:** 1. Question no. 1 is compulsory.
 2. Attempt any four out of remaining six.
 3. Assume suitable data if required.

Q.1 Attempt any four-


(20)

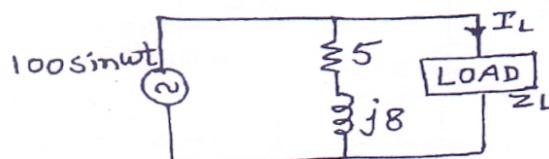(a) Calculate current I_L 

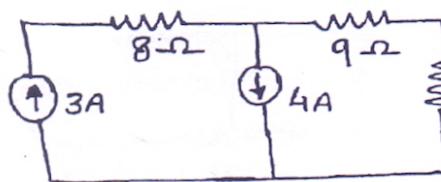
- (b) The Z parameters of two port networks are $Z_{11}=5\Omega$, $Z_{22}=7\Omega$, $Z_{12}=Z_{21}=3\Omega$, calculate ABCD parameters.
 (c) Determine current through 10Ω resistance.



- (d) Draw pole-zero plot for the function $F(s) = \frac{5(s+4)}{(s^2 + 6s + 9)(s^2 + 64)}$
 (e) How many trees are possible for the given graph.

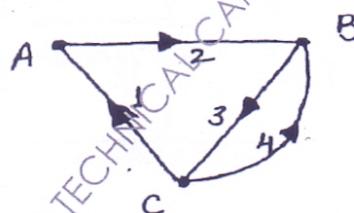
Q.2(a) Find current through 1Ω resistor.

(10)

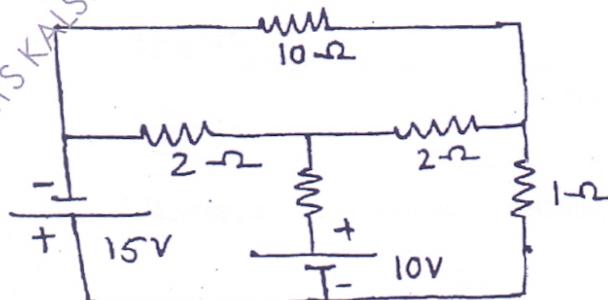


PTO

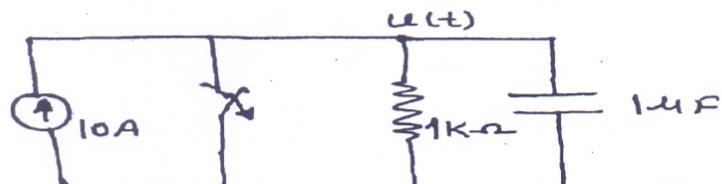
- Q.2(b)** In the given network switch is open at $t=0$, determine $v(t)$, $\frac{dv(t)}{dt}$, $\frac{d^2v(t)}{dt}$ at $t=0^+$. (10)



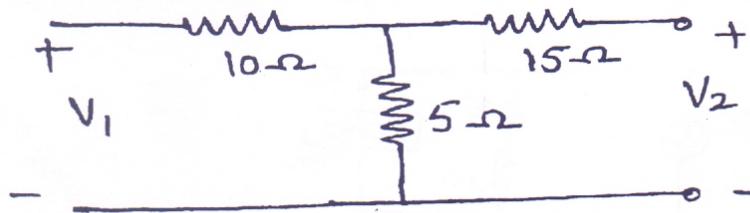
- Q.3(a)** Find the Y parameters of the given network. (10)



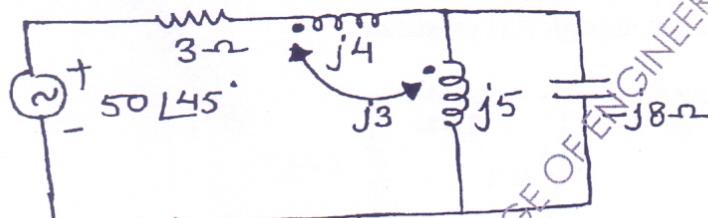- (b)** Find the current through 3Ω using mesh analysis. (10)



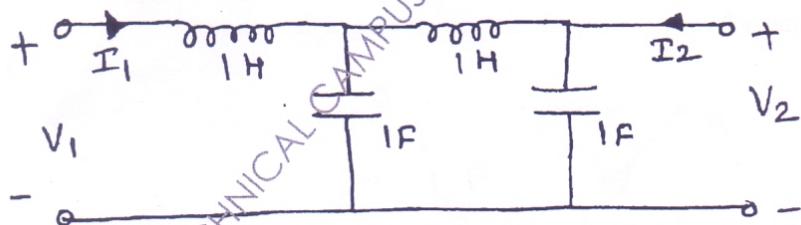- Q.4(a)** Find the network function $\frac{V_1}{I_1}$, $\frac{V_2}{I_1}$ and $\frac{V_1}{V_2}$ for the given network. (10)



- (b)** Check the positive realness of the following function and give reason. (05)

$$Y(S) = \frac{s^3 + 5s}{s^4 + 2s^2 + 1}$$

- (c)** Test whether the following polynomials are Hurwitz (05)

$$s^5 + 8s^4 + 24s^3 + 28s^2 + 23s + 1$$

$$+ 2s^3 + s$$

- Q.5(a)** Realize the driving point impedance in Foster I and Foster II (10)


$$Z(S) = \frac{3(s^2 + 1)(s^2 + 49)}{(s^2 + 9)}$$

PTO

— 3 —

- (b) Determine Z parameters for the given network.

(10)

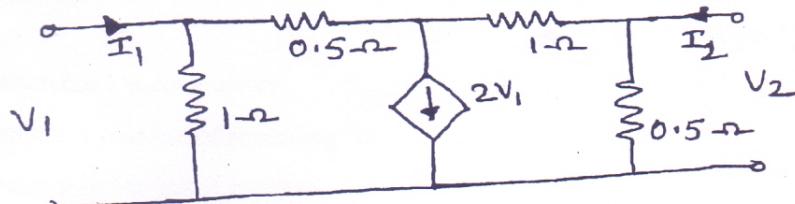


- Q.6(a) Draw the Bode plot for the given Transfer Function.

(10)

$$G(S)H(S) = \frac{10(S+1)}{S(1+0.02S)(1+0.2S)}$$


- (b) For the given network calculate $i_1(t)$ when switch S closed at $t=0$. Consider zero initial conditions.

(10)

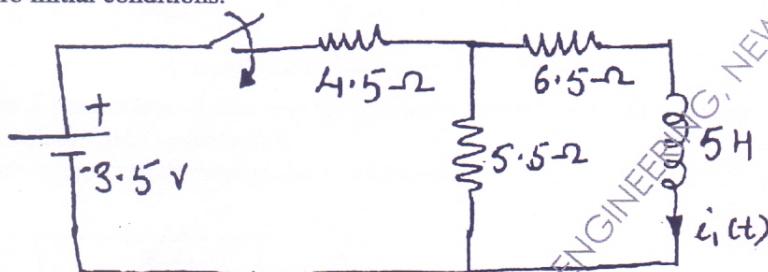

- Q.7(a) Find the current in 10 ohm resistor using Thevenin's theorem.

(10)

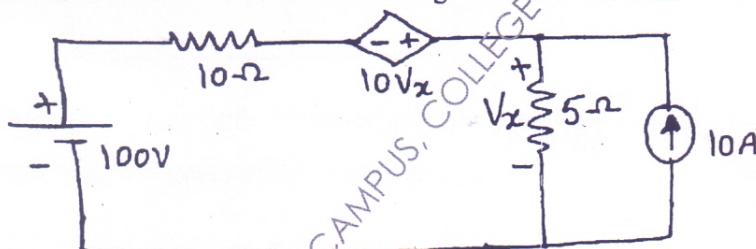

- (b) For the given network write Tie-set matrix and obtain the network equilibrium equation in matrix form using KVL

(10)

