

Q.P. Code : 29249

(3 Hours)

[Total Marks :100

- N.B. : (1) Question No. 1 is compulsory.
(2) Answer any four out of remaining six questions.
(3) Assume suitable data wherever required but justify the same.

1. (a) Assuming the dielectric and conductor losses in transmission line are small (i.e. $G \ll \omega C$ and $R \ll \omega L$), show that propagation constant k can be written

$$\text{as } k = \alpha + j\beta = \frac{1}{2} \left(\frac{R}{Z_0} + GZ_0 \right) + j\omega \sqrt{LC}$$

Where $Z_0 = \sqrt{L/C}$ is the characteristic impedance of the line in the absence of loss.


- (b) Show that the maximum value of normalized resistance is numerically equal to the voltage standing wave ratio i.e. $r_{\max} = \rho$ 5
- (c) You are required to build a low pass butterworth filter that provides an attenuation value of atleast 50 dB at $f = 1.5 f_{3dB}$. What is filter order? How many components (inductors and capacitors) are required to realize this filter? 5
- (d) Explain the current flow in pn junction and give the expression for I diff in terms of diffusion constant and Vdiff in terms of doping concentration. 5
2. (a) Starting from definition of time - averaged power, obtain expression for the power absorbed by the load for lossless and lossy transmission line. 10
- (b) The electric wave field of a positive z-travelling wave in a medium with relative dielectric constant of $\epsilon_r = 4$ and with frequency of 5 GHz is given by $E_x = E_0 \cos(\omega t - kz)$ V/m 10
- (i) Find the magnetic field if $E_0 = 10^6$ v/m
- (ii) Determine phase velocity and wavelength.
- (iii) Compute the spatial advance of the travelling wave between time intervals $t_1 = 3 \mu s$ and $t_2 = 7 \mu s$
3. (a) An $N = 3$ chebyshev bandpass filter is to be designed with a 3dB passband ripple for a communication link. The center frequency is at 2.4 GHz and filter has to meet a bandwidth requirement of 20%. The filter has to be inserted into a 50Ω characteristic line impedance. Find the inductive elements and plot the attenuation response in the frequency range of 1 to 4 GHz. 10

[TURN OVER

Q.P. Code : 29249

2

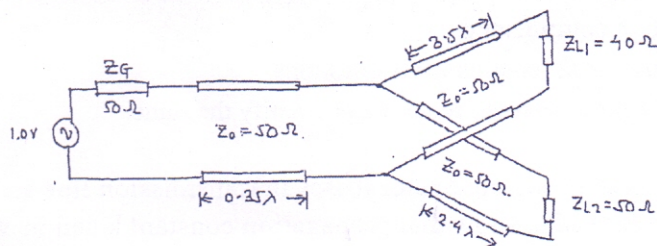- (b) For the following system, find the both the power produced by the source and the power delivered to each load. 10



4. (a) A short circuited 50 W transmission line section is operated at 1 GHz and possesses a phase velocity of 75% of the speed of light. Use both the analytical and the smith chart approach to determine the shortest length required to obtain an 4.7 nH inductor 10
- (b) Explain different filter parameters with generic attenuation profile diagram. 10
5. (a) Explain high frequency resistors, capacitors and inductors by giving related equations and wave forms. 10
- (b) Explain stocky contact with the help of energy band diagram for (i) metal and semiconductor do not interact 10
(ii) metal semiconductor contact.
6. (a) Explain the design procedure of small signal BJT amplifier. (DC circuit design and RF circuit design) 10
- (b) For two pn-diodes with abrupt junction, one of which is made of Si and another is made of GaAs, with $N_A = 10^{17} \text{ cm}^{-3}$ and $N_D = 2 \times 10^{14} \text{ cm}^{-3}$ in both cases : 10
- (a) Find the barrier voltage.
- (b) Find the maximum electric field and the space charge region width.
- (c) Plot the space charge, potential, and electric field distribution along the diode axis.
7. Write short note on following : 20
- (a) One to one mapping between the normalized impedance plane and the reflection coefficient plane.
- (b) Chip components.
- (c) Parallel and series connections.
- (d) Microstrip transmission lines.