

(3 Hours)

| Total Marks :100

- N.B. :** (1) Question No. 1 is **compulsory**.  
 (2) Attempt any **four** questions from remaining **six** questions.  
 (3) **Use smith chart** if **necessary**  
 (4) **Figures** to the **right** indicate **full** marks.

1. (a) Explain the terms conversion loss and Isolation with reference to mixer. **5**  
 (b) Find S- parameters of two port series network,  $Z=500\Omega$  and  $Z_0=50\Omega$ . **5**  
 (c) Explain 1-dB compression point. **5**  
 (d) What are the characteristic of the power amplifier? **5**
2. (a) Derive the transducer Power Gain equation as **10**
- $$G_T = \frac{P_L}{P_{avg}} = \frac{|s_{21}|^2 (1-|\Gamma_s|^2)(1-|\Gamma_L|^2)}{|1-\Gamma_s \Gamma_{in}|^2 |1-s_{22} \Gamma_L|^2}$$
- (b) A BJT has the following S- parameters. Is the transistor unconditionally stable? **10**  
 Draw input and output stability circle?  
 $S_{11} = 0.65 \angle -95^\circ$ ,  $S_{21} = 0.5 \angle 115^\circ$ ,  $S_{12} = 0.035 \angle 40^\circ$ ,  $S_{22} = 0.8 \angle -35^\circ$
3. (a) For the two port network ABCD matrix is given by **10**
- $$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.5 & j1.6 \\ j1.6 & 0.5 \end{bmatrix}$$
- Find scattering matrix if  $Z_0 = 100\Omega$ . Find condition of reciprocity.
- (b) Discuss various mixer topologies. Compare performance of them. **10**
4. (a) Discuss amplifier linearization methods. **10**  
 (b) Define and explain noise correlation matrix for general noise two port network. **10**  
 What is congruence transformation?
5. (a) Explain broad band microwave amplifier using balance amplifier design technology. **10**  
 (b) Compare microwave amplifier with microwave oscillators. **10**

[Turn Over

6. (a) Discusses generator tuning networks for microwave oscillators. **10**  
(b) A GaAs FET is biased for minimum noise figure and has following S- parameters **10**  
and noise parameters at 4 GHz ( $Z_0 = 100\Omega$ ). Design an amplifier with 2dB  
noise figure maximum gain compatible with this noise figure. Assume device  
is unilateral.

$$S = \begin{bmatrix} 0.6 \angle -60^\circ & 0.05 \angle 26^\circ \\ 1.9 \angle 81^\circ & 0.5 \angle -60^\circ \end{bmatrix}$$

$$F_{\min} = 1.6\text{dB}, \quad (\Gamma_{\text{opt}}) = 0.62 \angle 100^\circ, \quad R_N = 20\Omega$$

7. Write short note on (any **two**):- **20**
- (a) Noise figure test equipments
  - (b) Power distributed amplifiers
  - (c) Microwave resonators
-