

MODULE 2

Page No.

Date: / /

* Analysis of simple Rectifier circuits:

(lec 3)

• Assumptions & justifications:

- AC voltage has no impedance & delivers constant voltage of sinusoidal waveform & constant frequency (phase shifted by 120°)
 - If poly phase source it delivers balance voltages
 - Transformers have no leakage impedance or exciting admittance (\therefore practically we should go for large leakage 'Z'. For analysis, here 'Z' = 0)
 - The dc load has infinite inductance (ie. dc current is constant & ripple free) (o/p voltage is not ripple free)
 - Valve is ideal (ie. offers zero resistance during conduction & infinite resistance during non-conducting state).
- ### • Some definitions:
- The Volt-Ampere rating of the valve is taken as the product of average current & peak inverse voltage.
 - Peak inverse voltage (PIV) is the peak voltage that appears across the valve during non conduction state.
 - Rating (VA) of the transformer is the product of rms voltage & rms current.

Page No.

Date: / /

- Pulse no of a converter is the number of pulsations (cycle of ripples) of dc voltage per cycle of ac voltage.

- A group of valves in which only one valve conducts at a time (neglecting overlap) is known as commutation group (q).

- V_{do} is the average dc voltage the terminal of converter when delay angle is zero.


- Number of series valves is represented by 's'

- Number of parallel valves is represented by 'r'

- Thus;

$$p = q \times s \times r$$

Half wave Rectifier (1ϕ):

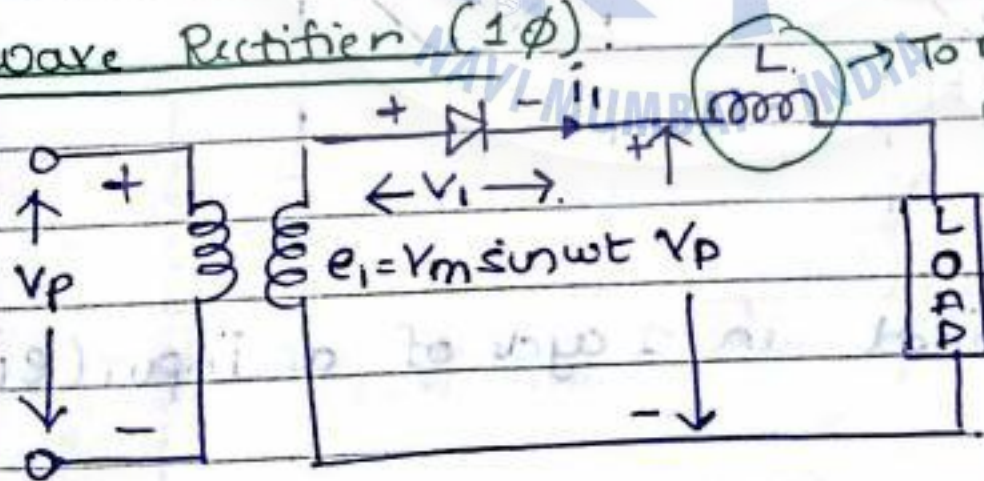


→ To make dc current ripple free but doesn't affect much because we get only half cycle of p. (\therefore dc current cannot be constant) ↓

- It is the simplest rectifier

- Current is inherently intermittent; so dc current cannot be constant.

- DC current & voltage pulsate at the same freq as the ac voltage & current.

- Useful for small power applications

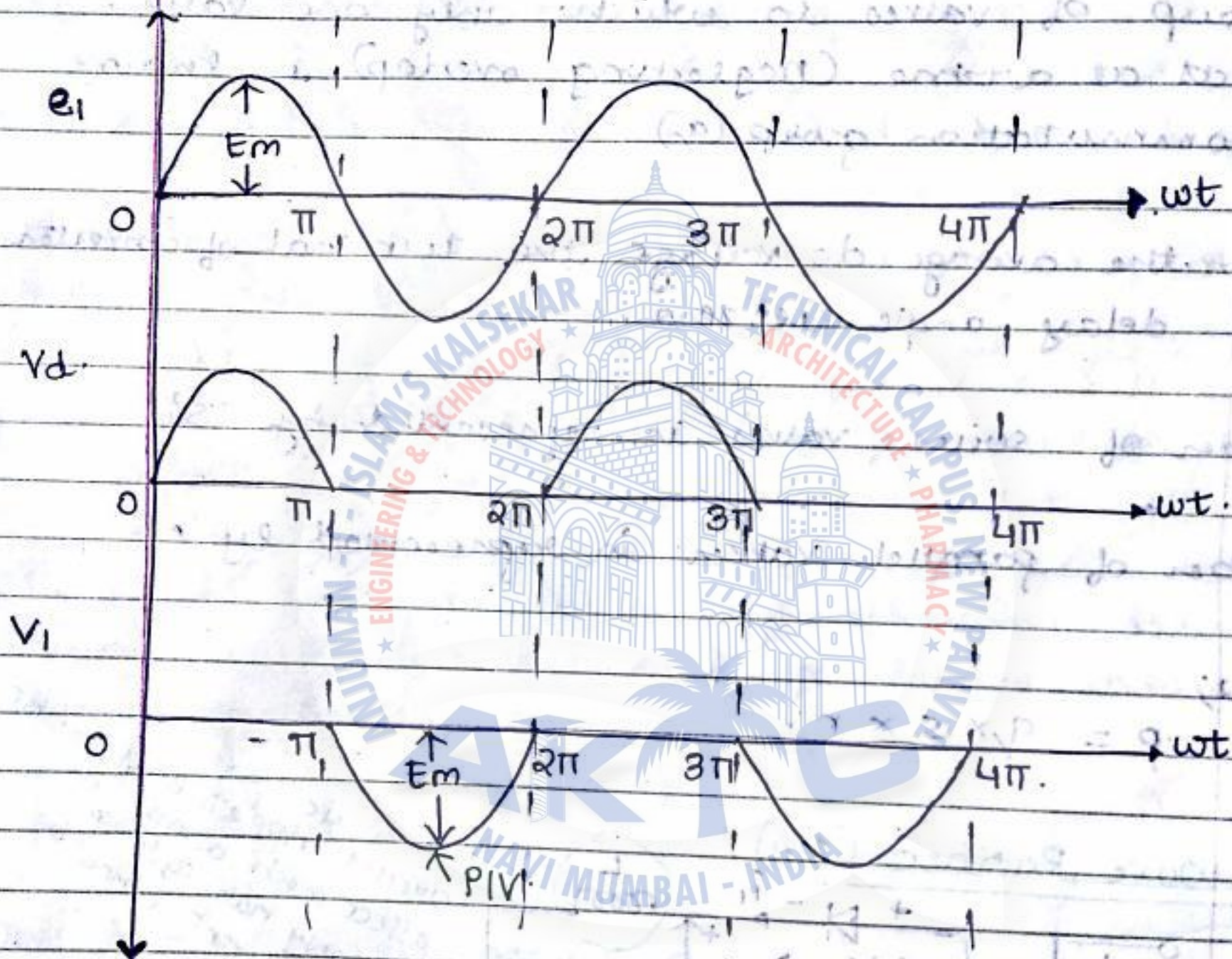

- No of pulses ^(of V_d) obtained in 1 cycle of ac input (e_1) is just 'one'

$$V_1 = e_1 - V_d$$

$$e_1 = E_m \cos \omega t$$

- V_{do} (Average dc voltage in one cycle)

$$V_{do} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t)$$

We cant take $(0-2\pi)$ because +ve half is present but -ve half is zero. So considering $(0-\pi)$ & dividing by 2π

$$= \frac{1}{2\pi} (V_m) (-\cos \omega t)_0^{\pi} = \frac{V_m}{\pi}$$


- $PIV = V_m$ (or E_m)


- Pulse Number $(P) = 1$

• Full Wave Rectifier (1ϕ)

- It has two valves & one transformer with center tapped secondary ($T:1:1$)

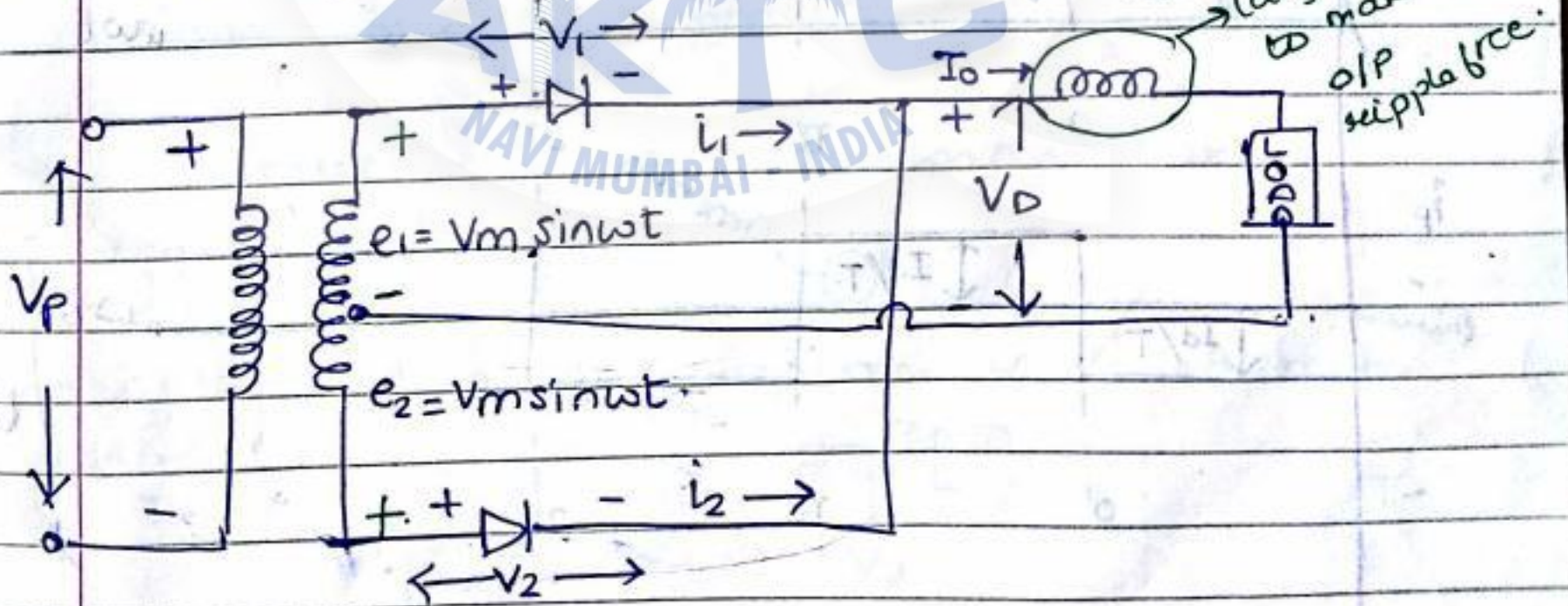- e_1 & e_2 are having phase difference of 180° .



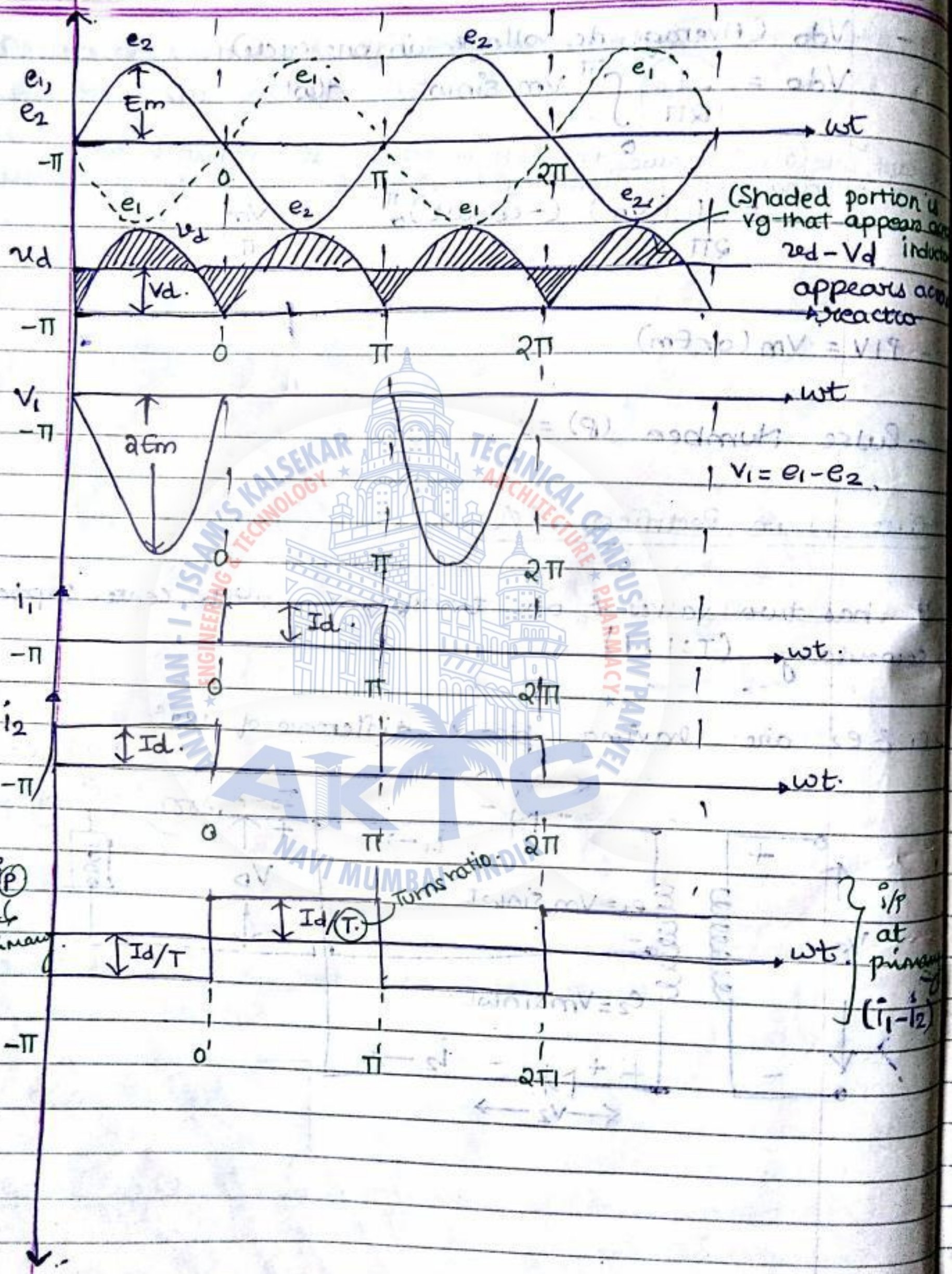

(Shaded portion is V_d that appears across $2\omega L$ inductor appears across reactor

$V_1 = e_1 - e_2$

i/p at primary $(i_1 - i_2)$

$$e_1 - V_1 - V_D - V_2 = 0 \quad \therefore e_1 - V_D = V_1 + V_2$$

$$V_1 = e_1 - V_D - V_2$$

Page No.
 Date: / /

$$\rightarrow V_{do} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{\pi} (-\cos \omega t) \Big|_0^{\pi} = \frac{2V_m}{\pi}$$

We are taking the average of one pulse only i.e. one half cycle. cuz after that the waveform is continuous i.e. its cyclic.

$\rightarrow PIV = 2V_m$

\rightarrow Pulse Number (P) = 2. (\because 2 pulses in 1 cycle)

\rightarrow Average current = $I_d/2$.


\rightarrow Valve Rating = $V_m I_d$.

\rightarrow Transformer is not utilized properly so we go for the bridge rectifier ckt.


• Full Wave Bridge Rectifier (1ϕ).

- It has 4 valves and one transformer having tap ratio T:1

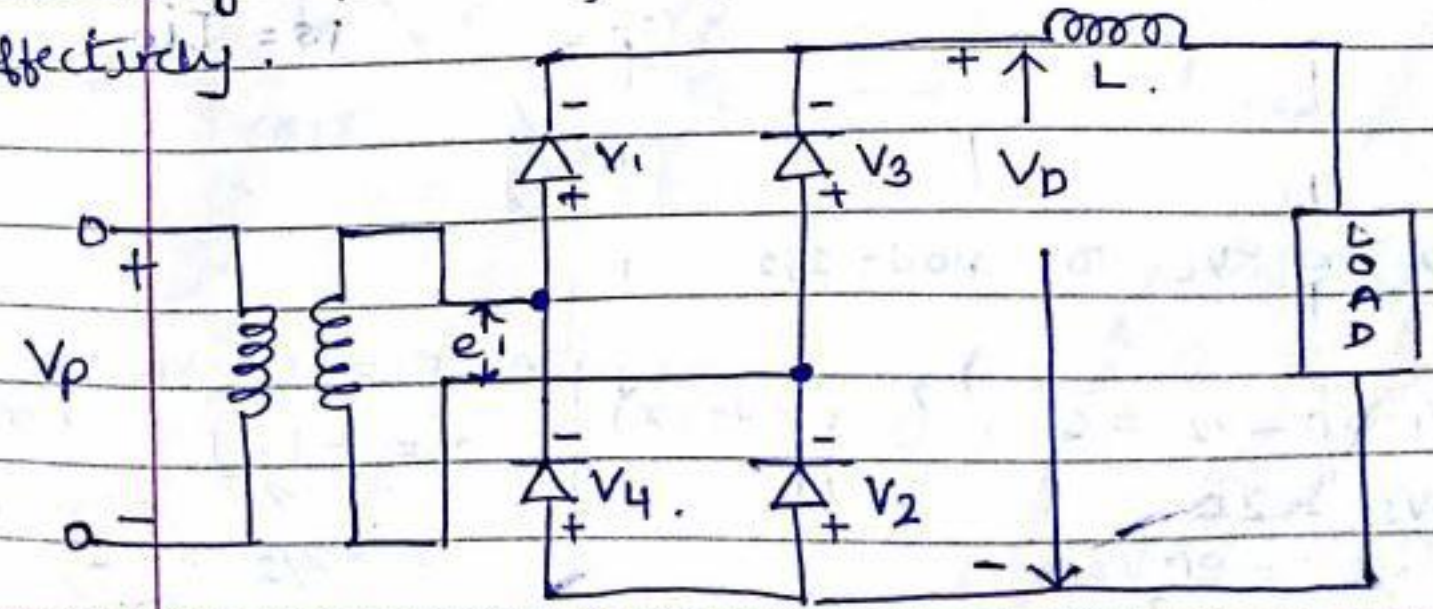- Secondary winding of transformer is used more effectively.



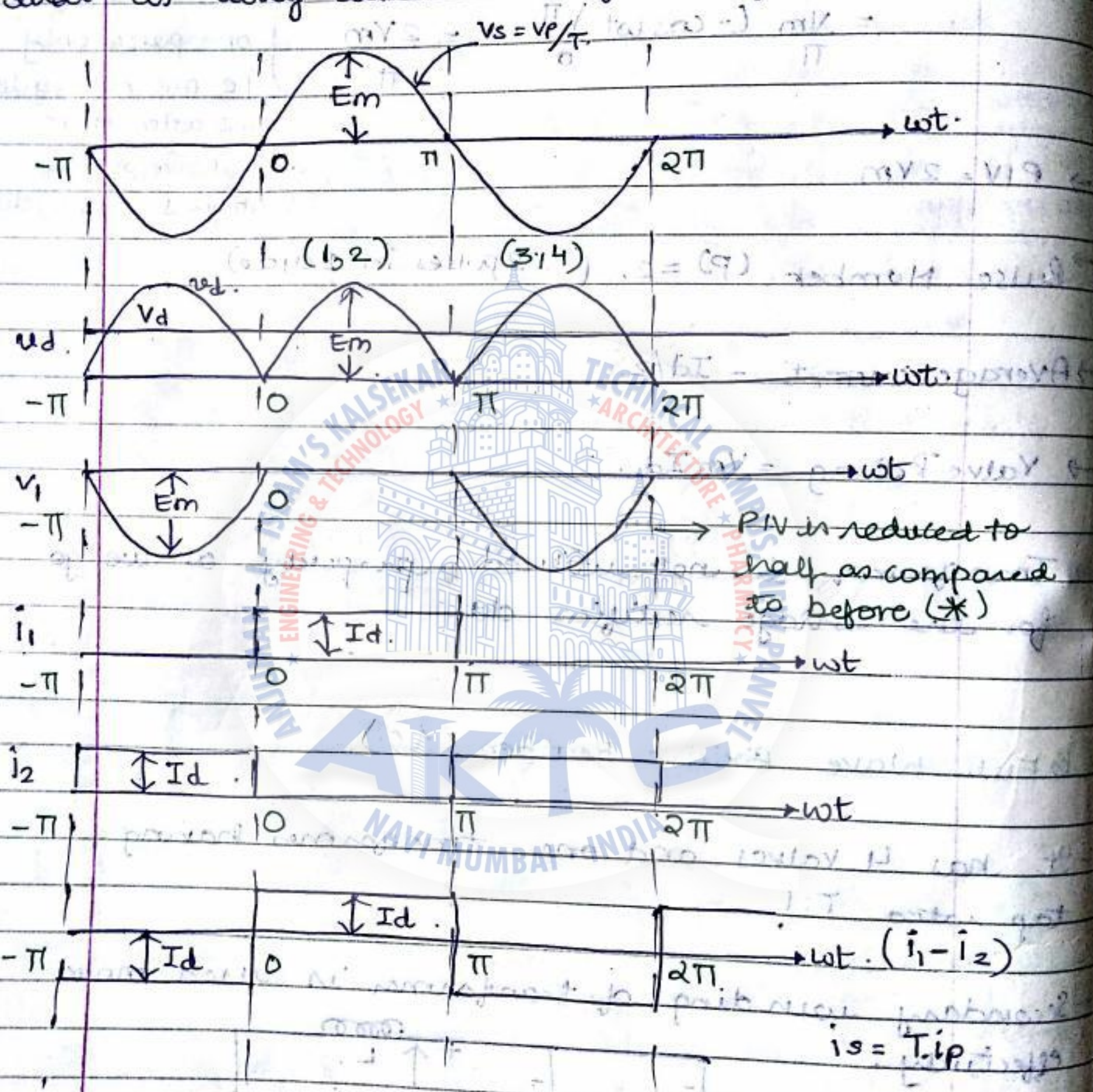Transformer is utilized twice in one cycle, that is why utilization of transformer is more.



PIV is reduced to half as compared to before (*)

* On applying KVL to diode 1, 2.

$$e_1 - v_1 - v_D - v_2 = 0 \quad (\because v_1 = v_2 = x)$$


$$e_1 - v_D = 2x$$

$$\therefore x = \frac{e_1 - v_D}{2}$$

$$\text{let } e_1 = -1; v_D = 1$$

$$\therefore x = \frac{-1 - 1}{2} = -2/2 = -1$$

hence \rightarrow surge PIV

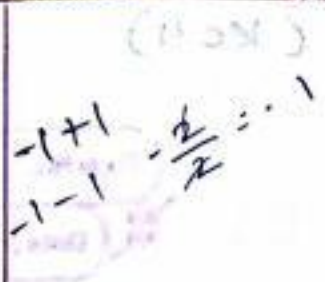


$$V_{do} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{1}{\pi} V_m (-\cos \omega t) \Big|_0^{\pi} = \frac{2V_m}{\pi}$$

- $PIV = V_m$

- Pulse Number (p) = 2
- Average Current = $I_d/2$
- Valve Rating = $0.5 V_m I_d$ } Power rating reduced by half & hence cheaper.
- Four valves are used.
- It is used for high voltage applications where valve PIV is a limiting factor.

• 3φ Rectifiers (one way)

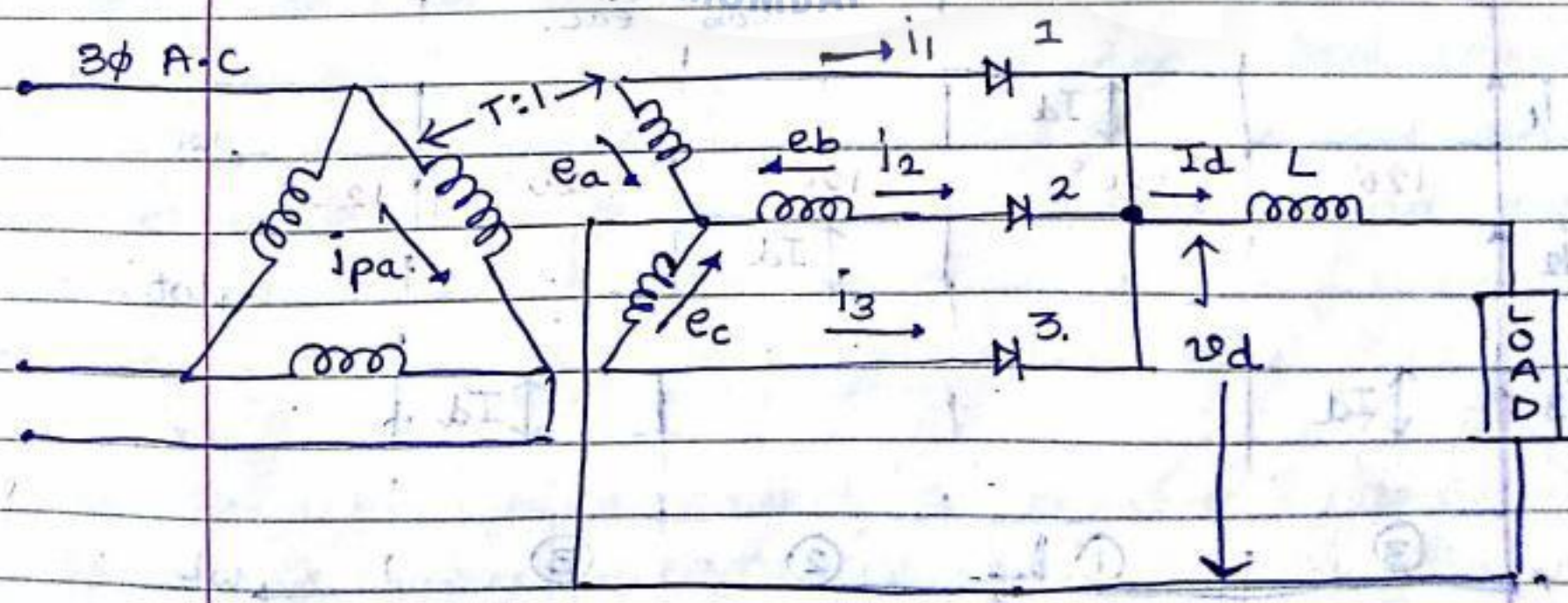


nce
single
PIV

- There is a continuous conduction of valves (Valve 1-2) ... and so on.

- It is assumed 'dc' o/p 'I' is ripple free & the dc o/p voltage is v_d which is instantaneous value.

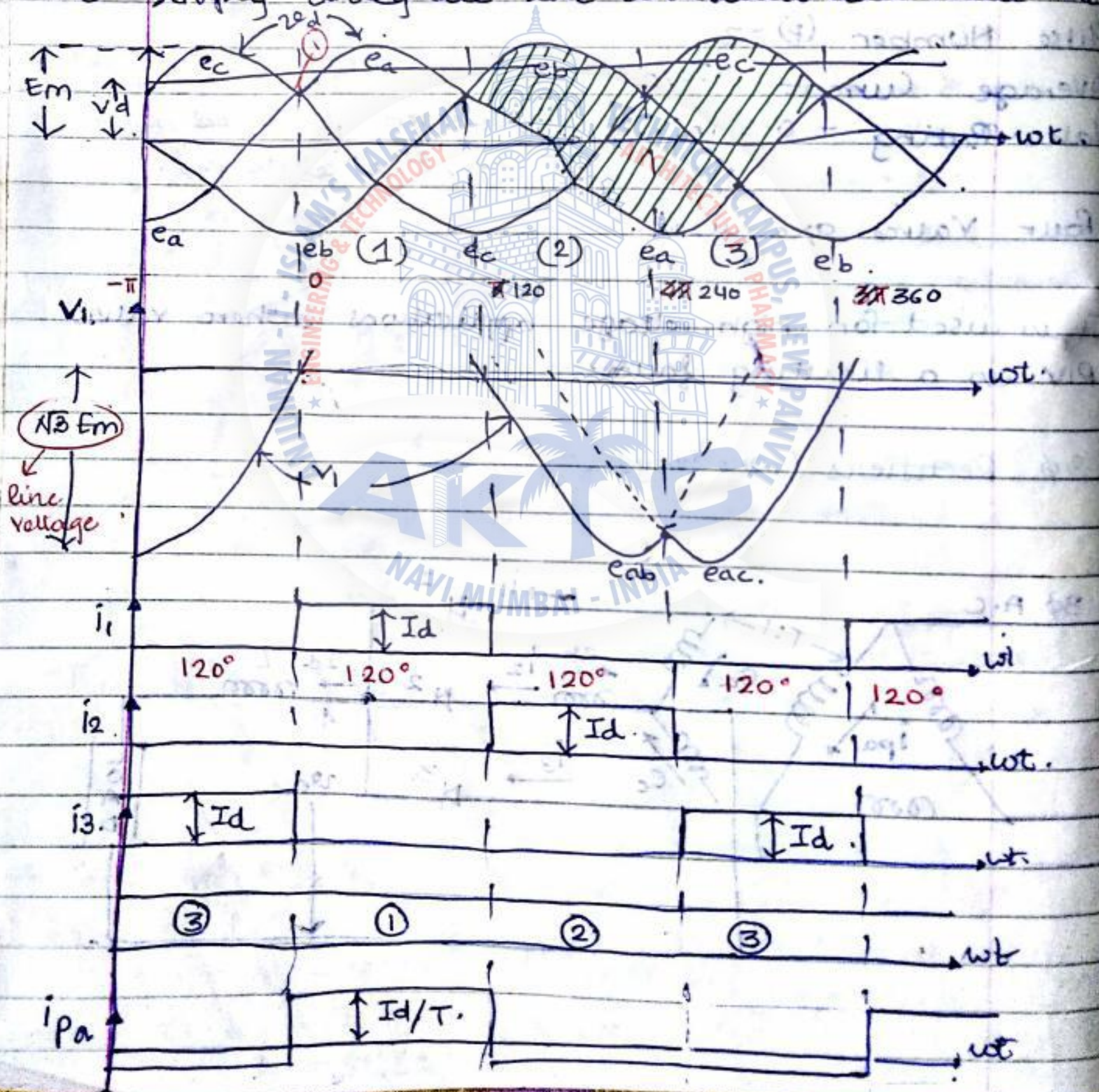- In order to obtain average value of v_d i.e. (V_d) we simply integrate the instantaneous value v_d .



3) ① At that instant $e_a = e_c$ & beyond point on e_a , $e_a > e_c$ & valve 1 can be fired because the condition for any valve to ignite/conduct is that if it is forward biased.

- When valve 3 is conducting the voltage across valve 1 i.e. V_1 is

3 phases in one cycle of V_1 :

$\left\{ \begin{array}{l} V_1 = e_a - e_c \\ V_1 = 0 \\ V_1 = e_a - e_b \end{array} \right.$	→ when it is off (\because valve 3 is conducting)
	→ when it is conducting
	→ when it is off (\because valve 2 is conducting)

- commutation voltage is the voltage at which valve is going to be fired.

- Hence the commutation voltage for valve ① when valve 3 is conducting is $(e_a - e_c)$ & should be +ve for firing of valve 1.

- One cycle has 3 pulses. $(PIV = \sqrt{3} E_m)$
 $(VA \text{ rating} = V_{peak} \cdot I_{av} = \sqrt{3} V_m \cdot \frac{I_d}{3})$

- The problem is however about the transformer which is not utilized properly. In the primary side only 120° current is being conducted in one cycle.



Remaining time the 2 phases are idle. ($\because X_{mer}$ is not symmetrically loaded)

- Thus there is appearance of 'dc' current in the secondary winding of transformer, which is again a disadvantage.

* Three phase Rectifier circuit

(Lec 5)


⇒ Consider the previous circuit,

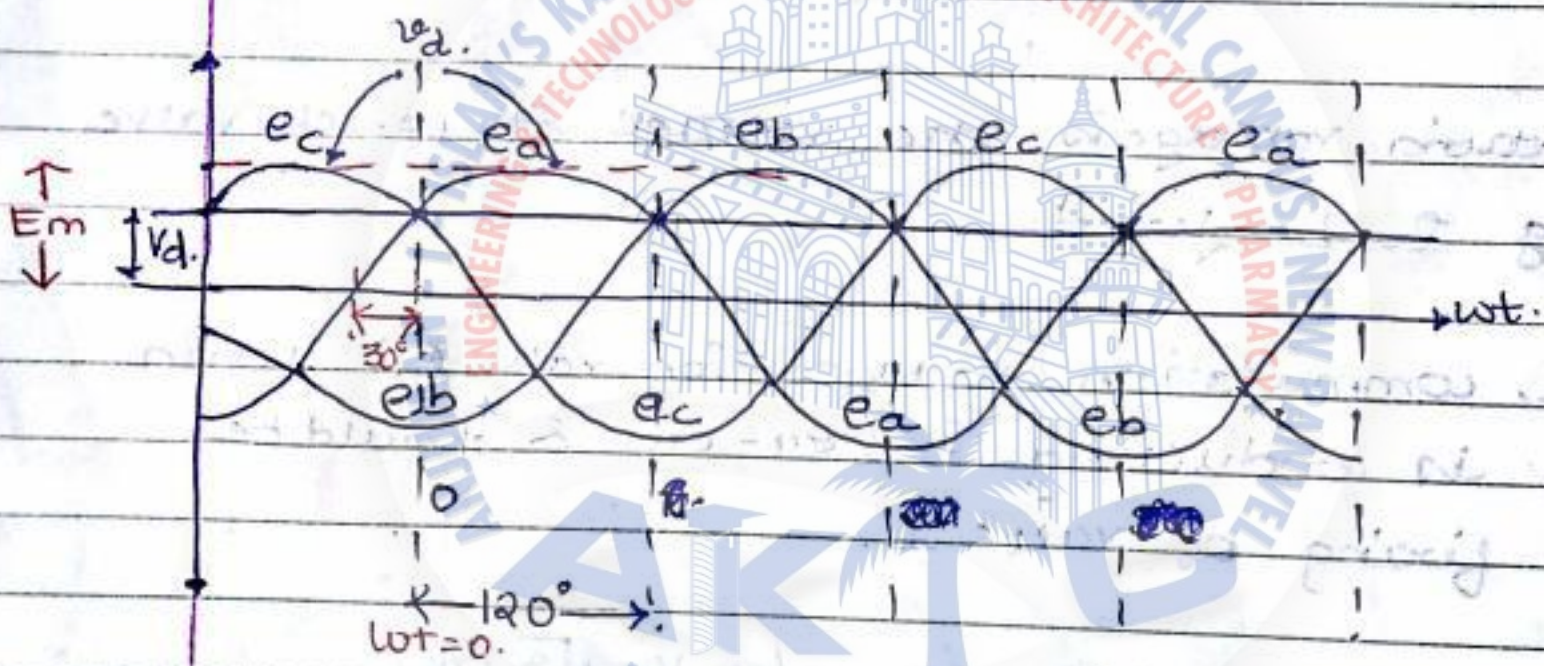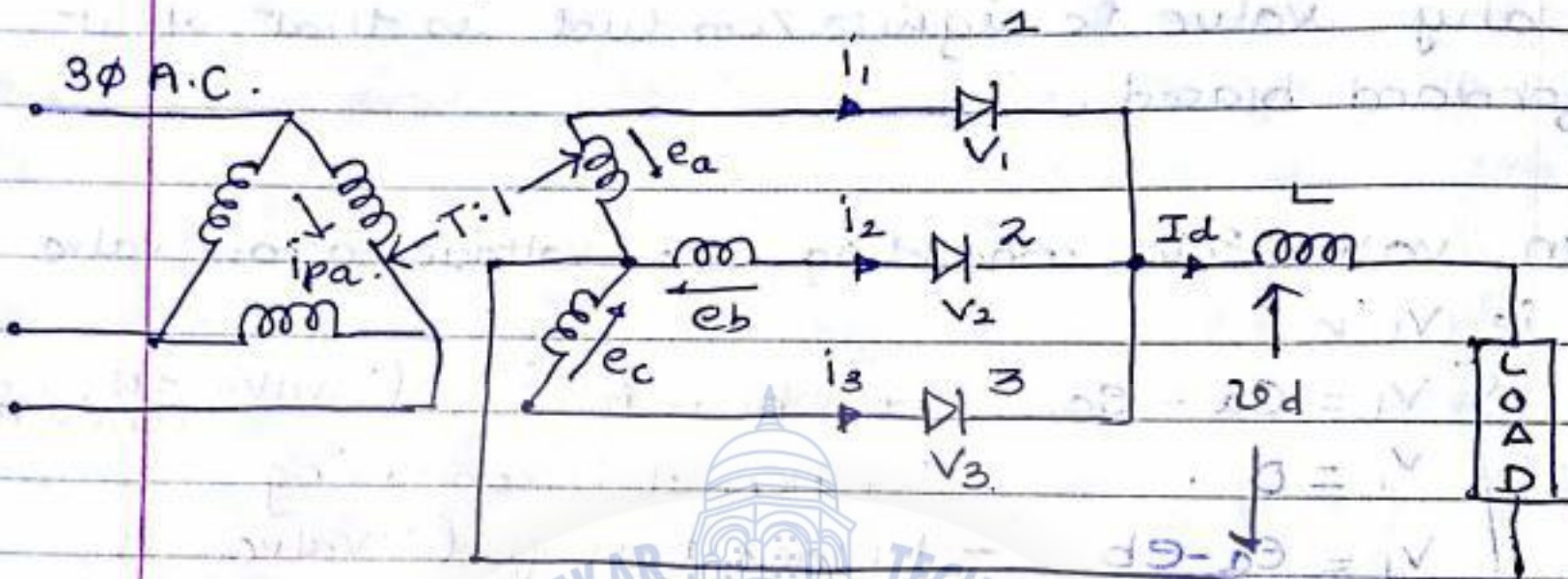

- $e_a = E_m \sin(\omega t + 30^\circ)$

- $V_{d0} = \frac{1}{\frac{2\pi}{3}} \int_0^{120^\circ} E_m \sin(\omega t + 30^\circ) d(\omega t)$

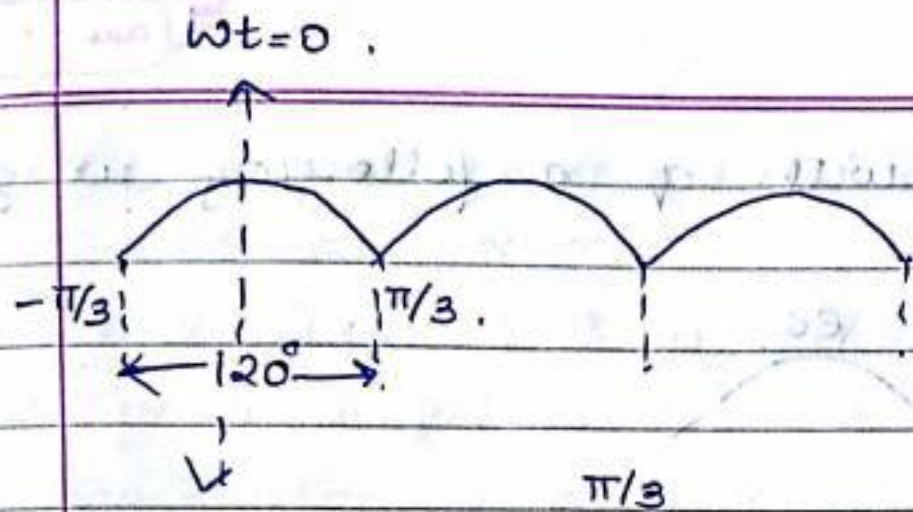- To convert the sin term into cos term the following is done. It is done to make integration simple



$$V_{do} = \frac{1}{2\pi/3} \int_{-\pi/3}^{\pi/3} E_m (\sin \omega t) d(\omega t)$$

$$= \frac{1}{2\pi/3} (E_m) (\sin \omega t) \Big|_{-\pi/3}^{\pi/3}$$

$$= \frac{1}{2\pi/3} (E_m) (\sqrt{3})$$

$$V_{do} = \frac{3\sqrt{3} E_m}{\pi}$$

- PIV = $\sqrt{3} E_m$

- Pulse Number (P) = 3


- Valve 1 voltage $V_1 = 0$ $0 \leq \omega t \leq 120^\circ$
 $= e_a - e_b$ $120^\circ \leq \omega t \leq 240^\circ$
 $= e_a - e_c$ $240^\circ \leq \omega t \leq 360^\circ$

- To calculate $P = r \times s$, we have;

$$P = 3 \times (3 \times 1 \times 1)$$

Annotations:
 - 3 is labeled as "one parallel path of valves"
 - $(3 \times 1 \times 1)$ is labeled as "one series path of valves"

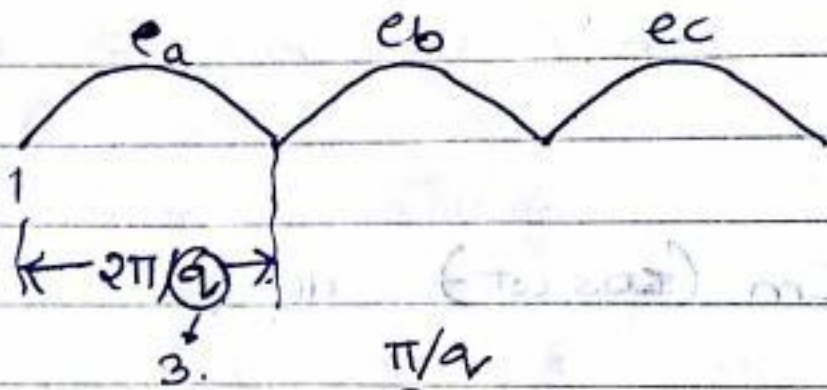- Now replacing '3' with q as following we get.



$$V_{do} = \frac{1}{2\pi/q} \int_{-\pi/q}^{\pi/q} E_m \cos \omega t \, d\omega t.$$

$$V_{do} = \frac{S \cdot q}{2\pi} E_m \sin\left(\frac{\pi}{q}\right)$$

[s is added because there is one valve for a phase, if there are two valves, the voltage is doubled $s=2$, so on...] i.e. ' s ' no. of series valves].

- It is worthwhile to mention that when '1' conducts 2 & 3 will be off. Now as '1' gets turned off, '2' will go 'on'. This however does not take place instantaneously & there is a short period for which '1' & '2' will both be 'ON' which results in short circuiting causing maloperation of the converter ckt.

- But here we are considering the ideal analysis, where we assume the current is instantaneously taken up by valve 2 as valve one turns off.

→ If q is even, PIV occurs when the valve with a phase displacement of 180° is conducting & will be equal to $PIV = 2E_m$.

Date: / /


• PIV in general terms

$PIV = 2E_m$ → q is even

→ If q is odd, PIV occurs when the valve with a phase displacement of $\pi \pm \pi/q$ is conducting & will be equal to $PIV = 2E_m \cos(\pi/2q)$ → q is odd.

• Commutation group is chosen such that only one valve is conducting

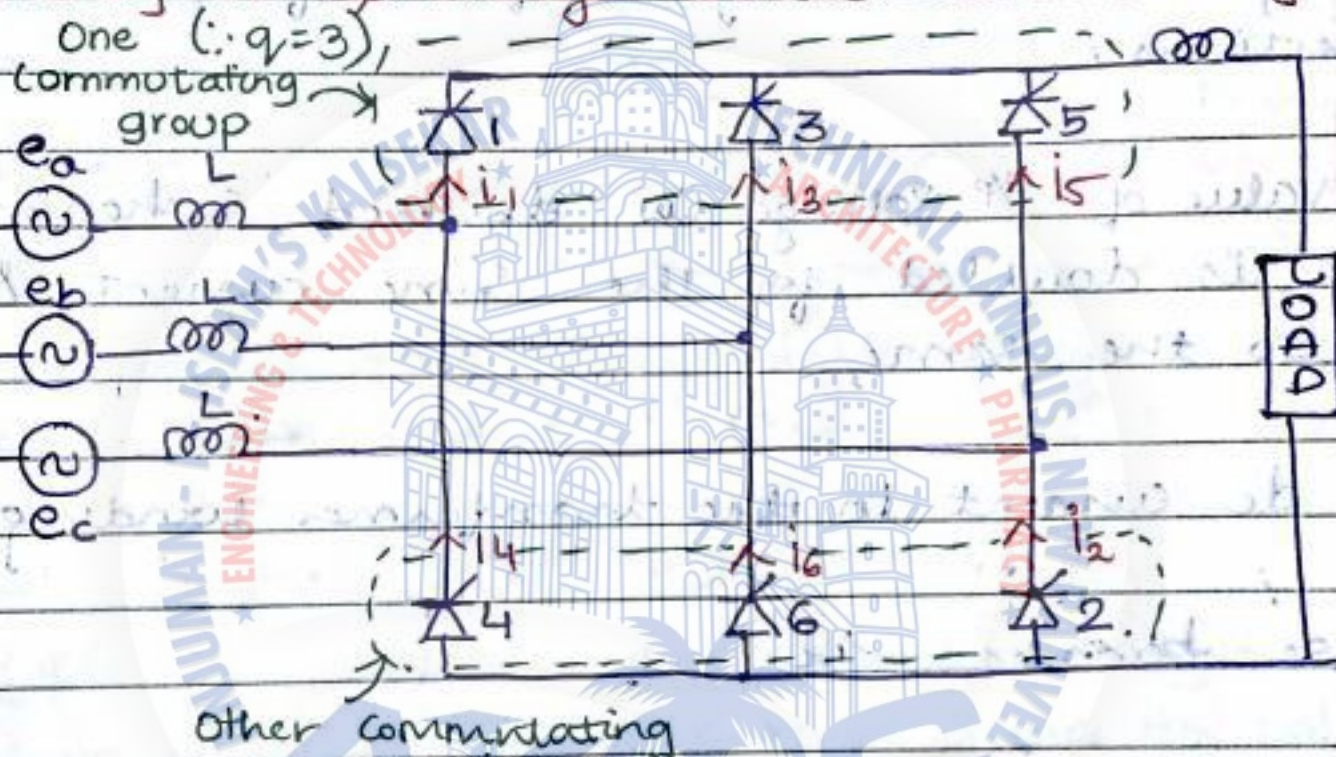* 3 ϕ two way or 3 ϕ Bridge Rectifier (Graetz Bridge)



- For the circuit shown above,

$q=3$ (one valve of the commutating group will be conducting at a time)

- For the circuit shown,

$S=2$ (two valves/path are conducting at a time)


therefore o/p voltage will be double compared to previous case i.e. the one way rectifier ckt.

- This is a connection of two one way rectifier ckt.
- In the 3 ϕ , one way ckt, if the three volts are reversed, the circuit operates as before except the direction of dc voltage & current are reversed.
- In the bridge converter, the same transformer is feeding two one way rectifiers of opposite connections.
- The value of %P voltage is doubled & hence the power is doubled for the same current & the PIV is also the same.
- No dc current in the transformer winding.
- Pulse becomes six.

* Desired features of Converter circuit

- (1) High pulse number (p) [to reduce harmonics on ac & dc side. P cannot be \uparrow a lot, else it makes ckt complex]
- (2) PIV/V_{do} should be as low as possible
- (3) V_{do}/E should be as high as possible
- (4) Transformer utilization factor (TUF) should be near to unity

(1) High Pulse Number (p)

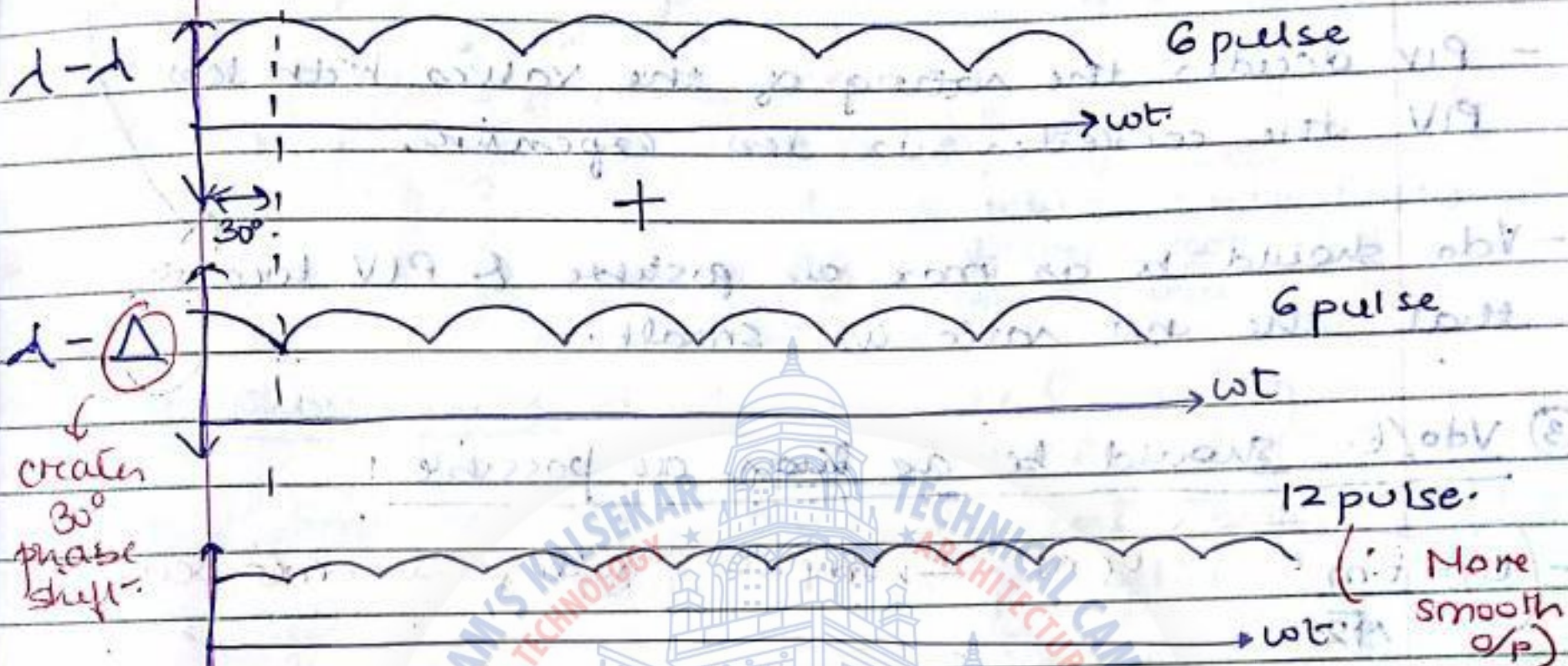

Harmonic $H_n = np \pm 1$

- 6 pulse → 5, 7, 11, 13, ...

- 12 pulse → \otimes , 11, 13, ...

5, 7 are cancelled by the Δ - Δ transformer hence do not reflect on ac side.

- It is worthwhile to mention that the lower order harmonics have the larger magnitude as compared to higher order harmonics.
- With the cancellation of 5, 7 (having ↑ magnitude), we just have to get rid of 11, 13 ... i.e. the higher order harmonics which are easier to filter out.

We know; $PIV = 2 E_m$ ($q = \text{even}$)
 $= 2 E_m \cos(\pi/2q)$ ($q = \text{odd}$)

$$V_{do} = \frac{s q E_m \sin(\pi/q)}{2\pi}$$

$$\therefore \frac{PIV}{V_{do}} \begin{cases} = \frac{2\pi}{s q \sin(\pi/q)} & (q = \text{even}) \\ = \frac{\pi}{s q \sin(\pi/2q)} & (q = \text{odd}) \end{cases}$$

② PIV/V_{do} should be as low as possible:

- PIV decides the rating of the valves. With less PIV the converter is less expensive.
- V_{do} should be as max as possible & PIV low so that the net ratio is small.

③ V_{do}/E should be as high as possible:

- $E = \frac{E_m}{\sqrt{2}}$ Erms \rightarrow Impressed voltage in Xmer Secondary

$$- V_{do} = \frac{s q E_m}{2\pi} \sin(\pi/q)$$


or: \rightarrow o/p dc voltage:

$$- \frac{V_{do}}{E} = \frac{s q (\sqrt{2}) \sin(\pi/q)}{2\pi}$$

\downarrow
Voltage in secondary of Xmer

- The above means that for a small value of 'E' the resulting 'V_{do}' should be high, in other words the ratio of V_{do}/E should be high.
- The ratio of V_{do}/E is dependent on the two parameters i.e. 's' & 'q'.
- Following combinations of q, r, s are possible to get 'G' = pulse.

$$P = q \times r \times s$$

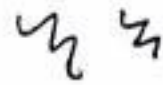

Page No.

Date: / /

Pulse.	q	r	s
6	6	1	1
	3	2	1
	3	1	2
	2	3	1
	2	1	3


→ optimal configuration is the Gartz Bridge which gives all the desired features of converter circuit.

④ TUF should be unity

$$- TUF = \frac{\text{Rms secondary Power}}{\text{dc Power}} = \frac{V_{rms} \cdot I_{rms}}{V_{dc} \cdot I_{dc}} = 1$$

$$= \frac{P_t}{V_d \cdot I_d} = \frac{V_t I_t}{V_d \cdot I_d}$$

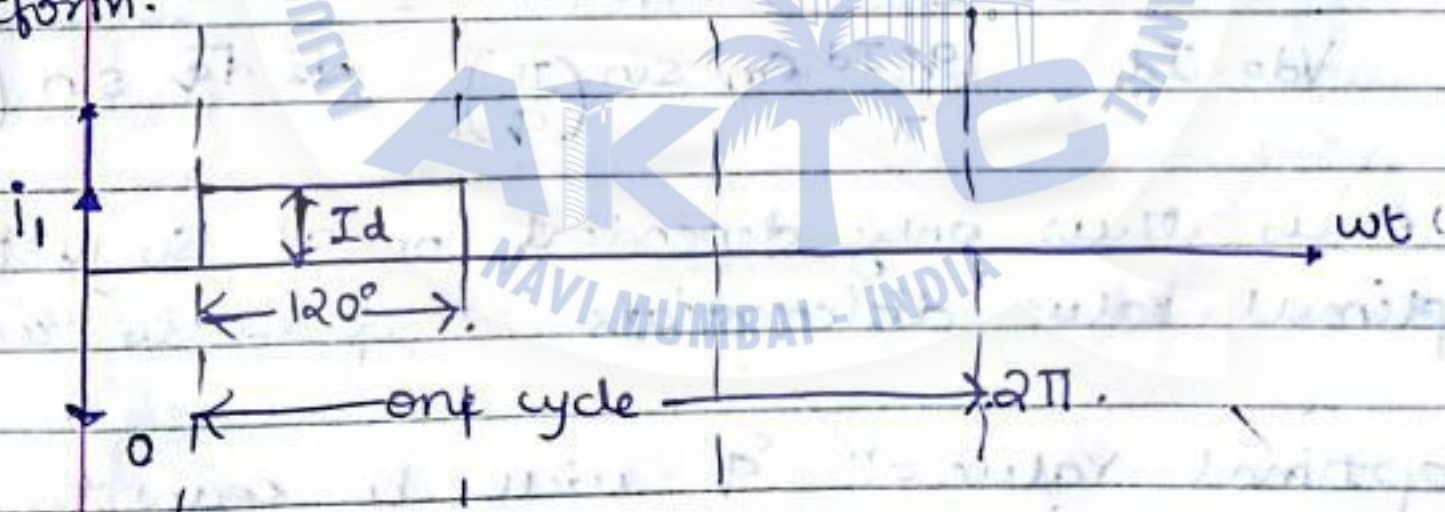- Consider a 3 ϕ Rectifier one way we have the following waveform.



we get

$$I_t^2 = \frac{1}{2\pi} \int_0^{2\pi/3} I_d^2 d(\omega t)$$

$$I_t^2 = \frac{I_d^2}{3}$$

$$I_t = \frac{I_d}{\sqrt{3}}$$

3 values in commutating group ie 'q'

$$I_t = \frac{I_d}{r \sqrt{q}}$$

'r' is the no of parallel valves

$$P_t = p \frac{E_m}{\sqrt{2}} I_t$$

No of pulses.

rms value of secondary Xmer voltage

$$= p \frac{E_m}{\sqrt{2}} \frac{I_d}{r \sqrt{q}}$$

$$P_t = \frac{p E_m I_d}{r \sqrt{2} q}$$

TUF (reciprocal of Xmer utilization efficiency) can be calculated using above eqs.

$$TUF = \frac{P_t}{V_{do} \cdot I_d} = \frac{p E_m I_d / r \sqrt{2} q}{\frac{q_s I_d E_m \sin(\frac{\pi}{q})}{\pi} \sqrt{2} \sqrt{q} \sin(\frac{\pi}{q})} = \frac{\pi}{\sqrt{2} \sqrt{q} \sin(\frac{\pi}{q})}$$

The TUF is thus only dependent on 'q'. So just to get the optimal value differentiate & equate to zero.

The optimal value of 'q' will be equal to 3.

For 6 pulse converter the various values are presented in the table.

quap parameter of 220V?

$$\frac{E_m}{\sqrt{2}} = \frac{230}{\sqrt{2}}$$

Page No.

Date: / /

For 6 pulse we have; ($P=6$)

SINo	q	r	s	PIV/ V_{do}	V_{do}/E	TUF
1	2	1	3	1.047	2.700	1.571
2	2	3	1	3.142	0.900	1.571
3	3	1	2	1.047	2.340	1.481
4	3	2	1	2.094	1.169	1.481
5	6	1	1	2.094	1.350	1.814

Best option

- On comparing ③ & ① we realize

- ① has lower PIV/ V_{do} Same as ③
- ① has higher V_{do}/E than ③
- ① has higher TUF than ③ (TUF should be closest to unity)


- It is preferable to use ③ because we have 3 ϕ & very easily we can identify the no of valves in a group. q can't be three or multiple of three.

- The TUF in ③ can be ^{made} better by using improved configuration.

→ The current rating of transformers can be further increased by a factor of $\sqrt{2}$ while decreasing the number of winding by factor 2.

Current waveform of Graetz Bridge

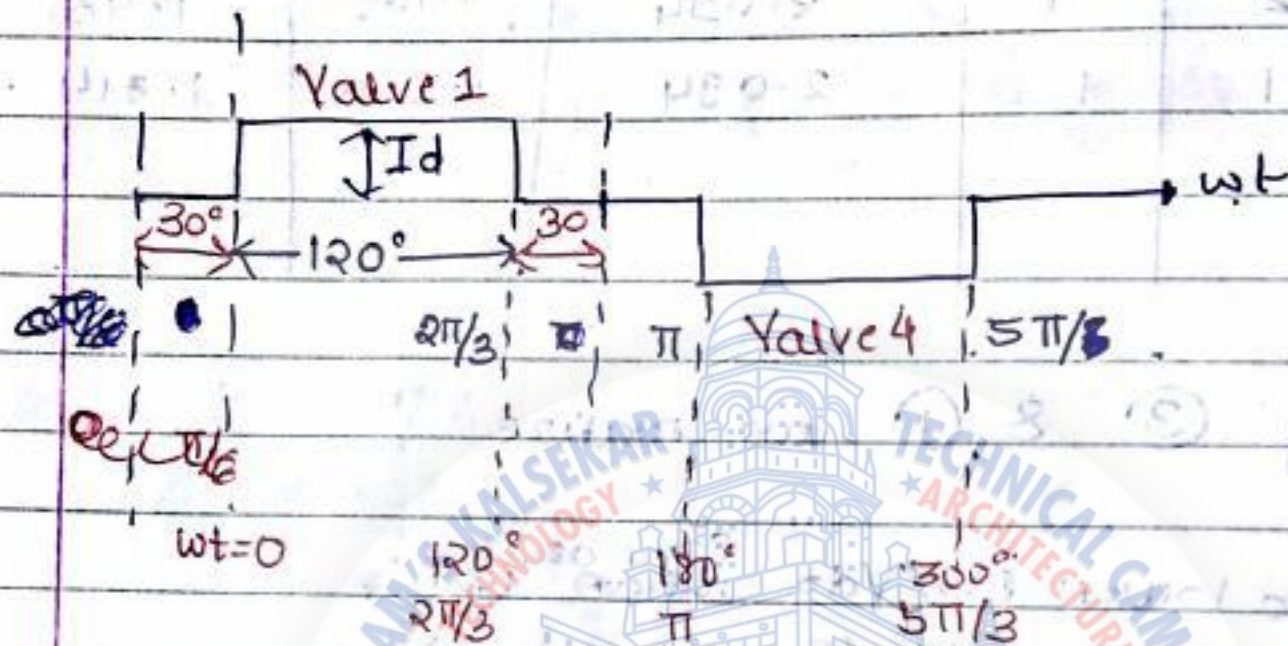- Consider the Graetz circuit. Valve '1' is conducting for 120° . The phase current 'I_a' of phase 'a' will apply a +ve current to Valve '1' for 120° & then -ve current to Valve '4' for 120° as shown below.



$$I_t^2 = \frac{1}{2\pi} \left[\int_0^{2\pi/3} I_d^2 d(\omega t) + \int_{\pi}^{5\pi/3} I_d^2 d(\omega t) \right]$$

$$I_t^2 = \frac{2}{3} I_d^2$$

$$I_t = \sqrt{\frac{2}{3}} I_d \quad \text{or} \quad I_t = \frac{\sqrt{2}}{\sqrt{3}} I_d$$

improved by factor $\sqrt{2}$

- For a 12 pulse converter, the same analysis can be performed and it is found that 2 six pulse converters connected in series by two transformers with phase displacement of 30° i.e. if one transformer is Δ & other should be star-delta.

25/30
6.Page No.
 Date: / /


- Different cases depend on the conduction of valves in a commutating group can be analysed separately.
- If at all instants only one valve in the commutating group conducts there will be no overlap.
 - ↳ Two valves of same commutating group conducting for a short period simultaneously. This happens when current from one valve is transferred to other valve of same commutating group.
- For 12 pulse converter, the same analysis can be repeated by making the tabular format of q, r, s . & then choose the optimum option from the wide range of options. (Can be given as assignments to students)
- The sudden change of current from one valve to another is not instantaneous due to the presence of source inductance & the concept of overlap comes into picture.
- First we will analyse the ideal case with no overlap & ignition delay & check; what will be the % P.V.G, pulses, harmonics, current in each valve & how the currents are shared will be analysed deeply for this 6 pulse etc

Conduction Sequence

Conducting valve	6	1	2	3	4	5
Next fired Valve	1	2	3	4	5	6
Conduction period	60°	60°	60°	60°	60°	60°

← 360° →

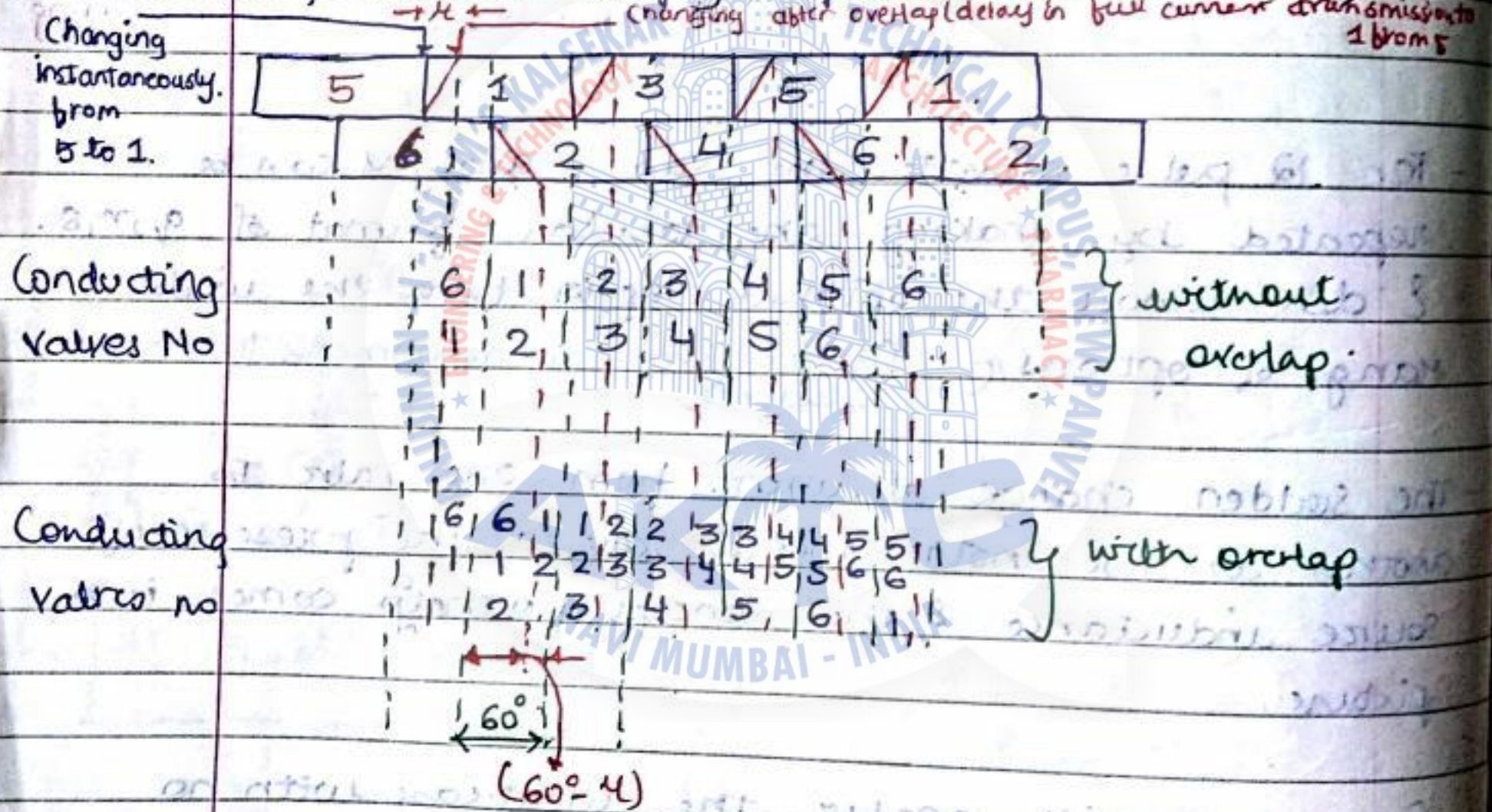The overlap can be simply represented as under:



- If 'H' value is more, there is possibility of getting 4 Valve conduction. It behaves like short circuits

- Here ~~three~~ ^{four} cases arise

- Modes $\mu = 0 \rightarrow$ 2 valves conduction
- MODE 1 : $(\mu < 60^\circ \rightarrow 2, 3 \text{ valves}) \rightarrow$ best option
- MODE 2 : $\mu = 60^\circ \rightarrow 3 \text{ valves}$
- MODE 3 : $(\mu > 60^\circ \rightarrow 3, 4 \text{ valves}) \rightarrow$ undesirable, results in short circuit

3 ϕ voltages :

- Taking eba as reference voltage as shown in the fig, the other voltages can be written as;

$e_{ba} = \sqrt{3} E_m \sin(\omega t)$

$e_a = E_m \sin(\omega t + 5\pi/6)$


$e_b = E_m \sin(\omega t + \pi/6)$

$e_c = E_m \sin(\omega t - \pi/2)$

$e_{cb} = e_c - e_b = \sqrt{3} E_m \sin(\omega t - 120^\circ)$

$e_{ac} = \sqrt{3} E_m \sin(\omega t + 120^\circ)$

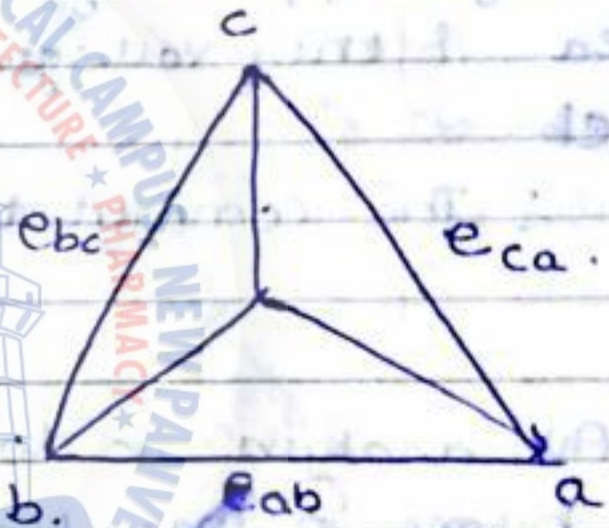
$e_{bc} = \sqrt{3} E_m \sin(\omega t + 60^\circ)$



- To understand the concept of commutation voltage consider the gaetz bridge.


- Suppose '1' & '2' were conducting, now '1' will go off for '3' to conduct

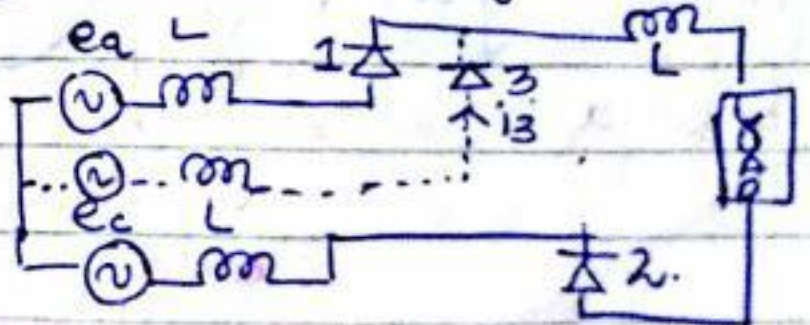- Voltage at cathode of '3' is e_a since '1' is now off & the voltage at anode of '3' is e_b so;



- $e_b - e_a$ should be '+ve' for valve '3' to conduct. & this voltage is commutation voltage.

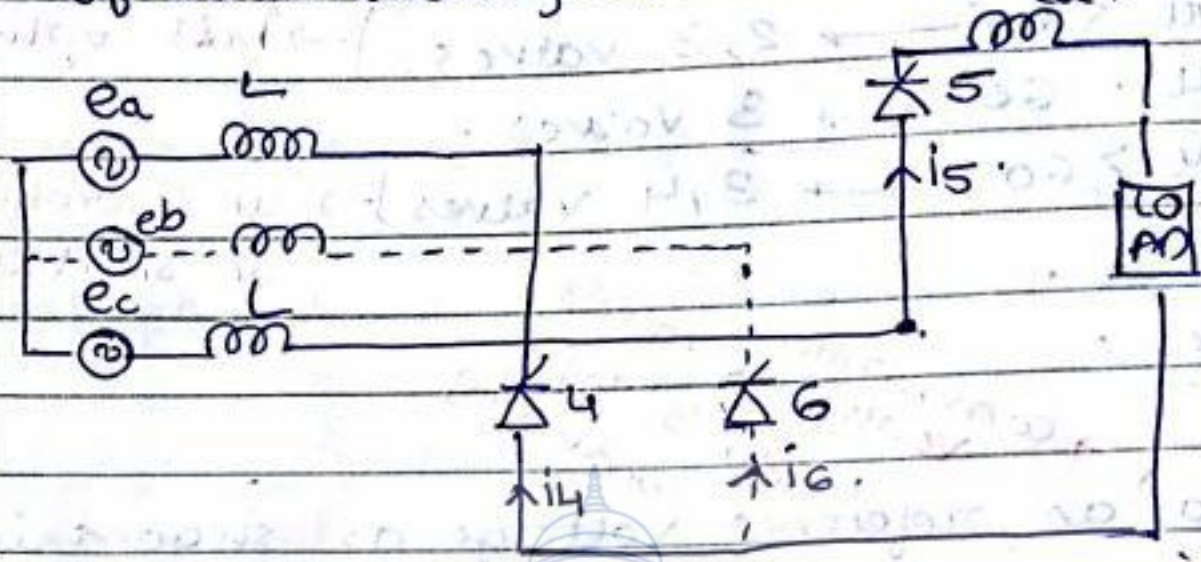
- Similarly we can calculate the commutation voltage of other valves, consider valve '6'




- Note; valves 4, 5 were conducting before '6' was fired
 - Voltage appearing at the Anode of '6' as '4' goes off is ea & the voltage appearing at the Cathode of '6' is eb

∴ The commutation voltage = $e_a - e_b$ [should be π to ~~be~~ conduct '6']

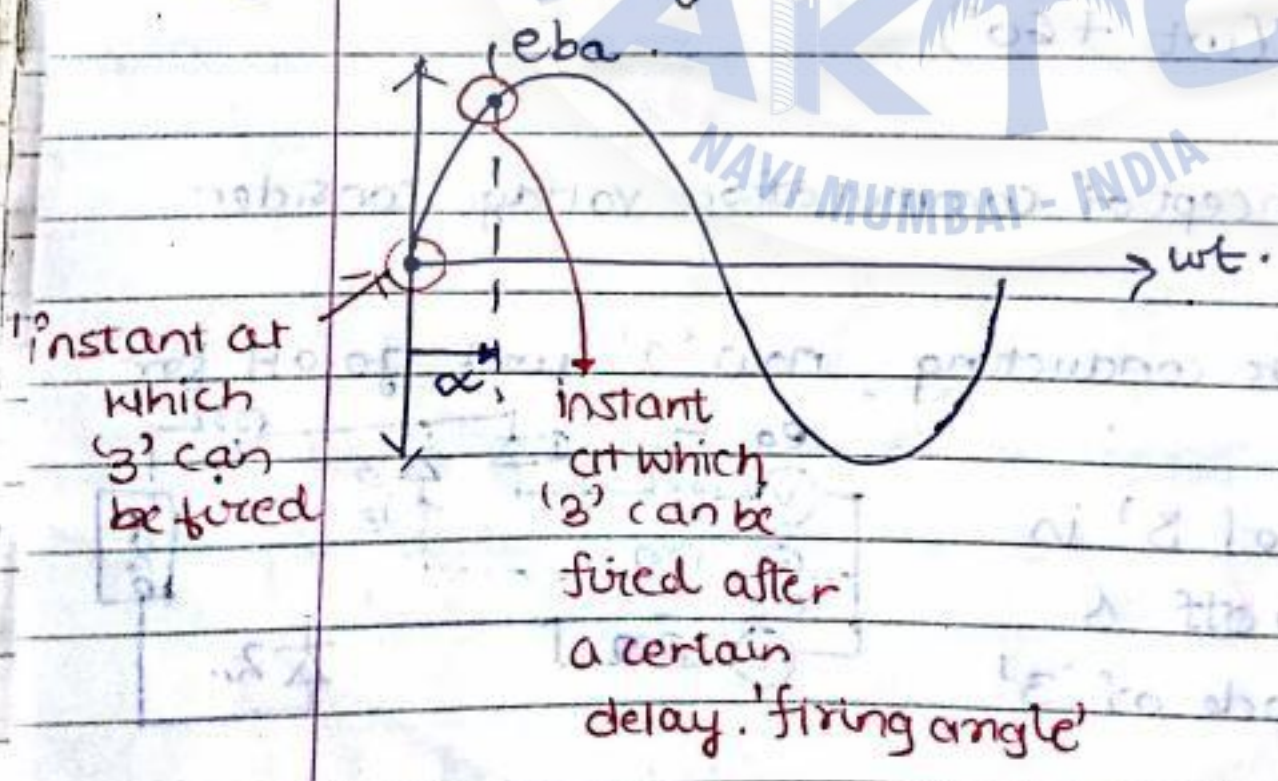- All analysis is done assuming '1' & '2' were conducting before '3' was fired.




$V_L = \sqrt{3} V_{ph}$

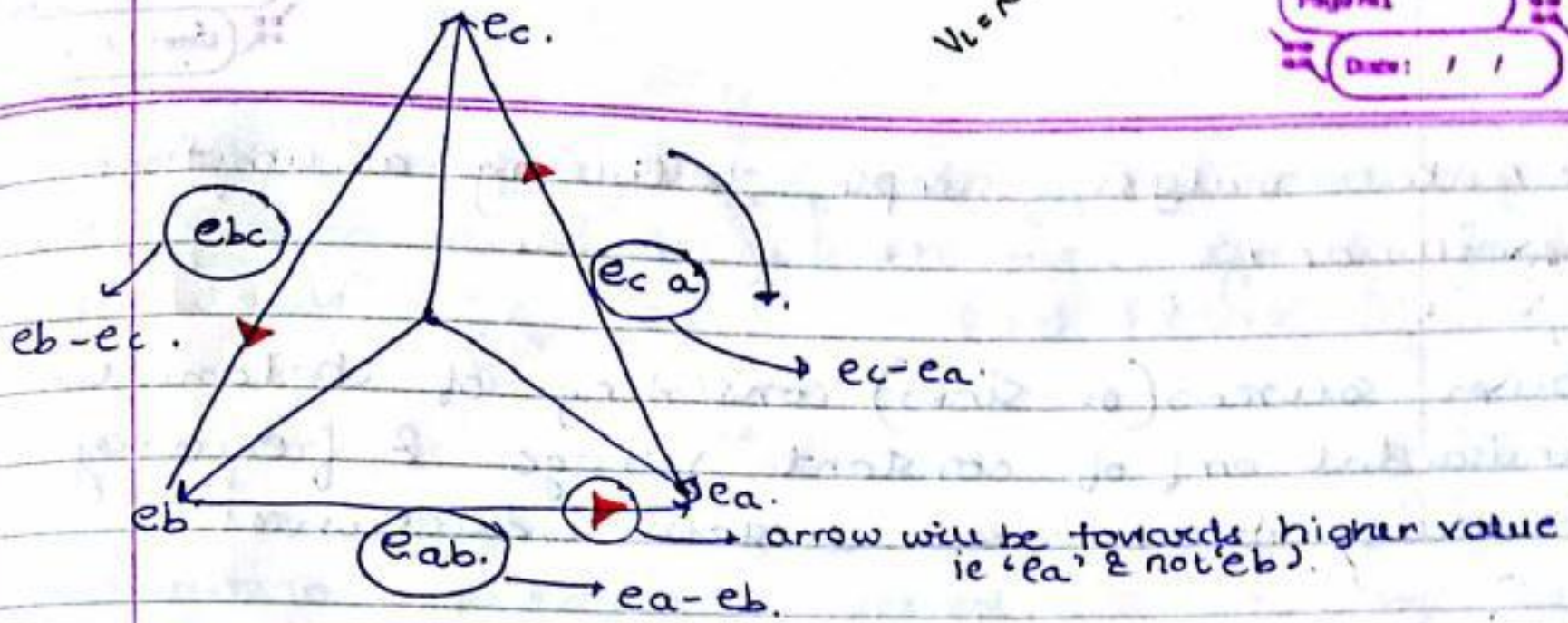

$eba.$
↑ this is the reference.

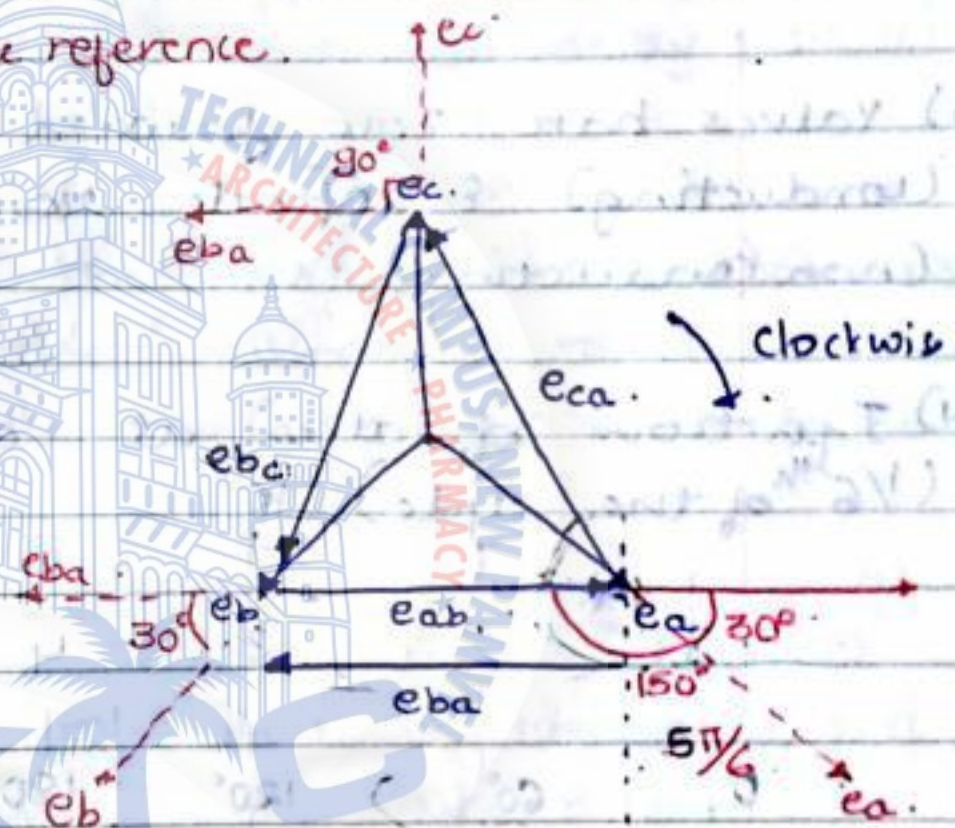- $e_{ba} = \sqrt{3} E_m \sin \omega t$ (Line value)
- $e_a = E_m \sin(\omega t + 5\pi/6)$ (Phase value)




- $e_b = E_m \sin(\omega t + \pi/6)$
- $e_c = E_m \sin(\omega t - \pi/2)$

Similarly

- $e_{ac} = \sqrt{3} E_m \sin(\omega t + 2\pi/3)$
- $e_{bc} = \sqrt{3} E_m \sin(\omega t + \pi/3)$

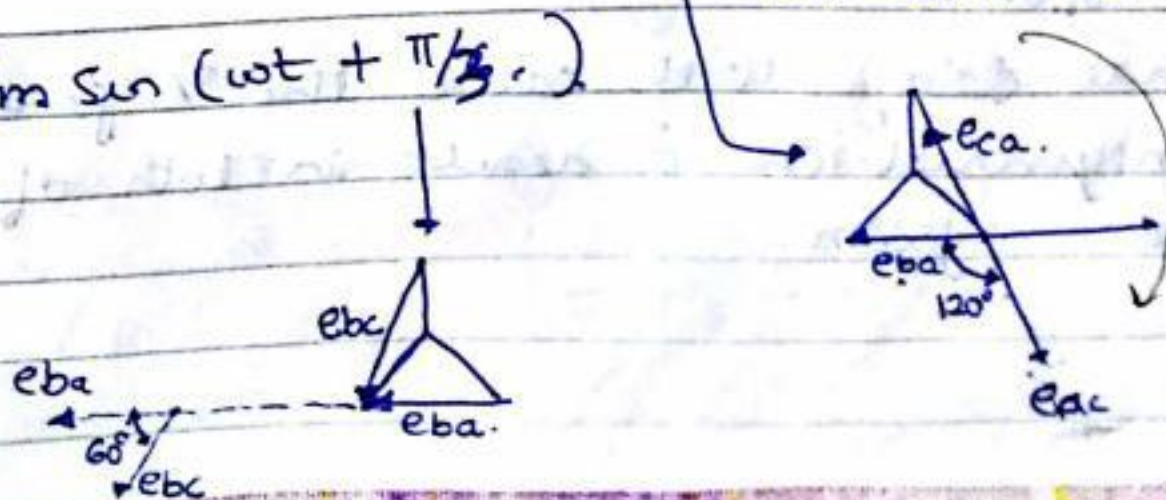Angle between e_a & e_{ba} is found & the sign of angle is taken '+ve' because in clockwise direction ' e_a ' leads ' e_{ba} '.



• To make analysis simple following assumptions are made.

(1) Power sources (or sinks) consisting of balanced sinusoidal emf of constant voltage & frequency in series with equal lossless inductances.

(2) The dc current is constant i.e. ripple free.

(3) Valves have zero forward resistance when on (conducting) & infinite resistance when off (non conducting).

(4) Ignition of valves at equal intervals of 60° ($1/6^{\text{th}}$ of the cycle) i.e.



- We assume a symmetrical conduction pattern which appears across O/P.

- There is a possibility that you fire 2 after 80° instead of 60° .

- But that delay will cause the O/P pattern to be unsymmetrical & result in lots of harmonics to the system.

(5) A valve can only be fired if the gate signal appearing across it is +ve & the gate signal is available.

- Overlap angle (μ):

- The duration when the current is shared by the conducting valves in a commutating group is called overlap angle & is measured by the overlap (commutation) angle ' μ '.

- Let us consider that the valve 1, & 2 are conducting. Voltage appearing at the cathode of valve 3 is e_a . Since valve 1 is conducting & the anode will have voltage e_b .

- The valve '3' will only conduct if $e_b \geq e_a$, i.e. when voltage e_{ba} is '+ve'. This is known as the commutation voltage of valve 3. Valve 3 can now be fired by any gate pulse with any delay angle ' α ' which is α° after the zero crossing of the commutation voltage of valve 3.

• Valve 2, 3, conduction case:



- On observation of fig;

$$i_a = 0 \quad [\because \text{Phase A O.C}]$$

$$i_b = I_d$$

$$i_c = -I_d$$

Here we want to know current in valve phase 'c' which has conventional direction as shown, But I_d flows in reverse so; $i_c = -I_d$

• Currents in valves:

$$i_1 = 0$$

$$i_2 = +I_d$$

$$i_3 = I_d$$

$$i_4 = 0$$

$$i_5 = 0$$

$$i_6 = 0$$


Note: Here we want to know the current flowing in valve 2, which is from anode to Cathode so it's '+ve'

• %P Voltage (Without overlap)

$$\%P \text{ Voltage} = e_b - e_c = e_{bc}$$

- We need to be careful here; the commutating voltage of '3' is e_{ba} . But %P voltage is e_{bc} , so care is to be taken about the difference

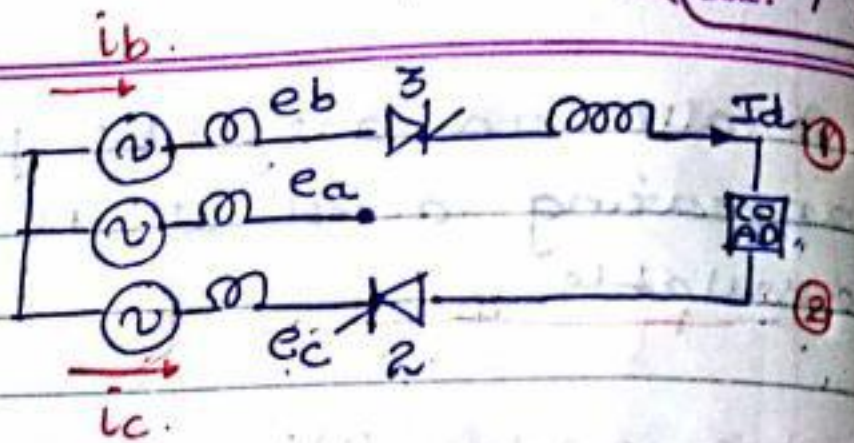- Since the pair of valves 2,3 will conduct for 60° & valves 3,4 will conduct for next 60° for the dc %P voltage only one interval can be considered (because %P pattern is symmetrical)



o/p Voltage (with overlap)

- If the delay angle is α , the instantaneous DC voltage e_{bc} will appear across the DC terminal from α to $60^\circ + \alpha$, the average dc voltage will be given by;

$$V_d = \frac{1}{(\pi/3)} \int_{\alpha}^{(\pi/3 + \alpha)} e_{bc} d(\omega t)$$

$$= \frac{3}{\pi} \int_{\alpha}^{(\alpha + \pi/3)} \left(\sqrt{3} E_m \sin(\omega t + \pi/3) \right) d(\omega t)$$

from phasor

$$= \frac{3\sqrt{3} E_m}{\pi} \left[-\cos(\omega t + \pi/3) \right]_{\alpha}^{(\pi/3 + \alpha)}$$

$$= \frac{3\sqrt{3} E_m}{\pi} \left[-\cos\left(\frac{2\pi}{3} + \alpha\right) + \cos\left(\alpha + \frac{\pi}{3}\right) \right]$$


$$= \frac{3\sqrt{3} E_m}{\pi} \left[\underbrace{2 \sin\left(\frac{\pi}{2} + \alpha\right)}_{\cos \alpha} \cdot \underbrace{\sin\left(\frac{\pi}{6}\right)}_{1/2} \right] \cdot \sin\left(\frac{A+B}{2}\right)$$

$$V_d = \frac{3\sqrt{3} E_m}{\pi} \cos \alpha$$

$$V_d = V_{d0} \cos \alpha$$

→ Avg dc voltage appearing across the dc link.


- This eq indicates that the avg dc voltage across the bridge will vary with firing angle α .
- The dc o/p voltage will be max when $\alpha=0^\circ$ & zero at $\alpha=90^\circ$
- When the voltage across the bridge is +ve, it acts as a rectifier & when it is negative it is known as inversion operation of bridge.
- $(0 - 90^\circ) \rightarrow$ no overlap \rightarrow o/p v_g +ve
 90° onwards \rightarrow inversion o/p \rightarrow o/p v_g -ve

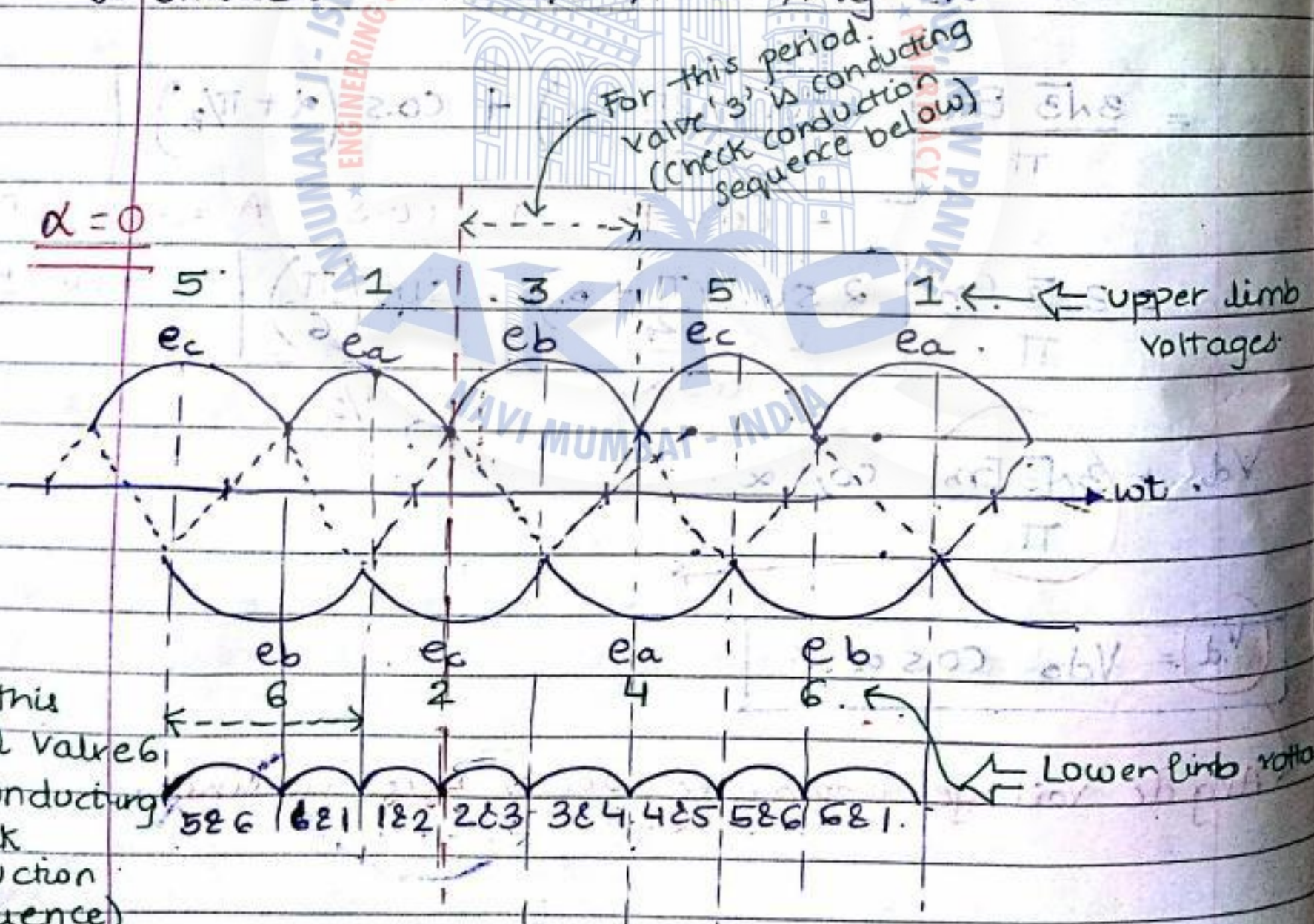

For this period valve 6 is conducting (Check conduction sequence)

Conduction sequence & o/p v_g waveform.

- Although delay angle (α) can vary from 0° - 180° . delay angle cannot be less than certain minimum limit (say 5°) in order to ensure firing of all series connected thyristors.
- Similarly the upper limit of delay angle is also restricted due to turn off time of valve.
- delay angle is not allowed to go beyond $(180^\circ - \gamma)$ where γ is extinction angle.
- It is the minimum margin angle which is typically 15° .
- However in normal operation of inverter it is not allowed to go below 15° . The typical values of γ is $15^\circ - 20^\circ$.
- Effect of firing angle on voltage waveform ($\alpha < 90^\circ$)
 - The line voltages $\underbrace{e_{ab}, e_{bc}, e_{ca}}_{+ve}$ and $\underbrace{e_{bc}, e_{cb}, e_{ba}}_{-ve}$ can be plotted if only 'one' voltage is known.
 - 1st e_{ab}, e_{bc}, e_{ca} are plotted with difference of 120°
then opposite wave of e_{ab} is e_{ba}
 - e_{bc} is e_{cb}
 - e_{ca} is e_{ac} .

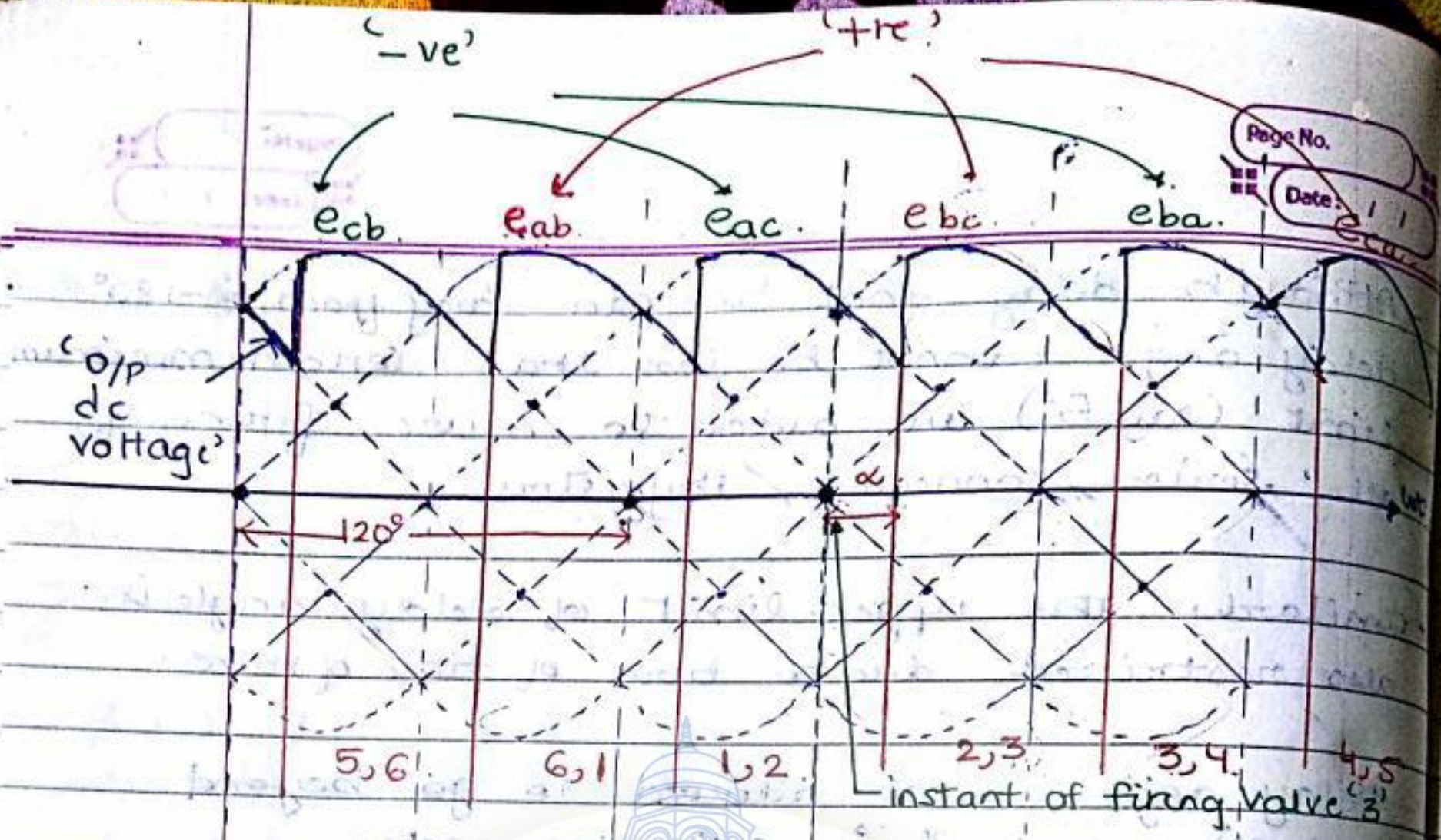


• AC current waveform:


- If the reactance of smoothing reactor is very large the % DC current can be assumed as constant (ripple free)

- It means there are no harmonics in DC current the ac current which will flow in the secondary winding of Xmer is shown

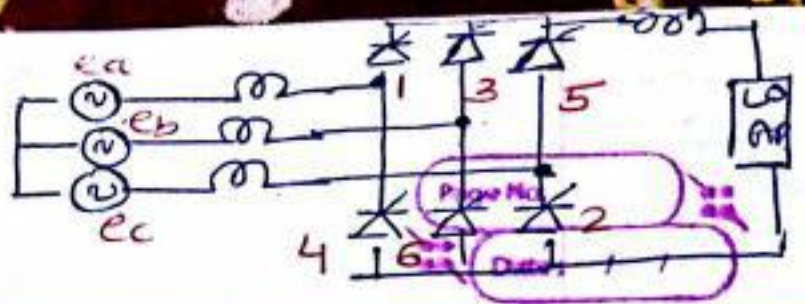
- Since '3' is about to conduct let us draw phase 'b' voltages.



Phase B.

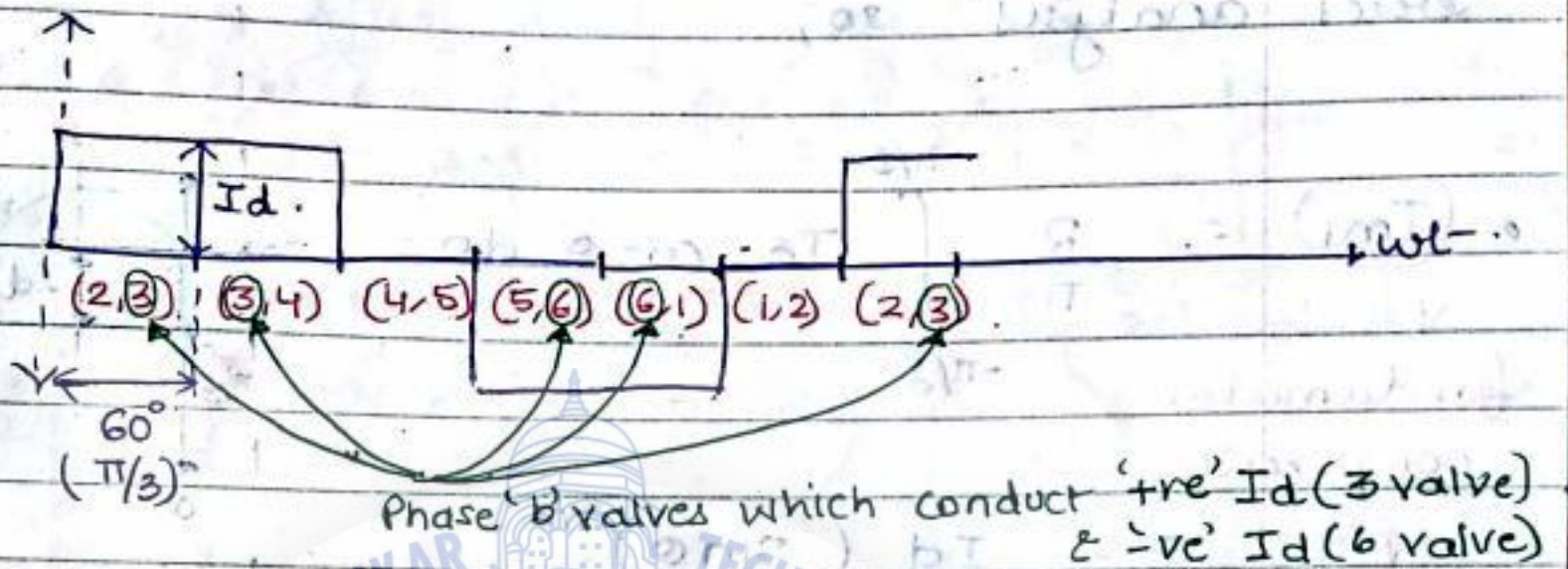

Phase A.

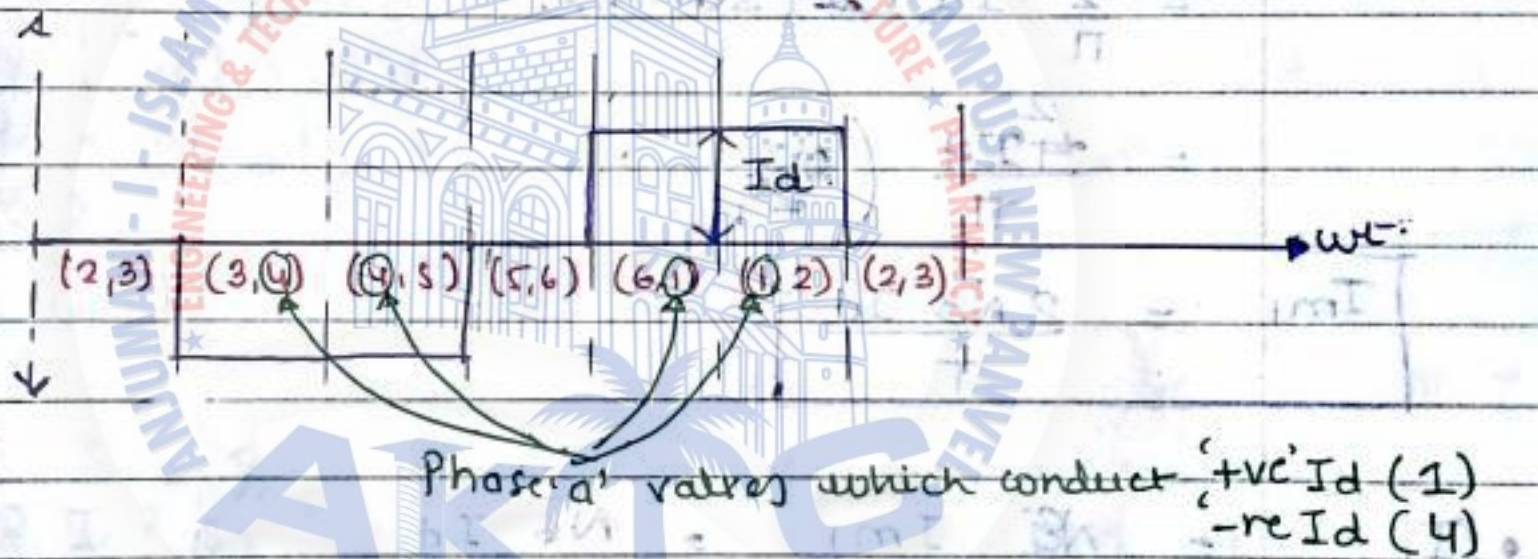

- In a similar fashion 'phase c' current can be drawn.

- Now we need to calculate the fundamental component of the waveform shown above. (ie rms).

- It is not perfect sinusoidal, but looks like pulsating

- fundamental component is calculated by fourier series analysis so;

$$I_{m1} = \frac{2}{\pi} \int_{-\pi/3}^{\pi/3} I_d \cos \theta \, d\theta$$

fundamental component

$$\text{peak value} = \frac{2}{\pi} I_d (\sin \theta) \Big|_{-\pi/3}^{\pi/3}$$

$$= \frac{2}{\pi} I_d (4) \sin \pi/3$$

$$= \frac{2}{\pi} \cdot 4 I_d \left(\frac{\sqrt{3}}{2} \right)$$

$$I_{m1} = \frac{2\sqrt{3}}{\pi} I_d$$

$$I_1 = \frac{\sqrt{2}}{\sqrt{2}} \frac{I_{m1}}{\sqrt{2}} = \frac{\sqrt{6}}{\pi} I_d$$


rms value of

fundamental component

$$I_1 = \frac{\sqrt{6}}{\pi} I_d$$

⇒ Active Power is defined by the fundamental component flowing

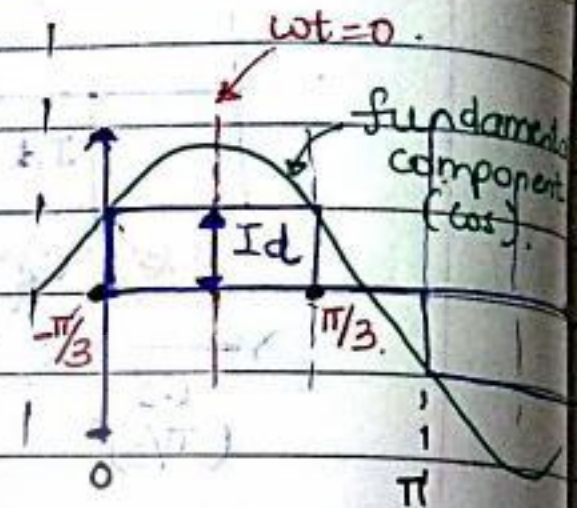through the phase circuit & therefore I_1 is to be calculated.



A 220012


Note: $I_h = \frac{I_1}{h}$, we know for 6 pulse $h = (6 \times \pi) = 180^\circ$; ie 5, 7, 11, 13

less value I_h as I_h is more less.
 Dis: more

$I_{Total} = I_1 + I_h$

$$I = \left[\frac{1}{2\pi} \int_0^{2\pi} I_d^2 d\theta \right]^{1/2}$$
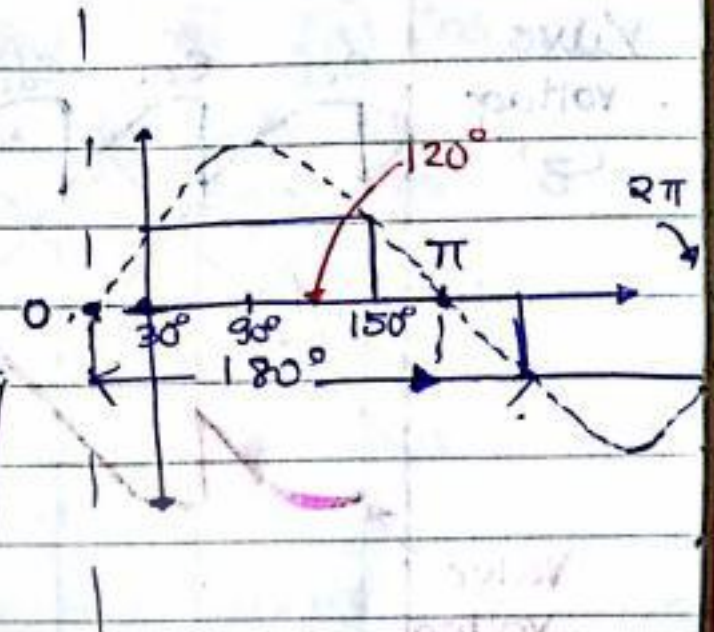
$$= \left[\frac{1}{2\pi} \int_0^{2\pi/3} I_d^2 d\theta + 0 + \int_{\pi}^{5\pi/3} I_d^2 d\theta \right]^{1/2}$$



$$I = \left[\frac{1}{2\pi} (2) \int_0^{2\pi/3} I_d^2 d\theta \right]^{1/2}$$

$$= \left[\frac{1}{2\pi} (2) I_d^2 \left(\frac{2\pi}{3} - 0 \right) \right]^{1/2}$$


$$= \left[\frac{2}{3} I_d^2 \right]^{1/2}$$

$I = \sqrt{\frac{2}{3}} I_d$	→ Total I including I_1 & I_h .
------------------------------	-------------------------------------

Valve Voltages:

Valve - Assignment

Page No. _____
 Date: / /



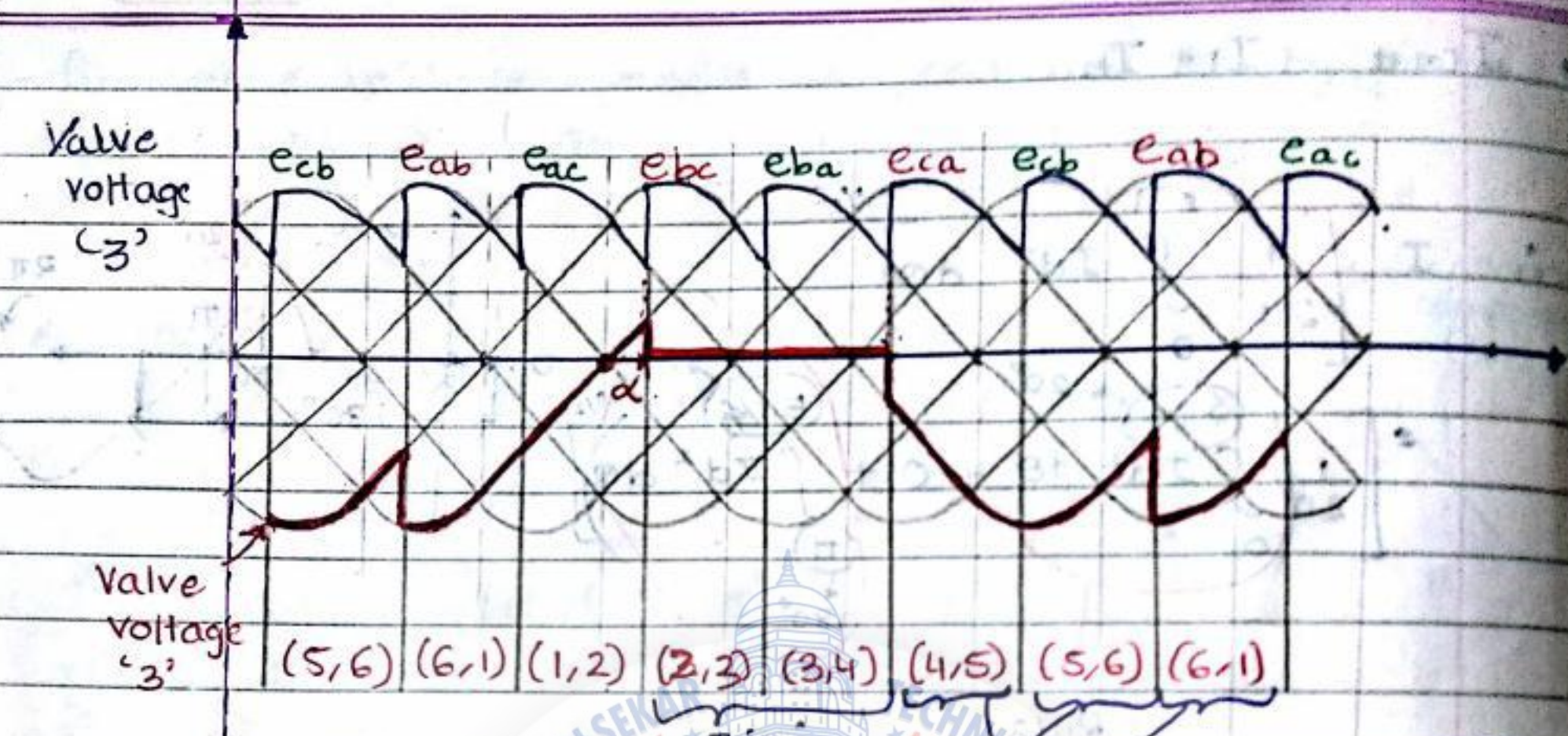


→ kbas volt

3 is conducting so zero voltage.

- In the rectification ckt shown above, the valve voltages are almost ~ 0

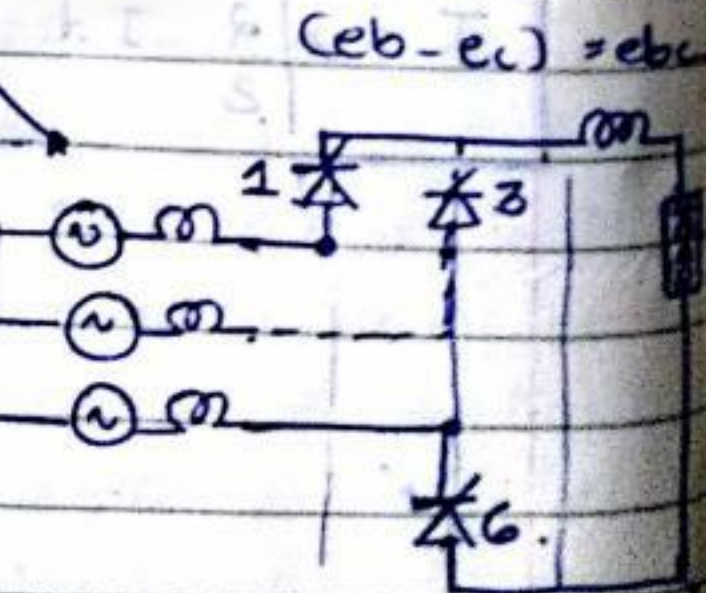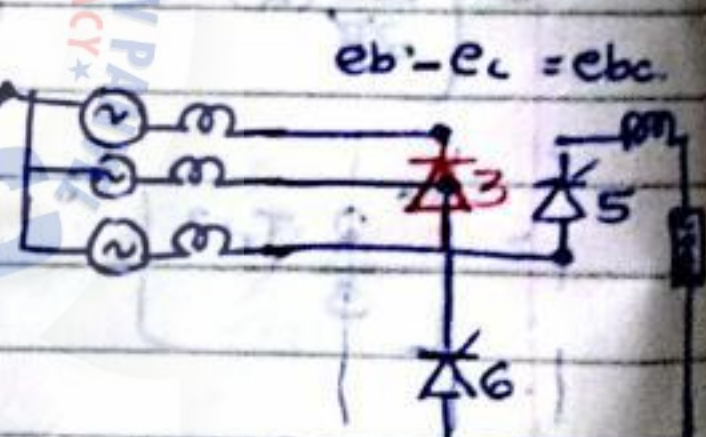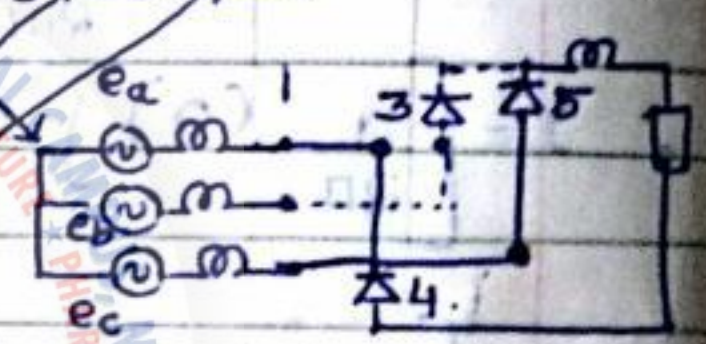- Rectifier ckt is therefore very stable ckt because if the pulse is given by mistake the ~ 0 voltage wont make a valve to conduct.



$eb - ea = eba$

• Power factor

$$\rightarrow P_{ac} = \sqrt{3} E_{LL} I_L \cos \phi = \sqrt{3} E_{LL} \left(\frac{\sqrt{6}}{\pi} I_d \right) \cos \phi$$

fundamental
component
power.

$$P_{ac} = \frac{3\sqrt{2}}{\pi} E_{LL} I_d \cos \phi$$

$$\rightarrow P_{dc} = V_d I_d = \frac{3\sqrt{3}}{\pi} E_m I_d \cos \alpha$$

$$P_{dc} = \frac{3\sqrt{2}}{\pi} E_{LL} I_d \cos \alpha$$

→ In a lossless converter;

$$P_{ac} = P_{dc}$$

→ ∴ on equating P_{ac} & P_{dc} .

$$\cos \phi = \cos \alpha$$

- This means the delay angle is directly proportional to P.F.
- If α of θ terminal is reduced, the P.F. of ac becomes very less.
- There is a limit put on α to prevent the above.
- α is therefore not delayed too much.
- ' α ' is varied to control the dc power because the current in dc link ' I_d ' is constant & V_d is changed to change ' P_{dc} '.


- α has a lower limit called α_{min} & also can't be increased beyond certain value because the reactive power requirement will be excessive i.e. α_{max} .

- Therefore the controller has to keep up with the various limits making control complex.

- If α becomes more than 90° , the $\cos \alpha$ term will be '+ve' but lagging, the V_d becomes '-ve' $\therefore P_{dc}$ becomes '-ve'



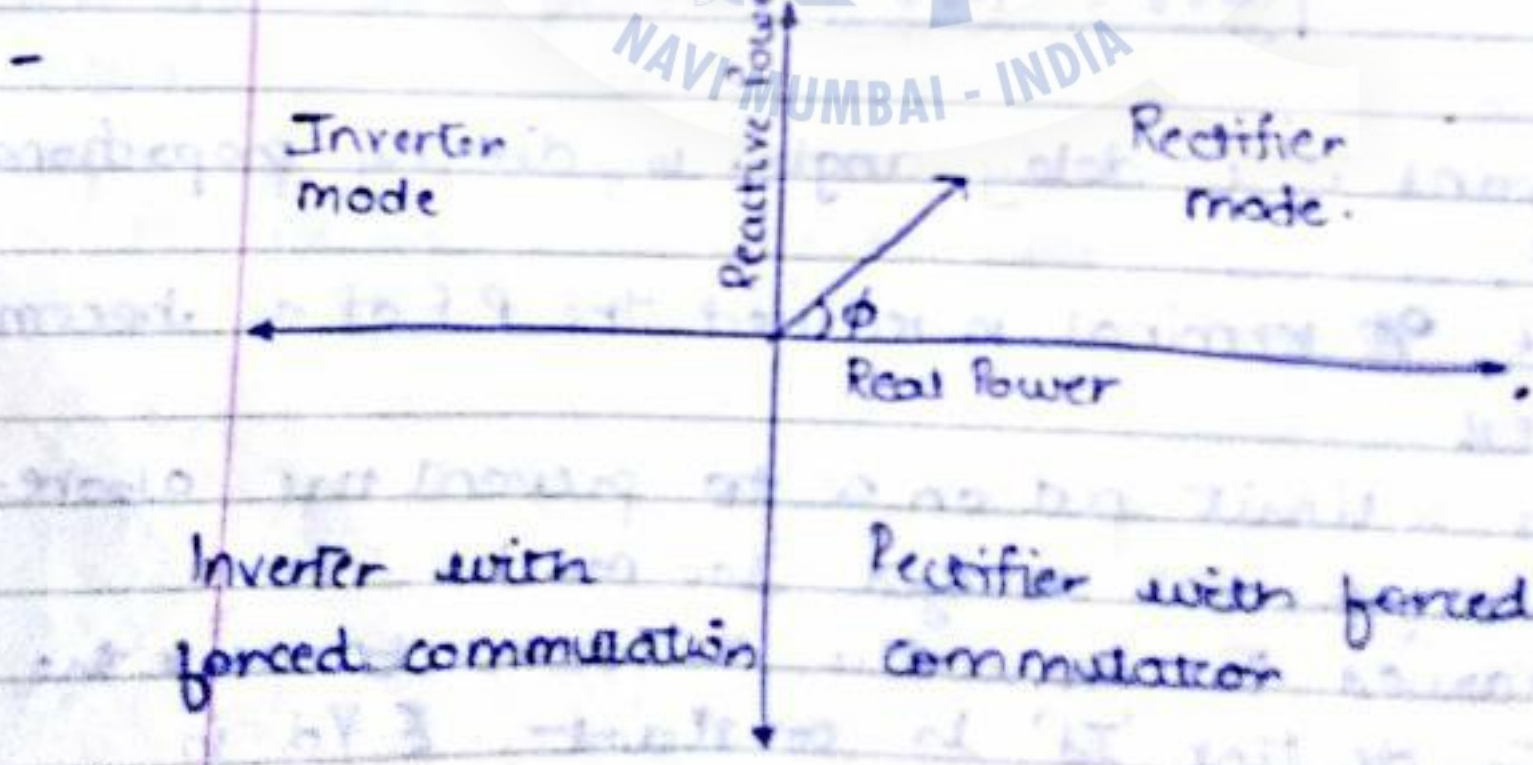
from above it's clear that Rectifier & inverter requires huge amount of 'Q'




- $\cos \alpha = \cos \phi$ holds true only in ideal case with no overlap.
- Extra commutation ckt/valves can be employed to charge the reactive power requirement & cause the p.f. to lead.

* Inverter Operation

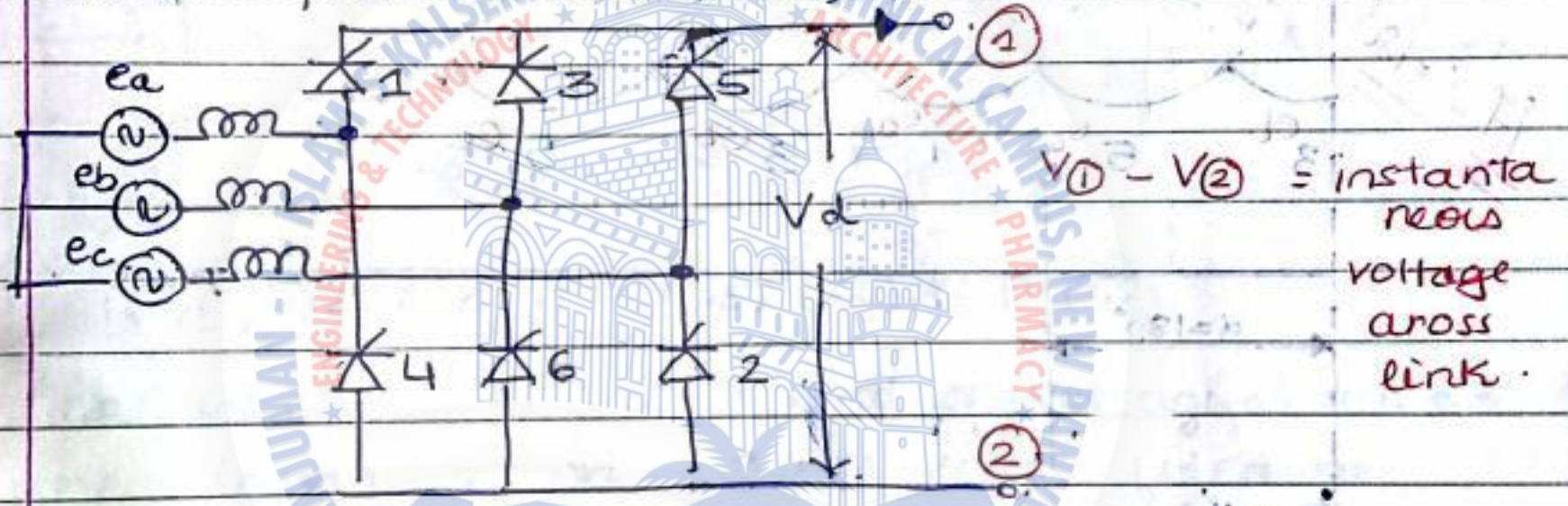- Consider a 6 pulse Rectifier ckt, I_d .



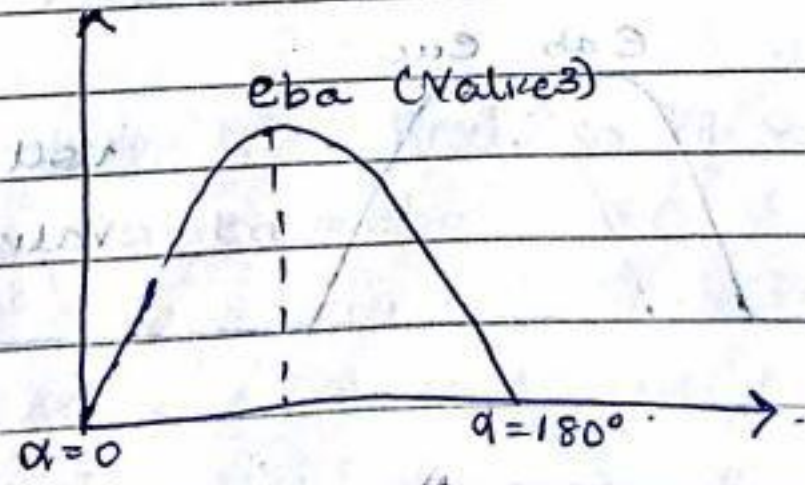
- In the inverter operation we have to delay the firing angle.
- The commutation voltage of valve e_{ba} as shown below;



- In the rectification mode, if $\alpha = 90^\circ$, we get the zero voltage. $\alpha < 90^\circ$ we get '+ve' o/p across ① & ②.


and when $\alpha > 90^\circ$, voltage will be $-V_c$ across (1) & (2)

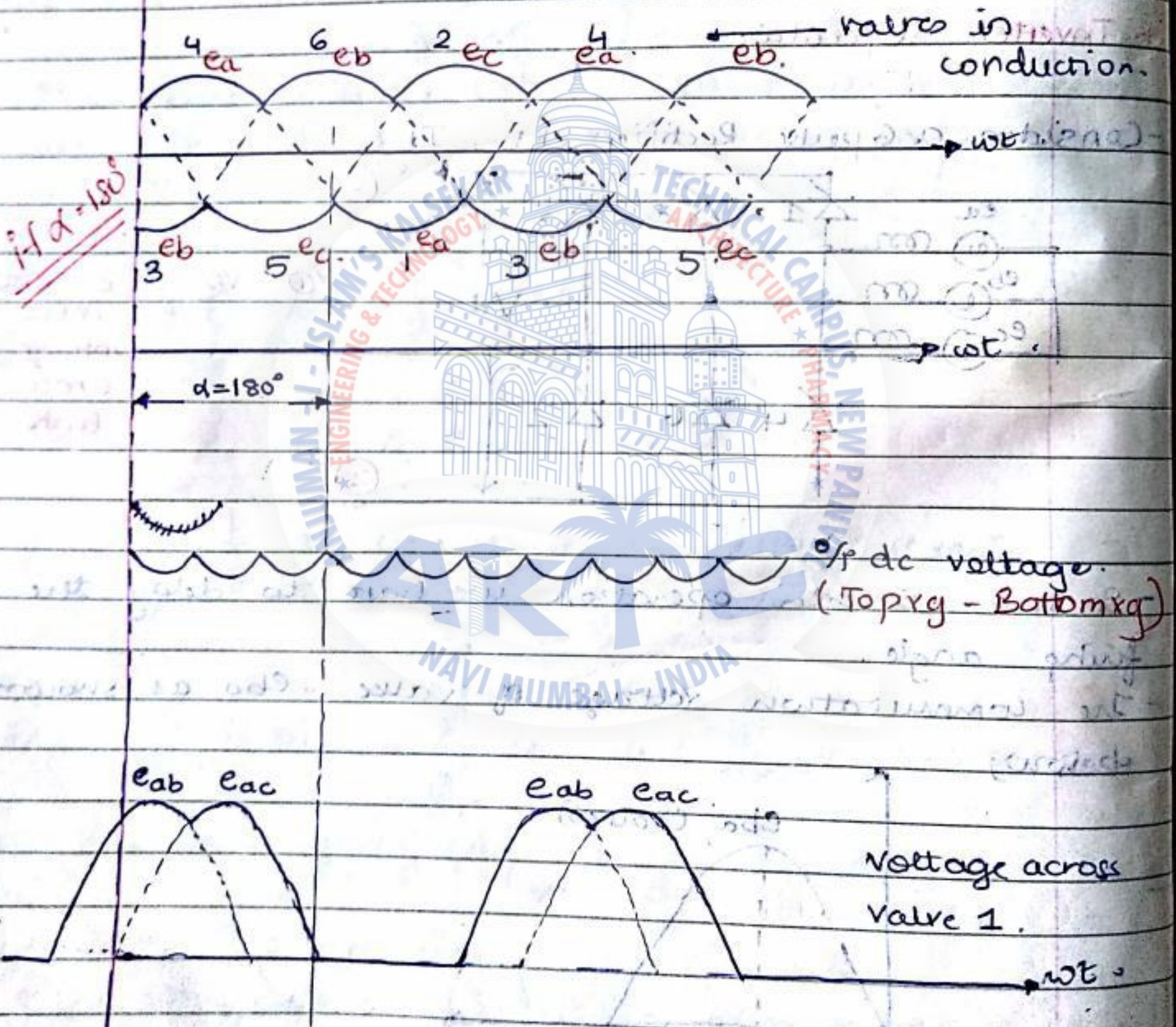- So for inverter operation $\alpha > \pi/2 (90^\circ)$. In ideal case if $\alpha = 180^\circ$ (although there is a min. angle required before 180° called (y) extinction angle in practical applications) we get the following voltages.



Voltages in inverter mode

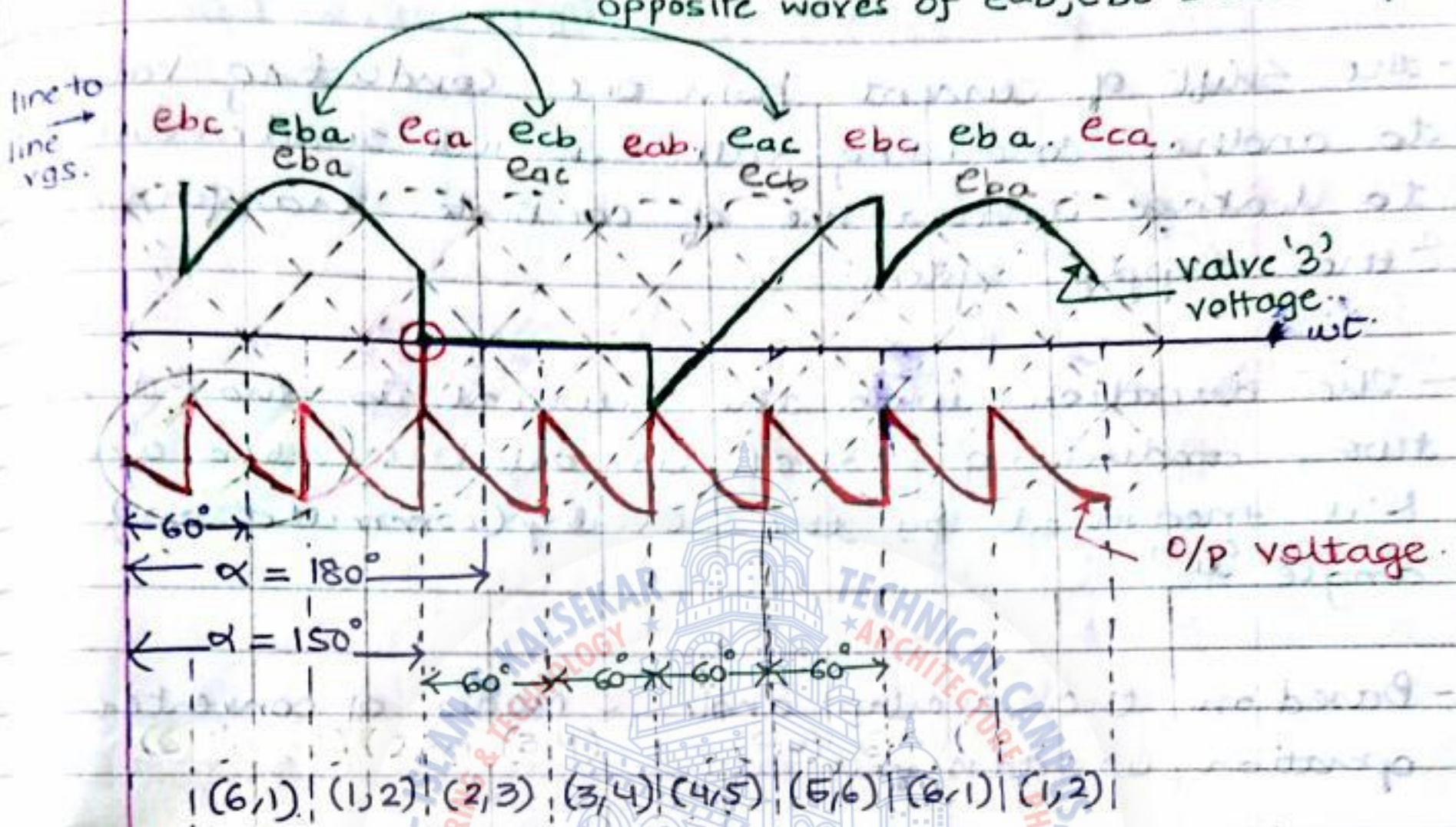• O/P voltage in case of inversion ($\alpha = 150^\circ$)
 opposite waves of e_{ab}, e_{bc} & e_{ca} resp.



- Here 'eba' is focussed i.e. commutating voltage of valve '3'
 let the instant at which valve '3' be fired be $(\alpha = 150^\circ)$

- when '3' is fired; '1' & '2' are conducting
 ∴ voltage across link = $e_b - e_c = e_{bc}$.
 ∴ the waveform of e_{bc} will be followed as O/P across valve '3' link.

- After 60° , Valve '4' is fired, so O/P voltage becomes;
 $e_b - e_a = e_{ba}$

- After 60° , valve '5' is fired; so O/P voltage becomes.
 $e_c - e_a = e_{ca}$. So on & so forth.

• Converter analysis with overlap:

- The shift of current from one conducting valve to another conducting valve is not sudden due to leakage inductance of converter transformer & the supply system.

- The duration when the current is shared by two conducting valves is called overlap angle & is measured by the overlap (commutation) angle μ .

- Based on the overlap angle, 3 modes of converter operation is classified as:

(1) Mode 1 : 2 and 3 Valve conduction ($\mu < 60^\circ$)

Very common mode. $\left\{ \begin{array}{l} \text{Where;} \\ - \text{two valve conduct for } (60^\circ - \mu) \\ - \text{three valve conducts for } \mu; \end{array} \right.$

(2) Mode 2 : 3 valve conduction ($\mu = 60^\circ$)

- where: 3 valve conduct during each interval for 60° .


(3) Mode 3 : 3 and 4 valve conduction ($\mu > 60^\circ$)

- where 3 valves conduct for $(120^\circ - \mu)$


4 valves conduct for $(\mu - 60^\circ)$

Not so common happens during faults.


Mode 1 ($u < 60^\circ$)

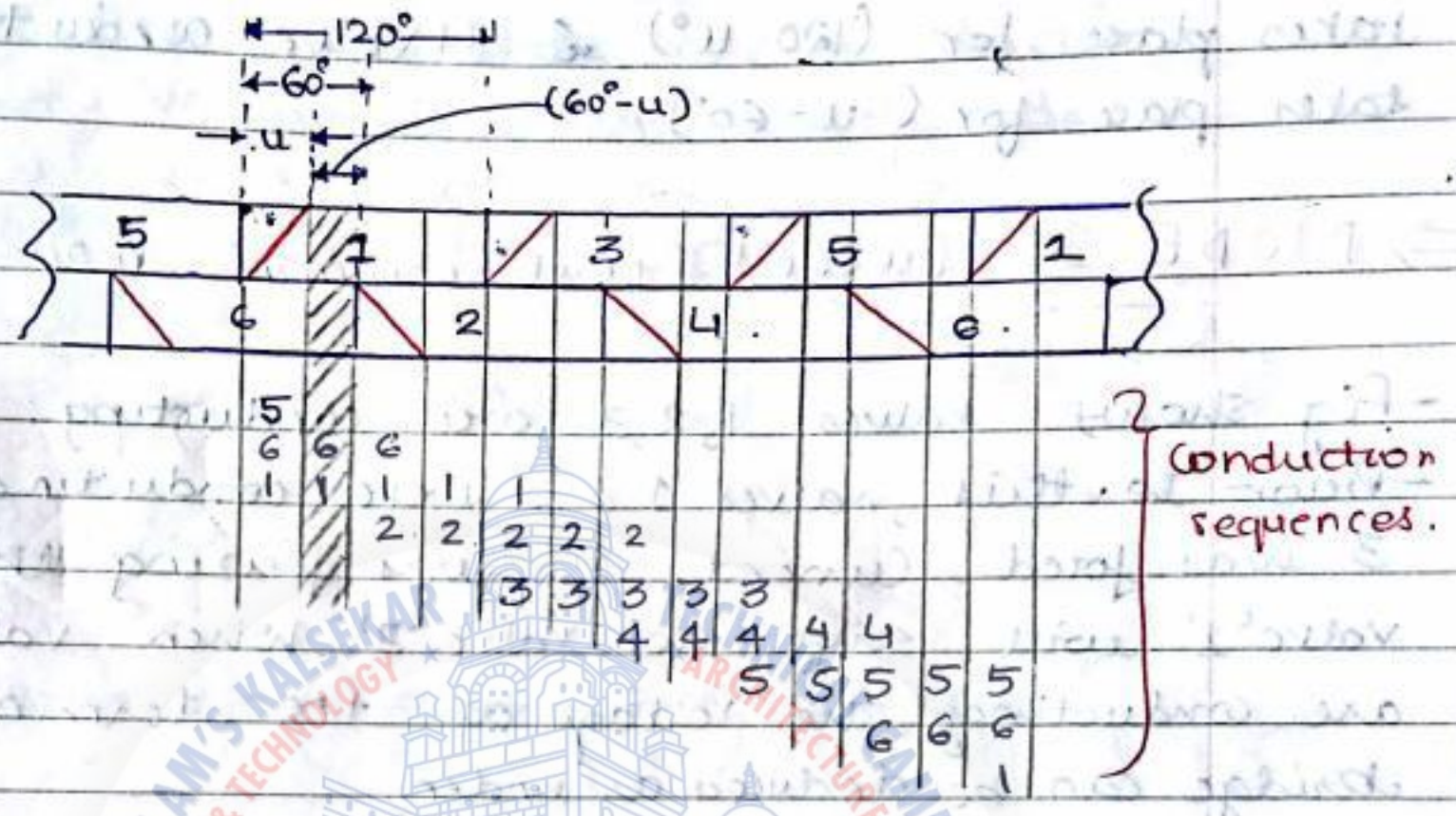

Mode 2 ($u = 60^\circ$)

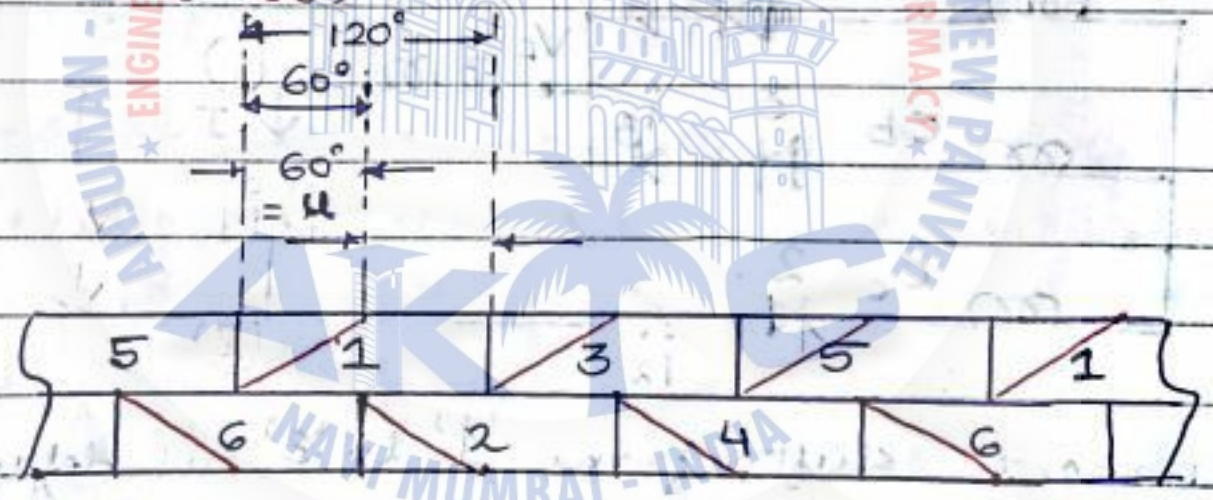


Mode 3 ($u > 60^\circ$)

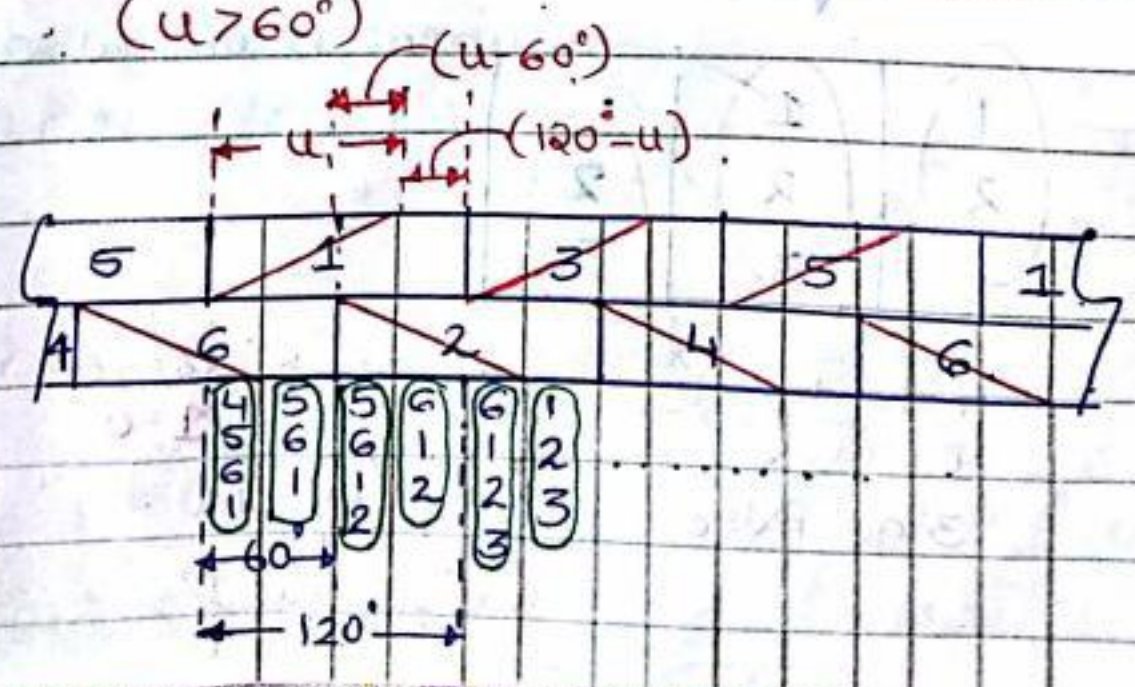

- From the above it is clear that 3 valve conduction takes place for $(120 - \mu)^\circ$ & 4 valve conduction takes place for $(\mu - 60)^\circ$.


MODE 1 ($\mu < 60^\circ$) [Most common mode of operation]

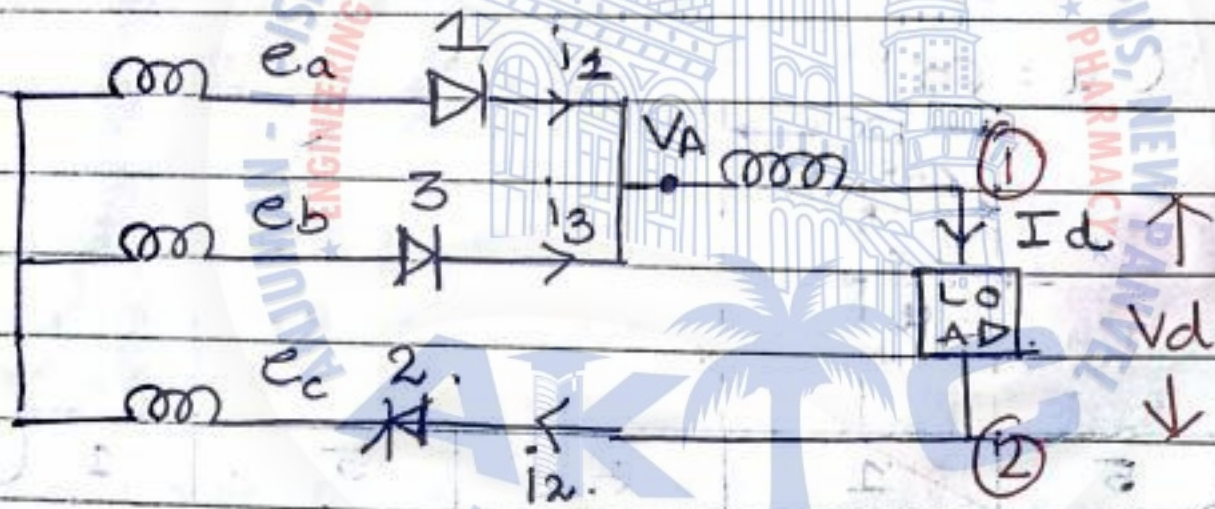- Fig shows valves 1, 2, 3 are conducting.
 - Prior to this, valves 1 & 2 were conducting & valve 3 was fired. Current i_1 was flowing through valve '1' will shift to valve '3'. When valves '1' & '3' are conducting, the voltage at the terminal of bridge can be deduced as under;



- The current shift from '1' to '3' is delayed by angle μ which is $< 60^\circ$.

- The conduction pattern is shown below.

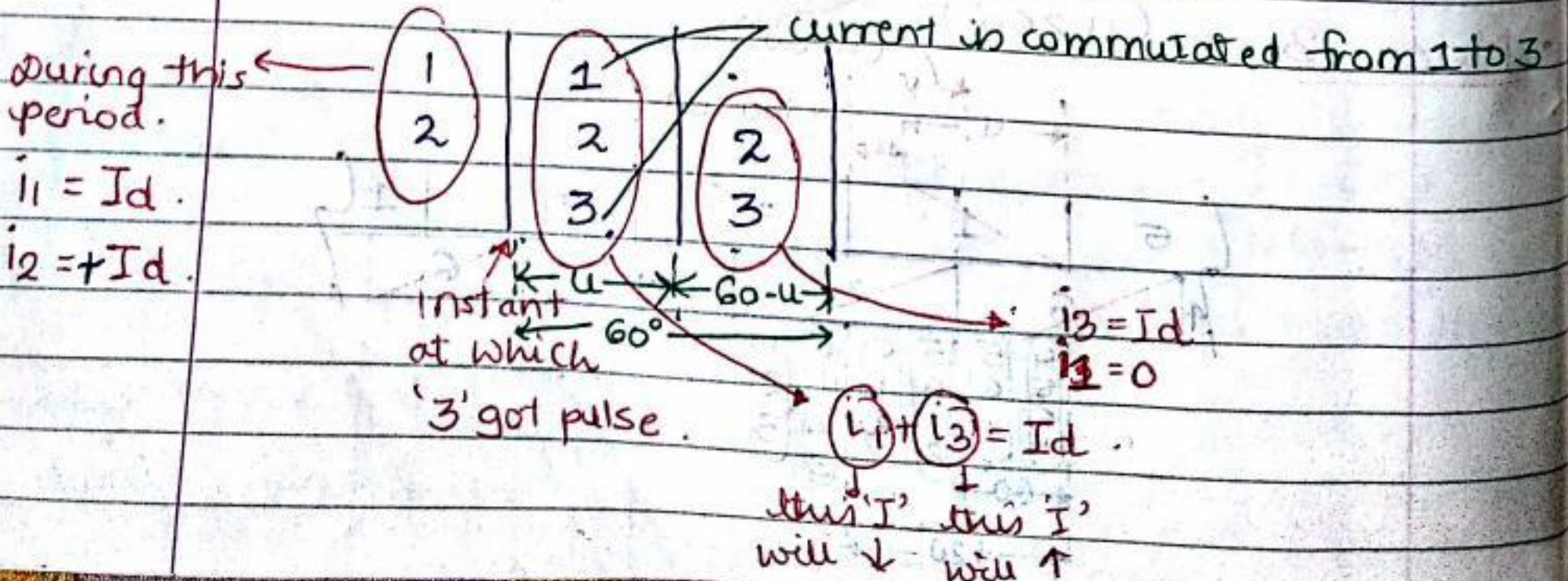

Page No.

Date: / /

- Now as seen phase 'A' is short circuited with phase 'B' as '1' & '3' both are conducting therefore V_A can be deduced as under

$$e_a - L \frac{di_1}{dt} = V_A \quad \text{--- (1)}$$

$$e_b - L \frac{di_3}{dt} = V_A \quad \text{--- (2)}$$

adding (1) & (2)

$$(e_a + e_b) - \left(L \frac{di_1}{dt} + L \frac{di_3}{dt} \right) = 2V_A$$

$$(e_a + e_b) - \left(2L \frac{d(I_d)}{dt} \right) = 2V_A$$

$I_d = \text{constant}$

$$(e_a + e_b) - (0) = 2V_A$$

$$\therefore V_A = \frac{e_a + e_b}{2}$$

$$\therefore V_A = \frac{e_a + e_b}{2} = \frac{-e_c}{2}$$

$$e_a + e_b + e_c = 0$$

$$\therefore e_a + e_b = -e_c$$

- The o/p voltage V_d is ;

$$V_d = \left\{ \frac{e_b + e_a}{2} - e_c \right\} = -\frac{3}{2} e_c \quad ; \quad 0 < \omega t < \pi$$

$$(e_b - e_c) = e_{bc} \quad ; \quad \pi < \omega t < 60 - \pi$$

when '1' is off x_g is e_b at (1)

tot x_g at (2) is e_c [check conduction pattern]

- The average dc voltage can be obtained by taking average over period of 60° thus;

$$V_d = \frac{1}{\pi/3} \left[\int_{0+\alpha}^{u+\alpha} \frac{-3 e_c}{2} d\omega t + \int_{u+\alpha}^{60+\alpha} e_{bc} d\omega t \right]$$

60° won't be considered because upper limit = $60+\alpha$ lower limit = α on subtraction $60+\alpha - \alpha = 60^\circ$

$V_c = \sqrt{3} E_m$

$e_c = E_m \sin(\omega t + \pi/2)$
 $e_{bc} = -E_m \cos \omega t$

$(+\alpha)$ is added if '3' is fired after a certain delay angle.

$$= \frac{3}{\pi} \left[\int_{\alpha}^{\alpha+u} \left(\frac{-3 e_c}{2} \right) d\omega t + \int_{\alpha+u}^{60+\alpha} (e_{bc}) d\omega t \right]$$

$$= \frac{3}{\pi} \left[\int_{\alpha}^{\alpha+u} \frac{3}{2} (E_m \cos \omega t) d\omega t + \int_{\alpha+u}^{60+\alpha} \sqrt{3} E_m \sin(\omega t + 60^\circ) d\omega t \right]$$

$$= \frac{3}{\pi} \left[\frac{3 E_m}{2} (\sin(\alpha+u) - \sin \alpha) + \sqrt{3} E_m (\cos(\alpha+u+60^\circ) - \cos(\alpha-120^\circ)) \right]$$


$$= \frac{3}{\pi} E_m \left[\frac{3 \sin(\alpha+u)}{2} - \frac{3 \sin \alpha}{2} + \frac{\sqrt{3} \cos(\alpha+u)}{2} - \frac{3 \sin(\alpha+u)}{2} + \frac{\sqrt{3} \cos \alpha + 3 \sin \alpha}{2} \right]$$

$$= \frac{3}{\pi} E_m \left[\frac{\sqrt{3} \cos(\alpha+u)}{2} + \frac{\sqrt{3} \cos \alpha}{2} \right]$$

$$V_d = \frac{3\sqrt{3} E_m}{2\pi} [\cos \alpha + \cos(\alpha+u)]$$

$$V_d = \frac{V_{d0}}{2} [\cos \alpha + \cos(\alpha+u)]$$

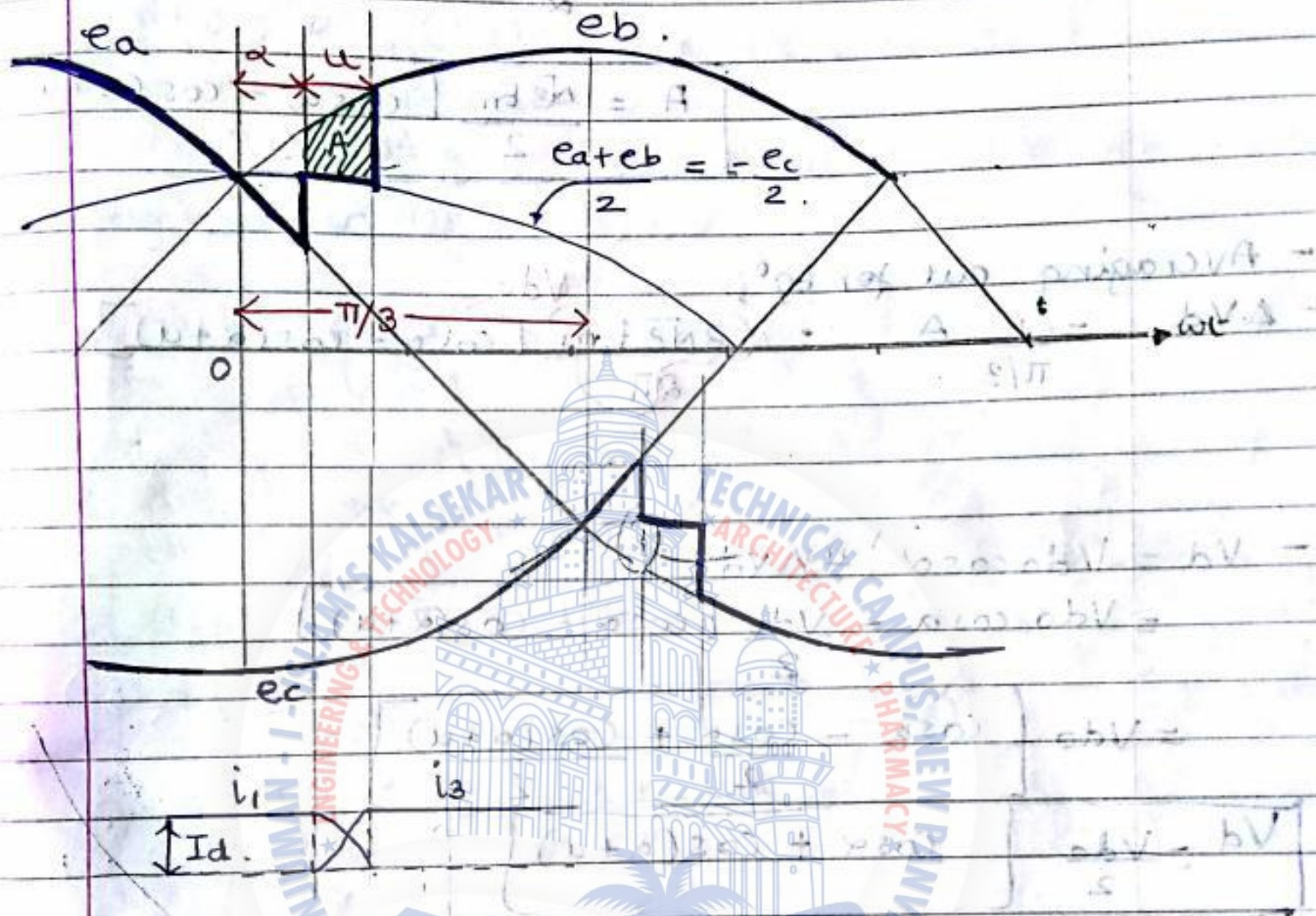The commutation from valve 1 to valve 3 is shown;



- From the above it is clear that the presence of overlap 'u' reduces the % r.v.g.

'Average dc voltage (Alternate Method)

- When $u = 0$;

$$V_d = V_d \cos \alpha$$

- Area $A = \int_{\alpha}^{\alpha+u} (e_b - \frac{e_a + e_b}{2}) d(\omega t)$

$= \int_{\alpha}^{\alpha+u} \frac{e_b - e_a}{2} d(\omega t)$

upper waveform (pointing to e_b)
lower waveform (pointing to $\frac{e_a + e_b}{2}$)

$-\frac{\sqrt{3}E_m \cos wt}{2}$
 Page No.
 Date: / /

$$= \int_{\alpha}^{\alpha+\mu} \frac{e_b a}{2} d(\omega t) = \int_{\alpha}^{\alpha+\mu} \frac{\sqrt{3} E_m \sin \omega t}{2} d\omega t$$

$$A = \frac{\sqrt{3} E_m}{2} [\cos \alpha - \cos(\alpha + \mu)]$$

- Averaging out for 60° .

$$-\Delta V_d = \frac{1}{\pi/3} \cdot A = \frac{3\sqrt{3} E_m}{2\pi} [\cos \alpha - \cos(\alpha + \mu)]$$

- $V_d = V_{do} \cos \alpha - \Delta V_d$

$$= V_{do} \cos \alpha - \frac{V_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)]$$


$$= V_{do} \left[\cos \alpha - \frac{\cos \alpha}{2} + \frac{\cos(\alpha + \mu)}{2} \right]$$

$$V_d = \frac{V_{do}}{2} [\cos \alpha + \cos(\alpha + \mu)]$$

• The Value current can be deduced as under:

We have;
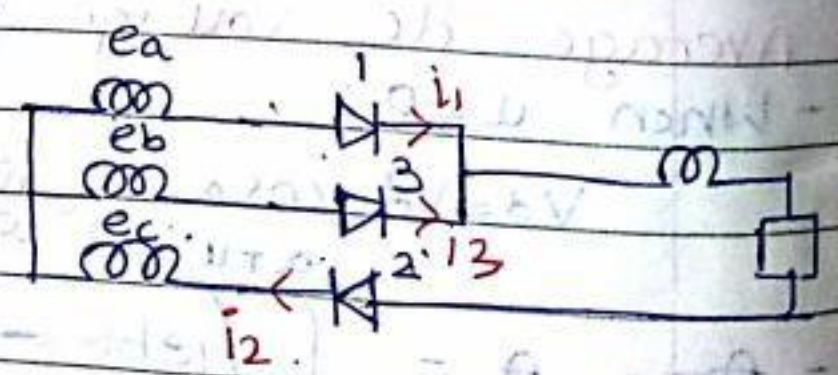
$$e_a - L \frac{di_1}{dt} = e_b - L \frac{di_3}{dt}$$



$$\therefore L \frac{di_3}{dt} - L \frac{di_1}{dt} = e_b - e_a \quad \text{--- (1)}$$

we also know;

$$i_1 + i_3 = I_d \quad \text{constant}$$

or $\frac{di_1}{dt} + \frac{di_3}{dt} = \frac{dI_d}{dt} \rightarrow 0$

$$\frac{di_1}{dt} = -\frac{di_3}{dt} \quad \text{--- (2)}$$

- putting (2) in (1)

$$L \frac{di_3}{dt} - L \left(-\frac{di_3}{dt} \right) = e_b - e_a$$

$$\therefore 2L \frac{di_3}{dt} = e_b - e_a$$

$$\therefore 2L \frac{di_3}{dt} = \sqrt{3} E_m \sin \omega t$$

$$\therefore i_3 = \frac{-\sqrt{3} E_m \cos \omega t + A}{2\omega L} \quad \text{--- (3)}$$

Because we have \int w.r. to 't' not 'wt'

• When $\omega t = \alpha$ (ie at the instant of firing '3')

$$i_3 = 0$$

$$\therefore A = \frac{\sqrt{3} E_m \cos \alpha}{2\omega L} \quad \text{from (3)} \quad \text{--- (4)}$$

Substituting (4) in (3)

$$\therefore i_3 = \frac{\sqrt{3} E_m}{2\omega L} (\cos \alpha - \cos \omega t)$$

$$= I_{s2} (\cos \alpha - \cos \omega t) \quad 0 \leq \omega t \leq \alpha$$

- Now;


$$i_1 = I_d - i_3$$

$$i_1 = I_d - I_{s2} (\cos \alpha - \cos \omega t) \quad \alpha \leq \omega t \leq \alpha + \pi$$

• Waveform of i_3 & i_1

↑ constant term added to i_3
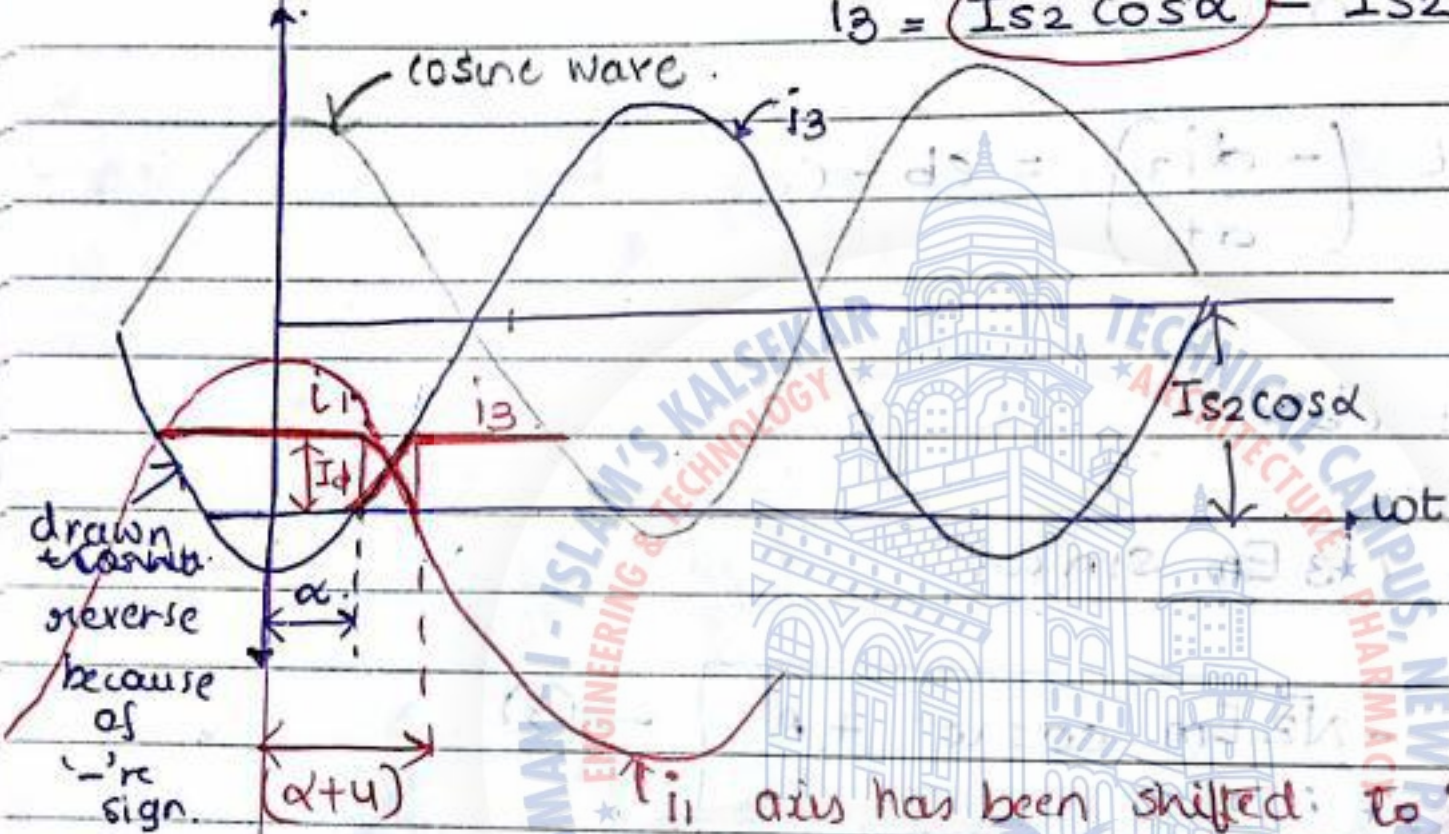
$$i_3 = I_{s2} \cos \alpha - I_{s2} \cos \omega t$$



drawn reverse because of -ve sign.

axis has shifted up coz of $I_{s2} \cos \alpha$ constant.

ii axis has been shifted to ' I_d '

& -ve of i_3 is taken to obtain

$$\text{this wave shape } [\because i_1 = I_d - i_3]$$



NAVI MUMBAI - INDIA

Handwritten notes in Urdu on the right page of the notebook, partially visible.

(lec 9: 26:52)

Page No.
 Date: / /

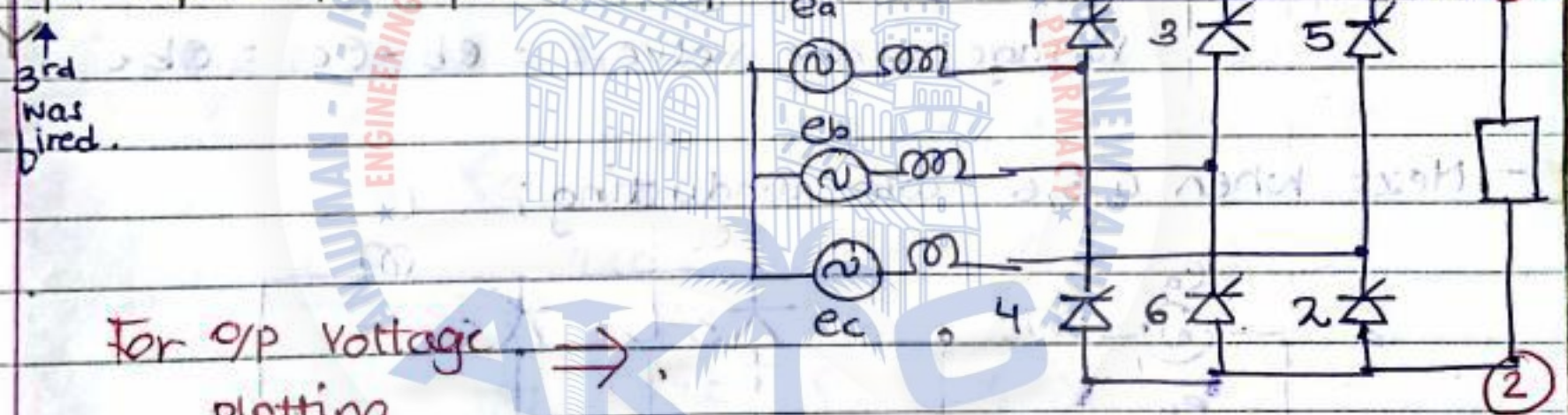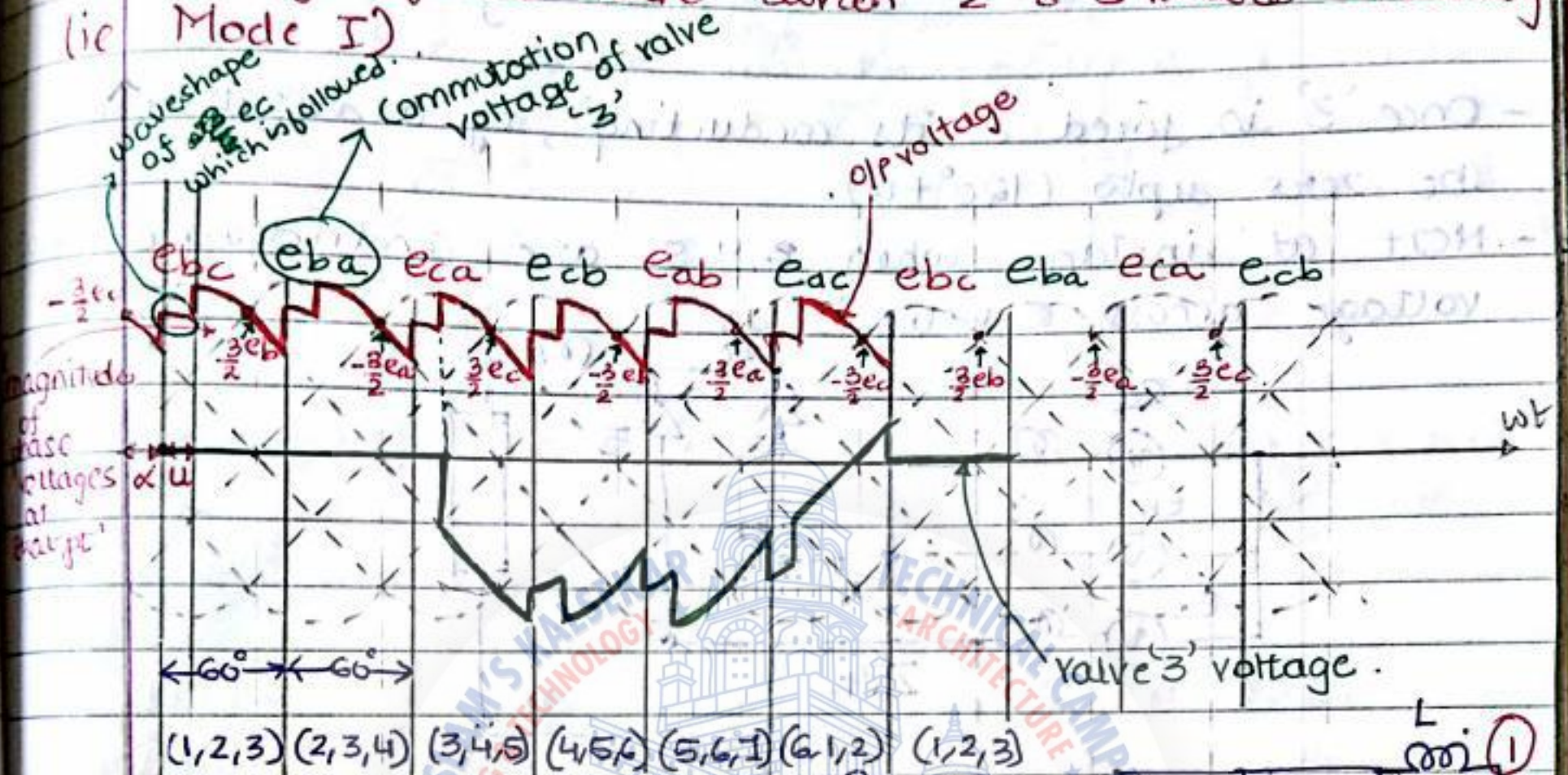o/p Voltage of the valve when '2' & '3' valve are conducting (Mode I)




For o/p voltage plotting

• When 1, 3, 2 are conducting
 v_g at terminal ① = $e_a + e_b = -\frac{e_c}{2}$
 v_g at terminal ② = e_c
 \therefore Net voltage = $-\frac{e_c}{2} - e_c = -\frac{3e_c}{2}$

• When 2, 3, 4 are conducting
 v_g at terminal ① = e_b
 v_g at terminal ② = $\frac{e_a + e_c}{2} = -\frac{e_b}{2}$
 \therefore Net voltage = $e_b - (-\frac{e_b}{2})$
 $= \frac{3e_b}{2}$


⇒ For Voltage across Valve '3' plotting

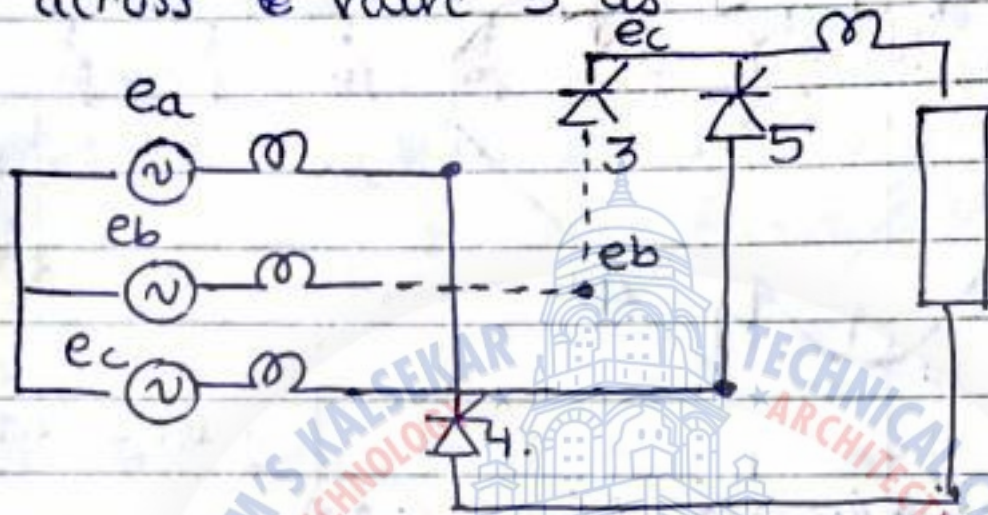- Once '3' is fired & its conducting, v_g across it will be zero upto $(120^\circ + \alpha)$.
- Next at instant when 3, 4, 5 are conducting & '3' is off voltage across valve '3' is



∴ Voltage across Valve 3 = $e_b - e_c = e_{bc}$


- Next when 4, 5, 6 are conducting;

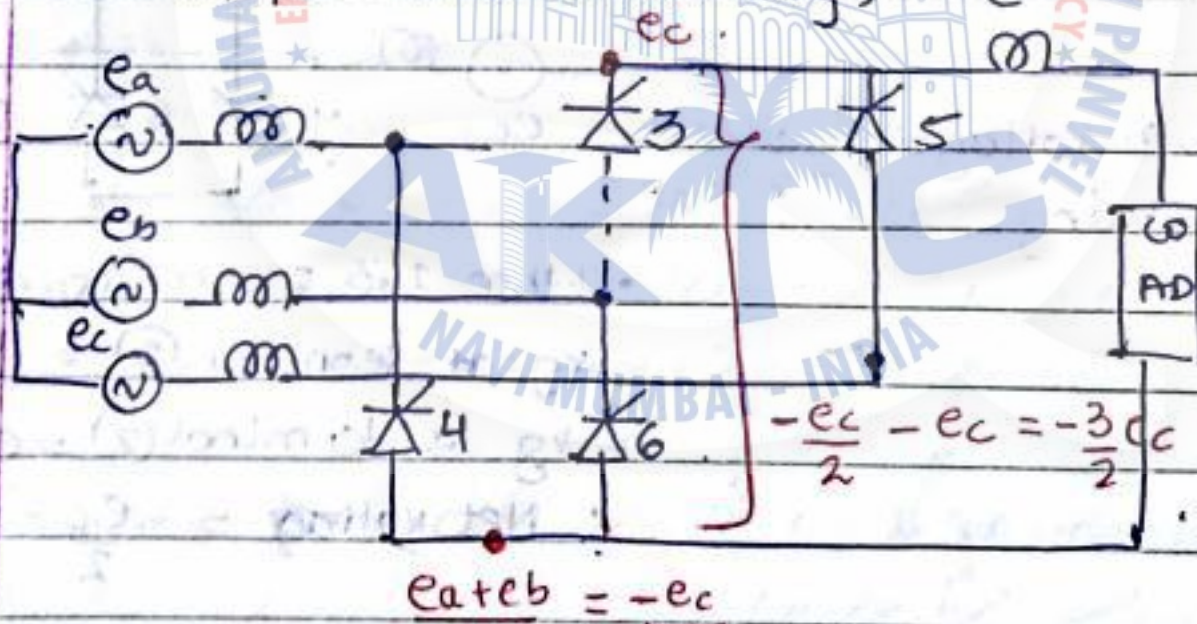

- So when 4, 5, 6 conducting; voltage across Valve '3' = $-\frac{3}{2}e_c$

- When 5, 6 conducting (after α) = $e_b - e_c = e_{bc}$.


- Next when 5, 6, 1 are conducting;

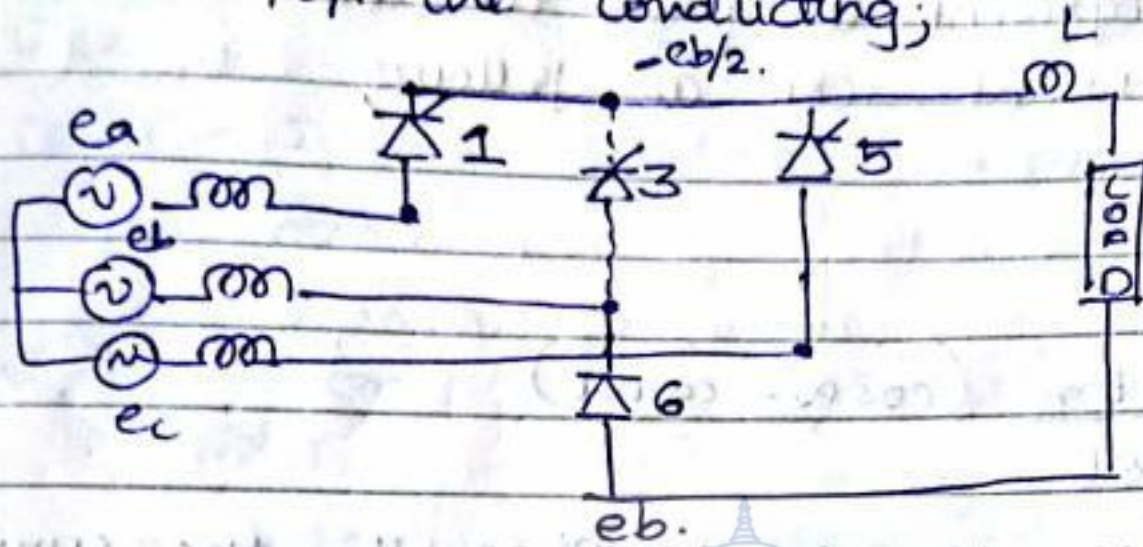

$$\therefore eb - \left(-\frac{eb}{2}\right) = \frac{eb + eb}{2} = \frac{3eb}{2}$$

- when 6, 1 are conducting; $eb - ea = eba$

- Next when 6, 1, 2 are conducting

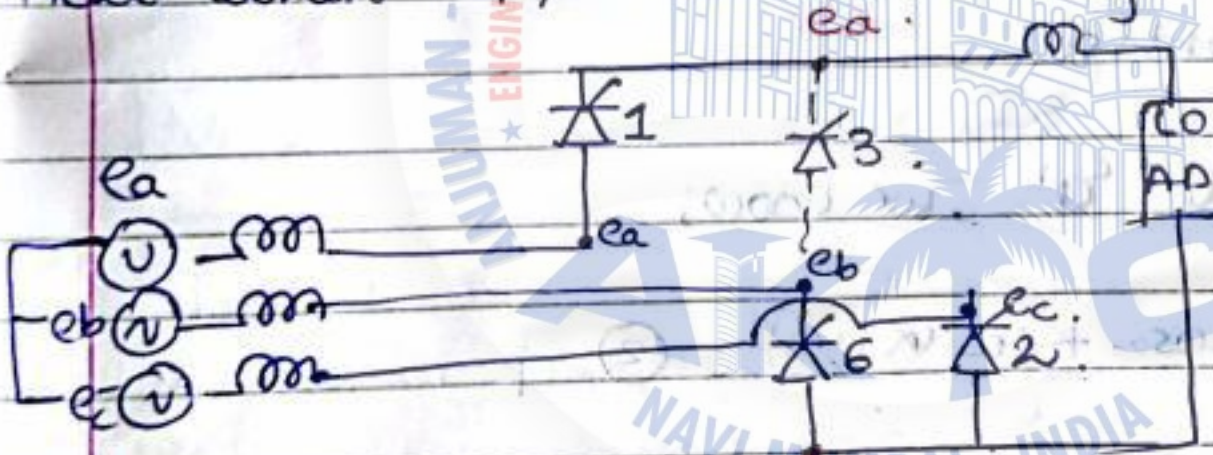

$$= -\frac{ea}{2} - ea = -\frac{3}{2}ea$$

when 1, 2 are conducting; $eb - ea = eba$

$$V_d = \frac{3\sqrt{3}}{2} V_m \cos \alpha$$

- We can relate represent the power electronic ckt in terms of electrical ckt as follows;

We know;

$$i_b = \frac{\sqrt{3} E_m}{2\omega L} (\cos \alpha - \cos \omega t)$$

once commutation is over at $\omega t = \alpha + \mu$, the current becomes;

$$I_d = \frac{\sqrt{3} E_m}{2\omega L} (\cos \alpha - \cos(\alpha + \mu)) \quad \text{--- (1)}$$

- We need the expr in the above in electrical ckt because the measurement 'u' is difficult because it depends on 'L' on source etc which is not under our control.

- So we eliminate 'u', we know;

$$V_d = \frac{V_{d0}}{2} (\cos \alpha + \cos(\alpha + \mu)) \quad \text{--- (2)}$$

from (1) & (2) we can eliminate 'u'

$$\text{so; } I_d = \frac{\sqrt{3} E_m}{2\omega L} [\cos \alpha - \cos(\alpha + \mu)]$$

$$V_d = \frac{3\sqrt{3} E_m}{2\omega L} (\cos \alpha + \cos(\alpha + \mu))$$

or;

Page No.

Date: / /

$$\frac{I_d}{I_{s2}} = \cos \alpha - \cos(\alpha + \mu)$$

or $\cos \alpha - \frac{I_d}{I_{s2}} = \cos(\alpha + \mu) \rightarrow$ put this in V_d .

$$\therefore V_d = \frac{3\sqrt{3} E_m}{2\pi} (\cos \alpha + \cos(\alpha + \mu))$$

$$= \frac{V_{d0}}{2} \left(\cos \alpha + \cos \alpha - \frac{I_d}{I_{s2}} \right)$$

$$= V_{d0} \cos \alpha - \frac{V_{d0} \cdot I_d}{2 I_{s2}}$$


$$= V_{d0} \cos \alpha - \left(\frac{3 \omega L}{\pi} \right) I_d$$

$$V_d = V_{d0} \cos \alpha - R_c I_d$$

\rightarrow Equivalent commutation resistance.

$$\text{or } R_c = \frac{3 \omega L}{\pi} = \frac{3 X_c}{\pi}$$

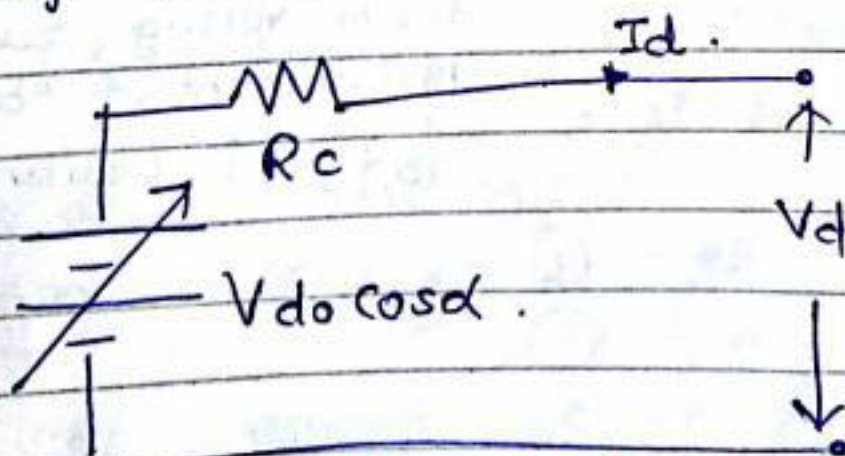- From above eq, it is clear that since ' I_d ' is constant % Voltage V_d can be varied by varying ' α ' alone.



Eq. ckt of Rectifier

* Inverter operation, ($u < 60^\circ$)

- The analysis of inverter operation is not different from the rectification, i.e. (α is delayed $> 90^\circ$).


- However the inverter eqs are normally expressed in terms of the angle of advance.

$$(\beta = \pi - \alpha)$$

or extinction angle,


$$(\gamma = \beta - u)$$

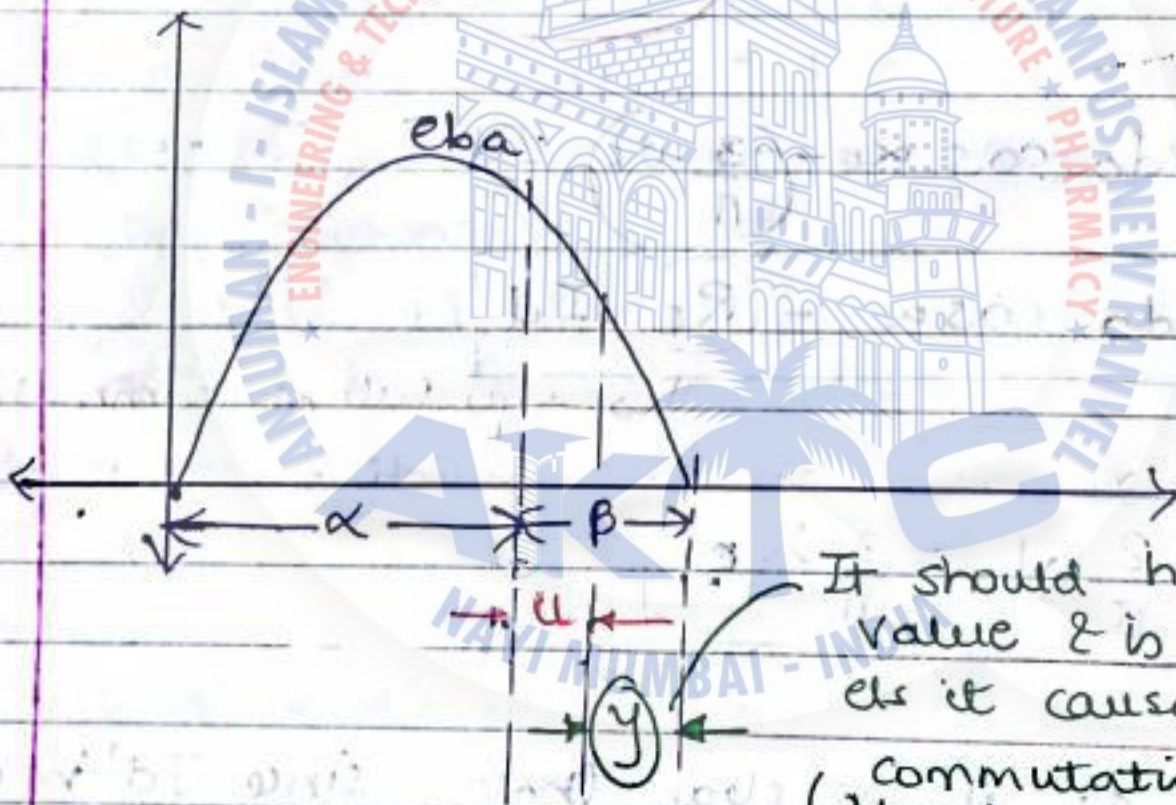- To understand α, γ, u, β consider the following



It should have minimum value & is important. else it causes unsuccessful commutation (Meaning normally $i_1 \downarrow, i_2 \uparrow$, if γ_{min} is not maintained due to voltage reversal at 180° instant of eba, $i_3 \downarrow, i_1 \uparrow$ causing maloperation)

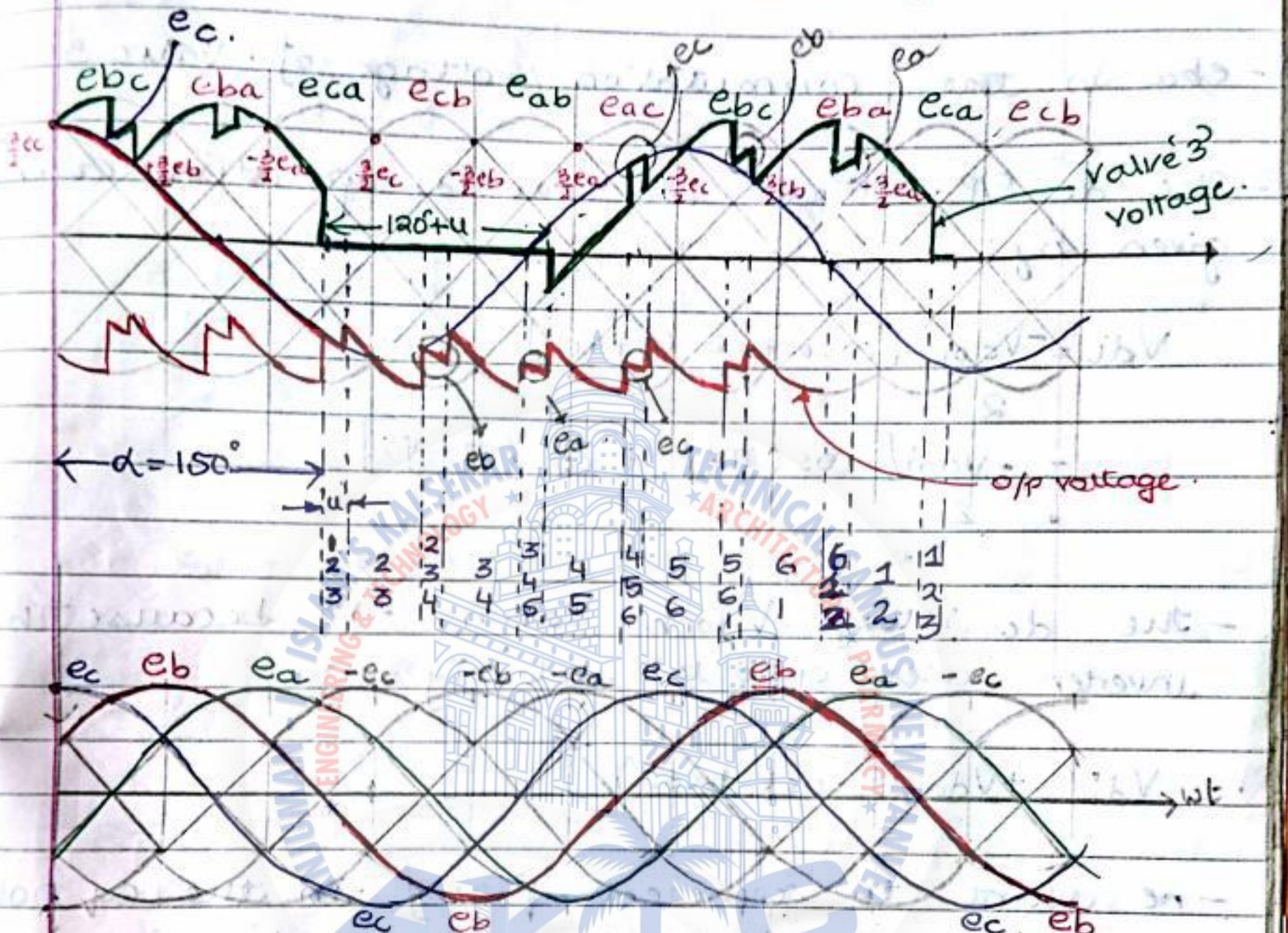* o/p voltage of inverter / valve voltage for '3' valve.



When 1, 2 are conducting & 3 is given pulse;
 o/p voltage at terminal ① = $e_a - e_b = -e_c$
 Voltage at terminal ② = e_c
 Net voltage = $\frac{-e_c - e_c}{2} = -1.5e_c$

for o/p voltage plotting

When 2, 3 are conducting;
 Voltage at terminal ① = e_b
 Voltage at terminal ② = e_c
 Net voltage = $e_b - e_c = e_{bc}$

- Assume $\alpha = 150^\circ$, $\beta = 30^\circ$, $\mu = 15^\circ$, $\gamma = 15^\circ$
- eba is the commutation voltage of valve 3.
- The dc o/p voltage in inverter operation can be given by;

$$V_{di} = \frac{-V_{doi}}{2} [\cos \alpha + \cos (\alpha + \mu)]$$

$$= \frac{-V_{doi}}{2} [\cos (\pi - \beta) + \cos (\pi - \gamma)]$$

- The dc voltage V_{doi} is taken -ve because the inverter uses opposite polarity.

$$V_{di} = \frac{+V_{doi}}{2} [\cos \beta + \cos \gamma]$$

- we want to represent β or γ in the eq, not both because both value estimation is risky

$$- V_{di} = - (V_{doi} \cos \alpha - R_c I_d) \quad \checkmark \text{ (check rectifier part for this derivation)}$$

$$= - (V_{doi} \cos (\pi - \beta) - R_c I_d)$$

$$\boxed{V_{di} = V_{doi} \cos \beta + R_c I_d}$$

or;

Page No.

Date: / /

$$\rightarrow \frac{2V_{doi}}{V_{doi}} = \cos \beta + \cos \gamma$$

$$\text{or } -\cos \gamma + \frac{2V_{di}}{V_{doi}} = \cos \beta$$



$$\rightarrow V_{di} = V_{doi} \cos \beta + R_c I_d$$

$$= V_{doi} \left(\frac{-\cos \gamma + 2V_{di}}{V_{doi}} \right) + R_c I_d$$


$$V_{di} = -V_{doi} \cos \gamma + 2V_{di} + R_c I_d$$

$$-2V_{di} + V_{di} = -V_{doi} \cos \gamma + R_c I_d$$
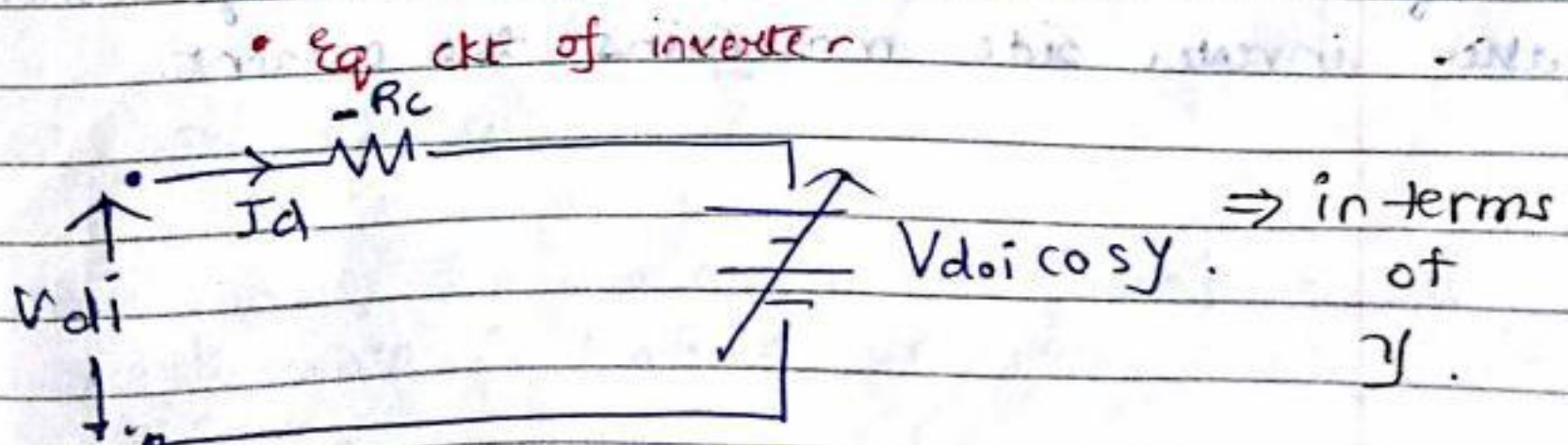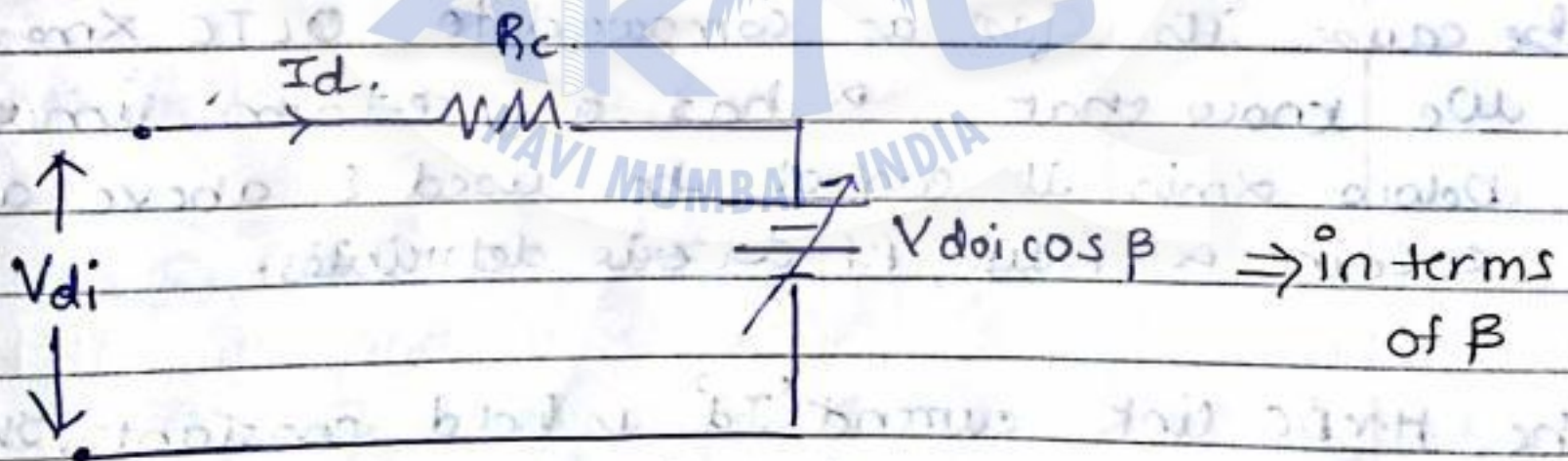
$$V_{di} = V_{doi} \cos \gamma - R_c I_d$$



* Equivalent ckt of HVDC link.

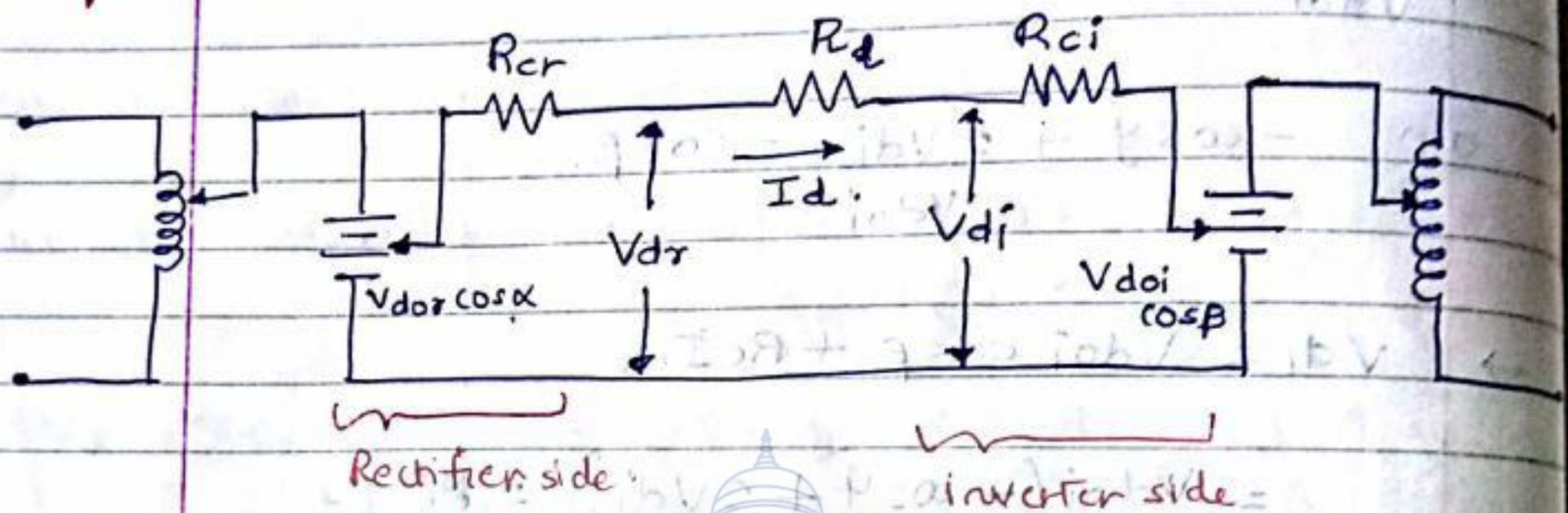

- The OLTC transformer which acts as controller for varying voltage

- From above it is clear that the voltage at two ends can be varied by

(1) the OLTC Xmer

(2) By varying α , β .


- But it is preferred voltage is varied by varying ' α ' because it's fast as compared to OLTC Xmer

- We know that α has a certain limit range below α_{min} it cannot be used & above a certain α value, P.F deteriorates.

- The HVDC link current ' I_d ' is held constant. The rectifier side maintains the voltage whereas the inverter side maintains the current.

* Mode III (3-4 Valves conduction mode) (abnormal mode of operation)

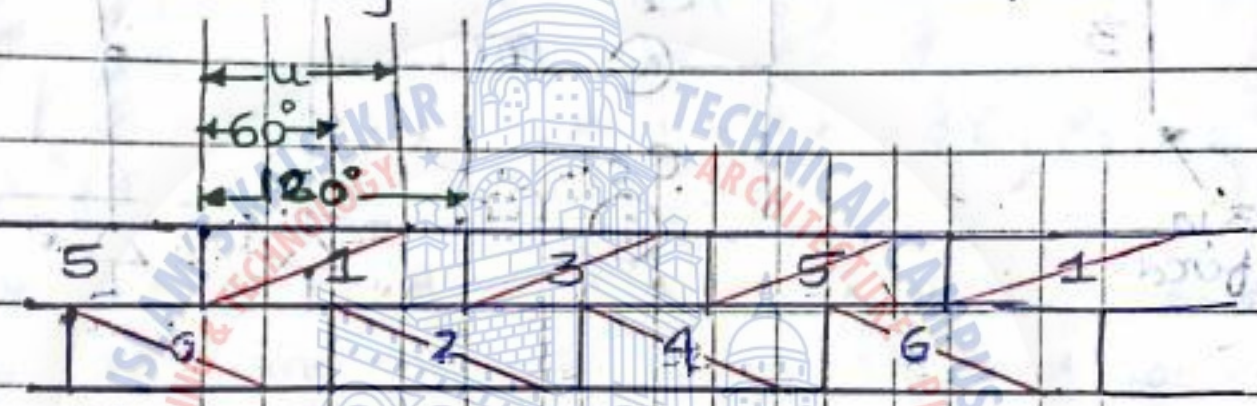
- Operation of bridge converter with overlap angle $60^\circ \leq \mu \leq 120^\circ$ is abnormal.
- This condition is encountered under overload dc short ckt or low ac voltage.
- However it is self curing, i.e. after overlap time it starts conducting in 3 valves mode.



4	5	5	6	6	1	1	2	2	3	3	4	4
5	6	6	1	1	2	2	3	3	4	4	5	5
6	1	1	2	2	3	3	4	4	5	5	6	6
1	2	2	3	3	4	4	5	5	6	6	1	1

} valve conduction


- Consider a 4 Valve-Conduction Case:

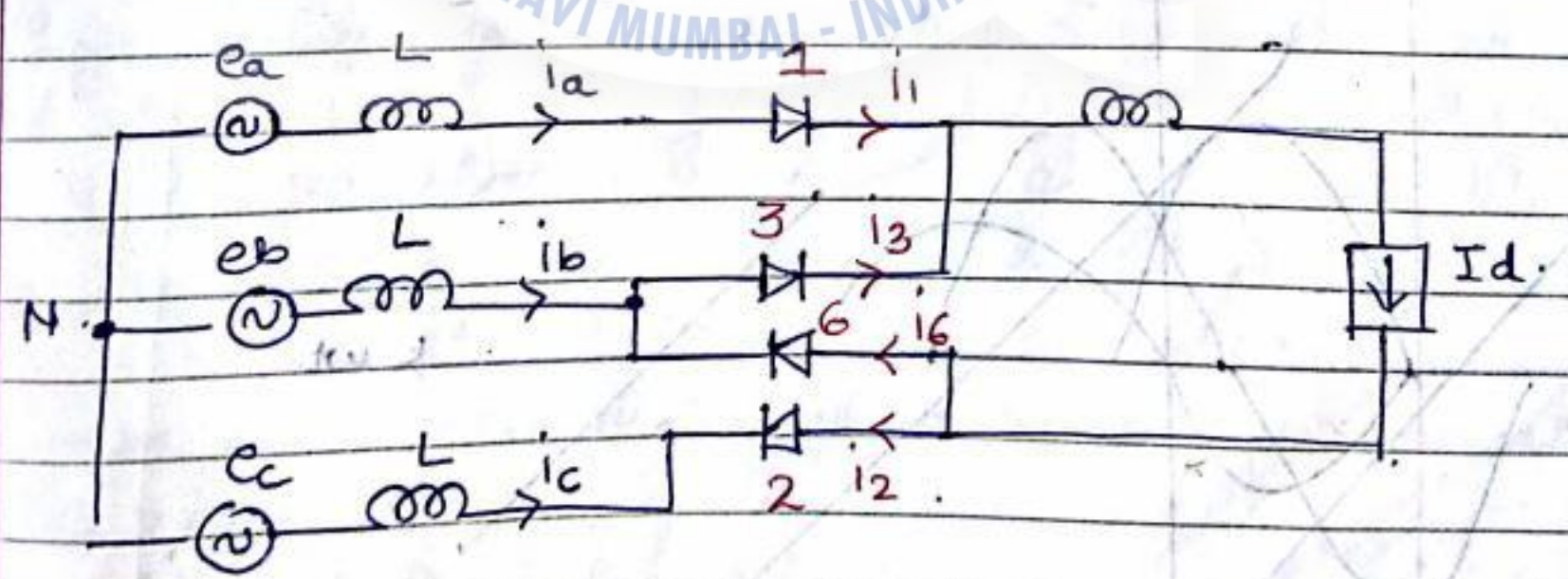


In this case, 3, 6 are conducting, that results in short circuit \therefore No voltage at o/p.


- In this condition ' α ' cannot be less than 30° .
In 2-3 valve conduction mode α could be varied between $0-180^\circ$.

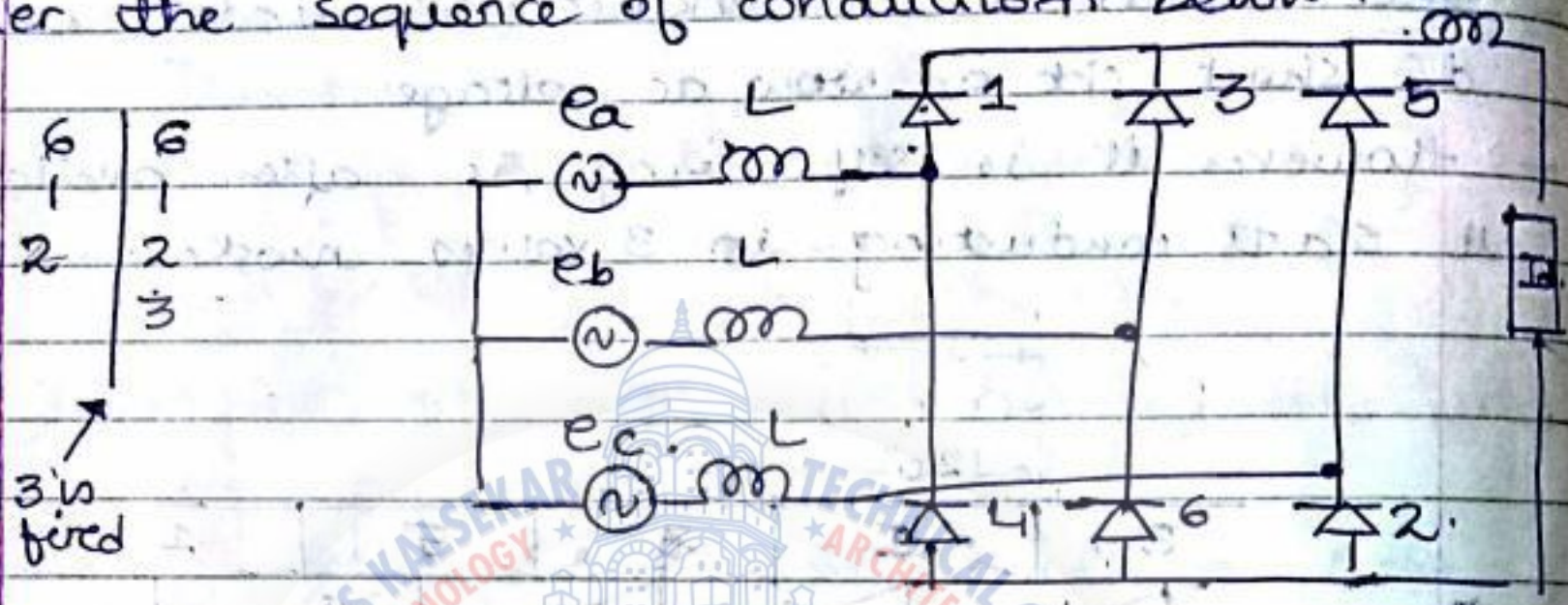- Consider the sequence of conduction below.



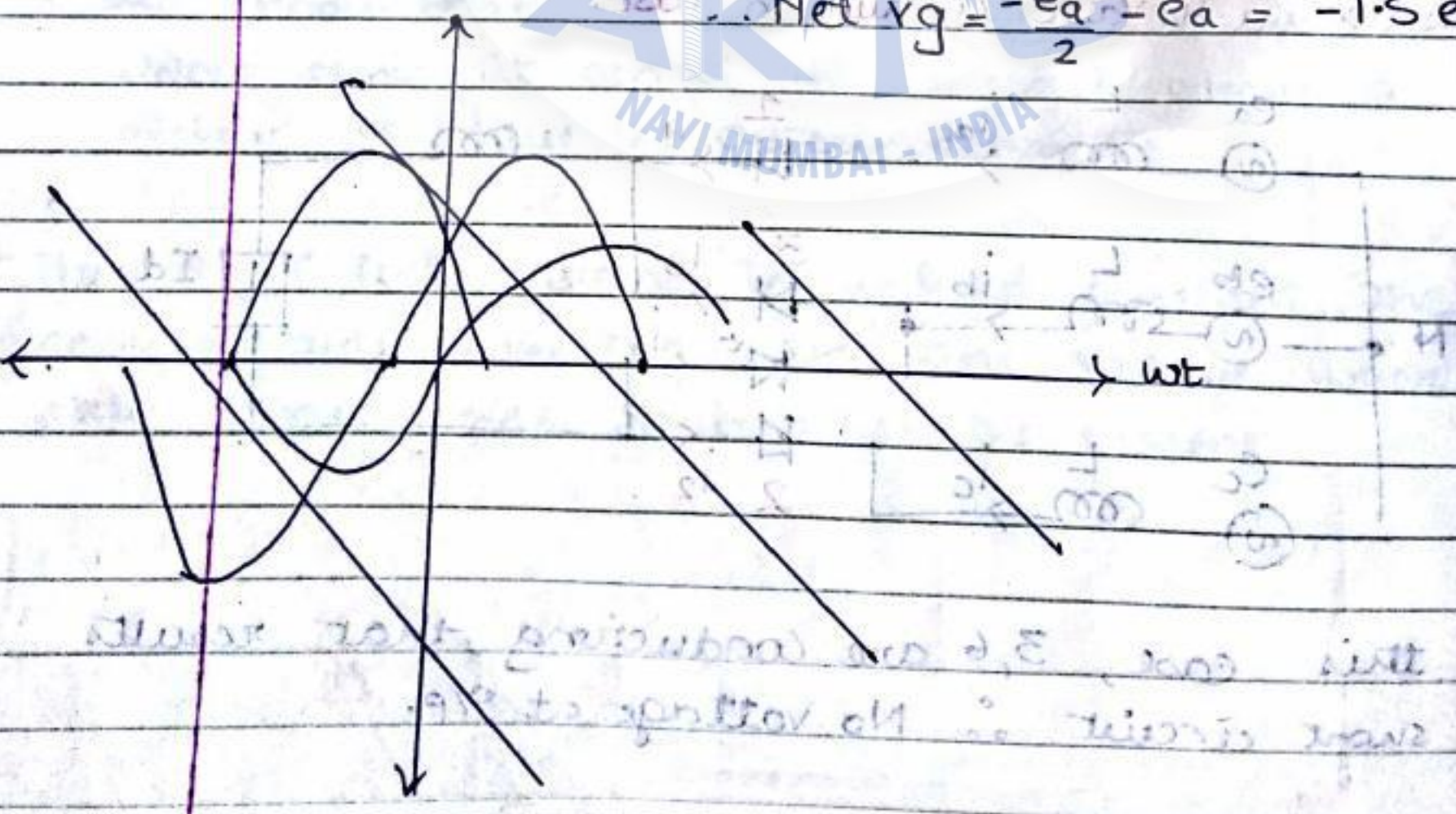• When 6, 1, 2 conducts;
The v_{gk} at terminal 1 = e_a .
Therefore
→ v_g across cathode of '3' = e_a .
→ " " anode of '3' = $-e_a/2$.
∴ Net $v_g = \frac{-e_a - e_a}{2} = -1.5 e_a$.



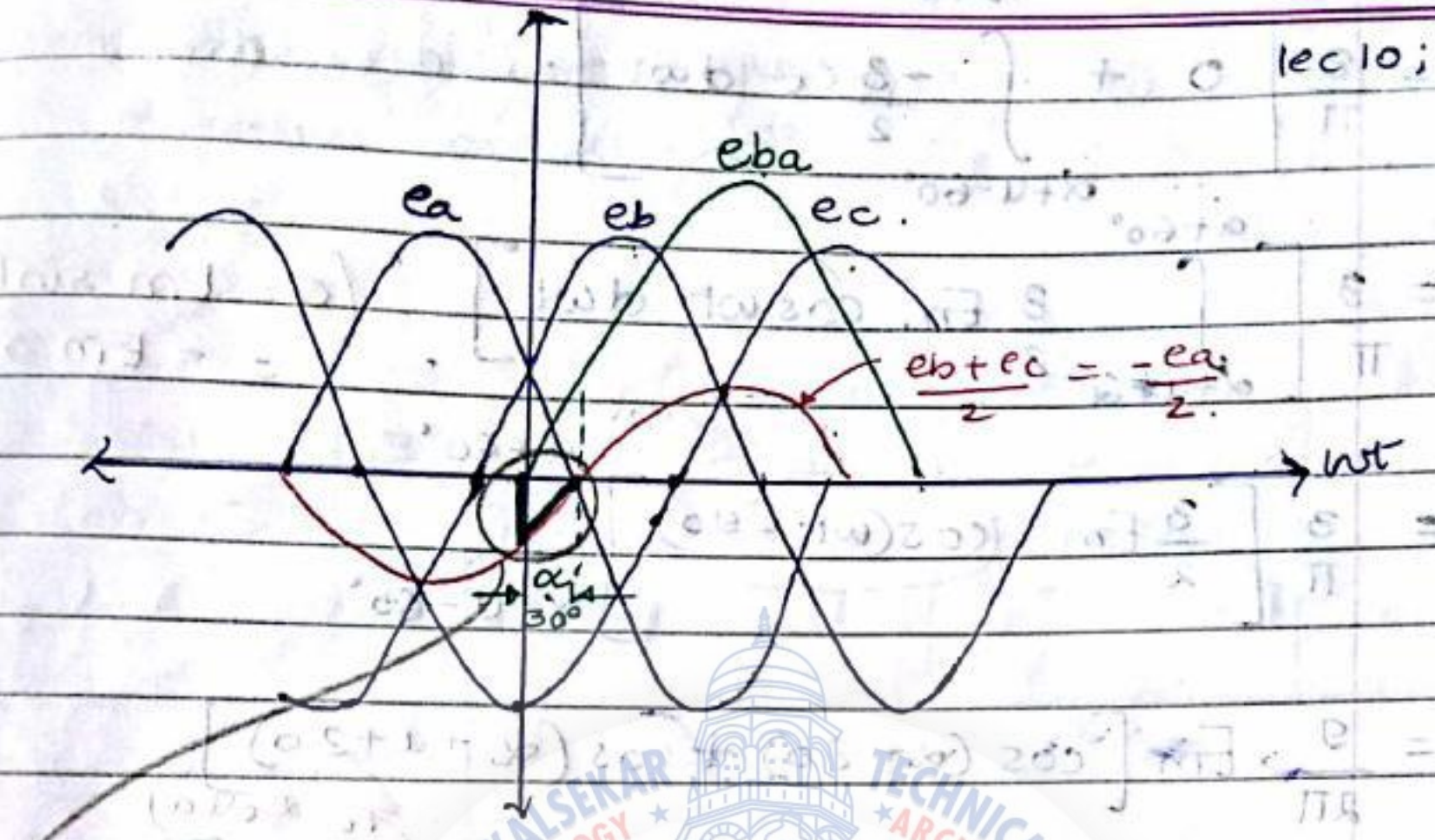

→ It will not conduct since the voltage across '3' is '-ve' and only after 30° do the voltage becomes '+ve'

check valve conduction fig

$$V_d = \begin{cases} 0 & \text{4 valve conduction} & (\alpha \leq \omega t \leq (\alpha + u - 60^\circ)) \\ -1.5 e_d & \text{3 valve conduction (ie, 1, 2, 3 conduction)} & (\alpha + u - 60^\circ) \leq \omega t \leq \alpha + 60^\circ \end{cases}$$

→ voltage is drastically low hence this mode is to be avoided.

$$\alpha + 60 - \alpha - u + 60 = (120 - u)$$

cos()
Date: / /


$$\begin{aligned}
 -V_d &= \frac{3}{\pi} \left[0 + \int_{\alpha+u-60^\circ}^{\alpha+60^\circ} \frac{-3 e_c}{2} d\omega t \right] \\
 &= \frac{3}{\pi} \left[\int_{\alpha+u-60^\circ}^{\alpha+60^\circ} \frac{3 E_m \cos \omega t}{2} d\omega t \right] \quad (e_c = E_m \sin(\omega t - \pi/2) = -E_m \cos \omega t) \\
 &= \frac{3}{\pi} \left[\frac{3 E_m}{2} \cos(\omega t - 90^\circ) \right]_{\alpha+u-60^\circ}^{\alpha+60^\circ} \\
 &= \frac{9}{2\pi} E_m \left[\cos(\alpha - 30^\circ) + \cos(\alpha + u + 30^\circ) \right] \\
 &= \frac{\sqrt{3}}{2} V_{do} \left[\cos(\alpha - 30^\circ) + \cos(\alpha + u + 30^\circ) \right] \quad \delta(\text{delta})
 \end{aligned}$$

* IP voltage waveforms in Rectification mode with 3-4 valve conduction
 $u > 60^\circ$
 $\alpha > 30^\circ$
 Let's take ; $\alpha = 45^\circ$
 $u = 75^\circ$


Conduction values	from	To	DC Voltage	Valve voltage	(lec 11 7:06)
6123	$45^\circ + 15^\circ = 60^\circ$	60°	0 (DC short ckt)	0	
123	$60^\circ + 45^\circ = 105^\circ$	105°	$-1.5 e_c$	0	
1234	$105^\circ + 15^\circ = 120^\circ$	120°	0	0	
234	120	165	$1.5 e_b$	0	
2345	165	180	0	0	
345	180	225	$-1.5 e_a$	0	
3456	225	240	0	0	
456	240	285	$1.5 e_c$	$-1.5 e_c$	
4561	285	300	0	0 (S.C across all phases)	
561	300	345	$-1.5 e_b$	$1.5 e_b$	

When 3 valves conduct - 45°
 4 valves conduct - 15°

5612	345	360°	0	0 (S.C across all phase)
612	360°	45°	$-1.5ea$	$-1.5ea$

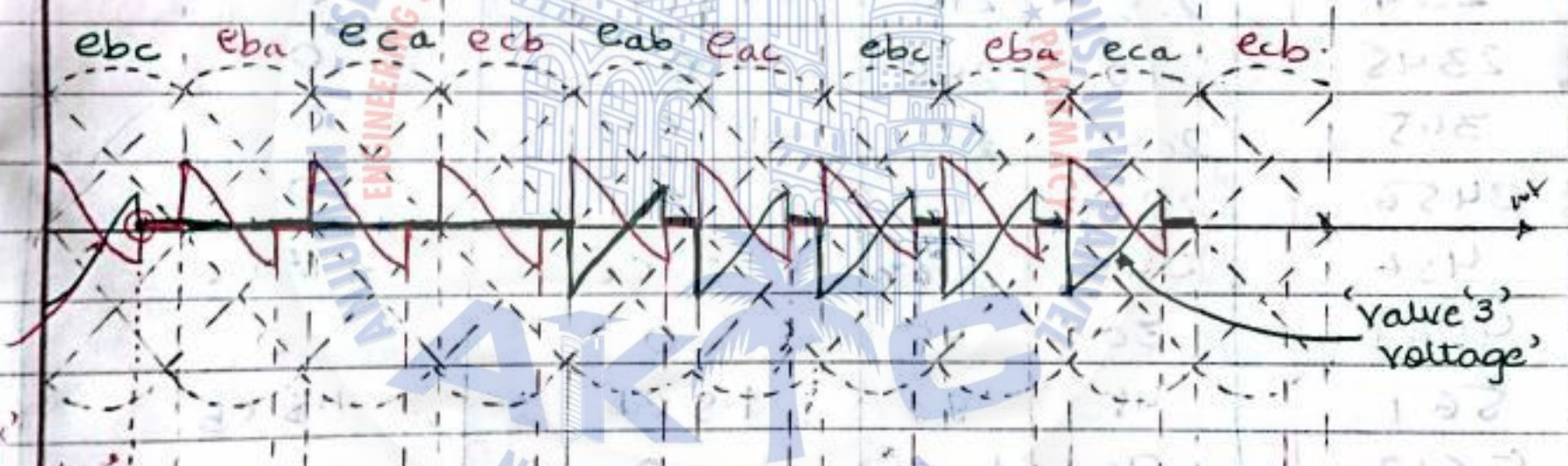

6	1	1	2	2	3	3	4	4	5	5	6	6	1	2	2	3	3	
1	2	2	3	3	4	4	5	5	6	6	1	1	2	2	3	3	4	4
2	3	3	4	4	5	5	6	6	1	1	2	2	3	3	4	4	5	5
3	4	4	5	5	6	6	1	1	2	2	3	3	4	4	5	5	6	6

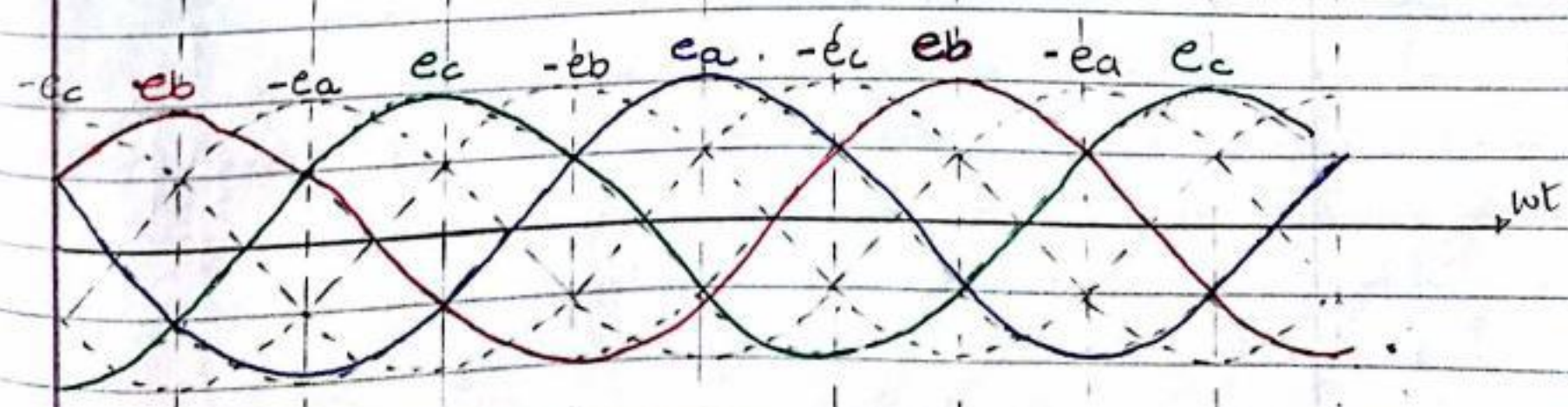


* o/p voltage waveforms for inversion mode with 3-4 valve conduction

$\alpha = 75^\circ$
 $\omega = 75^\circ$

3 valves — 45°
4 valves — 15°

Conduction Valves	From	To	DC voltage	Valve 3 Voltage
6123	$150^\circ + 15^\circ = 165$	165	0	0
123	$165 + 45 = 210$	210	-1.5 ec	0
1234	210	225	0	0
234	225	270	+1.5 eb	0
2345	270	285	0	0
345	285	230	-1.5 ea	0
3456	230	345	0	0
456	345	$360 + 90 = 390$ 230	+1.5 ec	-1.5 ec
4561	30	45	0	0
561	45	90	-1.5 eb	1.5 eb
5612	90	105	0	0
612	105	150	+1.5 ea	-1.5 ea
6123				

s/p voltage

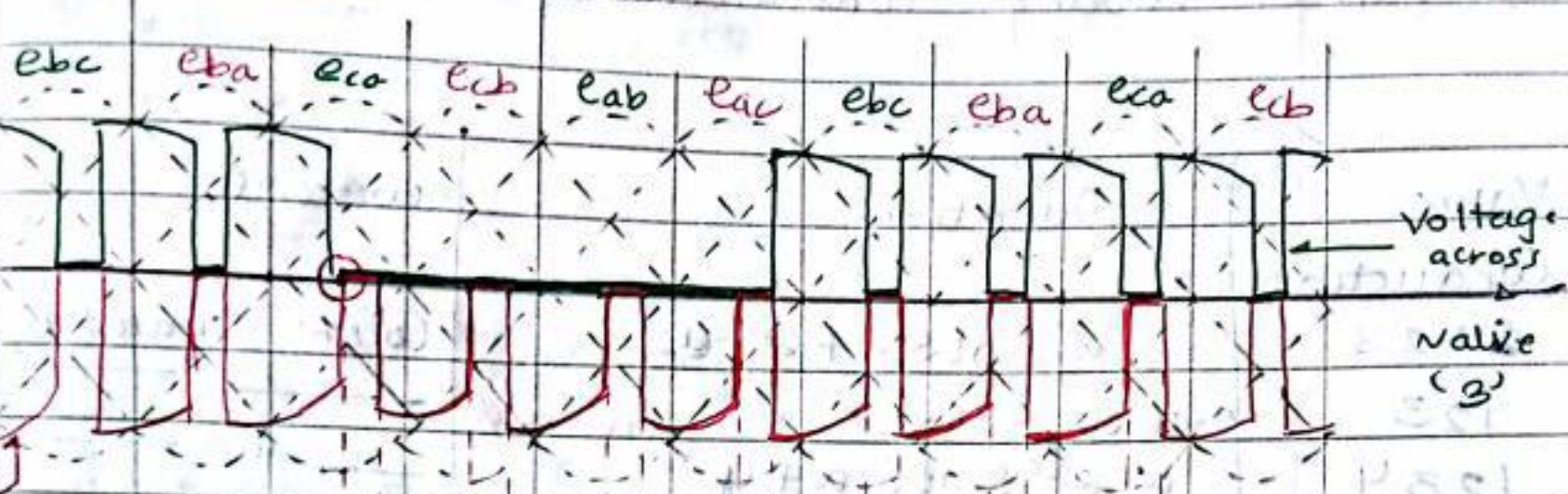


$\alpha = 150^\circ$

$u = 75^\circ$

60°

6	1	2	2	3	3	4	4	5	5	6	6
1	2	3	4	5	6	1	2	3	4	5	6
2	3	4	5	6	1	2	3	4	5	6	1
3	4	5	6	1	2	3	4	5	6	1	2

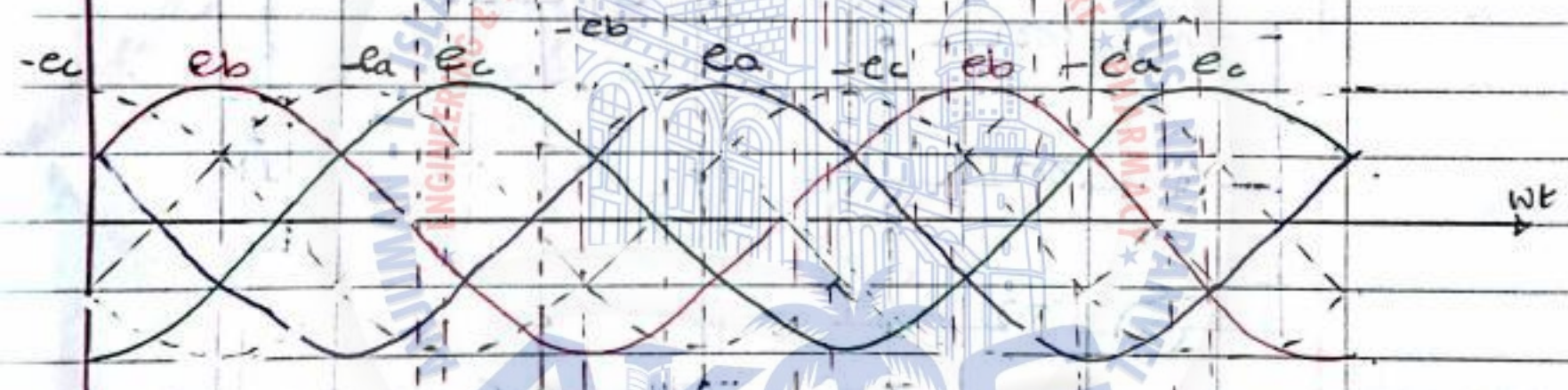


NAVI MUMBAI, INDIA


* Current during commutation;

(lec II, 45:00)

Valve Conduction	Duration	Current
6 1 2 3	$\alpha \leq \omega t \leq \alpha + \mu - 60^\circ$	Current Shared by '1' & '3'
1 2 3	$\alpha + \mu - 60 \leq \omega t \leq \alpha + 60^\circ$ <small>$\alpha + 60^\circ + (\mu - 60)$</small>	"
1 2 3 4	$\alpha + 60^\circ \leq \omega t \leq (\alpha + \mu)$	"
2 3 4	$\alpha + \mu \leq \omega t \leq \alpha + 120^\circ$	Valve '3' will carry I_d

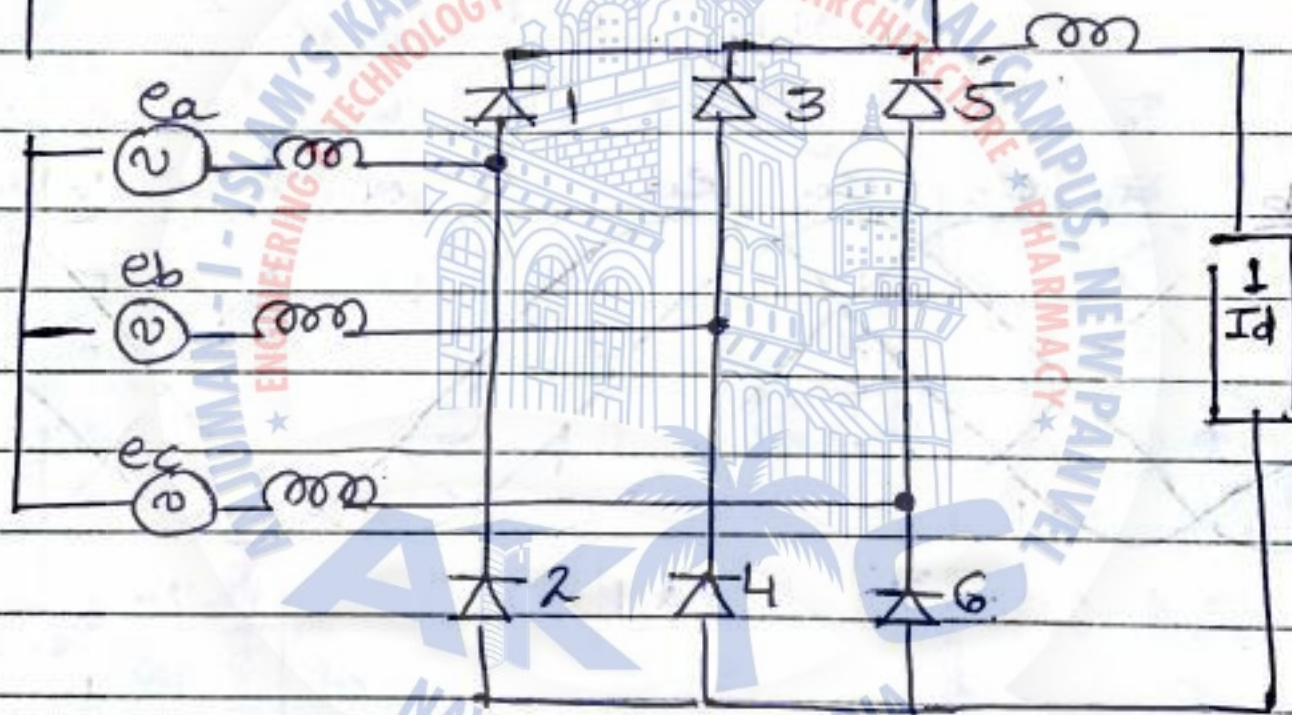

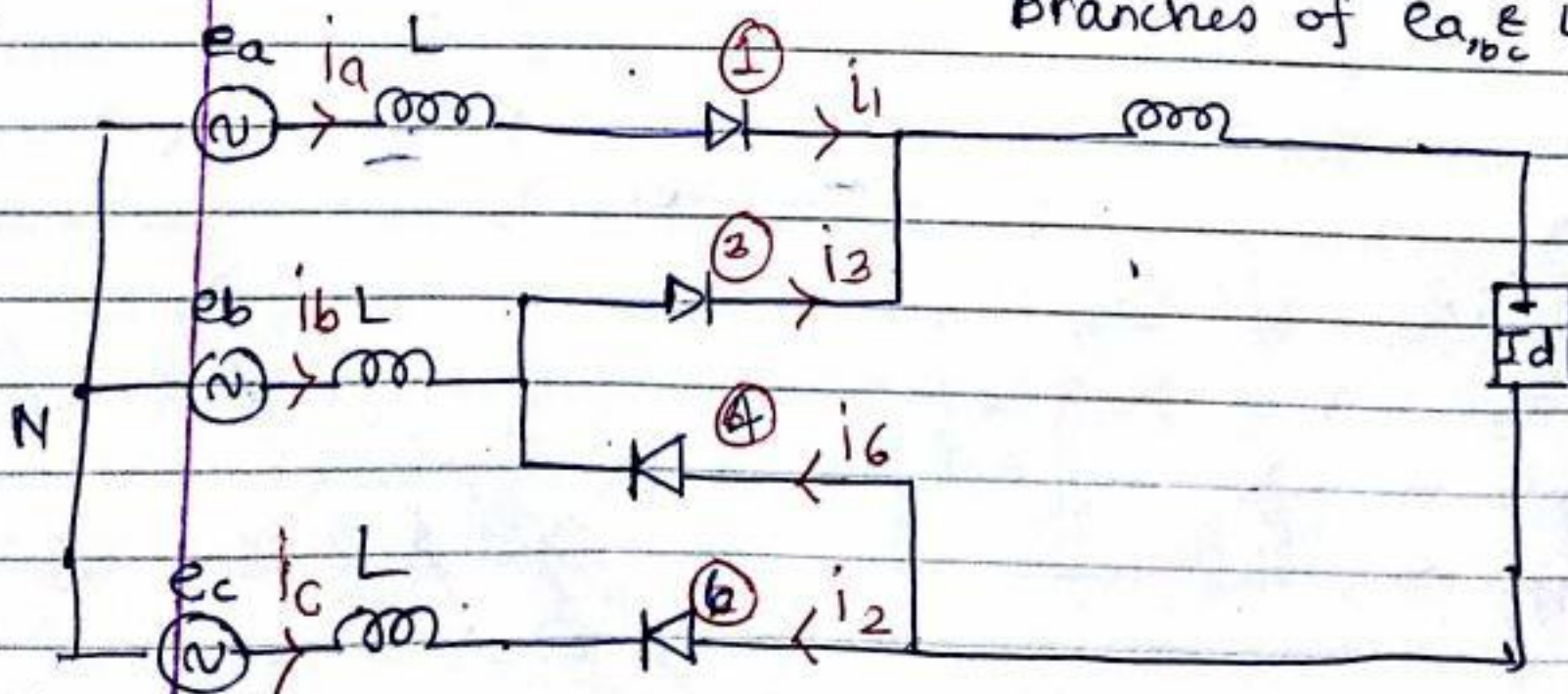• Consider conduction of 6 1 2 3; (S.C will cause 3 parallel branches of e_a, e_b, e_c & L).



$$\rightarrow e_a - L \frac{di_a}{dt} = e_b - L \frac{di_b}{dt} \quad \text{--- (1)}$$

and;

$$\rightarrow e_a - L \frac{di_a}{dt} = e_c - L \frac{di_c}{dt} \quad \text{--- (2)}$$

Adding (1) & (2)

$$\frac{2e_a}{a} - 2L \frac{di_a}{dt} = (e_b + e_c) - L \left(\frac{di_b}{dt} + \frac{di_c}{dt} \right)$$

$$2e_a - e_b - e_c = 2L \frac{di_a}{dt} - L \frac{di_b}{dt} - L \frac{di_c}{dt}$$

$$2e_a + e_a = 2L \frac{di_a}{dt} - L \frac{di_b}{dt} - L \frac{di_c}{dt}$$

$$3e_a = 2L \frac{di_a}{dt} + L \frac{di_a}{dt}$$

$$\therefore e_a = \frac{3L}{3} \frac{di_a}{dt}$$

$$\rightarrow \frac{di_a}{dt} = \frac{e_a}{L} = \frac{di_a}{dt} = -\frac{di_3}{dt} = \frac{E_m \sin(\omega t + 150^\circ)}{L}$$

\downarrow
 e_a

$$\begin{aligned} \therefore e_b &= \sqrt{3} E_m \sin \omega t \\ \therefore e_c &= E_m \sin(\omega t + 30^\circ) \\ e_a &= E_m \sin(\omega t + 150^\circ) \end{aligned}$$

$$\rightarrow -\frac{di_3}{dt} = \frac{E_m \sin(\omega t + 150^\circ)}{L} \quad (\text{lec 11; 52:00})$$

$$\therefore i_3 = \int \frac{-E_m \sin(\omega t + 150^\circ)}{L}$$

$$= \frac{E_m}{\omega L} [\cos(\omega t + 150^\circ) - \cos(\alpha + 150^\circ)]$$

$$= \frac{E_m}{\omega L} [-\cos(\omega t - 30^\circ) + \cos(\alpha - 30^\circ)]$$

$$\rightarrow i_3 \text{ (at } \omega t = \alpha + \mu - 60^\circ) = \frac{E_m}{\omega L} \left[\frac{-\cos(\alpha + \mu - 90^\circ) + \cos(\alpha - 30^\circ)}{(\alpha - 30^\circ)} \right]$$

• When waves 1, 2, 3 are conducting, $(\delta - 60) \leq \omega t \leq \alpha + 60$

$$\rightarrow \frac{di_3}{dt} = \frac{e_b - e_a}{2L} = \frac{\sqrt{3} E_m}{2L} \sin \omega t \quad (\text{from previous derivation})$$

$$\rightarrow i_3 = \frac{\sqrt{3} E_m}{2\omega L} \int_{\delta - 60}^{\omega t} \sin \omega t (d\omega t) + I_3 \text{ (at } \delta - 60) \quad \text{initial current}$$

$$\rightarrow i_3 = \frac{\sqrt{3} E_m}{2\omega L} [-\cos \omega t + \cos(\delta - 60)] + I_3 \text{ (at } \delta - 60)$$

$$I_3 \text{ (at } \omega t = \alpha + 60) = \frac{\sqrt{3} E_m}{2\omega L} [\cos(\delta - 90) - \cos(\alpha + 60)] +$$

$$\frac{E_m}{\omega L} [-\cos(\delta - 90) + \cos(\alpha - 30)]$$

$$= \frac{E_m}{\omega L} \left[\cos(\alpha - 30) + \frac{1}{2} \cos(\delta + 30) - \frac{\sqrt{3}}{2} \cos(\alpha + 60) \right]$$

* when valves 1, 2, 3, 4 are conducting (please note $i_a \neq i_a$)

$$e_a - L \frac{di_a}{dt} = e_b - L \frac{di_b}{dt} ; e_b - L \frac{di_b}{dt} = e_c - L \frac{di_c}{dt}$$

$$2 e_b - e_a - e_c = 2 L \frac{di_b}{dt} - L \frac{di_a}{dt} - L \frac{di_c}{dt}$$

$$e_b = L \frac{di_b}{dt} = L \frac{di_c}{dt} = E_m \sin(\omega t + 30^\circ)$$

lec 12


3 21

$$i_b = \frac{E_m}{\omega L} [\cos(\alpha + 60 + 30) - \cos(\omega t + 30)] +$$

$$I_b \text{ (at } \alpha + 60)$$

$$\text{at } \omega t = \delta$$
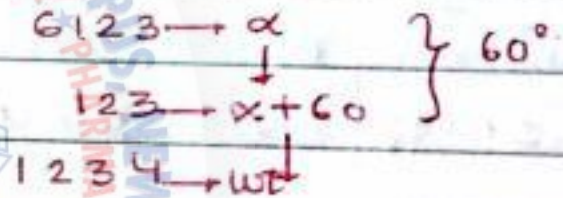
$$I_d = I_b = \frac{E_m}{2\omega L} [\cos(\alpha - 30) - \cos(\delta + 30)]$$



for $\omega > 60$

We want to express V_d & I_d without 'u' term;

We know that for ($u < 60$) we have the following expression;

$$V_d = \frac{V_{d0}}{2} (\cos \alpha + \cos \delta)$$

$$V_{d0} = \frac{3\sqrt{3}}{\pi} E_m$$

• Relation between Current & Voltage:


$$V_d = \frac{9 E_m}{2 \omega L} [\cos(\alpha - 30) + \cos(\delta + 30)]$$

$$I_d = \frac{E_m}{2 \omega L} [\cos(\alpha - 30) - \cos(\delta + 30)]$$

Shift terms of this eq, to get in term of 'Id'. Then substitute in above 'Vd' to get below 'Vd'

$$V_d = \sqrt{3} V_{d0} \cos(\alpha - 30) - 3 R_c I_d \quad \because R_c = \frac{3 \omega L}{\pi}$$

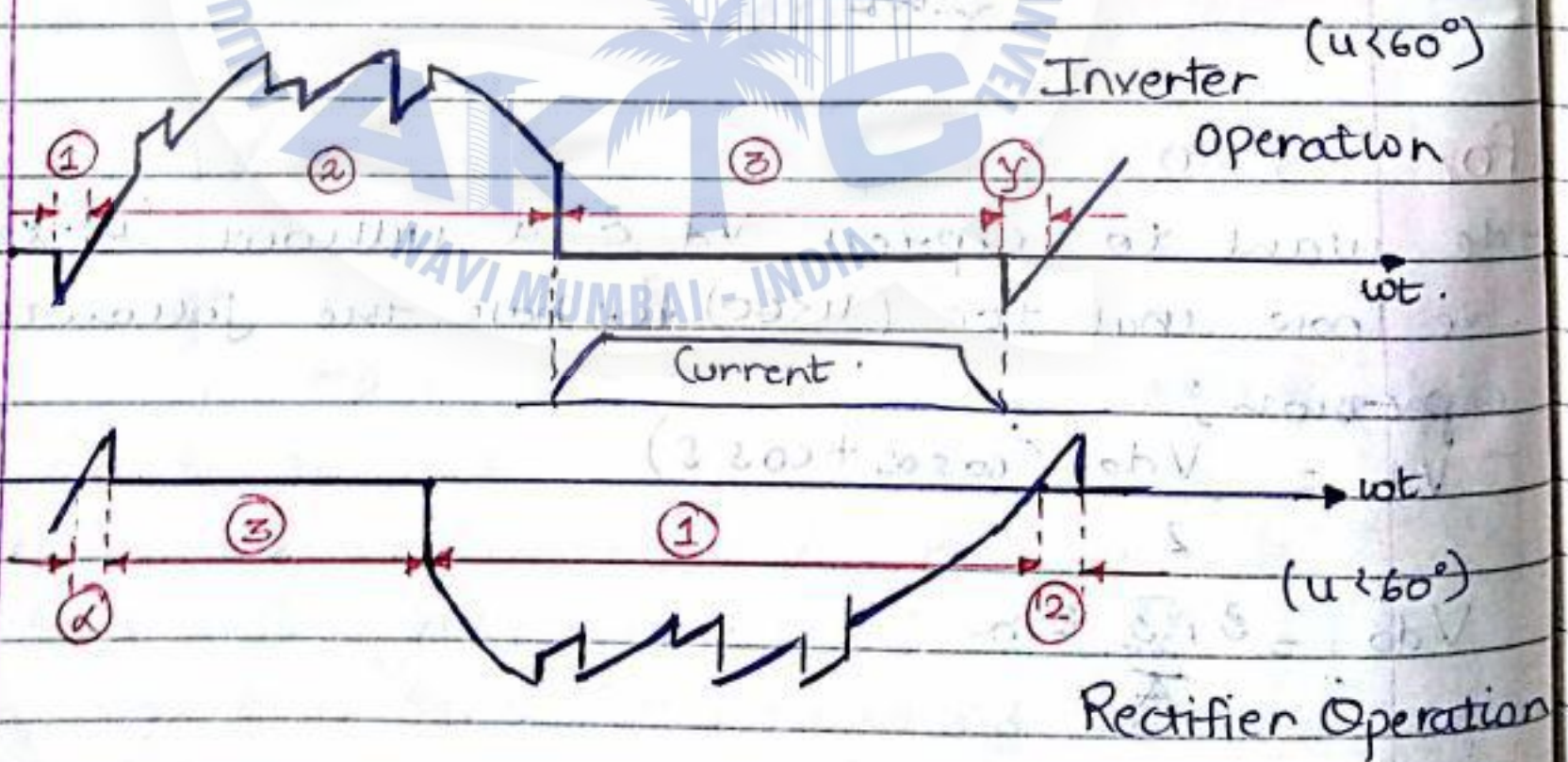* Concept of Extinction Angle & Commutation margin angle



• Valve Voltages

Page No.

Date: / /

- Extinction Advance ^(μ) angle is the time angle between the end of conduction & the reversal of sign of sinusoidal ^{commutation} voltage of the source.


- Commutation Margin ^{(ζ) Zeta} angle is the time angle between the end of conduction & the reversal of the sign of non-sinusoidal voltage across outgoing valve.

- The inverter is very much prone to commutation failure. In rectifier, most of the time the valve voltage is $-V_e$. If there is any spurious signal appearing at the gate of thyristor it can't conduct. The positive portion of wave is very small.

The reverse happens in inverter operation. Most of the time valve voltage is positive. So due to improper commutation, the valve which is conducting will continue to conduct. This is the commutation failure.

For eg; commutation between 1 & 3 is taking place. Current in 1 is \downarrow and in 3 is \uparrow but due to reversal of voltage across 3, the current begins to flow back to 1 & so the commutation may not occur.

(1)

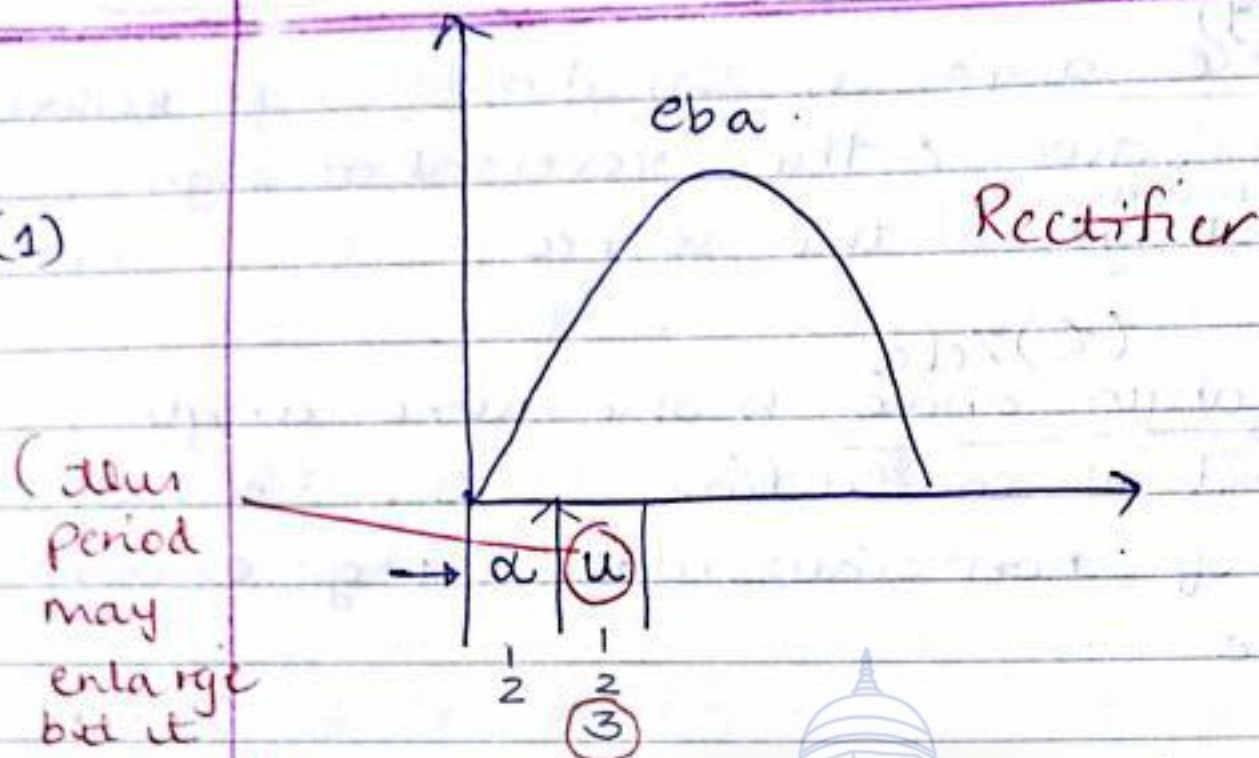


(This period may enlarge but it comes under

Commutation Voltage of valve 3.

eba wave & doesn't go beyond)

- If valve '3' is fired at lower value of ' α ' as shown above it has enough time to turn off since ' u ' period can be more.

(2)

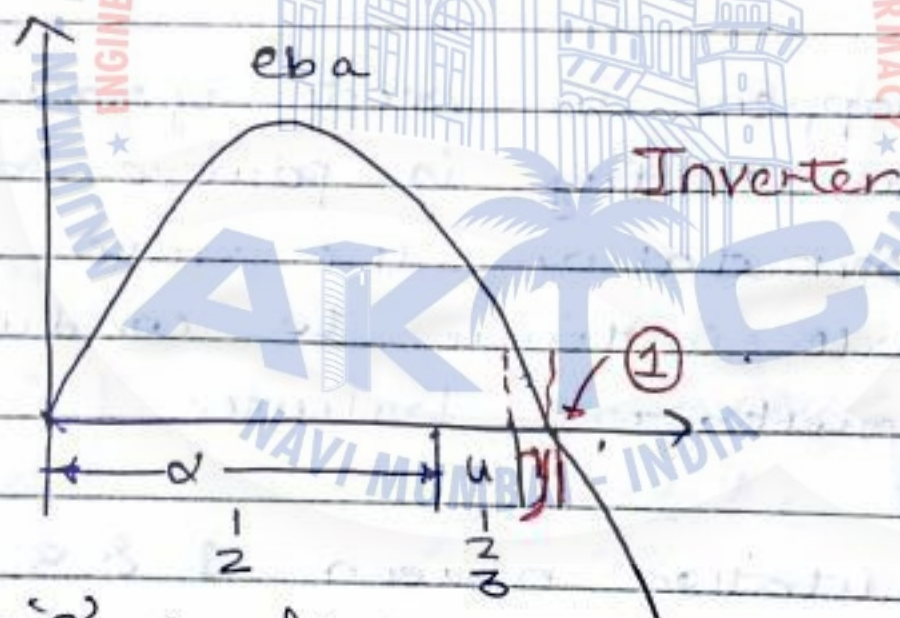

- If valve '3' is fired at higher value of ' α ' ' u ' period may extend beyond point (1) where voltage gets reversed & current flow between the commutating valves is reversed & results in commutation failure.
- Thus the angle ' γ ' is to be maintained constant.