

Con. 3638-12.

GN-7409

(3 Hours)

[Total Marks : 100]

N.B. : (1) Question No. 1 is **compulsory**.(2) Solve any **four** questions out of the remaining from Question Nos. 2 to 7.

1. (a) Prove that  $\int_0^{\infty} e^{-t} \frac{\sin^2 t}{t} dt = \frac{1}{4} \log 5$ . 20

(b) Is the matrix orthogonal? If not then can it be converted to an orthogonal matrix :-

$$A = \begin{bmatrix} -8 & 1 & 4 \\ 4 & 4 & 7 \\ 1 & -8 & 4 \end{bmatrix}$$

(c) Obtain the complex form of Fourier series for  $f(x) = e^{ax}$  in  $(-l, l)$ (d) Find the z-transform of  $f(k) = a^k, k \geq 0$ .

2. (a) Find the Fourier sine transform of  $f(x)$  if  $f(x) = \sin kx, 0 \leq x < a$  6  
 $= 0, x > a$

(b) Find the Matrix A if— 6

$$\begin{bmatrix} 2 & 1 \\ 3 & 2 \end{bmatrix} A \begin{bmatrix} -3 & 2 \\ 5 & -3 \end{bmatrix} = \begin{bmatrix} -2 & 4 \\ 3 & -1 \end{bmatrix}$$

(c)  $(D^2 - 3D + 2)y = 4e^{2t}$ , with  $y(0) = -3, y'(0) = 5$  solve using Laplace transform. 8

3. (a) Reduce the matrix to normal form and find its rank :— 6

$$\begin{bmatrix} 2 & 3 & -1 & -1 \\ 1 & -1 & -2 & -4 \\ 3 & 1 & 3 & -2 \\ 6 & 3 & 0 & -7 \end{bmatrix}$$

(b) Find the inverse Laplace transform of— 6

(i)  $\frac{e^{-2s}}{s^2 + 8s + 25}$

(ii)  $\frac{e^{-3s}}{(s+4)^3}$

(c) If  $f(x) = \pi x, 0 \leq x \leq 1$   
 $= \pi(2-x), 1 \leq x \leq 2$  } with Period 2. 8  
 Find the Fourier series expansion.

4. (a) Show that the set of functions  $\sin\left(\frac{\pi x}{2l}\right), \sin\left(\frac{3\pi x}{2l}\right), \sin\left(\frac{5\pi x}{2l}\right), \dots$  is orthogonal 6  
 over  $(0, l)$ .

(b) If  $f(k) = 4^k U(k), g(k) = 5^k U(k)$ , then find the z-transform of  $f(k) + g(k)$ . 6(c) Solve the following equations by Gauss-Seidel Method. 8

$$28x + 4y - z = 32, 2x + 17y + 4z = 35,$$

$$x + 3y + 10z = 24.$$

[TURN OVER

## Con. 3638–GN-7409-12.

2

5. (a) Obtain Fourier series for—

6

$$f(x) = x + \frac{\pi}{2}, \quad -\pi < x < 0$$

$$= \frac{\pi}{2} - x, \quad 0 < x < \pi \text{ and}$$

hence deduce that,  $\frac{\pi^2}{8} = \frac{1}{1^2} + \frac{1}{3^2} + \frac{1}{5^2} + \dots$

- (b) State Convolution theorem and hence find the inverse Laplace transform of the function using the same :—

6

$$f(s) = \frac{(s+3)^2}{(s^2+6s+5)^2}$$

- (c) For what value of
- $\lambda$
- the equations
- $3x - 2y + \lambda z = 1$
- ,
- $2x + y + z = 2$
- ,
- $x + 2y - \lambda z = -1$
- will have no unique solution? Will the equations have any solution for this value of
- $\lambda$
- ?

8

6. (a) Show that every square matrix
- $A$
- can be uniquely expressed as
- $P + iQ$
- when
- $P$
- and
- $Q$
- are Hermitian matrices.

6

- (b) If
- $L(f(t)) = f(s)$
- , then prove that
- $L(t^n f(t)) = (-1)^n \frac{d^n}{ds^n} f(s)$
- , hence, find Laplace transform of
- $f(t) = t \cos^2 t$
- .

6

- (c) Obtain the half range sine series for
- $f(x)$
- when
- $f(x) = x$
- $0 < x < \frac{\pi}{2}$

8

$$= \pi - x \quad \frac{\pi}{2} < x < \pi$$

hence, find the sum of  $\sum_{2n-1}^{\infty} \frac{1}{n^4}$ .

7. (a) Find the Fourier transform of—

6

$$f(x) = (1-x^2), \quad |x| \leq 1$$

$$= 0, \quad |x| > 1, \quad \text{then } f(s) = -2 \sqrt{\frac{2}{\pi}} \left[ \frac{s \cos s - \sin s}{s^3} \right]$$

- (b) Find the inverse
- $z$
- transform of
- $F(z) = \frac{z}{(z-1)(z-2)}, |z| > 2$
- .

6

- (c) Find the non-singular matrices
- $P$
- and
- $Q$
- such that—

8

$$A = \begin{bmatrix} 1 & 2 & 3 & 2 \\ 2 & 3 & 5 & 1 \\ 1 & 3 & 4 & 5 \end{bmatrix}$$

is reduced to normal form. Also find its rank.

(3 Hours)

[Total Marks : 100

- N. B. :** (1) Question No. 1 is compulsory.  
 (2) Attempt any **four** questions from **remaining** questions.  
 (3) **All** questions carry **equal** marks.

1. (a) Calculate  $(-6)_{10} - (-2)_{10}$  using 2's complement method. 5  
 (b) What is difference between combinational circuits and sequential circuits ? 5  
 (c) Explain in brief 'state tables' and 'state graphs'. 5  
 (d) What are salient features of CMOS logic family ? 5
2. (a) Design a mod 6 ripple counter using T type flip-flop. Draw the circuit designed and output waveforms. 12  
 (b) What is FPGA ? What are its salient features ? 8
3. (a) Design a full adder using 2 half adders. Explain its working. 10  
 (b) Minimize  $y = \sum m (1, 5, 7, 9, 11, 13, 15)$  and realise using universal gates. 10
4. (a) Minimize the following function using Quine McCluskey method : 12  
 $f(A, B, C, D) = \pi m (2, 7, 8, 9, 10, 12)$   
 (b) Design a full adder using two 4:1 mux. 8
5. (a) Convert  $(0.42)_{10}$  into binary. 4  
 (b) Solve  $111110.1 \div 0101$ . 4  
 (c) Convert  $(11011)_2$  into gray code. 4  
 (d) List various characteristics of digital ICs and explain their significance in brief. 8
6. (a) Design a 4 bit universal shift register and explain its working. 12  
 (b) Implement the following boolean expression using 8:1 mux 8  
 $f(A, B, C, D) = \bar{A}\bar{B}\bar{D} + ABC + \bar{B}CD + \bar{A}CD$ .
7. (a) Design a 3 bit up/down ripple counter. 10  
 (b) What is half subtractor ? Explain its working. 10

Con. 3753-12.


(3 Hours)

GN-5354

[Total Marks : 100


- N.B. : (1) Question Nos. 1 and 2 are compulsory.  
 (2) Out of remaining questions attempt any three questions.  
 (3) In all five questions to be attempted.  
 (4) Figures to the right indicate full marks.

1. a. Design single stage R-C coupled CE audio frequency amplifier employing BC147B BJT to satisfy the following requirements. [15]  
 $|A_v| \geq 100$ ,  $S_{IC0} \leq 10$ , Load resistor  $R_L = 10K\Omega$  and Output voltage  $V_o = 3$ volts.
- b. For the designed amplifier in part (a) determine; expected voltage gain, input impedance, output impedance and current supplied by source voltage  $V_{CC}$  {Use complete h-model for part (a) and (b)} [05]
2. a. Design single stage R-C coupled CS audio frequency amplifier employing JFET BFW-11 to satisfy the following requirements. [12]  
 $|A_v| \geq 10$ ,  $V_{CSQ} = 0.3V_p$ ,  $R_L = 120 K\Omega$ ,  $V_{DD} = 20$  volts and Output peak voltage  $V_o = 4.5$ volts.
- b. For the above designed circuit with source resistor 'Rs' unbypassed determine; voltage gain, input impedance, output impedance and output voltage for input voltage of  $20V_{pp}$ . [08]
3. a. For the circuit shown in Fig A. determine the following :
  - i. Voltage at collector terminal VC [02]
  - ii. Voltage at base terminal VB [02]
  - iii. Stability  $S_{IC0}$  [02]
  - iv. Voltage gain [04]

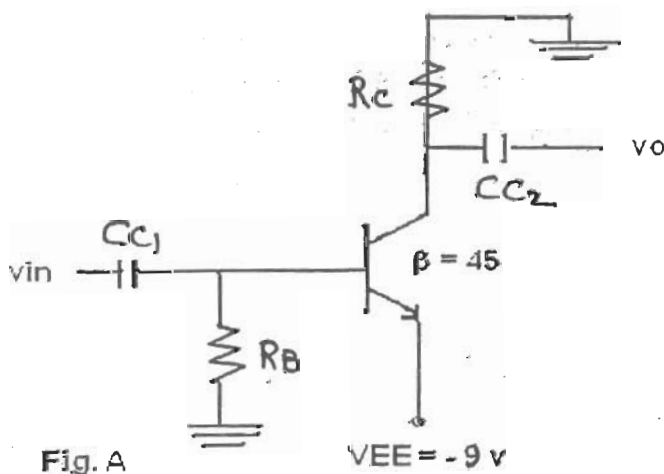

b. For the network of Fig B. with  $R_D = 2k\Omega$ ,  $R_S = 0.68k\Omega$  and  $V_{DD} = 20\text{volts}$  determine the following :

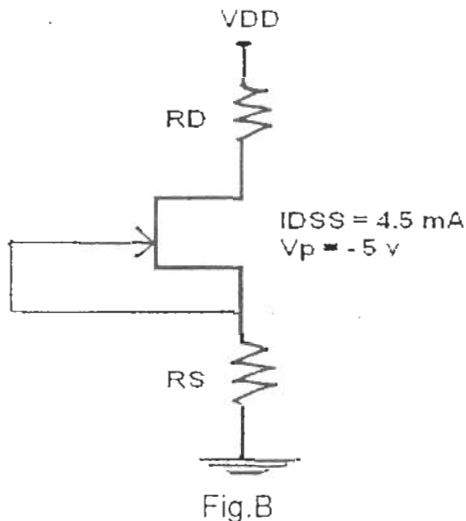- i.  $I_{DQ}$  and  $V_{GSQ}$  [03]
- ii.  $V_{DSQ}$  and  $V_D$  [03]
- iii.  $V_G$  and  $V_S$  [02]
- iv.  $I_{DQ}$  if  $R_S$  is bypassed by capacitor  $C_S$  [02]



4. Compare the following (Any four) [5x4]
- i. Output characteristic of common emitter (CE) and common source (CS) amplifier
  - ii. BJT series and BJT shunt voltage regulator
  - iii. D-MOSFET and E-MOSFET
  - iv. SCR and TRIAC
  - v. LC and C-L-C filter


5. a. Design a full wave rectifier dc supply using centre tapped transformer with two diodes to give dc output voltage at 300 volts to a variable resistive load. The load current expected is  $75 \pm 25 \text{ mA}$  with ripple factor not to exceed 0.07. Use C-L-C filter. [12]

- b. For the network of Fig C with  $R_D=2K\Omega$ ,  $R_G=10M\Omega$ , and  $V_{DD}=12\text{volts}$ . Determine the following :

- i.  $I_{DQ}$
- ii.  $V_{DSQ}$

[04]

[04]

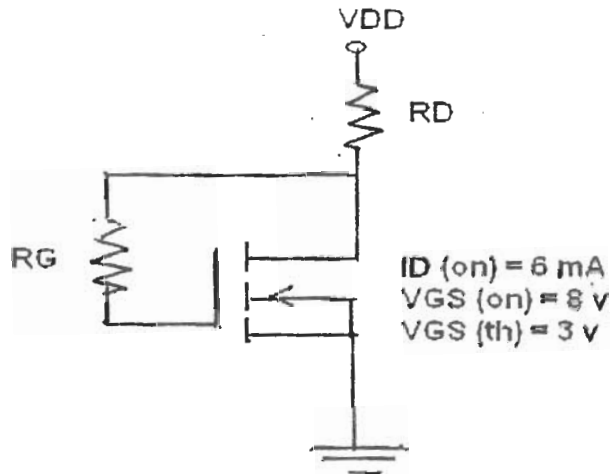

6. a. Describe the operation of BJT series regulator and derive an expression for line regulation ( $S_v$ ) and load regulation ( $R_o$ )

[12]

- b. Explain with the help of a circuit diagram the working of a UJT relaxation oscillator.

[08]

7. Explain the following (Any four)

[5x4]

- i. Self thermal stability of JFET
- ii. Utility of h-parameter
- iii. Graphical determination of FET parameters
- iv. Features of IGBT
- v. BJT as a switch
- vi. Power MOSFET

DBEC DATA SHEET

Transistor type	P <sub>dmax</sub> @ 25°C Watts	I <sub>cmax</sub> @ 25°C Amps	V <sub>ce(sat)</sub> volts d.c.	V <sub>ce(sat)</sub> volts d.c.	V <sub>ce(sat)</sub> volts d.c.	V <sub>ce(sat)</sub> volts d.c.	V <sub>ce(sat)</sub> volts d.c.	V <sub>be(sat)</sub> volts d.c.	D.C. current gain		Signal typ.	h <sub>FE</sub> max.	V <sub>BE</sub> max.	θ <sub>JA</sub> °C/W	Derate above 25°C W/°C
									min	max.					
2N3055	115.5	15.0	1-1	100	60	70	98	7	200	20	50	120	1.8	1.5	0.7
ECN055	50.0	5.0	1-0	60	50	55	60	5	200	25	75	125	1.5	3.5	0.4
ECN149	30.0	4.0	1-0	50	40	—	—	8	150	30	31	60	1.2	4.0	0.3
ECN100	5.0	0.7	0-6	70	60	65	—	6	200	50	90	280	0.9	35	—
BC147A	0.25	0.1	0-25	50	45	50	—	6	125	115	125	220	0.9	—	—
2N525(PNP)	0.225	0.5	0-25	85	30	—	—	—	100	35	—	45	—	—	—
BC147B	0.25	0.1	0-25	50	45	50	—	6	125	200	290	450	0.9	—	—

BFV 11—JFET MUTUAL CHARACTERISTICS

Transistor type	k <sub>is</sub>	h <sub>oe</sub>	h <sub>re</sub>	o <sub>ja</sub>
BC 147A	2.7 K Ω	18μ Ω	1.5 × 10 <sup>-4</sup>	0.4°C/mw
2N 525 (PNP)	1.4 K Ω	25μ Ω	3.2 × 10 <sup>-4</sup>	—
BC 147B	4.5 K Ω	30μ Ω	2 × 10 <sup>-4</sup>	0.4°C/mw

-V <sub>GS</sub> volts	I <sub>D</sub> max. mA	I <sub>D</sub> typ. mA	I <sub>D</sub> min. mA	I <sub>DSS</sub> max. mA	I <sub>DSS</sub> min. mA	I <sub>DSS</sub> typ. mA	r <sub>ds</sub> min. Ω	r <sub>ds</sub> max. Ω	r <sub>ds</sub> typ. Ω	-V <sub>P</sub> Volts	r <sub>ds</sub> max. Ω	Derate above 25°C	θ <sub>JA</sub>
0-0	0-2	0-4	0-6	0-8	1-0	1-2	1-6	2-0	2-4	2-5	3-0	3-5	4-0
10	9-0	8-3	7-6	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
7-0	6-0	5-4	4-6	4-0	3-3	2-7	1-7	0-8	0-2	0-0	0-0	0-0	0-0
4-0	3-0	2-2	1-6	1-0	0-5	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0

N-Channel JFET

Type	V <sub>GS</sub> max. Volts	V <sub>DS</sub> max. Volts	V <sub>GS</sub> max. Volts	P <sub>D</sub> max. @25°C	I <sub>D</sub> max. mA	I <sub>D</sub> typ. mA	I <sub>D</sub> min. mA	r <sub>ds</sub> min. Ω	r <sub>ds</sub> max. Ω	r <sub>ds</sub> typ. Ω	-V <sub>P</sub> Volts	r <sub>ds</sub> max. Ω	Derate above 25°C	θ <sub>JA</sub>
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μΩ	6	50 KΩ	2 mW/°C	0.59°C/mW	0.59°C/mW	—	—
BFV 11 (typical)	30	30	30	300 mW	200°C	7 mA	5000 μΩ	2.5	50 KΩ	—	—	—	—	—

UJT type	P <sub>D</sub> max. @25°C	I <sub>B</sub> max. @25°C	I <sub>P</sub> peak pulse current	V <sub>BE</sub> Volts max.	V <sub>BE(sat)</sub> Volts	T <sub>J</sub> max	η min.	η max.	R <sub>BB</sub> KΩ min.	R <sub>BB</sub> KΩ typ.	Max.	I <sub>P</sub> μA max.	I <sub>V</sub> min. mA	I <sub>EO</sub> μA
2N2646	300mW	50mA	2Amp.	30	35	125°C	0.56	0.75	4.7	7.0	9.1	5.0	4.0	-2.0

Con. 4474-12.

(3 Hours)

[ Total Marks : 100

**N.B. :** (1) Question No. 1 is **compulsory**.

(2) Attempt any **four** questions from the remaining **six** questions.

1. Attempt any **four** questions :- 20
  - (a) Why delay line is used in the vertical section of the oscilloscope?
  - (b) What is universal counter?
  - (c) Explain capacitive sensors.
  - (d) Explain various sources of error in measurement system.
  - (e) Explain the significance of  $3\frac{1}{2}$  and  $4\frac{1}{2}$  digit displays.
2. (a) Explain the elements of a digital FFT analyzer with a suitable block diagram. 10
  - (b) What is the basic principle of ADC ? Explain the operation of successive approximation type of ADC. 10
3. (a) Explain the principle of working of LVDT. How do stray magnetic fields effect the performance and how it can be protected? 10
  - (b) Draw and explain the block diagram of a general purpose CRO. 10
4. (a) Derive an expression for vertical deflection of electron beam in CRT. 10

What is the minimum distance that will allow full deflection of 4cm at oscilloscope screen with deflection factor of 100V/cm and with accelerating potential of 2k.


  - (b) Explain PAM telemetry system. 10
5. (a) With a block diagram explain the elements of Network analyzer with its applications.
  - (b) Draw and explain the block diagram of DSO. Describe the various modes of operation.
6. (a) Explain the need of data transmission and telemetry. What are the different modulation methods used in RF telemetry systems?
  - (b) Write a note on Automatic test equipment. A coil with resistance of  $5\Omega$  is directly connected to test terminals of Q-meter, for a 130 PF capacitance of a tuning capacitor, resonance is obtained at oscillator frequency of 1MHz. Calculate % error introduced in calculated value of Q by  $0.01\Omega$  insertion resistance.
7. (a) Draw and explain true RMS voltmeter with thermocouple. Why there is error in reading a voltmeter calibrated to read RMS values when it is used to read signals other than sine wave.
  - (b) Explain briefly the different pulse modulation techniques. 10



- N.B. :** (1) Question No. 1 is compulsory and solve any four from remaining questions 2 to 7.  
 (2) In all five questions to be attempted.  
 (3) Figures to the right indicate full marks.  
 (4) Assume suitable data if any.


1. (a) How many trees are possible for the graph given below :-

5

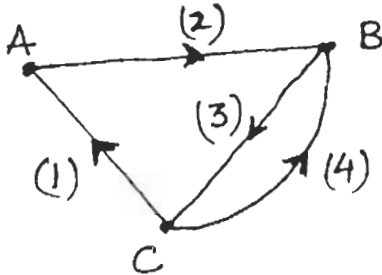

(b) By mesh analysis determine the current through  $2\ \Omega$  resistor.


5

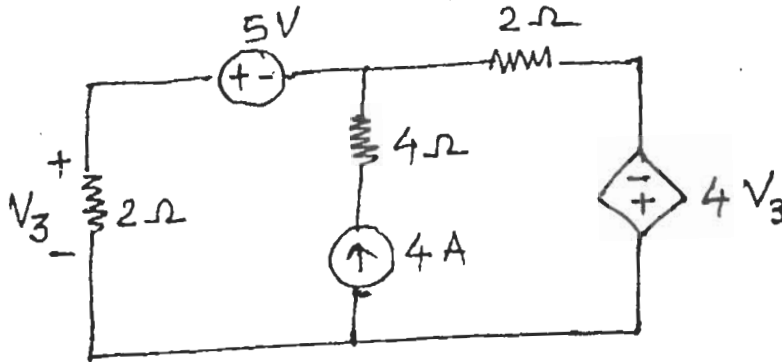

(c) Find the condition of reciprocity for Z-Parameters.


5

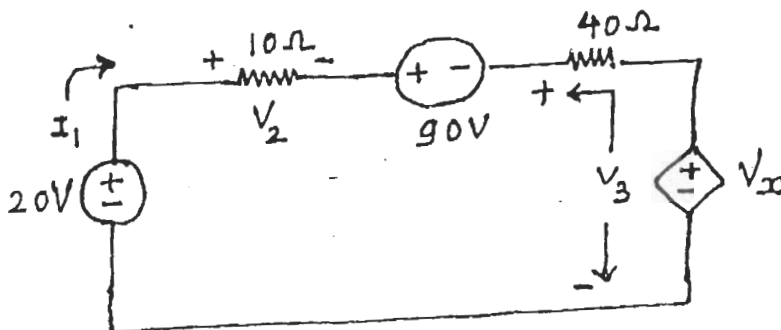(d) Find  $I_1$  in the circuit shown in the Figure if the dependent voltage source is  
 (i)  $2V_2$       (ii)  $1.5V_3$ .




2. (a) Find the current through  $5\Omega$  resistor.

10

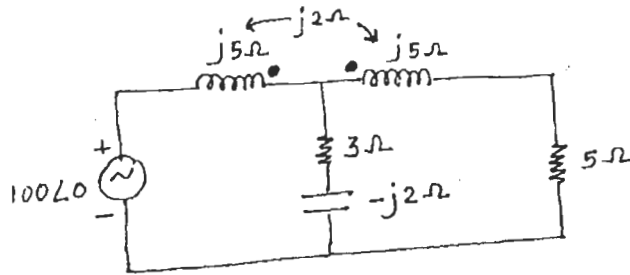

(b) Find the network functions  $\frac{V_1}{I_1}$ ,  $\frac{V_2}{I_1}$  and  $\frac{V_2}{I_2}$  for the network shown.


10

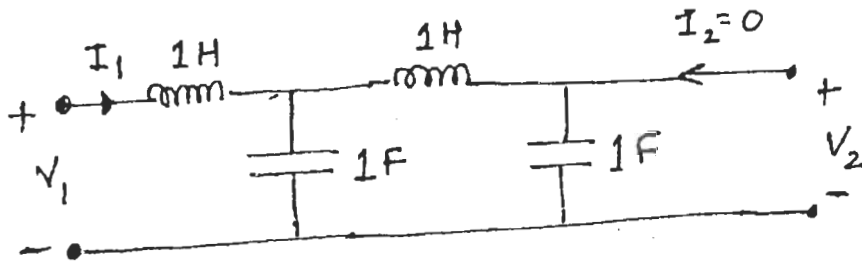

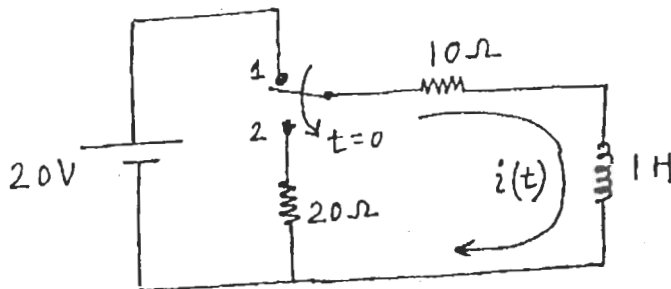3. (a) In the network, the switch is changed from position 1 to the position 2 at  $t=0$ , steady condition having reached before switching. Find the values of


10

$i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ .




(b) In the network, the switch is opened at  $t = 0$ . Find  $i(t)$ .


10

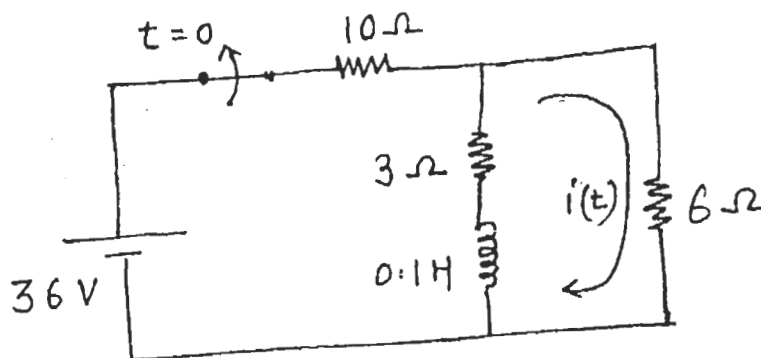

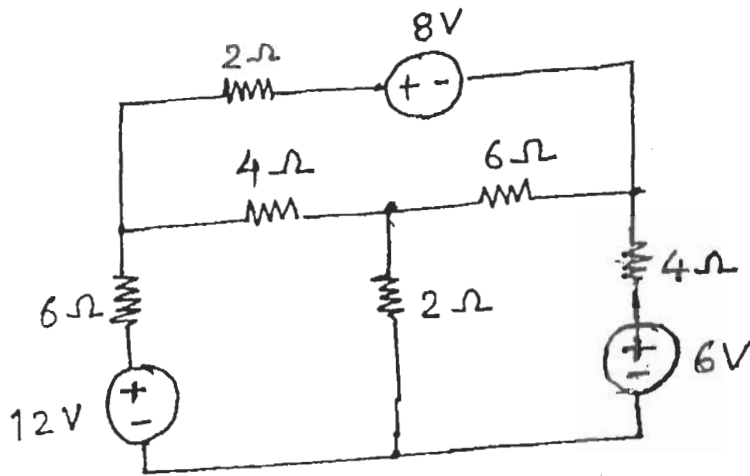4. (a) For the network, write down the tieset matrix and obtain the network equilibrium equation in Matrix form using KVL. Calculate loop currents. 10



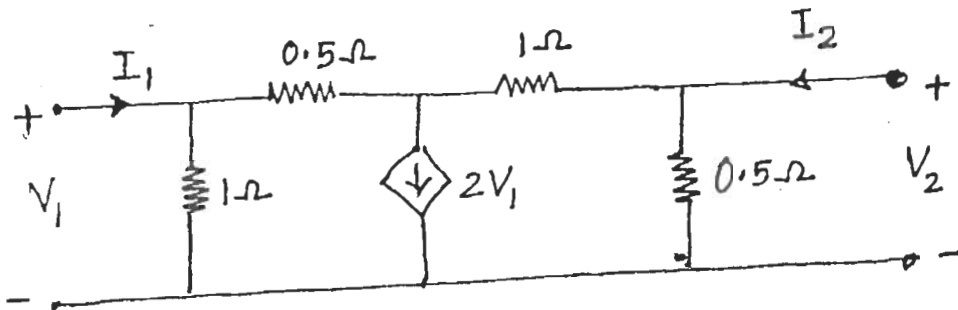- (b) Determine the Y and Z-parameters for the given network. 10



5. (a) Synthesize the following function :- 8

$$Z(s) = \frac{6(s+2)(s+4)}{s(s+3)}$$

Use Foster-II Method.

- (b) A driving point R-L admittance function is given by- 6


$$Y_{RL}(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

Realize the given function as R-L form using Cauer -I

- (c) Synthesize the following  $Y_{RL}(s)$  using Cauer-II term- 6

$$Y_{RL}(s) = \frac{(s+1)(s+4)}{s(3s+4)}$$

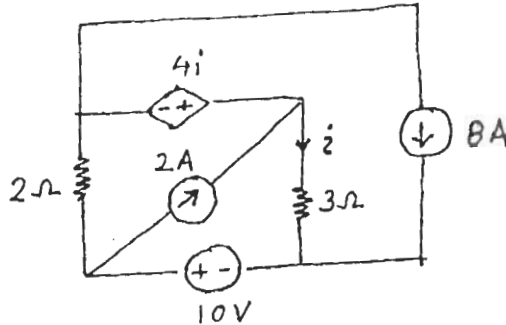
6. (a) Find the current  $i$  in the network shown in **figure**, using superposition theorem. 10



- (b) (i) Check the given polynomial for Hurwitz or not—  
 $P(s) = s^5 + 8s^4 + 24s^3 + 28s^2 + 23s + 6$  10

- (ii) Test whether  $F(s) = \frac{5(s+1)^2}{s^3+2s^2+2s+40}$  is positive real function.

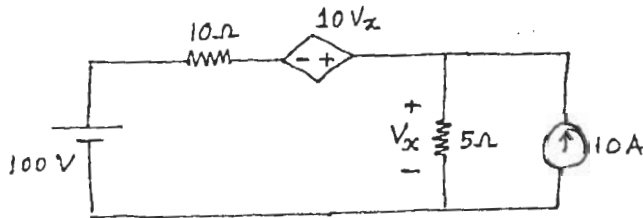7. (a) Find the current in  $10\Omega$  resistor of the network, using Thevenin's theorem. 10



- (b) Determine the hybrid parameter of the network. 10

