


(3 Hours)

[Total Marks : 100]

- N.B. :** (1) Question No. 1 is **compulsory**.
 (2) Solve any **four** out of remaining **six** questions.
 (3) **Figures to the right** indicate **full marks**.
 (4) Assume suitable data if **necessary**.


1. (a) Solve any
- four**
- :-

20

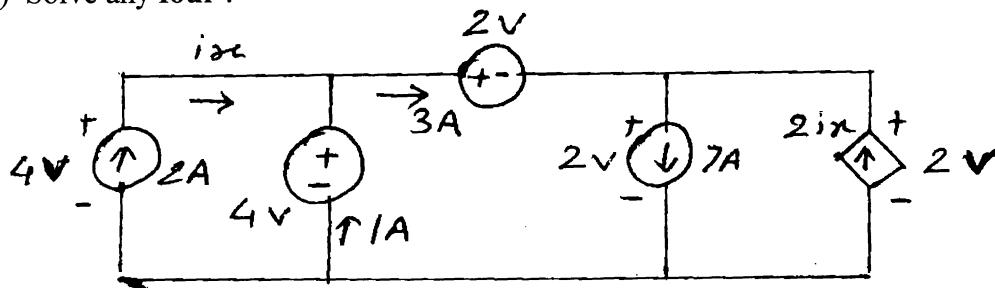


Show that the algebraic sum of the five absorbed power values in **figure** is zero.

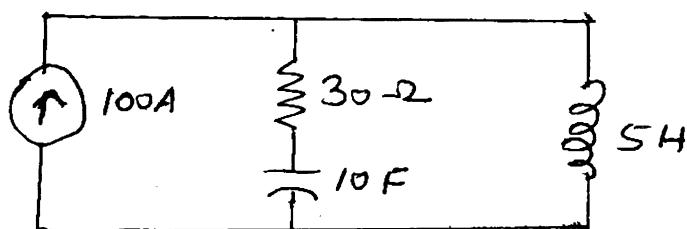
- (b) Draw the dual circuit of
- figure**
- shown below :-



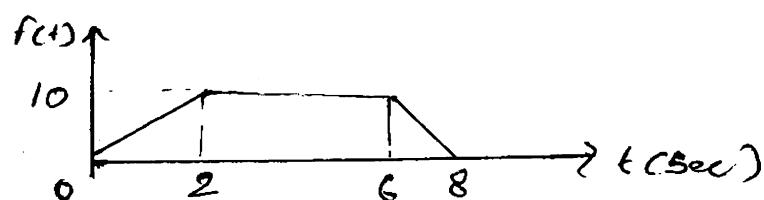- (c) Use step function to write the expression for the following function :-



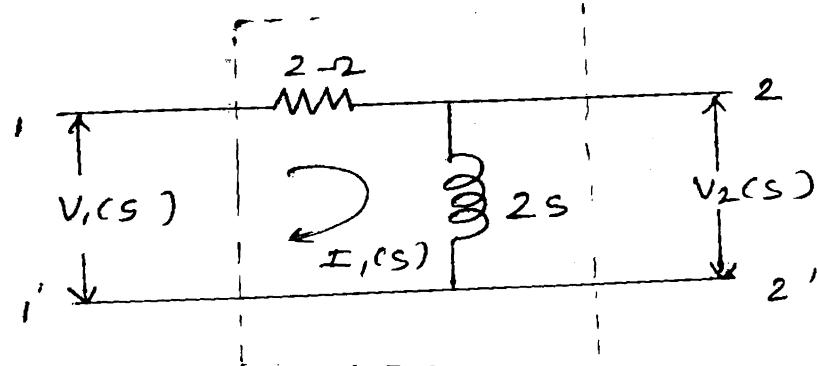
- (d) For the network shown in
- figure**
- obtain the transfer function
- G_{21}
- and
- Z_{21}
- and the driving point impedance
- $Z_{11}(s)$
- .



[TURN OVER]

Con. 6506-LJ-10415-13.

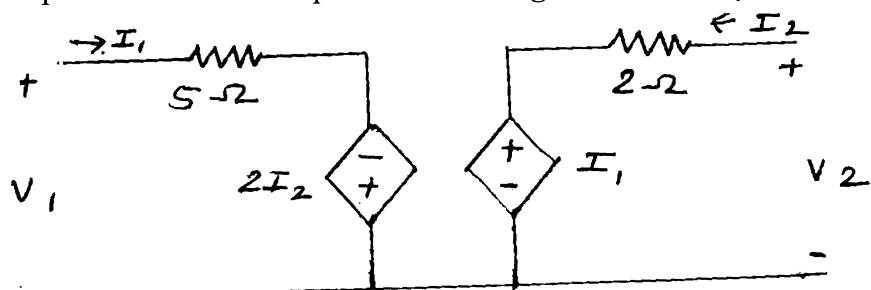
- (e) Find the z parameters of the two part Network in figure.



- (f) Define properties of positive real function.


2. (a) Use mesh analysis to find
- V_x
- in the circuit shown in figure.

10

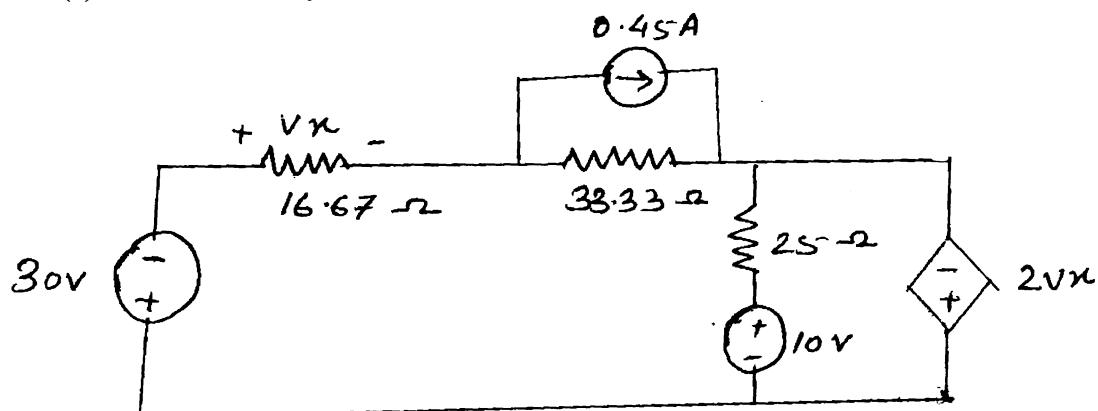


- (b) Define statement of Millman's theorem also calculate current I shown in figure using Millman's

10

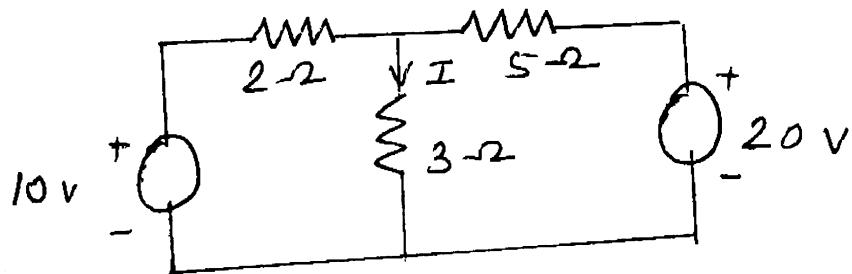

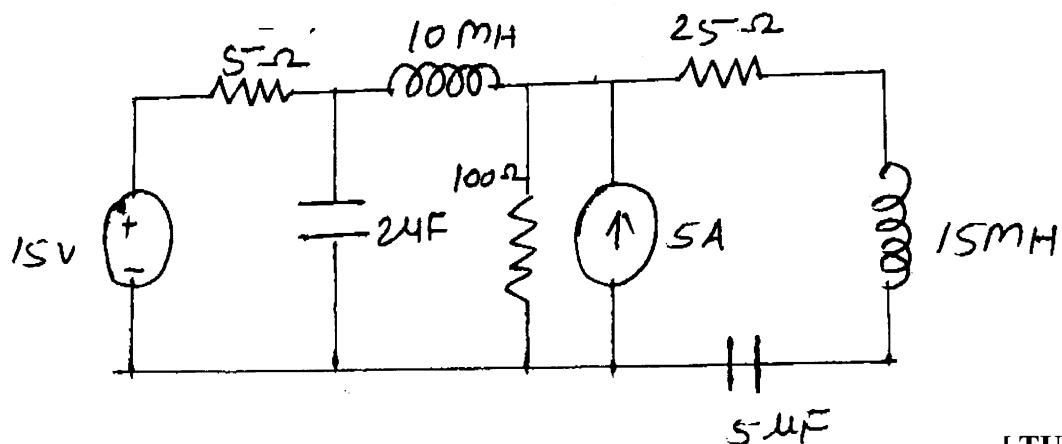
3. (a) For the electrical network shown in figure draw the topological graph and write its incidence Matrix, He-set Matrix, Link current transformation equation and branch currents.





[TURN OVER

(b) For the circuit shown in **figure** determine the load current I_L by using Norton's theorem.


10

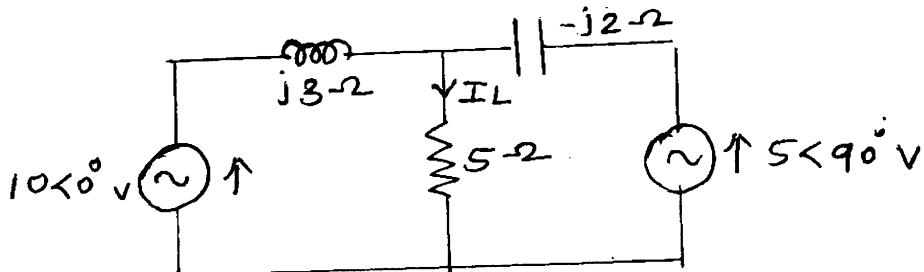4. (a) Find the voltage across the 10Ω resistor for the network shown in **figure**.

10

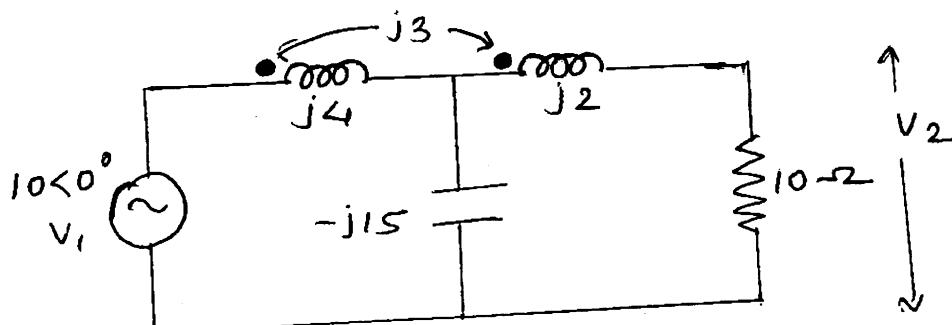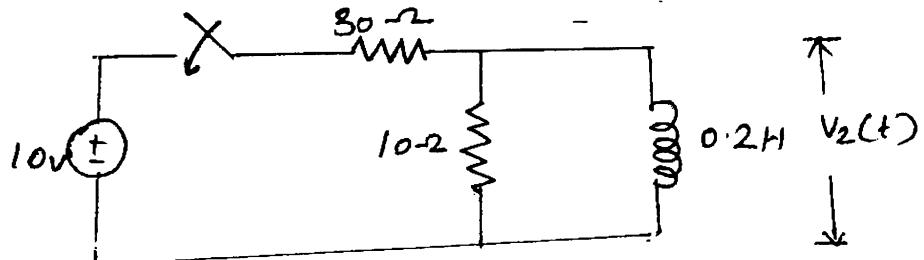(b) The switch in the circuit shown in **figure** is closed at $t=0$. Find $V_2(t)$ for all $t \geq 0$ by time domain method. Assume zero initial current in the inductance.5. (a) In the two-mesh network of **figure** the current which result when the switch is closed.

10

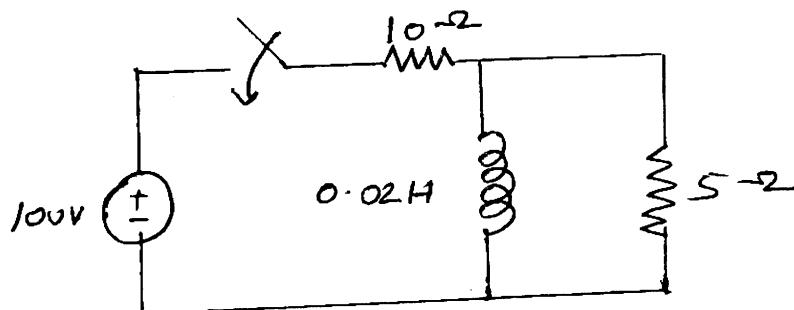(b) For the given network function draw the pole zero diagram and hence obtain the time domain response $i(f)$


$$I(s) = \frac{5s}{(s+1)(s^2 + 4s + 8)}$$

[TURN OVER

Con. 6506-LJ-10415-13.

6. (a) Determine Z and Y parameters for the circuit shown in **figure**.

10

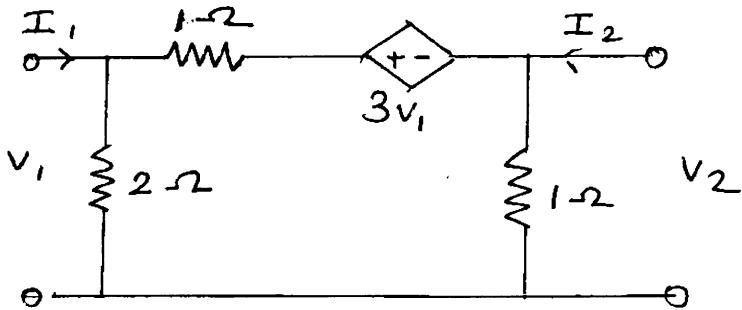

- (b) Test ff the following polynomial for Hurwitz property—

10

- (i) $F(s) = s^5 + s^4 - 6s^3 + 4s^2 + 8s + 3$
- (ii) $F(s) = s^4 + s^3 + 2s^2 + 4s + 1$

7. (a) The driving point impedance of an LC network is given by $z(s) = \frac{s^4 + 4s^2 + 3}{(s^3 + 2s)}$.

10

Determine the second Cauer form of the network.

- (b) Find the first Foster form of the network.

10

$$z(s) = \frac{2s^3 + 8s}{s^2 + 1}$$
