

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question No. 1 is **compulsory**.
 (2) Answer any **three** from remaining **five** questions.
 (3) **Figures** to the **right** indicate **full** marks.
 (4) Assume the **data** if it is **necessary**.

- Q.1** Answer any four from the following [20]
 a) Explain thermal runaway and stabilization
 b) Barkhausen criterion for sustained oscillation
 c) Zener diode as a voltage regulator
 d) Explain criterion for the selection of emitter by pass capacitor in an CE amplifier.
 e) FET as differential amplifier
- Q.2** a) Explain how the amplification factor, input impedance, output impedance and bandwidth are modified with negative feedback [10]
 b) Explain the operation of C type filter in full wave rectifier with all necessary diagrams and waveforms. [10]
- Q.3** a) Explain UJT as a relaxation oscillator in detail. Find frequency of oscillator [10]
 b) What is MOSFET? Explain the construction and characteristics of N – channel MOSFET with the help of suitable diagram. [10]
- Q.4** a) Derive the expression for voltage gain, current gain, input impedance and output impedance of CB amplifier. [10]
 b) Explain the AC Analysis of Dual Input Unbalance Output Differential Amplifier. [10]
- Q.5** a) Explain the working of CS FET amplifier. [10]
 b) Derive the equation for frequency of oscillation of Colpitts oscillator. Also derive the condition for sustained oscillation. [10]
- Q.6** a) What is Darlington pair? What are its features? How to bias the pair? Derive expression for its ac parameters. [10]
 b) Explain the differences between LC and RC oscillators. Give examples of each of oscillators with frequencies. [10]
-