

(3 Hours)

[Total Marks : 100

- N.B. :** (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions from **remaining** questions.
 (3) **Figures** to the **right** indicate **full** marks.
 (4) Use **suitable** data.

1. Solve the following :-
 - (a) Derive the dimension of the following quantities on L, M, T, I system :- **10**
 - (i) Magnetic flux
 - (ii) Resistance
 - (iii) Capacitance
 - (iv) Electric flux
 - (v) mmf.
 - (b) Explain with neat circuit diagram the applications of dc potentiometer. **10**
2. (a) A 4 – dial decade box has :- **10**
 - decade a of $10 \times 1000 \text{ W} \pm 0.1 \%$
 - decade b of $10 \times 100 \text{ W} \pm 0.1 \%$
 - decade c of $10 \times 10 \Omega \pm 0.5 \%$
 - decade d of $10 \times 1 \text{ Ohm}(\Omega) \pm 1.0 \%$

It is set at 4639Ω (ohm). Find the percentage limiting error and the range of resistance value.
- (b) Draw the circuit diagram of a Crompton's potentiometer and explain its working. **10**
 Describe the steps used when measuring an unknown resistance ?
3. (a) Describe construction and working of a ballistic galvanometer. Explain the difference in constructional details of a d' Arsonval galvanometer ? **12**
- (b) Derive the equations of balance for an Anderson's bridge. Draw the phasor diagram for conditions under balance ? **8**
4. (a) Describe the working of a low voltage Schering bridge. Derive the equations for capacitance and dissipation factor. Draw the phasor diagram also. **10**
- (b) Explain diamagnetism, paramagnetism and ferromagnetism in connection with magnetic measurements. **10**
5. (a) Explain the construction and working of single phase Induction type energy meter ? **10**
- (b) Describe the working and construction detail of an attraction type moving iron instrument. Discuss its advantage and dis-advantages. **10**

[TURN OVER

6. (a) Explain CT for measurement of current and power. Also define ratio and phase angle error for C.T ? **10**
- (b) A moving coil ammeter has a fixed shunt of 0.02 ohms. With a coil resistance of $R = 1000 \Omega$ (ohms) and a potential difference of 500 mV across it, full scale deflection is obtained. **10**
- (i) To what shunted current does this correspond ?
- (ii) Calculate the value of 'R' to give full scale deflection when shunted current I is (i) 10 Amp, (ii) 75 Amp.
- (c) With what value of R is 40% deflection obtained with $I = 100$ Amps. **10**
7. Write short notes on any **three** :- **20**
- (a) Power factormeter
- (b) PMMC Instrument
- (c) A.C. Vibration galvanometer
- (d) Maxwell's Inductance Bridge.
