
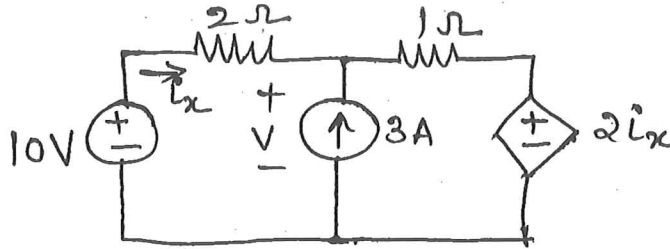


- N.B.** (1) Question No. 1 is **compulsory**.
 (2) Answer any **four** questions from **remaining** questions.
 (3) **Figures to the right** indicate **full** marks.

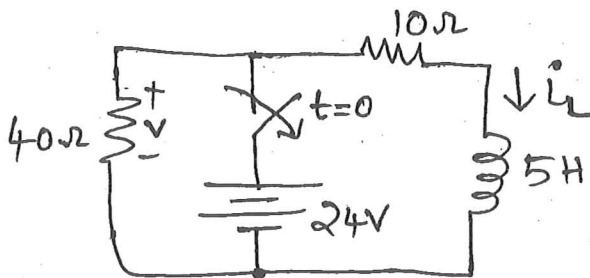1. (a) Use superposition principle to determine the value of i_x . 5




(b) Find $i_L(0^+)$ and $V(0^+)$ in the circuit shown 5




(c) Explain duality with suitable examples. 5

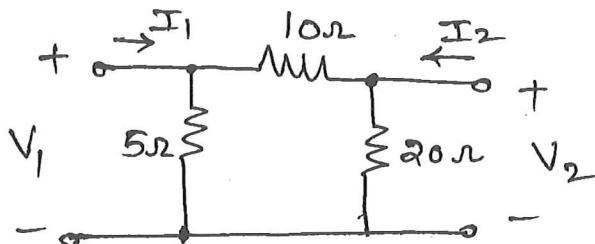(d) Find admittance parameters for the two port network shown. 5



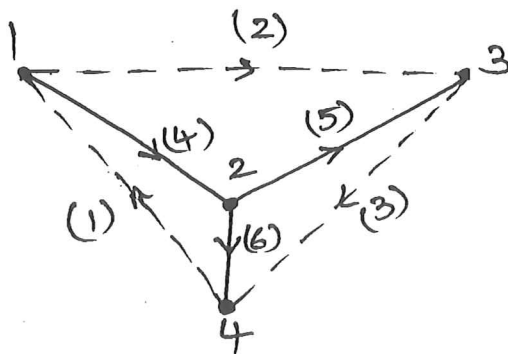2. (a) Find f-cutset and f-tieset matrices. 10




(b) Find the laplace transform of shifted step, ramp and impulse functions. 6

(c) Write any four restrictions on pole zero locations of driving point functions. 4


3. (a) After being in the configuration shown for hours, the switch in the circuit is closed at $t = 0$. At $t = 5 \mu s$, calculate

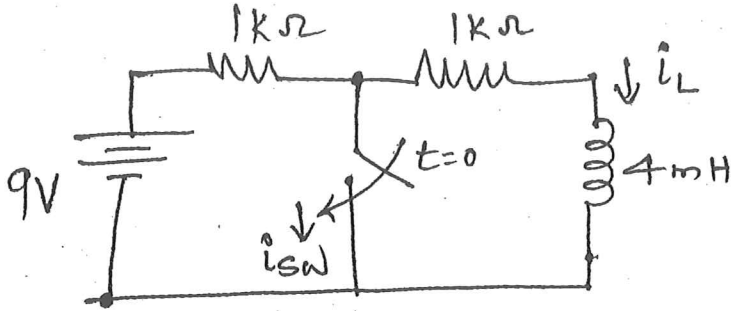- (i) i_L and.
 (ii) Prove that $i_{sw} = 7.71 \text{ mA}$ at $5 \mu s$.



- (b) Compute z parameters for the circuit shown and show that $z_{11} = z_{21}$

10

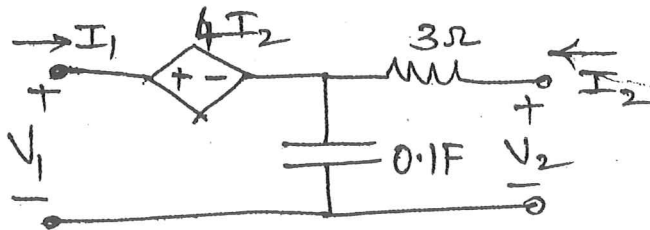


4. Find Foster I and II and Cauer I and II for the following impedance function—

20


$$z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

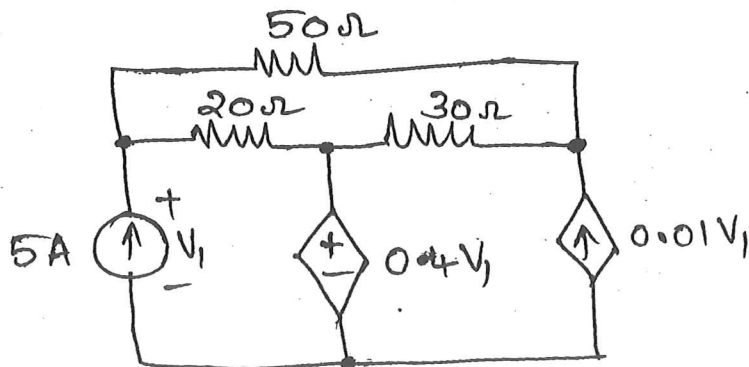5. (a) Write the procedure for testing a positive real function .
 (b) Use nodal analysis to determine V_1 and the power being supplied by the dependent current source in the circuit shown.



6. (a) Find the Thevenin equivalent of the network shown. What power would be delivered to a load of 100Ω at a and b ?

10

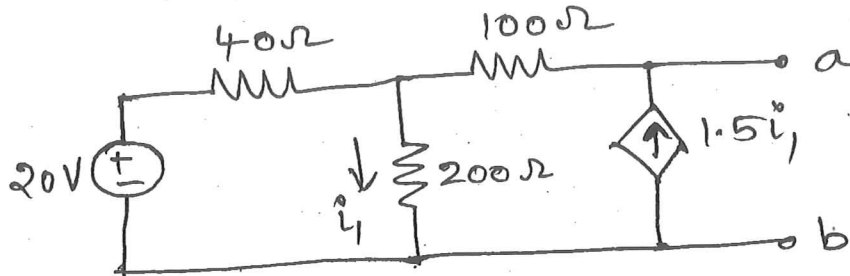

- (b) Write short notes on initial conditions and its significance.

10

7. Write short notes on any two :-

- (a) Network equilibrium equation
- (b) Waveform synthesis
- (c) Hybrid parameters
- (d) Properties of RC and RL functions.

20
