

(3 Hours)

[Total Marks : 100]


- N.B. :** (1) Question No. 1 and 2 is compulsory.
 (2) Answer any three from remaining questions.
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data if required.

Q1. a Design two stage R-C coupled amplifier using BC-547B transistor for the following parameters: $A_v \geq 600$, $V_{CC} = 12V$, $S_{IC0} \leq 10$, lower cutoff frequency $F_l = 10Hz$. 15

b For the above designed amplifier determine; A_v , V_{Omax} , R_{in} , and R_o . 05

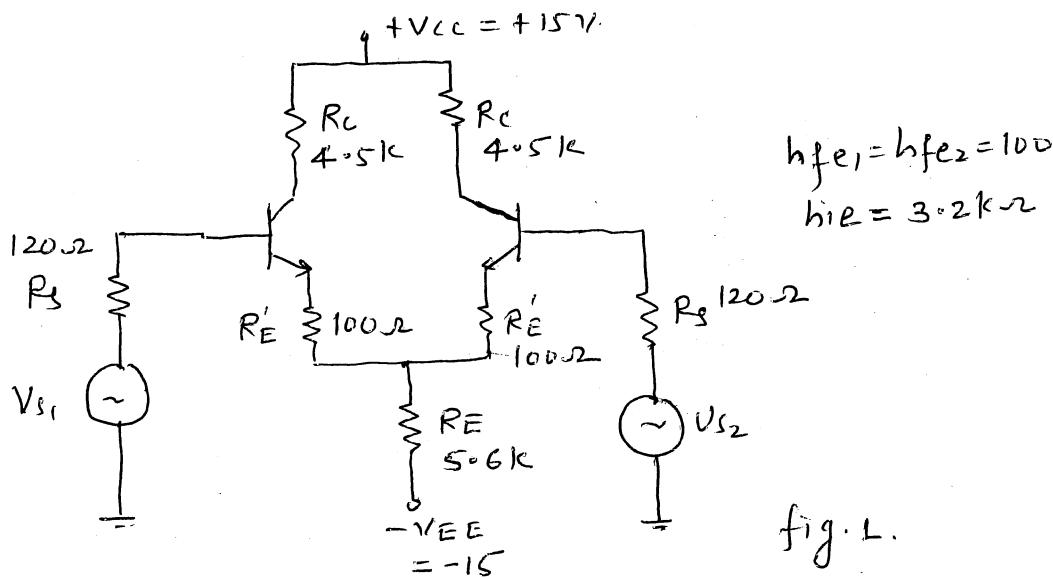Q2. a Design large signal transformer coupled class A power amplifier to provide 6w output power to the 4 ohms load. 10

b For the differential amplifier shown in fig.1 determine: 10
 i) DC bias conditions,
 ii) Differential mode gain A_d ,
 iii) Common mode gain A_c , and
 iv) Differential mode input impedance and output impedance.




Q3. a A three stage RC coupled amplifier uses FET with the following parameters: $g_m = 2.5 \text{ mA/V}$, $r_d = 7.5 \text{ k}\Omega$, $R_D = 10 \text{ k}\Omega$, $R_G = 1.2 \text{ M}\Omega$, coupling capacitor $C_c = 0.005 \mu\text{F}$ and $C_s = \infty$. Evaluate 08

- i) The overall mid-band voltage gain in dB
- ii) Lower 3-dB frequency of individual stages and
- iii) Overall lower 3-db frequency.

b Draw two stage CE amplifier and derive the expressions for i) Small signal mid-band voltage gain, ii) Input impedance, and iii) Output impedance. 12

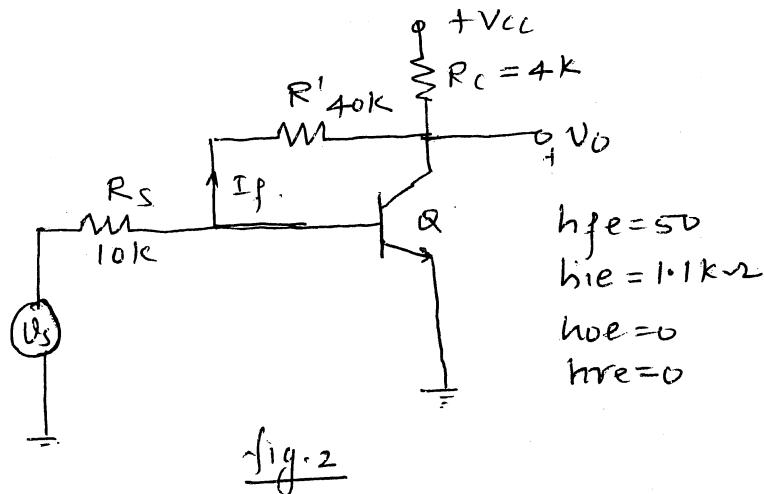
- Q4. a For the feedback amplifier shown in fig. 2, (i) Identify the type of feedback 12 and (ii) Derive the expression for A_{VF} , R_{IF} , and R_{OF} using negative feedback approach.



- b Explain the working principle of a Wein bridge oscillator. Derive the 08 expression for the frequency of oscillation and the value of gain required for sustained oscillation.

- Q5 a Enumerates the effects of negative feedback on i) gain, ii) frequency 08 response, iii) Distortion, iv) Noise and v) Input and output impedance.

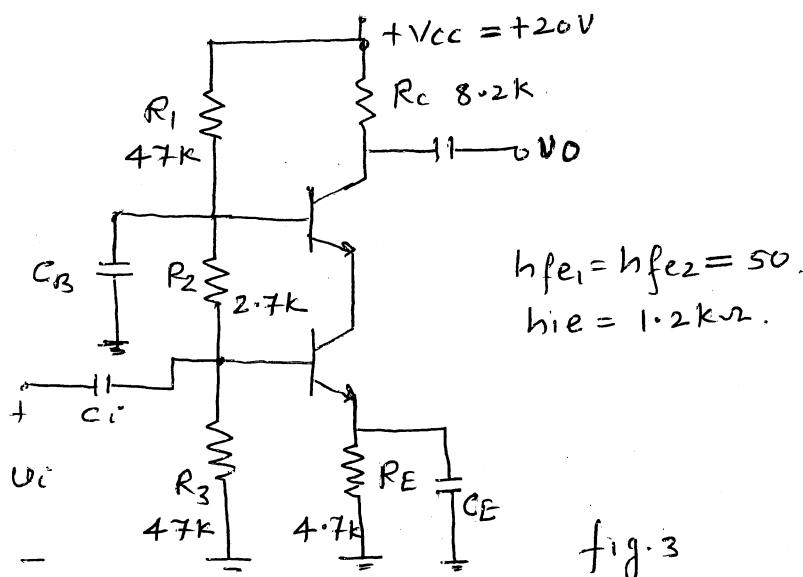- Q5 b For the amplifier shown in fig.3 determine V_{B1}, V_{B2}, I_{CQ}, Av, R_i and R_o. 12



- Q6**

 - a Draw the circuit diagram for class B push-pull power amplifier and derive the expression for conversion efficiency. 10
 - b With neat sketch, explain the working of an emitter coupled astable multivibrator. State the advantages of emitter coupled astable multivibrator. 10

Q7

 - Write a short note on following. 20
 - a Colpitt's oscillator.
 - b Frequency response of R-C, Direct coupled and transformer coupled amplifier
 - c Crossover Distortion in power amplifier.
 - d Class C power amplifier.

[TURN OVER

Transistor type	I_{Cmax} @ 25°C Watts	$V_{CE}^{(typ)}$ volts d.c.	V_{CE} volts (Sats) d.c.	V_{CE} volts (Sats) d.c.	V_{BE} volts d.c.	V_{BE} volts d.c.	T_j °C	D.C. current typ.	D.C. current min.	Small-signal gain typ.	A_f	V_{BR} max.	θ_{fW} above 25°C W/P	Derate above 25°C W/P	
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	70	15	50	120	1.5
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	25	75	125	1.5
ECN 149	30.0	4.0	1.0	50	40	—	—	—	150	30	50	110	33	60	115
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	260	260
2N 525(PNP)	0.225	0.5	0.25	85	70	—	—	—	100	35	—	65	—	45	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500

Transistor type	H_{FE}	H_{FE}	H_{FE}	θ_{fW}
BC 147A	2.7 KΩ	13μΩ	1.5×10^{-1}	$0.4^\circ\text{C}/\text{mW}$
2N 525 (PNP)	1.4 KΩ	25μΩ	1.2×10^{-1}	$-0.4^\circ\text{C}/\text{mW}$
BC 147B	4.5 KΩ	30μΩ	2×10^{-1}	$0.4^\circ\text{C}/\text{mW}$
ECN 100	500 Ω	—	—	—
ECN 149	250 Ω	—	—	—
ECN 055	100 Ω	—	—	—
2N 3055	25 Ω	—	—	—

N-Channel JFET

Type	V_{GS} max. Volts	V_{GS} max. Volts	P_d max. @25°C Volts	T_j max. °C	I_{DSR} (typical)	β_{ds}	$-V_F$ Vdss Volts	r_d	Derate above 25°C
2N822	50	50	50	175°C	2 mA	3000 μΩ	6	50 kΩ	2 mW/P
BFW 11 (typical)	30	30	30	200°C	7 mA	5600 μΩ	2.5	50 kΩ	—