
5

Con. 8880-13.

(3 Hours)

[Total Marks: 100

- **N.B.** (1) Question No.1 and 2 are compulsory.
 - (2) Attempt three questions from remaining five questions.
 - (3) Assume suitable data if necessary.
- 1. (a) Design two stage cascaded amplifier to meet following specifications. $AV \geq 600, \, \text{Ri} \geq 1 \, \text{M}\Omega, \, \text{S}_{\text{ICO}} \leq 10, \, \text{f}_{\text{L}} = 20 \text{Hz} \, \text{and} \, \text{V}_{\text{o}} = 3 \text{V}$
 What would be the voltage gain of the designed circuit if both bypass capacitors are removed? To design, use suitable transistor from data sheet.
- 2. (a) Design a class B push-pull power amplifier with appropriate biasing to minimize cross over distortion and using transformer coupling for 8 W output. Using 12 V d.c. supply. Assume $R_L = 5\Omega$. For the designed circuit, find efficiency at full load.
 - (b) A BJJ has gm = 38 m σ , rb'e = 5.9 k Ω , hie = 6 k, rbb' 100 Ω , Cb'c = 12 pF, cb'e = 63 pf and hfe = 224 at 1 kHz. Calculate α and β cut-off frequencies and $f_{\rm T}$.
- 3. (a) Explain Miller's Theorem.
 - (b) For a cascaded amplifier, show that overall lower 3dB frequency $F_{LT} = \frac{f_L}{\sqrt{2^{1/n}-1}}$ and 10 higher 3dB frequency $f_{HT} = f_H \sqrt{2^{1/n}-1}$ with 'n' stages.
 - (c) Determine maximum safe power dissipation in a transistor if the rated power is 25W, $T_{jmax} = 175^{\circ}c$. The transistor is mounted on a heat sink with $\theta_{cs} = 1^{\circ} c/w$ and $\theta_{5A} = 5^{\circ} c/w$.
- 4. (a) For the cascode amplifier circuit shown in **figure**, determine the values of resistors R_E and R_1 , such that the operating point is $I_{CQ} = 10$ mA and $V_{CEQ} = 10$ V. Given that the values of $R_2 = 10$ k, $\beta = 100$ and V_{BE} of each transistor is 0.7V.

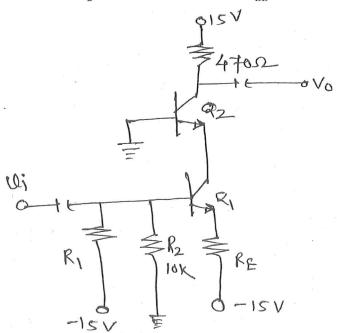


Con. 8880-GS-7128-13.

2

(b) Draw the circuit of Darlington configuration and derive the expression for current gain and Input Resistance.Also explain Principle of Bootstrapping with the help of appropriate circuit.

. 8

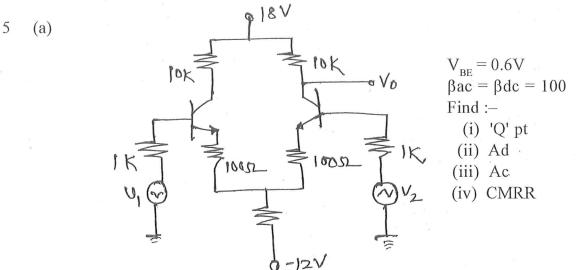

5 (b) Derive the expression for Rif and Rof using equivalent circuit for :-

12

- (i) Voltage series negative feedback
- (ii) Current shunt negative feedback.
- 6. (a) Explain Barkhausen's criteria. Also derive the expression for frequency of oscillation 10 of wein Bridge Oscillator.
 - 4.0


(b) Write short notes on :-

10

10

(i) Colpitt's Oscillator(ii) Clapp Oscillator.

7. (a)

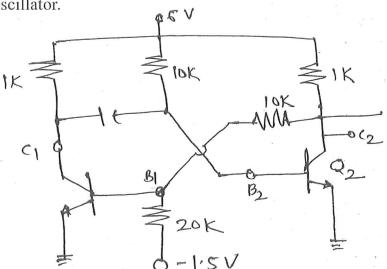

For the above circuit, compute voltage levels and sketch the waveform of voltages at B_1 , C_1 , B_2 and C_2 for permanant state and quasi Stable state.

Use silicon transistors with $r_{bb}^{1} = 100 \Omega$ and $h_{FE} = 30$.

(b) Explain the various negative feedback topologies.

10

DBEC DATA SHEET

| | Pdmax | Icmax | V (sal) | V _{CBO} | VCEO | VCER | VCEX | VBEO | 3 | D.C. | current | 1 gain | Small | | Signal | h_{fe} | VBE | O O | Derate above 25°C |
|--------------------|----------|--------------------------------|----------------------|------------------|---------------------|-------------|-------------|--------------------------------|-------|-------|-----------|--------|----------|-------|---------|------------|----------------|-------|-------------------------|
| Transistor type | Watts | (@ 25°C (@ 25°C) Watts Amps | d.c. | d.c. | volts d.c.volts d.c | volts d.c. | d.c. | | J°C | min | typ. | тах. | min. | | typ. | тах. | | i | J _o /M |
| 2N 3055 | 115.5 | 15.0 | 1:1 | 100 | 09 | 70 | 90 | 7 | 200 | 20 | 50 | 70 | 15 | | 50 | 120 | 1.8 | 1.5 | 1.0 |
| ECN 055 | 50-0 | 5.0 | 1.0 | 09 | 50 | 55 | 09 | 5 | 200 | 25 | 50 | 100 | 25 | • | 75 | 125 | 1.5 | 3.5 | 4.0 |
| ECN 149 | 30.0 | 4.0 | 1.0 | 20 | 40 | I | ĺ | ∞ | 150 | 30 | 20 | 110 | 33 | | 09 | 115 | 1.2 | 4.0 | 0-3 |
| ECN 100 | 5.0 | 0.7 | 9.0 | 70 | 9 | 65 | i I | 9 | 200 | 20 | 90 | 280 | 2(| | 06 | 280 | 6.0 | 35 | 0.05 |
| BC147A | 0.25 | 0.1 | 0.25 | 50 | 45 | 20 | I. | 9 | 125 | 115 | 180 | 220 | 125 | | 220 | 260 | 6-0 | ١ | 1 |
| 2N 525(PNP) | 0.225 | 0.5 | 0.25 | 85 | 30 | 1 | I | I | 100 | 35 | 1 | 65 | | | 45 | 1 | 1 | | 1 |
| BC147B | 0.25 | 0.1 | 0.25 | 20 | 45 | 20 | 1 | 9 | 125 | 200 | 290 | 450 | 240 | | 30 | 200 | 6.0 | I | 1 |
| | | | | | | | | | | | | | | | | | | | |
| Transistor type | hie | hoe | hre | | вја | | , | 3477777 | | 1766 | SOLLSI | | | | | | | | |
| BC 147A | 2.7 K \O | 18u 25 | 1.5×1 | | 0.4°C/mw | BFW | 11—Jrr | 11—JFEI MUIUAL CHARACIERISIICS | L CHA | CACIE | COLLEGE | | | - | - | | | - | Г |
| 2N 525 (PNP) | 1.4 K \O | 25u 75 | 3.2×10^{-4} | 10 | | -VGs volts | volts | 0.0 | 0.5 | 0.4 0 | 0.6 0.8 | 1.0 | 1.2 | 1.6 | 2.0 2.4 | 4 2.5 | 3.0 | 3.5 | 4-0 |
| BC 147B | 4.5 K D | 30 n 2 | 2×10^{-3} | | 0.4°C/mw | Ine ma | Ine may mA | 10 | 0.0 | 8.3 | 7.6 6.8 | 6.1 | 5.4 | 4.2 | 3.1 2.2 | 2 2.0 | 1.1 | 0.5 | 0-0 |
| ECN 100 | S00 Q | 1 | | 1 | | | | | + | + | 1 | 1 | , | ╀ | - | \vdash | 0 | 0 | 0 |
| ECN 140 | 0.050 | 1 | , | | | IDS typ. mA | . mA | 7.0 | 0.9 | 5.4 | 4.6 4.0 | 5.3 | 1.7 | 7 /-1 | 0.0 | 0-0 | 0.0 | + | 5 |
| FCN 055 | 100 00 | 1 | l | | | Ins mi | IDs min. mA | 4.0 | 3.0 | 2.2 | 1.6 1.0 | 0.5 | 0.0 | 0.0 | 0.0 0.0 | 0-0 | 0.0 | 0-0 | 0.0 |
| 2N 3055 | 25 Ω | 1 | | | | | | | | | | | | | | | | | |
| N-Channel JFET | £ | | | | | | | | | | | | | | | | | | |
| | | V max | V max | | V. max. | P. max. | T. | T. max. | Ince | | 00 | 1 | -V Volis | | 7 | Derate | sie | | 9. |
| Type | | Volts | | | Volts | @25°C | | | 227 | (1) | (typical) | | | | | above 25°C | 25°C | | |
| 2N3822 | | 50 | 50 | | 50 | 300 mW | 17 | 175°C | 2 mA | | 3000 µU | | 9 | 50 | 50 KΩ | 2 mW/°C |) _C | 0.59 | 0.59°C/mW |
| DEW 11 (Principal) | | 30 | 30 | | 30 | 300 mW | 20 | 200°C | 7 mA | 1 | 5600 µ 73 | | 2.5 | 50 | 50 KΩ | | | 0.59° | 0.59° C/mW |
| Brw 11 (typical) | | 2 | 8 | | 2 | | | | | | | | | | | | | | |