

Con. 6787-13.

LJ-11350

(3 Hours)

[Total Marks : 100

N.B. : (1) Question No. 1 is **compulsory**.(2) Attempt any **four** out of the remaining **six** questions.(3) Assume **suitable data** wherever **required** and **justify** the same.

1. (a) A typical PCB substrate consists of Al_2O_3 with a relative dielectric constant of 10 and a loss tangent of 0.0004 at 10 GHz. Find the conductivity of substrate. **5**
- (b) Draw the lumped element circuit model for a transmission line. Derive the expression for voltage and current travelling waves. **5**
- (c) Explain current flow in Pn junction and give the expression for I_{diff} in terms of diffusion constant and V_{diff} in terms of doping concentration. **5**
- (d) A lossless 50Ω microstrip line is terminated into a load with admittance of 0.05 mS . What additional impedance has to be placed in parallel with load to assure impedance of 50Ω . **5**
2. (a) A short circuited 50Ω transmission line section operated at 1 GHz and possesses a phase velocity of 75% of the speed of light. Use both the analytical and the Smith chart approach to determine the shortest length required to obtain : **10**
- (i) 5.6 pF Capacitor
- (ii) 4.7 nH inductor.
- (b) Explain various terminations used in Microstrip transmission line. **10**
3. (a) Starting with the equation for normalized admittance :— **10**
- $$y = g + jb = \frac{1 - \Gamma}{1 + \Gamma}$$
- Prove that the circle equations for the Y-Smith chart are given by the following two formulas :—
- (i) For the constant conductance circle as $\left(\Gamma_r + \frac{g}{g+1} \right)^2 + \Gamma_i^2 \left(\frac{1}{1+g} \right)^2$
- (ii) For the constant susceptance circle as $(\Gamma_r + 1)^2 + \left(\Gamma_i + \frac{1}{b} \right)^2 = \left(\frac{1}{b} \right)^2$
- (b) Explain with the equivalent circuits the radio frequency behaviour of resistor, inductor and capacitor. **10**
4. (a) State and prove Kuroda's four identities. **10**
- (b) Explain in brief the principle of operation of HEMT and RF FET along with their construction. **10**

[TURN OVER

Con. 6787-LJ-11350-13.**2**

5. (a) Design a prototype low pass butterworth filter that will provide atleast 20dB attenuation at the frequency of $f = 2f_{3dB}$. (Calculate order) **10**
- (b) What is Miller effect ? Show that :— **10**

$$C_{M1} = C_{cb} \left(1 - \frac{V_{ce}}{V_{be}} \right) \text{ on the i/p port.}$$

$$C_{M2} = C_{cb} \left(1 - \frac{V_{be}}{V_{ce}} \right) \text{ on the o/p port.}$$

6. (a) Derive expression for internal, external and loaded quality factors for standard series and parallel resonant circuit. **10**
- (b) Explain the function of BJT in detail. **10**
7. Write short notes on :—
- (a) Butterworth filter **5**
 - (b) Chip components **5**
 - (c) Schottky contacts **5**
 - (d) Richard's transformaiton **5**
-