

# KALSEKAR TECHNICAL CAMPUS, NEW PANVEL

Approved by : All India Council for Technical Education, Council of Architecture, Pharmacy Council of India New Delhi, Recognised by : Directorate of Technical Education, Govt. of Maharashtra, Affiliated to : University of Mumbai.

SCHOOL OF ENGINEERING & TECHNOLOGY

SCHOOL OF PHARMACY

SCHOOL OF ARCHITECTURE

#### **DEPARTMENT OF ELECTRICAL ENGINEERING**

REV:00	X O DO TITLE TO DE TENTO TENTO		M-04 B	
CLASS:- SE		SEM:-IV		
COURSE:- EN		DATE:- 16 2	2/19	
DURATION:- 6	0 min.	MARKS:- 20		
	Q.01 Attempt any two: (08 Marks)		Marks	СО
a) Write a sho	ort note on different types of sources.		4	1
b) Find the cu	rrent i by using mesh analysis for the network shown below	οΑ	4	1
c) Define a)or	iented graph b)connected graph c) Tree d) co-tree		4	2
	Q.02 Attempt any two: (12 Marks)			
a) Determine	1	3	6	
	10V T	-0 a		1
b) Find the pos	ssible number of tree in a given graph 3		6	2
For the netw	york shown below find I <sub>1</sub> K=0.6	Ω	6	3

CRITERION: 2.2.2, 3.2.2.

FILE NO: P25, P31

Innovative Teaching - Exuberant Learning
Vision: To be the most sought after academic, research and practice based department of Electrical Engineering

that others would wish to emulate.



# KALSEKAR TECHNICAL CAMPUS, NEW PANVEL

Approved by : All India Council for Technical Education, Council of Architecture, Pharmacy Council of India New Delhi, Recognised by : Directorate of Technical Education, Govt. of Mahacashtra, Affiliated to : University of Mumbai.

SCHOOL OF ENGINEERING & TECHNOLOGY

□ SCHOOL OF PHARMACY

□ SCHOOL OF ARCHITECTURE

2	DEPARTMENT OF ELECTRICAL ENGINEERING  REV:00 DEPARTMENT OF ELECTRICAL ENGINEERING		EXM-04	l(a)
	表 3 では、100 × 3 では、10	SEM:- IV	esi edilinetti esperatori ese e Ferre u	HARASIA CONTRACTOR OF THE
Annual Control		DATE:-15	/02/19	
Samuel Samuel		MARKS:- 2	20	***************************************
	CLASS TEST 01			
Q.(	01 Attempt any TWO: (08 Marks)		Marks	CO
1	Explain phasor diagram of transformer on no load.		4	CO1
.2	Derive condition for zero and max voltage regulation.		4	CO1
3	Explain polarity test on transformer.		4	CO1
Q.0	02 Attempt any TWO: (12 Marks)		annandandani, sitesi ir udtadiresi sust-unannuse ir aeras.	
1	Explain separation of hysteresis and eddy current losses.		6	CO1
2	Explain construction of auto transformer also explain saving of copper		6	CO2
3	Two transformer having same voltage regulation on no load in paralle supply a load of 1000 kva at 0.8 pf lag. One transformer rated at 400k has a pu eq impedances of (0.01+0.06) other is rated at 600kva and pu eq impedance (0.01+j0.05)ohm calculate load share by each transin kva and operating pf.	va and has a	6	C01



# ANJUMAN-I-ISLAM'S

# KALSEKAR TECHNICAL CAMPUS, NEW PANVEL

Approved by : All India Council for Technical Education, Council of Architecture, Pharmacy Council of India New Delhi, Recognised by : Directorate of Technical Education, Govt. of Maharashtra, Affiliated to : University of Mumbai.

SCHOOL OF ENGINEERING & TECHNOLOGY

□ SCHOOL OF PHARMACY

□ SCHOOL OF ARCHITECTURE

#### DEPARTMENT OF ELECTRICAL ENGINEERING

REV	100 DEPARTMENT OF ELECTRICAL ENGINEERING	EXM-04	1(a)	
CLASS:	- SE SEM:- IV			
SUBIEC	CT:- EMC-II DATE:-15/	/02/19		
		MARKS:- 20		
Ť	CLASS TEST 01			
Q.Q1 A	Attempt any TWO: (08 Marks)	Marks	CO	
1 .Ex	plain phasor diagram of transformer on no load.	4	CO1	
	rive condition for zero and max voltage regulation.	4	CO1	
:3 Ex	plain polarity test on transformer.	4	CO1	
Q.02 A	Attempt any TWO: (12 Marks)			
1 Exp	plain separation of hysteresis and eddy current losses.	6 -	CO1	
2 Exp	plain construction of auto transformer also explain saving of copper.	6	CO2	
sup has	o transformer having same voltage regulation on no load in parallel to oply a load of 1000 kva at 0.8 pf lag. One transformer rated at 400kva and s a pu eq impedances of (0.01+0.06) other is rated at 600kva and has a eq impedance (0.01+j0.05)ohm .calculate load share by each transformer kva and operating pf.	6	C01	

(RITERION : 2.2.2,

3.2.2.

FILE NO: P25, P31

Innovative Teaching - Exuberant Learning

Vision: To be the most sought after academic, research and practice based department of Electrical Engineering that others would wish to emulate.



# ANJUMAN-I-ISLAM'S KALSEKAR TECHNICAL CAMPUS, NEW PANVEL

Approved by : All India Council for Technical Education, Council of Architecture, Pharmacy Council of India New Delhi, Recognised by : Directorate of Technical Education, Govt. of Maharashtra, Affiliated to : University of Mumbai.

SCHOOL OF ENGINEERING & TECHNOLOGY

□ SCHOOL OF PHARMACY

☐ SCHOOL OF ARCHITECTURE

#### DEPARTMENT OF ELECTRICAL ENGINEERING

RE\	V:00		CHOIL		ER CLA	And the second of the second				
CLASS	S:-SE EE			,				SEM:- <u>IV</u>		
COUR	SE:-APPL	ED MATHS	<u>S-IV</u>	2					4/02/2019	
URA	TION:- 1	HOUR						MARKS:-	20	
0.01	Attempt	any two: (	(08 Marks	5)			\$ p		Marks	СО
a)	-	V	8		coefficient(I	R) from fo	llowing data	a.	04	CO5
1.0	X	10	12	18	18	15	40			
	Y	12	18	25	25	50	25			
b)				e y y e n		H 2		· .	04	CO1
			the following the given the			0 and wh	nen $x = \pi$ , y	y=0.		
(2	N								04	COE
-	$fA = \begin{bmatrix} 2 \\ -3 \end{bmatrix}$	3 _4] pro	ove that	$A^{100} = \begin{bmatrix} -2 \\ 3 \end{bmatrix}$	299 –30 00 303	[0]			04	CO3
11	-		ove that		299 –30 00 30	[0]			04	CO3
3.02 A	Attempt a	any two: (	12 Marks	9)			2 -1 1 1 2 - 1 -1 2	1)	04	
a.02 A	Attempt a	<b>nny two: (</b> d Eigen val	12 Marks	gen vector		atrix A =		1)		C03
0.02 A	Attempt a	<b>nny two: (</b> d Eigen val	12 Marks	gen vector ression fro	s for the ma	atrix A =		1)	06	C03
	Attempt a Fin  Marks	d Eigen val	12 Marks lues and Eiglines of reg	gen vector ression fro	s for the manner of the following the follow	atrix A =		1)	06	C03
(2.02 A	Fin Marks	d Eigen val	12 Marks lues and Eiglines of reg 36 3 (Y) 35 3	ression fro 2 34 33 3 31 30	s for the manner of the following the follow	wing data $ 34 $ 36		1)	06	C03

CRITERION: 2.2.2, 3.2.2.

FILE NO: P25, P31

 $\frac{I \quad n \quad n \quad o \quad v \quad a \quad t \quad i \quad v \quad e \quad T \quad e \quad a \quad c \quad h \quad i \quad n \quad g \quad - \quad E \quad x \quad u \quad b \quad e \quad r \quad a \quad n \quad t \quad L \quad e \quad a \quad r \quad n \quad i \quad n \quad g}{Vision : To \ be \ the \ most \ sought \ after \ academic, \ research \ and \ practice \ based \ department \ of \ Electrical \ Engineering}$ 

that others would wish to emulate.



# KALSEKAR TECHNICAL CAMPUS, NEW PANVEL

Approved by : All India Council for Technical Education, Council of Architecture, Phormocy Council of India New Delhi, Recognised by : Directorate of Technical Education, Govt. of Mahorashtro, Affiliated to : University of Mumbai.

SCHOOL OF ENGINEERING & TECHNOLOGY

□ SCHOOL OF PHARMACY

□ SCHOOL OF ARCHITECTURE

#### DEPARTMENT OF ELECTRICAL ENGINEERING

REV:00	QUESTION PAPER CLASS TEST 01/02	EXM-	-04 B	
CLASS:- S	E SEM:- I'	V		
COURSE:-	Power Systems - I DATE:-	14/2/19		
	I:- 60 min. MARKS	3:- 20		
Q.01 Attem	pt any 2 : (08 Marks)		Marks	CO
a) Compa	are AC and DC supply systems		4	CO1
b) Derive	the expression for calculating sag. How can the effect of wind and Ice loadings be taken into t?		4	CO2
c) What i	s Per Unit System? Mention its advantages.		4	CO3
Q.02 Attem	pt any 2 : (12 Marks)			
10 of	ng insulators has 5 units is connected across a 100 kV line. If the capacitance of each disc to the capacitance of the insulator, calculate i) the distribution of voltage on the insulator discs are Efficiency.		6	CO2
String Efficiency.  b) The towers of height 30m and 90m respectively support a transmission line conductor at water crossing. The horizontal distance between the towers is 500m. If the tension in conductor is 1600kg, find the minimum clearance of the conductor and water. Weight of conductor is 1.5kg/m. Bases of the towers can be considered at water level.				
c) With a	neat Single Line Diagram explain general AC Power Supply Scheme.		6	CO1



# ANJUMAN-I-ISLAM'S

# KALSEKAR TECHNICAL CAMPUS, NEW PANVEL

Approved by : All India Council for Technical Education, Council of Architecture, Pharmacy Council of India New Delhi, Recognised by : Directorate of Technical Education, Govt. of Mahorashtra, Affiliated to : University of Mumbai.

SCHOOL OF ENGINEERING & TECHNOLOGY

□ SCHOOL OF PHARMACY

□ SCHOOL OF ARCHITECTURE

### DEPARTMENT OF ELECTRICAL ENGINEERING

REV:00	QUESTION PAPER CLASS TEST 01/02 EXM		1-04 B	
CLASS:- SE	SI	EM:- IV		
COURSE:- Power Syst	ems - I D.	ATE:-		
DURATION:- 60 mi	n. M	ARKS:- 20		
Q.01 Attempt any 2:	(08Marks)		Marks	CO
a) Compare AC and	DC supply systems		4	CO1
b) Derive the expres account?	sion for calculating sag. How can the effect of wind and Ice loadings be taken	into	4	CO2
c) What is Per Unit	System? Mention its advantages.		4	CO3
Q.02 Attempt any 2:	(12 Marks)			
String Efficiency.	s has 5 units is connected across a 100 kV line. If the capacitance of each dance of the insulator, calculate i) the distribution of voltage on the insultor dis	scs and ii) the	6	CO2
horizontal distance clearance of the considered at water		he minimum	6	CO2
c) With a neat Single	Line Diagram explain general AC Power Supply Scheme.		6	C01

CRITERION: 2.2.2, 3.2.2.

FILE NO: P25, P31

Innovative Teaching - Exuberant Learning
Vision: To be the most sought after academic, research and practice based department of Electrical Engineering that others would wish to emulate.



# KALSEKAR TECHNICAL CAMPUS, NEW PANVEL

Approved by : All India Council for Technical Education, Council of Architecture, Pharmacy Council of India New Delhi, Recognised by : Directorate of Technical Education, Govt. of Maharashtra, Affiliated to : University of Mumbai.

SCHOOL OF ENGINEERING & TECHNOLOGY

□ SCHOOL OF PHARMACY

SCHOOL OF ARCHITECTURE

#### DEPARTMENT OF ELECTRICAL ENGINEERING

F	REV:00	2:00 QUESTION PAPER CLASS TEST 01 EXM-		M-04 B	
CLA	SS:-SE		SEM: IV		
COL	JRSE:- EFW		DATE:- 15//02	/ 2019	
DUF	RATION:- 60	min.	MARKS:- 20		1
			ý		
Q.01	Attempt any	Two: (08 Marks)		Marks	CO
a)	State and expl	ain Coulombs law in Electrostatics.Hence define unit charge.		4	CO2
b)	A point charge Q1 = 2 milli coulomb is located in free space at p1(-3,7,-4) while Q2=5 mc at P2(2,4,-1). Find force F2 & F1			4	CO2
c)	Discuss the va	rious practical application of Electrostatic field		4	CO1
Q.02	Attempt any	One: (12 Marks)	22		
a)	Transform giv	ven vector $\overline{A}$ into cylindrical coordinate system, $\overline{A} = y  \overline{\alpha} \times + x  \overline{\alpha}$	14 + J2+42 az	12	CO1
B)	If Irrational fiel	d ¬ KV = oFind constant a,b,c so that	is iirrotational.	12	CO2
	V = (?	x+2y+az) ax+(bx-3y-z)ay+(4x+c	y+22) az		
C)	Find the electri	c field intensity at point p(1,1,1) caused by four identical 3 nano could	omb point charges located	12	CO2
	p1(1,1,0),p2(-1,			1	



### ANJUMAN-I-ISLAM'S

SCHOOL OF ENGINEERING & TECHNOLOGY

□ SCHOOL OF PHARMACY

KALSEKAR TECHNICAL CAMPUS, NEW PANVEL
Approved by : All India Council for Technical Education, Council of Architecture, Pharmacy Council of India New Delhi,
Recognised by : Directorate of Technical Education, Govt. of Maharashtra, Affiliated to : University. of Munhai

□ SCHOOL OF ARCHITECTURE

#### DEPARTMENT OF ELECTRICAL ENGINEERING

	REV:00	QUESTION PAPER CLASS TEST 01 EX	M-04 B	
CL	ASS:-SE	SEM: IV		
CO	URSE:-EFW	DATE:- 15//02	/ 2019	
DU	RATION:- 60 min.	MARKS:- 20		
Q.01	Attempt any Two: (0	8 Marks)	Marks	СО
a)	State and explain Co	oulombs law in Electrostatics.Hence define unit charge.	4	CO2
b)	b) A point charge Q1 = 2 milli coulomb is located in free space at p1(-3,7,-4) while Q2=5 mc at P2(2,4,-1). Find force F2 & F1		4	CO2
c)	Discuss the various	practical application of Electrostatic field	4	CO1
Q.02	2 Attempt any One: (	the state of the second st		
a)	Transform given ve	ctor A into cylindrical coordinate system $A = y \alpha x + x \alpha y + \sqrt{x^2 + y^2} \alpha z$	12	CO1
<b>B</b> )	If Irrectional field *V	is iirrotational.  2y+az) ax + (bx-3y-z) ay + (4x+Cy+2z) az	12	CO2
C)		intensity at point p(1,1,1) caused by four identical 3 nano coulomb point charges located	12	CO2

CRITERION: 2.2.2,

FILE NO: P25, P31

Innovative Teaching - Exuberant Learning
Vision: To be the most sought after academic, research and practice based department of Electrical Engineering that others would wish to emulate.